

Sirindhorn International Institute of Technology

Thammasat University at Rangsit

School of Information, Computer and Communication Technology

## ECS 203: Problem Set and Tutorial 13

**Semester/Year:** 2/2015

**Course Title:** Basic Electrical Engineering

**Instructor:** Asst. Prof. Dr. Prapun Suksompong ([prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th))

**Course Web Site:** <http://www2.siit.tu.ac.th/prapun/ecs203/>

**Due date: Not Due**

### Instructions

1. All phasor should be answered in polar form where the magnitude is positive and the phase is between  $-180^\circ$  and  $180^\circ$ .
2. All sinusoid should be answered in the cosine form where the amplitude is positive and the phase is between  $-180^\circ$  and  $180^\circ$ .

### Questions

1. [Alexander and Sadiku, 2009, Q11.12] For the circuit shown in Figure 1, determine the load impedance  $Z_L$  for maximum power transfer (to  $Z_L$ ). Calculate the maximum power absorbed by the load.

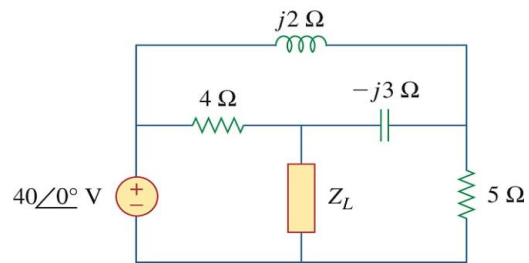


Figure 1

2. [F2010] Consider the circuit in Figure 2 below.

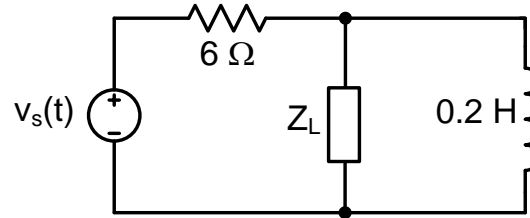


Figure 2

Suppose

$$v_s(t) = 7 \cos(200t + 30^\circ) \text{ V},$$

- Determine the **load impedance**  $Z_L$  for maximum power transfer (to  $Z_L$ ).
- How can you build the optimal  $Z_L$  which you got in part (a) from a combination of resistor(s)/inductor(s)/capacitor(s)? **Draw and explain** your answer. Indicate the values of each component (in  $\Omega$ /H/F).
- Calculate the **maximum power** absorbed by the load  $Z_L$ .

3. [Alexander and Sadiku, 2009, Q7.8] For the circuit in Figure 3 if  $v(t) = 10e^{-4t}$  V and  $i(t) = 0.2e^{-4t}$  A,  $t > 0$

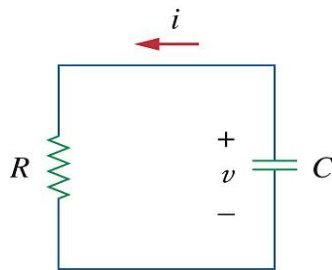


Figure 3

(a) Find  $R$  and  $C$ .

(b) Determine the time constant  $\tau$ .

(c) Calculate the initial energy in the capacitor.

(d) Obtain the time it takes to dissipate 50 percent of the initial energy.

4. [Alexander and Sadiku, 2009, Q7.3] Determine the time constant for the circuit in Figure 4.

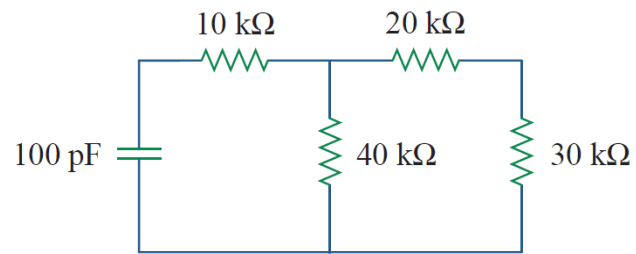


Figure 4: [Alexander and Sadiku, 2009, Figure 7.83]

5. [Alexander and Sadiku, 2009, Q7.2] Determine the time constant for the circuit in Figure 5.

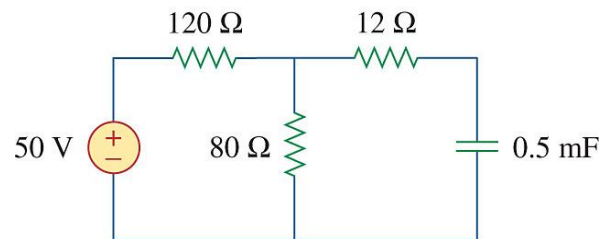


Figure 5

6. [Alexander and Sadiku, 2009, Q7.10] Consider the circuit in Figure 6.

(a) Find  $v_o(t)$  for  $t > 0$ .

(b) Determine the time necessary for the capacitor voltage to decay to one-third of its value at  $t = 0$ .

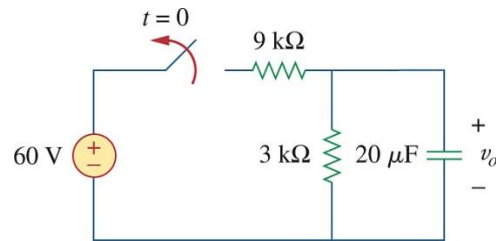


Figure 6

7. [Alexander and Sadiku, 2009, Q7.7] Assuming that the switch in Figure 7 has been in position A for a long time and is moved to position B at  $t = 0$ , find  $v_o(t)$  for  $t \geq 0$ .

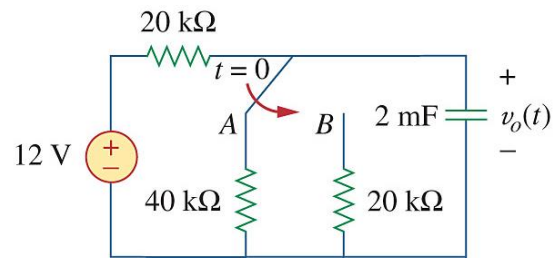


Figure 7

8. [F2010] Consider the circuit in Figure 8 below. **Assume** the switch has been **at position 1 for a long time** and moves to position 2 at  $t = 0$  sec.

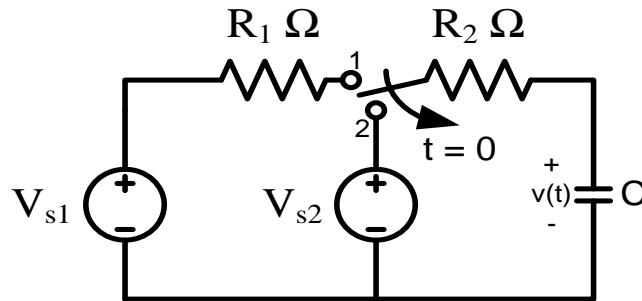


Figure 8

Let

$$V_{s1} = 5 \text{ V}, V_{s2} = 0 \text{ V}, R_1 = 6 \Omega, R_2 = 3 \Omega, \text{ and } C = 10 \text{ F}.$$

(a) (3 pt) Find  $v(0^-)$ . Do not forget to justify your answer.

(b) (1 pt) Find  $v(0)$ . Do not forget to justify your answer.

(c) (4 pt) Find  $v(t)$  for  $t > 0$ .



9. [F2010] Consider the circuit in Figure 9 below. Assume the switch has been at position 1 for a long time and moves to position 2 at  $t = 5$  sec.

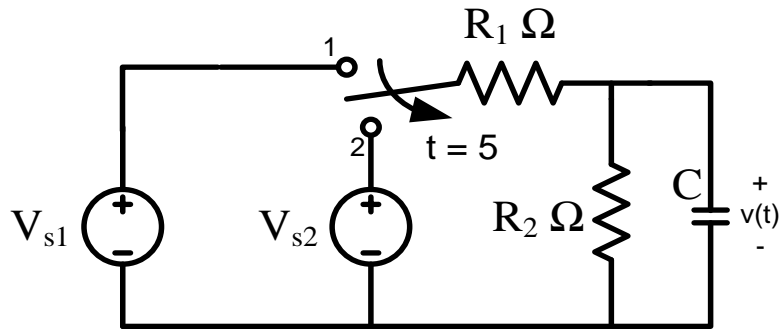


Figure 9

Let

$$V_{s1} = 16 \text{ V}, V_{s2} = 8 \text{ V}, R_1 = 3 \text{ } \Omega, R_2 = 5 \text{ } \Omega, \text{ and } C = 8 \text{ F.}$$

(a) (3 pt) Find  $v(0)$ .

(b) (2 pt) Find  $v(5)$ .

(c) (4 pt) Find  $v(t)$ .

(d) (1 pt) Evaluate  $v(t)$  at  $t = 7$ .

10. [Alexander and Sadiku, 2009, Q7.40] Find the capacitor voltage for  $t < 0$  and  $t > 0$  for each of the circuits in Figure 10.

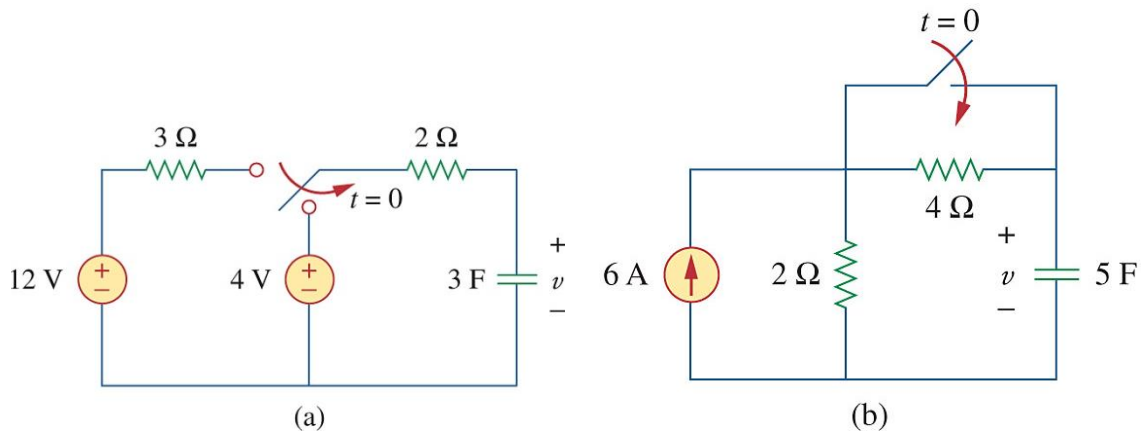


Figure 10

11. [Alexander and Sadiku, 2009, Q7.42]

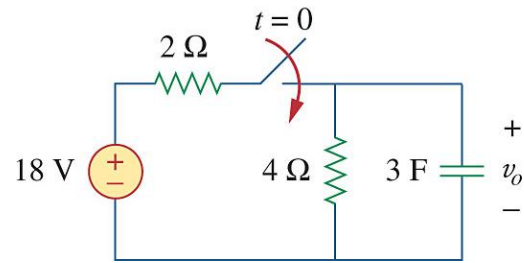


Figure 11

(a) If the switch in Figure 11 has been open for a long time and is closed at  $t = 0$ , find  $v_o(t)$ .

(b) Suppose, instead, that the switch has been closed for a long time and is opened at  $t = 0$ . (Note that this is not shown in the figure.) Find  $v_o(t)$ .

12. [Alexander and Sadiku, 2009, Q7.44] The switch in Figure 12 has been in position  $a$  for a long time. At  $t = 0$ , it moves to position  $b$ . Calculate  $i(t)$  for all  $t > 0$ .

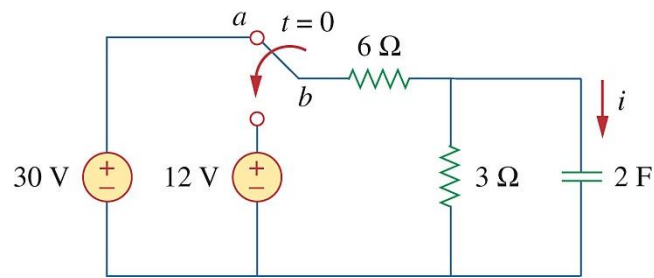


Figure 12

13. Consider the circuit in Figure 13 below. Let

$$V_s = 10 \text{ V}, R_1 = 30 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega, \text{ and } C = 4 \text{ }\mu\text{F}.$$

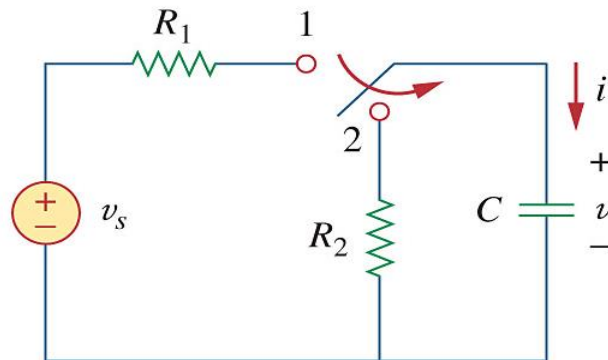


Figure 13

Assume that the switch has been in position 1 during time  $t < 0$ . Then, during time  $t \geq 0$  the switch changes its position five times: at  $t_1 = 0 \text{ ms}$ ,  $t_2 = 25 \text{ ms}$ ,  $t_3 = 50 \text{ ms}$ ,  $t_4 = 75 \text{ ms}$ ,  $t_5 = 100 \text{ ms}$ .

(At time  $t_1$ , the switch changes to position 2. At time  $t_2$ , the switch changes back to position 1. At time  $t_3$ , the switch changes again to position 2....)

**Plot** the voltage  $v(t)$  for time  $t > 0$ .

Hint: You should have  $v(t_5) \approx 4.59 \text{ V}$ .