

Sirindhorn International Institute of Technology
Thammasat University at Rangsit
School of Information, Computer and Communication Technology

ECS 203: Problem Set 2

Semester/Year: 2/2015

Course Title: Basic Electrical Engineering

Instructor: Asst. Prof. Dr. Prapun Suksompong (prapun@siit.tu.ac.th)

Course Web Site: <http://www2.siiit.tu.ac.th/prapun/ecs203/>

Due date: Feb 1, 5 PM


Instructions

1. Solve all problems. (5 pt)
 - a. Write your name and ID on the top of **every** submitted page.
 - b. For each part, write your explanation/derivation and answer in the space provided.
2. ONE sub-question will be graded (5 pt). Of course, you do not know which part will be selected; so you should work carefully on all of them.
3. There is no need to submit (or even print out) page 1 (this cover sheet).
4. Late submission will be rejected.
5. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

Questions

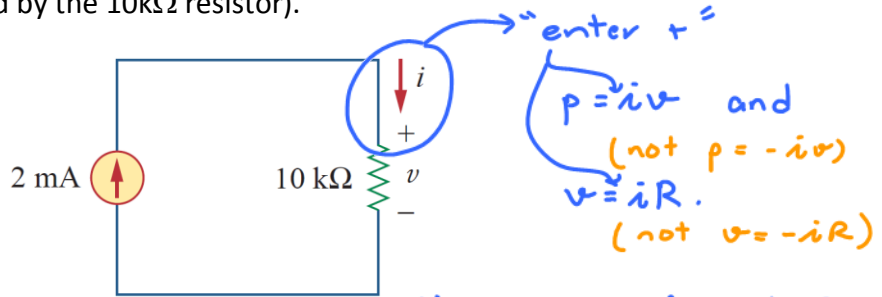- 1) [Alexander and Sadiku, 2009, PP2.2] For the circuit shown in Figure 1, calculate the voltage v and the power p (dissipated by the $10\text{k}\Omega$ resistor).

The 2 mA current source forces clockwise 2 mA current through the circuit (which is simply one loop and hence, by KCL, we have the same 2 mA current flowing through the loop).



The arrow of i agrees with the clockwise direction of the forced 2 mA current.

Here, $i = 2\text{ mA}$ and $R = 10\text{ k}\Omega$.

Therefore,

$$v = iR = 2\text{ mA} \times 10\text{ k}\Omega = 20\text{ V}$$

and

$$p = iv = 2\text{ mA} \times 20\text{ V} = 40\text{ mW}$$

Hence, $i = 2\text{ mA}$.
(not -2 mA)

- 2) [Alexander and Sadiku, 2009, Q2.4]

- a) Calculate current i in Figure 2 when the switch is in position 1.

Because the switch is in position 1, all the current i flows in the CCW direction through the left half of the circuit.

We define a voltage v across the resistor.

Because the 15 V voltage source is connected directly across v and their polarities (+, -) match. We have $v = 15\text{ V}$.


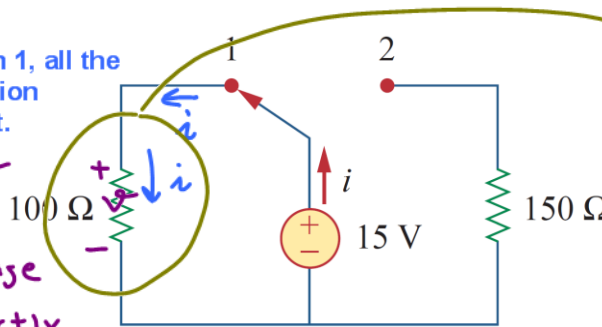


Figure 2

So, $i = \frac{v}{R} = \frac{15\text{ V}}{100\ \Omega} = 0.15\text{ A}$
or 150 mA .

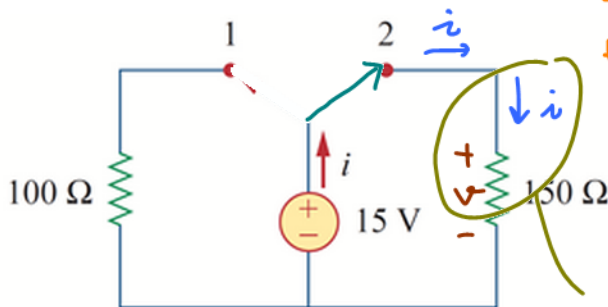
- b) Find the current when the switch is in position 2.

The same reasoning in part (a) also applies to this part except that now the current i is flowing through a new loop on the right half in the clockwise direction




$i = \frac{v}{R} = \frac{15\text{ V}}{150\ \Omega} = 0.1\text{ A}$
or 100 mA .

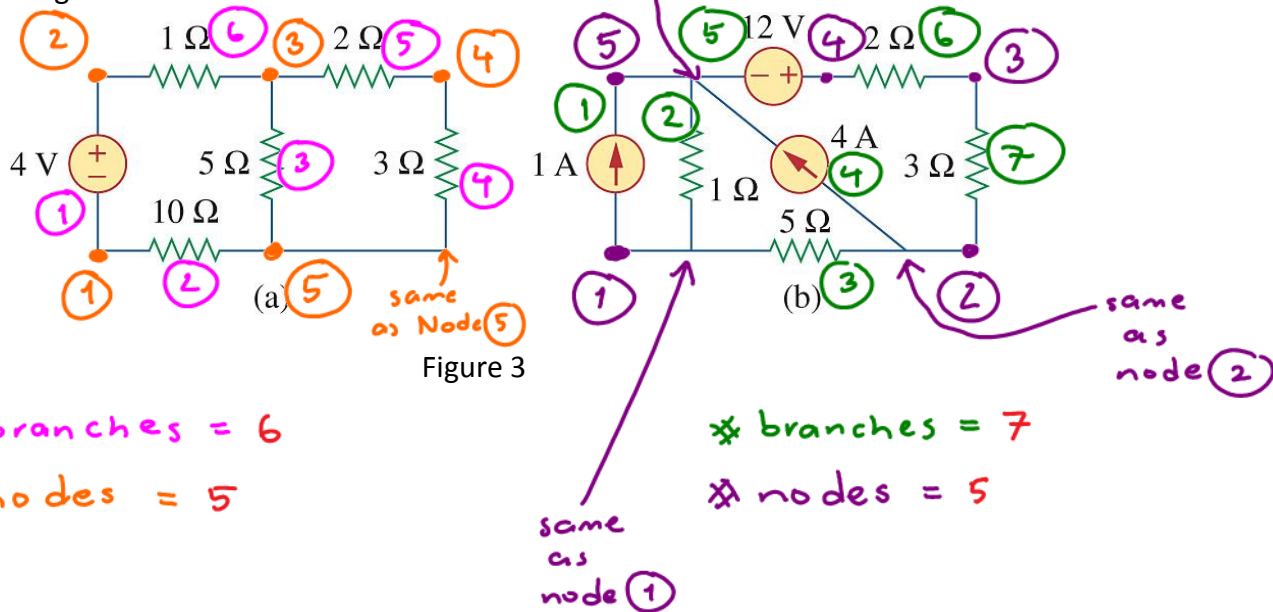3) [Alexander and Sadiku, 2009, Q2.7] Find the number of branches and nodes in each of the circuits of Figure 3.



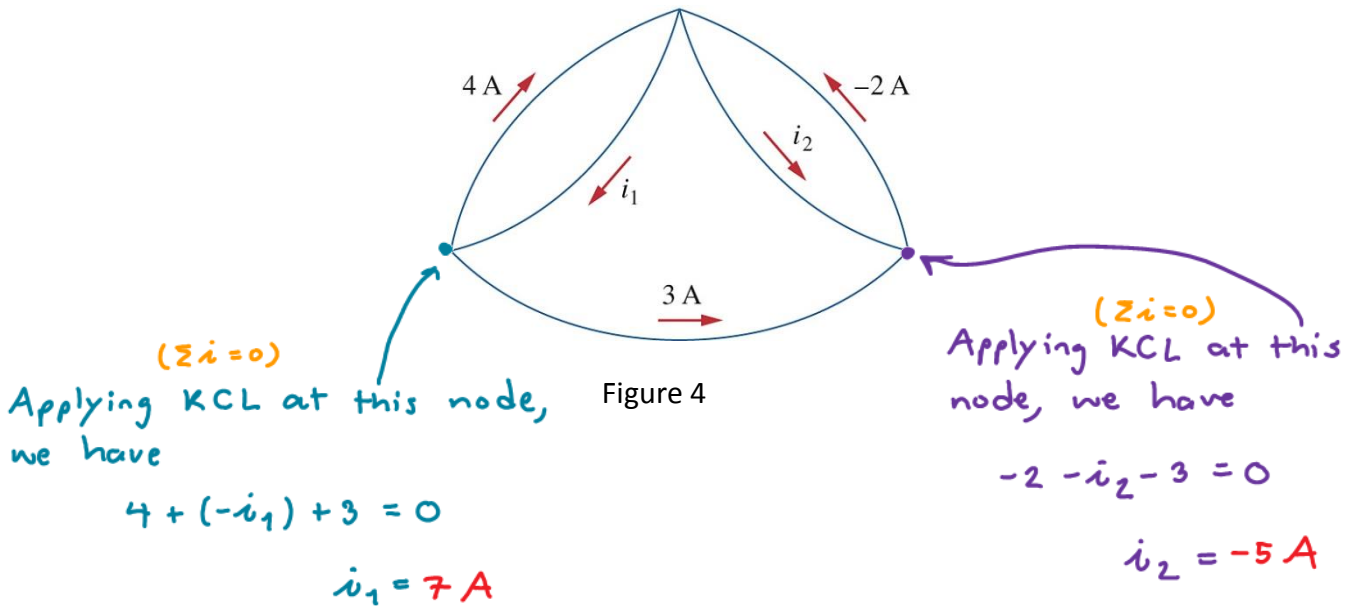4) [Alexander and Sadiku, 2009, Q2.10] Determine i_1 and i_2 in the circuit of Figure 4.



We may check the answers by applying KCL at the top node:

$$-4 + i_1 + i_2 - (-2) = 0$$

$$-4 + 7 - 5 + 2 = 0 \quad \checkmark$$

Use i_1, i_2 that we know.

5) [Alexander and Sadiku, 2009, Q2.14] Given the circuit in Figure 5, use KVL to find the branch voltages V_1 to V_4 .

As hinted, we need to apply KVL. ($\sum v = 0$)
 Because there are four unknowns, we need at least 4 loops.

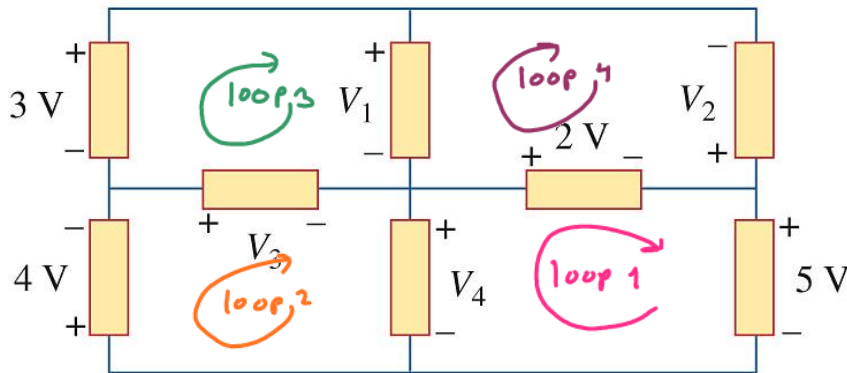


Figure 5

We will try to start with a loop that involves minimum of unknown variables

So, we start with "loop 1":

(only one unknown variable)

$$+V_4 - 2 - 5 = 0$$

With respect to the loop direction, we move from the "-" to "+" terminals of V_4 . So, we "gain" V_4 by moving in such direction

With respect to the loop direction, we move from the "+" to the "-" terminals of the 2V. So, we "lose" 2V by moving in such direction.

$$V_4 = 7V$$

Because we already know V_4 , "loop 2" now has only one unknown variable (V_3):

$$-4 - V_3 - V_4 = 0$$

$$V_3 = -4 - V_4 = -11V$$

Similarly, when we know V_3 , "loop 3" has only one unknown variable (V_1):

$$+3 - V_1 + V_3 = 0$$

$$V_1 = 3 - 11 = -8V$$

Finally, from "loop 4":

$$+V_1 + V_2 + 2 = 0$$

$$V_2 = 8 - 2 = 6V$$

$V_1 = -8V$
$V_2 = 6V$
$V_3 = -11V$
$V_4 = 7V$