

CH5: Op Amp

CH6: -general facts for C and L
 -"dc conditions" \rightarrow $i = C \frac{dv}{dt}$
 \rightarrow $v = L \frac{di}{dt}$

CH7,8,9: sinusoidal steady-state analysis
 (phasor, ac) (for second-order) circuit driven by sinusoidal source) CHAPTER 8

CH10: first-order circuits
 (RC (and RL))

will see that the steady-state of this

is the same as the "dc conditions"

Sinusoidal Steady-State Analysis

8.1. General Approach

In the previous chapter, we have learned that the steady-state response of a circuit to sinusoidal inputs can be obtained by using phasors. In this chapter, we present many examples in which nodal analysis, mesh analysis, Thevenin's theorem, superposition, and source transformations are applied in analyzing ac circuits.

8.1.1. Steps to analyze ac circuits, using phasor domain:

Step 1. Transform the circuit to the phasor or frequency domain.

- Not necessary if the problem is specified in the frequency domain.

Step 2. Solve the problem using circuit techniques (e.g., nodal analysis, mesh analysis, Thevenin's theorem, superposition, or source transformations)


- The analysis is performed in the same manner as dc circuit analysis except that complex numbers are involved.

Step 3. Transform the resulting phasor back to the time domain.


8.1.2. The superposition theorem applies to ac circuits the same way it applies to dc circuits. This is the case when all the sources in the circuit operate at the same frequency.

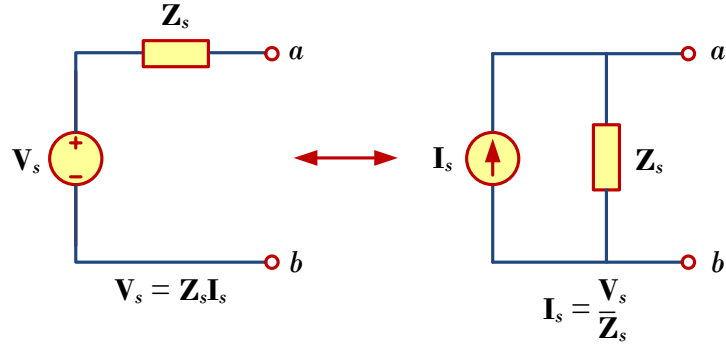8.1.3. Source transformation:

$$V_s = Z_s I_s, \quad I_s = \frac{V_s}{Z_s}$$




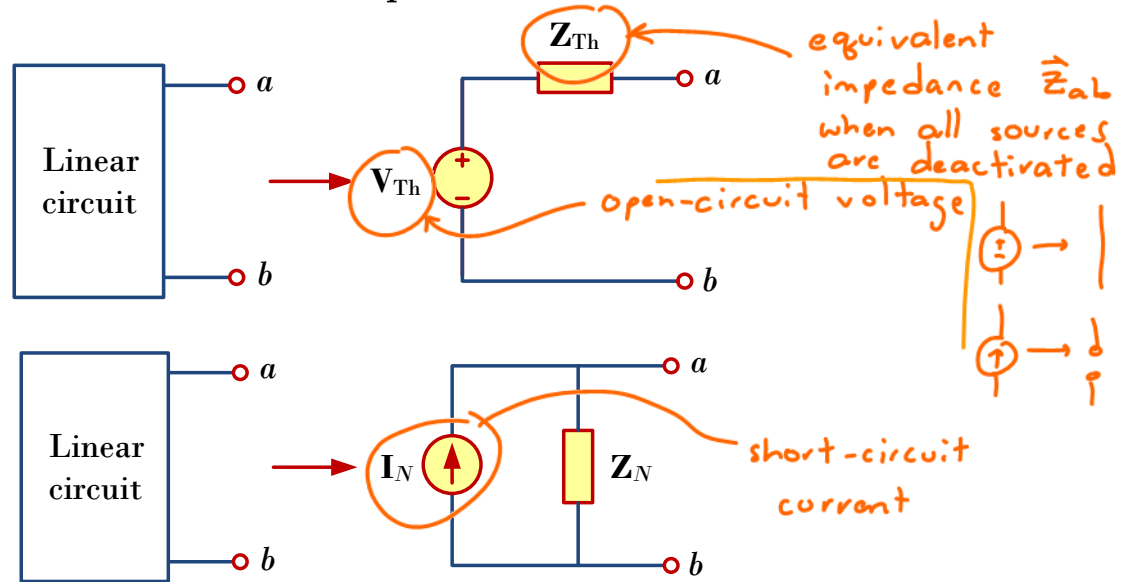8.1.4. Thevenin and Norton Equivalent circuits:



$$V_{Th} = Z_N I_N, \quad Z_{Th} = Z_N$$

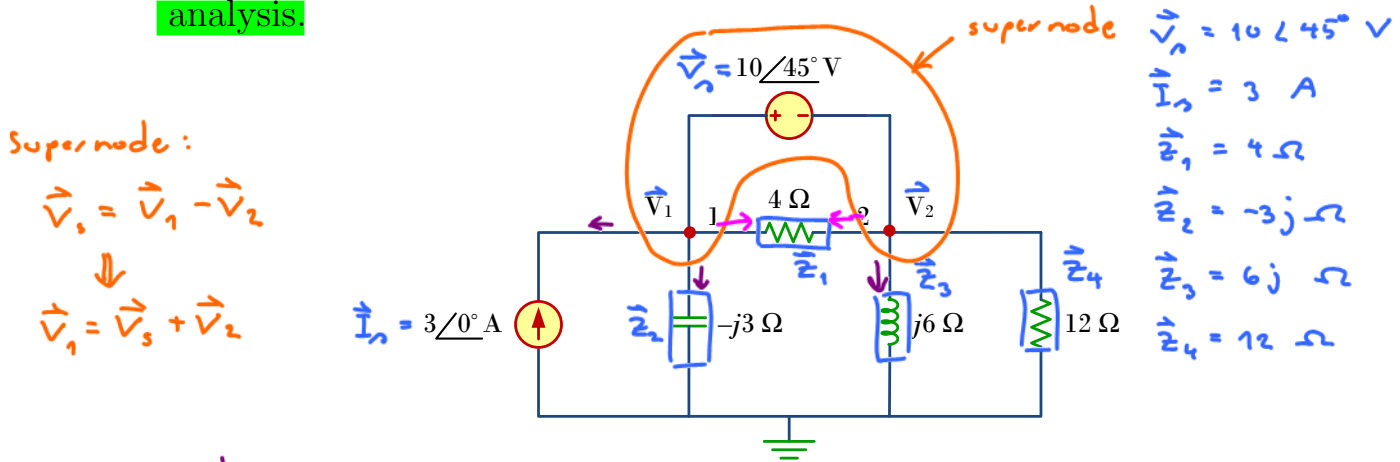EXAMPLE 8.1.5. Compute V_1 and V_2 in the circuit below using nodal analysis.



Supernode:

$$\vec{V}_s = \vec{V}_1 - \vec{V}_2$$

$$\vec{V}_1 = \vec{V}_s + \vec{V}_2$$

$$\vec{V}_s = 10 \angle 45^\circ \text{ V}$$

$$\vec{I}_s = 3 \text{ A}$$

$$\vec{Z}_1 = 4 \Omega$$

$$\vec{Z}_2 = -j3 \Omega$$

$$\vec{Z}_3 = j6 \Omega$$

$$\vec{Z}_4 = 12 \Omega$$

At supernode


KCL:

$$-\vec{I}_s + \frac{\vec{V}_1 - 0}{\vec{Z}_2} + \frac{\vec{V}_1 - \vec{V}_2}{\vec{Z}_1} + \frac{\vec{V}_2 - \vec{V}_1}{\vec{Z}_1} + \frac{\vec{V}_2 - 0}{\vec{Z}_3} + \frac{\vec{V}_2 - 0}{\vec{Z}_4} = 0$$

$$\frac{\vec{V}_1 + \vec{V}_2}{\vec{Z}_2} + \frac{\vec{V}_2}{\vec{Z}_3} + \frac{\vec{V}_2}{\vec{Z}_4} = \vec{I}_s \Rightarrow \vec{V}_2 = \frac{\vec{I}_s - \vec{V}_1 / \vec{Z}_2}{\frac{1}{\vec{Z}_2} + \frac{1}{\vec{Z}_3} + \frac{1}{\vec{Z}_4}} = 31.4 \angle -87^\circ \text{ [V]}$$

$$\vec{V}_1 = \vec{V}_s + \vec{V}_2 = 25.8 \angle -70.5^\circ \text{ [V]}$$

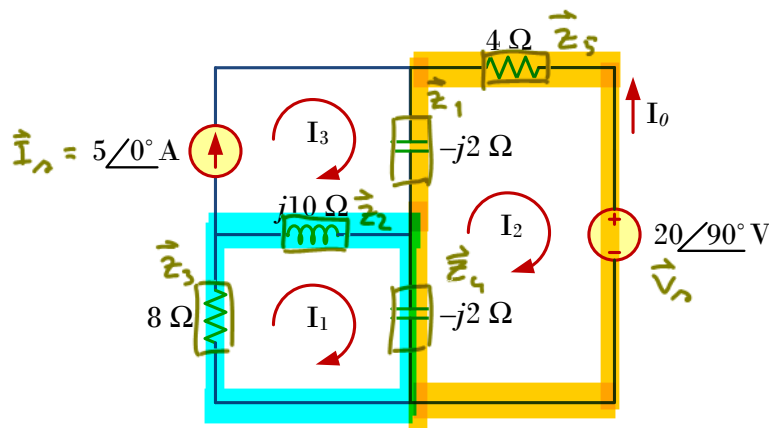EXAMPLE 8.1.6. Determine current I_o in the circuit below using mesh analysis.



$$\vec{V}_s = 20 \angle 90^\circ = 20j \text{ [V]}$$

$$\vec{I}_s = 5 \angle 0^\circ = 5 \text{ [A]}$$

$$\vec{Z}_1 = -j2 \Omega$$

$$\vec{Z}_2 = j10 \Omega$$

$$\vec{Z}_3 = 8 \Omega$$

$$\vec{Z}_4 = -j2 \Omega$$

$$\vec{Z}_5 = 4 \Omega$$

Mesh 3: $\vec{I}_3 = \vec{I}_s$

Mesh 1: $-\vec{I}_1 \vec{Z}_3 - (\vec{I}_1 - \vec{I}_3) \vec{Z}_2 - (\vec{I}_1 - \vec{I}_2) \vec{Z}_4 = 0$

Mesh 2: $-(\vec{I}_2 - \vec{I}_1) \vec{Z}_4 - (\vec{I}_2 - \vec{I}_3) \vec{Z}_1 - \vec{I}_2 \vec{Z}_5 - \vec{V}_s = 0$


$$\Rightarrow \vec{I}_2 = 5 - 3.53j \Rightarrow \vec{I}_o = -\vec{I}_2 = -5 + 3.53j = 6.12 \angle 144.8^\circ$$

EXAMPLE 8.1.7. Find the Thevenin equivalent at terminals $a-b$ of the circuit below.

$\vec{V}_{th} = \vec{V}_{ab} = \vec{V}_{ac} = \sqrt{\frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2}} \vec{V}_s = 47.7 \angle -51.6^\circ$ [V]
 $\vec{V}_{bc} = 0 \times \vec{Z}_3 = 0$
 $\vec{Z}_{th} = \vec{Z}_{ab} = (\vec{Z}_1 \parallel \vec{Z}_2) + \vec{Z}_3 = \frac{\vec{Z}_1 \vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} + \vec{Z}_3 = 12.4 - 3.2j \Omega$

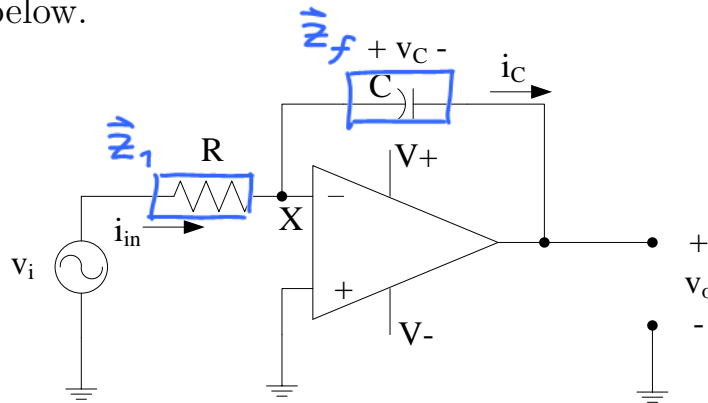EXAMPLE 8.1.8. Op Amp AC Circuits: Find the (closed-loop) gain of the circuit below.

Recall:
 If we write R_1 and R_f instead of \vec{Z}_1 and \vec{Z}_f , then this is an inverting amp. We know that



$$V_o = -\frac{R_f}{R_1} V_i \Leftrightarrow \vec{V}_o = -\frac{\vec{Z}_f}{\vec{Z}_1} \vec{V}_i$$

$$\frac{\vec{V}_o}{\vec{V}_i} = -\frac{\vec{Z}_f}{\vec{Z}_1} = -\frac{j\omega C}{R} = \boxed{j\left(\frac{1}{\omega C R}\right)} = j\left(\frac{1}{(2\pi f) C R}\right) = (1 \angle 90^\circ) \left(\frac{1}{2\pi f R C}\right)$$

In time domain,

$$\vec{V}_i = V_m \angle \phi \Leftrightarrow v_i(t) = V_m \cos(\omega t + \phi)$$

$$\vec{V}_o = (1 \angle 90^\circ) \left(\frac{1}{2\pi f R C}\right) (V_m \angle \phi)$$

$$= \frac{V_m}{2\pi f R C} \angle (90^\circ + \phi) \Leftrightarrow v_o(t) = \frac{V_m}{2\pi f R C} \cos(\omega t + \phi + 90^\circ)$$