


# ECS 203 2015: Exercise 1 Solution

## Instructions

- i. Separate into groups of no more than four persons.
- ii. Only one submission is needed for each group. Late submission will not be accepted.
- iii. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.
- iv. **Do not panic.**

Name	ID
Prapun	555

Consider the circuit below.

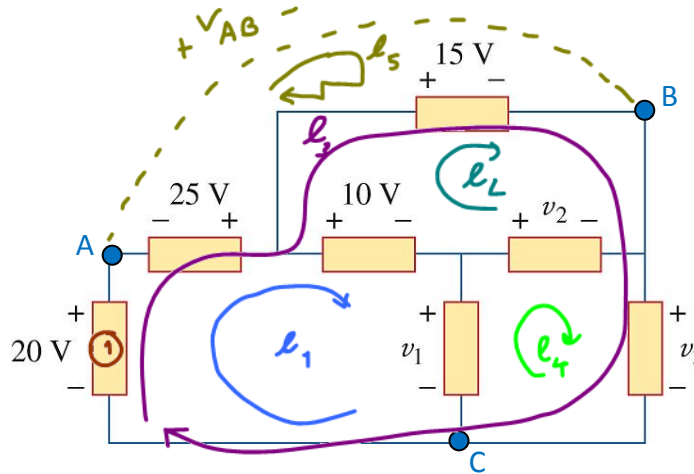

1. Use KVL to obtain  $v_1$ ,  $v_2$ , and  $v_3$ .

For each application of the KVL, make sure that you indicate (draw) the corresponding loop and write down the corresponding equation.

KVL around  $l_1$ :  $20 + 25 - 10 - v_1 = 0 \Rightarrow v_1 = 35V$

KVL around  $l_2$ :  $-15 + v_2 + 10 = 0 \Rightarrow v_2 = 5V$

KVL around  $l_3$ :  $20 + 25 - 15 - v_3 = 0 \Rightarrow v_3 = 30V$

Check:

KVL around  $l_4$ :  $v_1 - v_2 - v_3 = 0 \checkmark$

minor algebraic mistake: -0.1 each

Here, although loop 4 is easier because it involves less elements, we choose to use loop 3 because it does not involve  $v_1$  and  $v_2$ . So, in the case that we found  $v_1$  and/or  $v_2$  incorrectly in the earlier part of the problem, the error won't affect our calculation of  $v_3$  here.

We use loop 4 to double-check our answer here.

2. Find  $V_{AB}$  and  $V_{AC}$ .


KCL around  $l_5$ :

$-V_{AB} + 15 - 25 = 0$

$V_{AB} = -10V$

There are two ways to find  $V_{AC}$ .

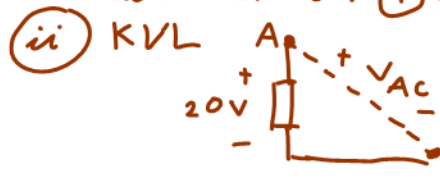- (i)  $V_{AC}$  is the voltage across element ① because node A is the '+' terminal of the '20V' and node C is the '-' terminal of the '20V' across element ①.



$20 - V_{AC} = 0$   
 $V_{AC} = 20V.$

Both techniques give  $V_{AC} = 20V.$