

(a)



The arrow of the current points from the positive to the negative polarity of the voltage.

This conforms with the passive sign convention.

In which case,  $P = IV$ .

$$\text{Power absorbed} = 4 \times 10 = 40 \text{ W}$$

(b)




In this diagram, the arrow of the current points from the negative to the positive polarity of the voltage.

This does not conform with the passive sign convention.

In which case,  $P = -IV$ .

$$\text{Power absorbed} = -2 \times 12 = -24 \text{ W}$$

(c)

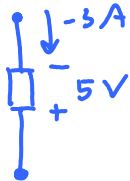



In this diagram, the arrow of the current points from the negative to the positive polarity of the voltage.

This does not conform with the passive sign convention.


In which case,  $P = -IV$ .

$$\text{Power absorbed} = -(-3) \times 5 = 15 \text{ W}$$

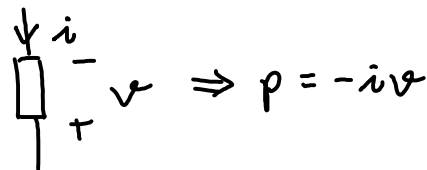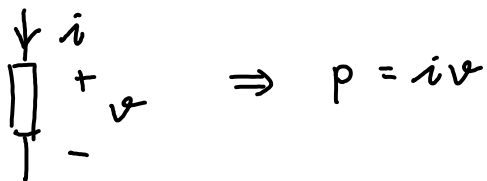We calculate the power using the passive sign convention.




(a)

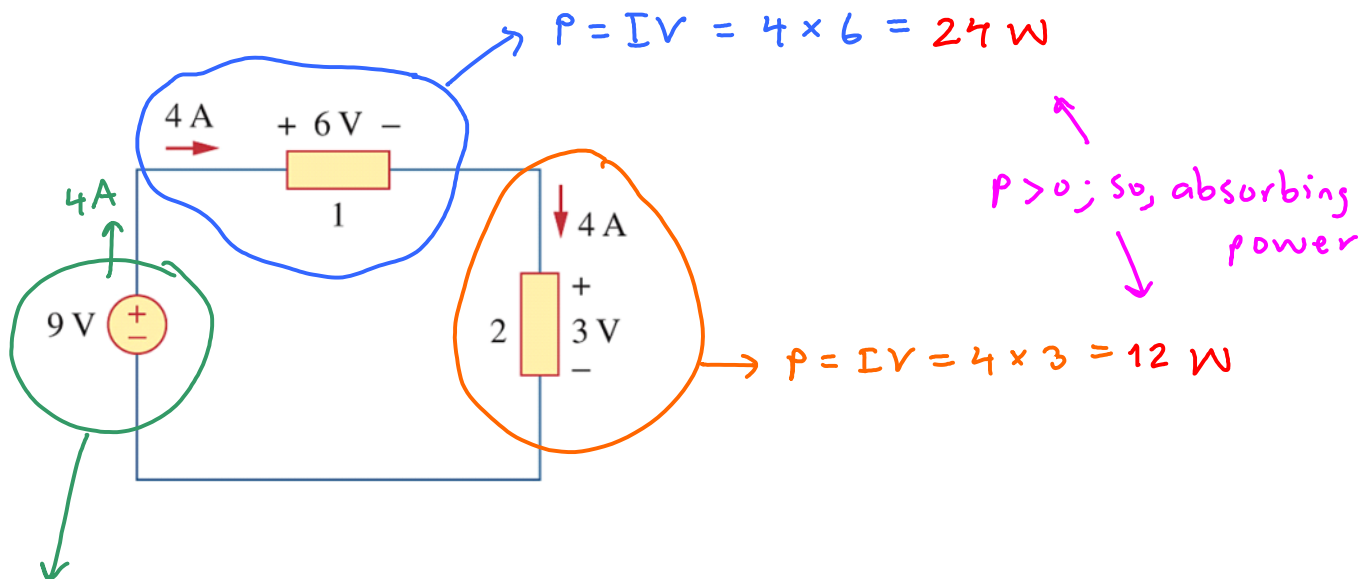


$P = -IV = -4 \times 9 = -36 \text{ W}$   $\leftarrow P < 0$ ; so, supplying power.

Again, the negative sign is here because the current flows from the negative to the positive polarity of the 9V.

(b)

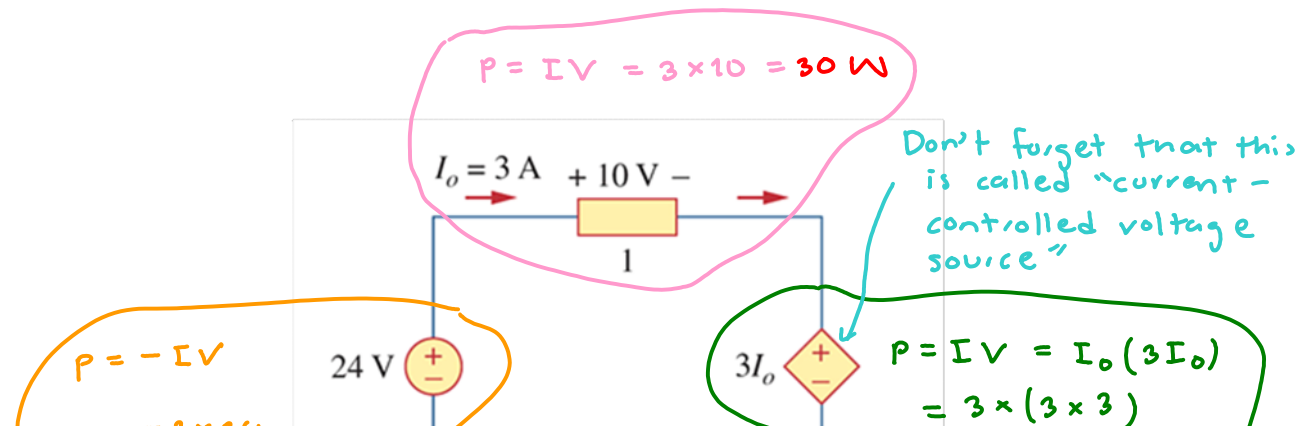

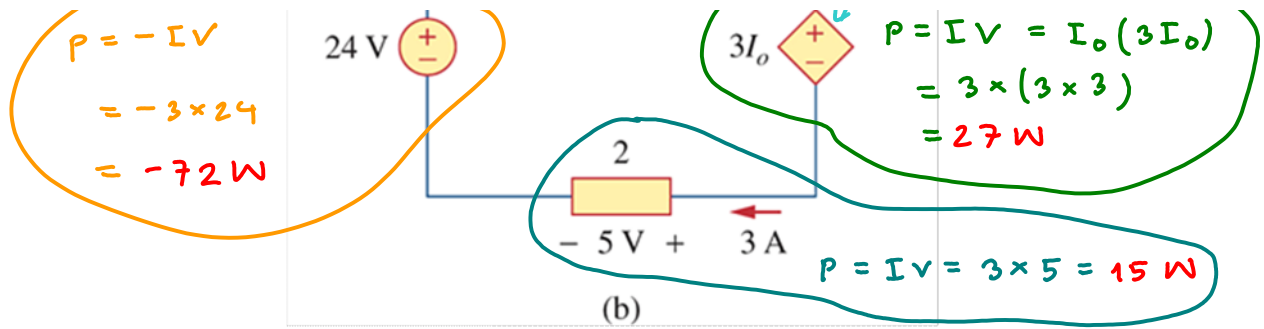

Note that when we add all the powers, we have  $-72 + 30 + 27 + 15 = 0$ .