

Sirindhorn International Institute of Technology  
Thammasat University at Rangsit  
School of Information, Computer and Communication Technology

## ECS 203: Problem Set 1

**Semester/Year:** 2/2014

**Course Title:** Basic Electrical Engineering

**Instructor:** Asst. Prof. Dr. Prapun Suksompong ([prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th))

**Course Web Site:** <http://www2.siiit.tu.ac.th/prapun/ecs203/>

**Due date:** Jan 23, 5 PM

### Instructions

1. Solve all problems. (5 pt)
2. ONE sub-question will be graded (5 pt). Of course, you do not know which part will be selected; so you should work carefully on all of them.
3. Late submission will be heavily penalized.
4. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

### Questions

- 1) [Alexander and Sadiku, 2009, Q1.16] Find the power absorbed by each element in Figure 1. (Note that if the power is actually supplied by the element, then your corresponding answer will be negative.)

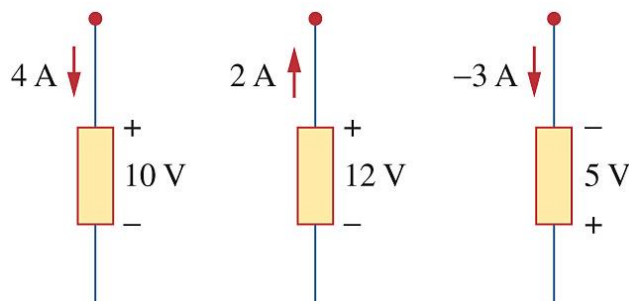


Figure 1

- 2) [Alexander and Sadiku, 2009, Q1.18] Calculate the power absorbed by each element in Figure 2. (Note that if the power is actually supplied by the element, then your corresponding answer will be negative.)

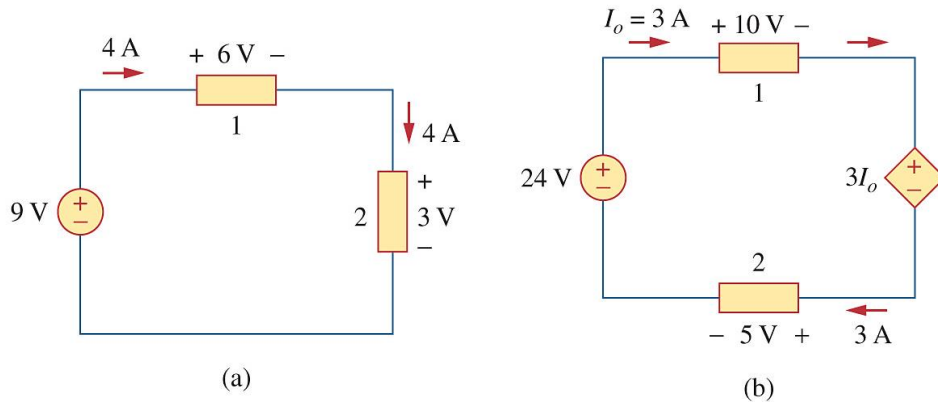


Figure 2

- 3) [Optional. However, see remark below] Play the “Free Energy Game!” on Facebook.

The game is available at <https://apps.facebook.com/freeenergygame/>.

You may play multiple times but record and submit (along with your solutions for the first two questions above) your best End Game Stats. (Screen-capture this as well in case you are asked to show a proof.)

Top five players of our class will get 1 extra credit for this HW.