

Sirindhorn International Institute of Technology
Thammasat University at Rangsit
School of Information, Computer and Communication Technology

ECS 203: Problem Set 12

Semester/Year: 2/2014

Course Title: Basic Electrical Engineering

Instructor: Asst. Prof. Dr. Prapun Suksompong (prapun@siit.tu.ac.th)

Course Web Site: <http://www2.siiit.tu.ac.th/prapun/ecs203/>

Due date: May 1

Instructions

- i. Solve all problems. (5 pt)
- ii. ONE sub-question will be graded (5 pt). Of course, you do not know which part will be selected; so you should work carefully on all of them.
- iii. Late submission will be heavily penalized.
- iv. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.
- v. All phasor should be answered in polar form where the magnitude is positive and the phase is between -180° and 180° .
- vi. All sinusoid should be answered in the cosine form where the amplitude is positive and the phase is between -180° and 180° .

Questions

1. Reconsider Example 7.6.2 in the lecture notes.
 - (a) Find $v_o(t)$ using nodal analysis.
 - (b) Find all mesh currents using mesh analysis and then find $v_o(t)$ from the mesh current(s) and some impedance value(s).
2. Use the superposition theorem to find
 - (a) \mathbf{V}_2 in Example 8.1.6 of the lecture notes
 - (b) \mathbf{I}_o in Example 8.1.7 of the lecture notes

3. [Alexander and Sadiku, 2009, Q11.5] Assuming that $v_s(t) = 16 \cos(2t - 40^\circ)$ V in the circuit shown in Figure 1, find the average power delivered to each of the passive elements.

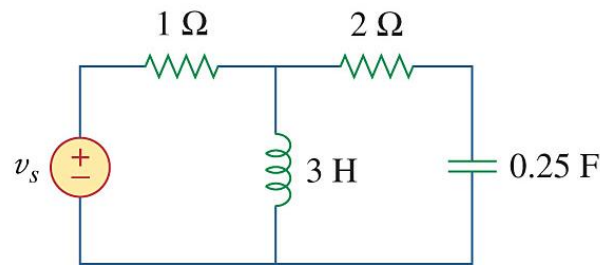


Figure 1

4. [F2010] Consider the circuit below.

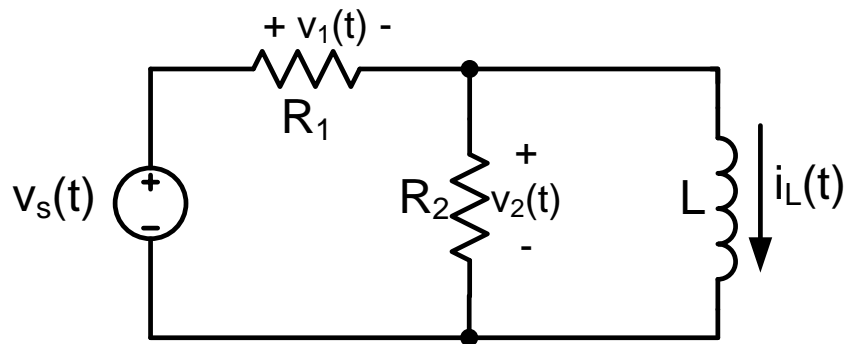


Figure 2

Suppose

$$v_s(t) = 7 \cos(200t + 30^\circ) \text{ V,}$$

$$R_1 = 6 \Omega, R_2 = 4 \Omega, \text{ and } L = 5 \text{ mH.}$$

Remark: Note that this is a continuation of a question from the previous assignments. Find the instantaneous power absorbed by R_1 .

- ~~b.~~ Find the average power absorbed by R_1
- ~~c.~~ Find the average power absorbed by L
- ~~d.~~ Find the average power absorbed by the voltage source.