

The 2mA current source forces clockwise 2mA current through the circuit (which, luckily, is one simple loop) The arrow of  $i$  agrees with the clockwise direction of the forced 2mA current. Hence,  $i = 2\text{mA}$ .  
(not -2mA)

Note that the arrow of  $i$  and the polarity (+, -) of  $v$  conforms with the passive sign convention.

( $\hookrightarrow$  arrow flows from + to -.)


This implies  $p = iv$  and  $v = iR$ .

(not  $p = -iv$ ) (not  $v = -iR$ )

Here,  $i = 2\text{mA}$  and  $R = 10\text{ k}\Omega$ .

Therefore,  $v = iR = 2\text{mA} \times 10\text{ k}\Omega = 20\text{ V}$  and  
 $p = iv = 2\text{mA} \times 20\text{ V} = 40\text{ mW}$ .

(a)

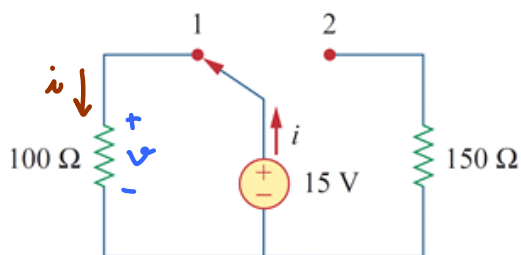


We need to apply Ohm's law.

First, note that the  $i$  that we draw near the resistor is the same as the  $i$  that is coming out of the voltage source.

We also add the voltage  $v$  across the resistor to use with the Ohm's law. Note that  $v$  is connected directly to the 15V source and their polarity matched. Therefore,  $v = 15\text{ V}$ .

The arrow of  $i$  and polarity of  $v$  satisfies the passive sign convention. Hence,  $v = iR$ . So,  $i = \frac{v}{R} = \frac{15\text{ V}}{100\ \Omega} = 0.15\text{ A}$   
or  
 $150\text{ mA}$ .


(b)

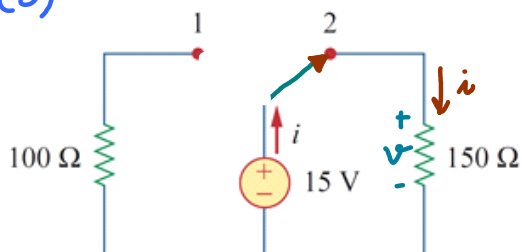

The same reasoning in part (a) also applies to this part except that now the current  $i$  is flowing through a new loop in the clockwise direction

$$i = \frac{v}{R} = \frac{15\text{ V}}{150\ \Omega} = 0.1\text{ A}$$

or  
 $100\text{ mA}$ .

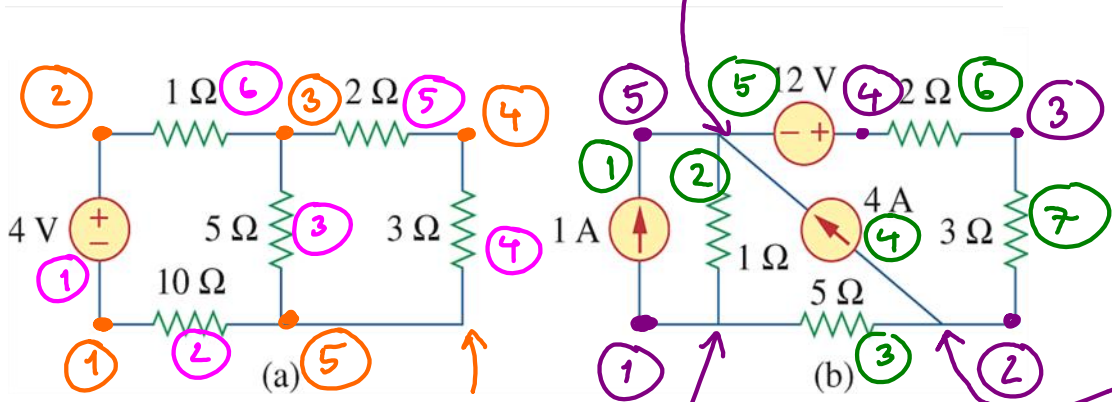


✱ branches = 6  
✱ nodes = 5

✱ branches = 7  
✱ nodes = 5

same as node 5

same as node 2

same as node 1

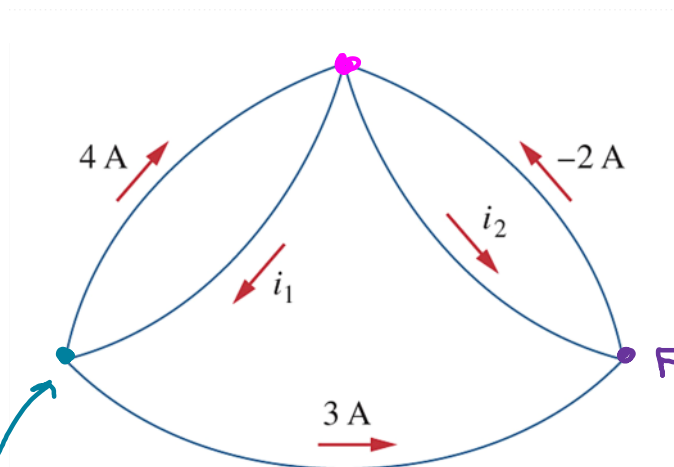

Applying KCL at this node, we have

$$4 + (-i_1) + 3 = 0$$

$$i_1 = 7 A$$

Applying KCL at this node, we have

$$-2 - i_2 - 3 = 0$$

$$i_2 = -5 A$$

We may check the answers by applying KCL at the top node:


$$-4 + i_1 + i_2 - (-2) = 0$$

$$-4 + 7 - 5 + 2 = 0 \quad \checkmark$$

Use  $i_1, i_2$  that we know.

( $\sum v = 0$ )

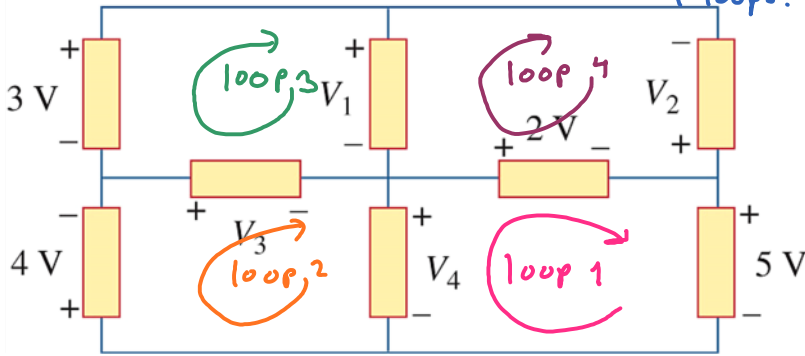As hinted, we need to apply KVL.  
Because there are four unknowns, we need at least 4 loops.



We will try to start with a loop that involves minimum of unknown variables

So, we start with "loop 1":

(only one unknown variable)

$$+V_4 - 2 - 5 = 0$$

With respect to the loop direction, we move from the "-" to "+" terminals of  $V_4$ . So, we gain  $V_4$  by moving in such direction

With respect to the loop direction, we move from the "+" to the "-" terminals of the 2V. So, we lose 2V by moving in such direction.

$$V_4 = 7V$$

Because we already know  $V_4$ , "loop 2" now has only one unknown variable ( $V_3$ ):

$$-4 - V_3 - V_4 = 0$$

$$V_3 = -4 - V_4 = -11V$$

Similarly, when we know  $V_3$ , "loop 3" has only one unknown variable ( $V_1$ ):

$$+3 - V_1 + V_3 = 0$$

$$-11V$$

$$V_1 = 3 - 11 = -8V$$

Finally, from "loop 4":

$$+V_1 + V_2 + 2 = 0$$

$$V_2 = 8 - 2 = 6V$$

$V_1 = -8V$
$V_2 = 6V$
$V_3 = -11V$
$V_4 = 7V$