

Sirindhorn International Institute of Technology  
Thammasat University at Rangsit  
School of Information, Computer and Communication Technology

## ECS 203: Problem Set 4

**Semester/Year:** 2/2014

**Course Title:** Basic Electrical Engineering

**Instructor:** Asst. Prof. Dr. Prapun Suksompong ([prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th))

**Course Web Site:** <http://www2.siiit.tu.ac.th/prapun/ecs203/>

**Due date:** Feb 13, 5 PM

### Instructions

1. Solve all problems. (5 pt)
2. ONE sub-question will be graded (5 pt). Of course, you do not know which part will be selected; so you should work carefully on all of them.
3. Late submission will be heavily penalized.
4. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

### Questions

- 1) [Alexander and Sadiku, 2009, Q3.18] Determine the node voltages in the circuit in Figure 1 using nodal analysis.

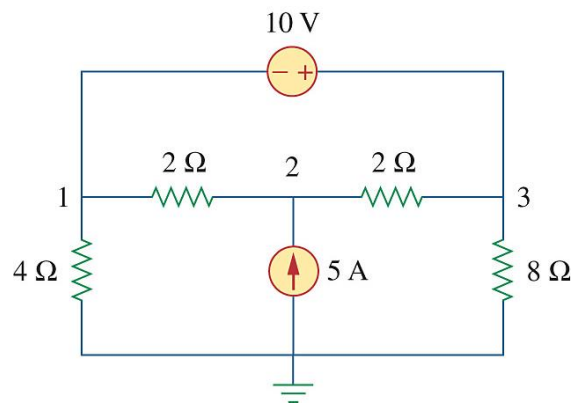


Figure 1

- 2) [Alexander and Sadiku, 2009, Q3.2] For the circuit in Figure 2, obtain  $v_1$  and  $v_2$  using nodal analysis.

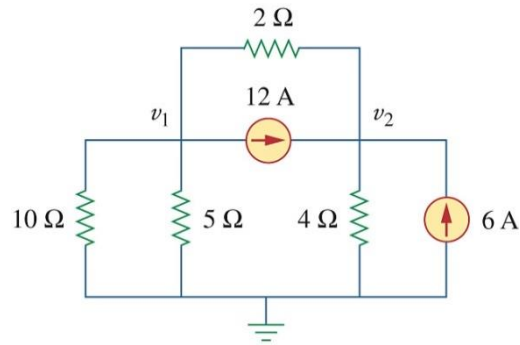


Figure 2

- 3) [Alexander and Sadiku, 2009, Q3.6] Use nodal analysis to obtain  $v_0$  in the circuit in Figure 3.

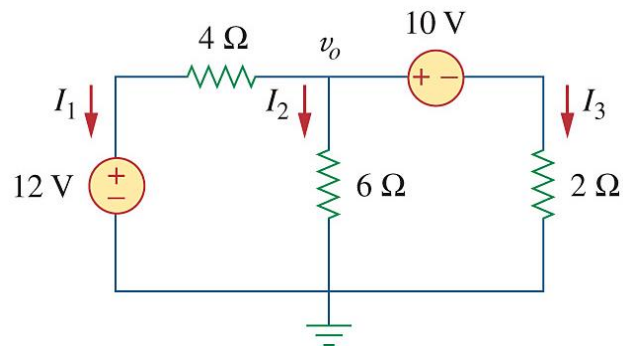


Figure 3

- 4) [Alexander and Sadiku, 2009, Q3.41] Apply mesh analysis to find  $i$  in Figure 4.

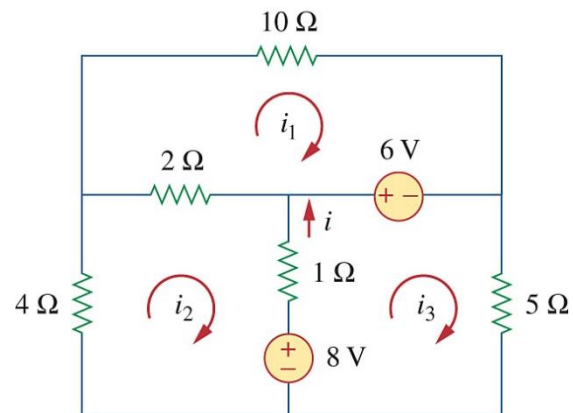


Figure 4

- 5) [Alexander and Sadiku, 2009, Q3.43] Use mesh analysis to find  $v_{ab}$  and  $i_o$  in the circuit in Figure 5.

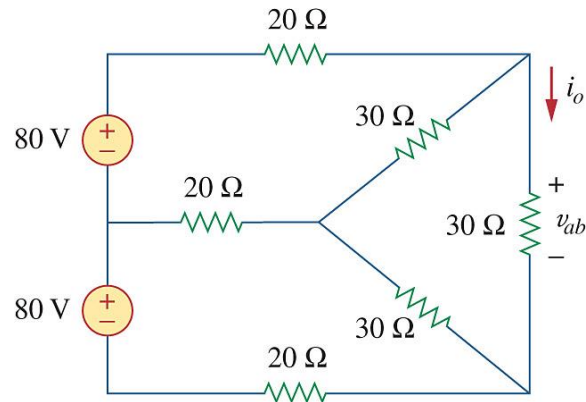


Figure 5

- 6) [Alexander and Sadiku, 2009, Q3.46] Use mesh analysis to solve for the mesh currents in Figure 6.

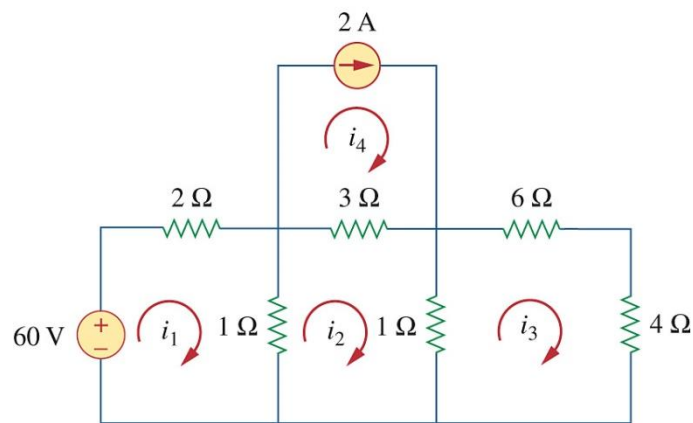


Figure 6