

Method 1:

From experiment 1,  $V_s^{(1)} = 12 \rightarrow V_o^{(1)} = 4$


For experiment 2,  $V_o^{(2)}$  becomes  $3 \times V_o^{(1)}$   
 so,  $V_s^{(2)}$  should be  $3 \times V_s^{(1)} = 48 \text{ V}$

For experiment 3,  $V_s^{(3)}$  becomes  $\frac{1}{12} V_s^{(1)}$   
 so,  $V_o^{(3)}$  should be  $\frac{1}{12} \times V_o^{(1)} = \frac{1}{12} \times 4 = \frac{1}{3} \text{ V}$

For experiment 4,  $V_o^{(4)}$  becomes  $-\frac{1}{2} V_o^{(1)}$   
 so,  $V_s^{(4)}$  should be  $-\frac{1}{2} V_s^{(1)} = -\frac{1}{2} \times 12 = -6 \text{ V}$

Method 2:

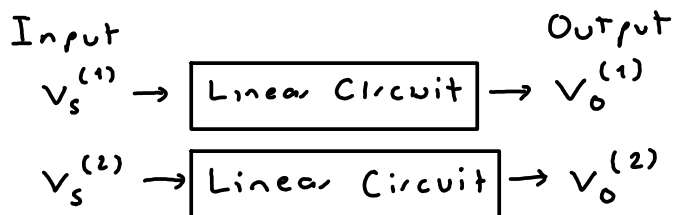Consider two experiments on the same linear circuit:



If we write  $V_s^{(2)} = \frac{V_s^{(2)}}{V_s^{(1)}} \times V_s^{(1)}$ ,

then

$V_o^{(2)}$  should be  $\frac{V_s^{(2)}}{V_s^{(1)}} \times V_o^{(1)}$  (use same factor)

Hence,  $\frac{V_o^{(2)}}{V_s^{(2)}} = \frac{V_o^{(1)}}{V_s^{(1)}} = \frac{V_o^{(3)}}{V_s^{(3)}} = \frac{V_o^{(4)}}{V_s^{(4)}}$  (By similar reasoning.)

In other words,  $\frac{V_o}{V_s}$  should be constant for all experiments.

From experiment 1, we have  $\frac{V_o}{V_s} = \frac{4}{12} = \frac{1}{3}$ .

From experiment 1, we have  $\frac{V_o}{V_s} = \frac{4}{12} = \frac{1}{3}$ .

For experiment 2, we should have  $\frac{V_o}{V_s} = \frac{16}{V_s} = \frac{1}{3} \Rightarrow V_s = 3 \times 16 = \boxed{48 \text{ V}}$

For experiment 3, we should have  $\frac{V_o}{V_s} = \frac{V_o}{1} = \frac{1}{3} \Rightarrow V_o = \boxed{\frac{1}{3} \text{ V}}$


For experiment 4, we should have  $\frac{V_o}{V_s} = \frac{-2}{V_s} = \frac{1}{3} \Rightarrow V_s = -2 \times 3 = \boxed{-6 \text{ V}}$

[Alexander and Sadiku, 2009, Q4.8]: Superposition; Two Voltage Sources


Monday, July 1, 2013 3:56 PM

We will activate one source at a time

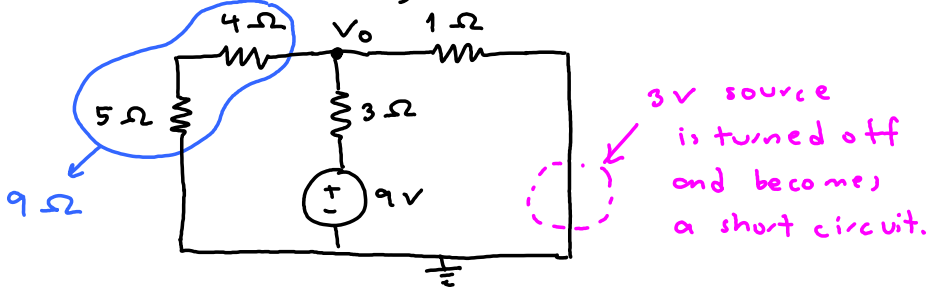a) When the 9V is on, the circuit becomes



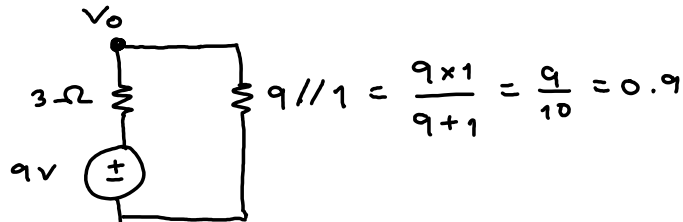
Note that the 9Ω and 1Ω are in parallel. Hence, we have




By the voltage divider formula,  $V_0 = \frac{0.9}{3 + 0.9} \times 9 = \frac{0.9}{3.9} \times 9 = \frac{27}{13} \text{ V}$

Refer to this by  $V_0^{(a)}$

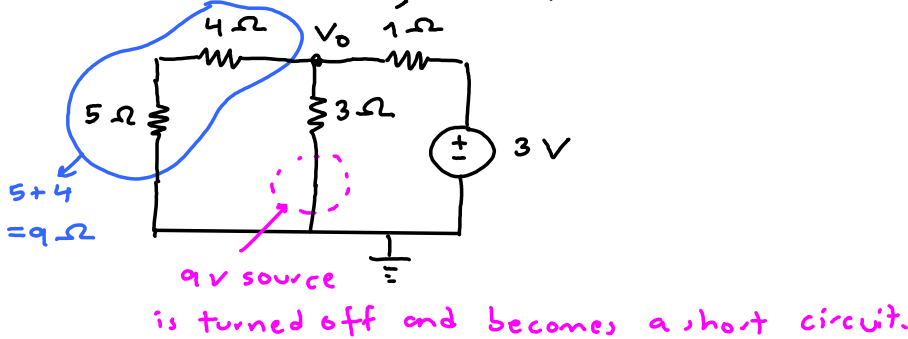b) When the 3V is on, the circuit becomes



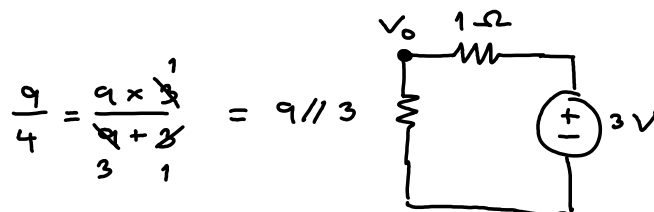Note that the 9Ω and 3Ω are in parallel. Hence, we have




By the voltage divider formula,  $V_0 = \frac{9}{9 + 4} \times 3 = \frac{9}{13} \times 3 = \frac{27}{13} \text{ V}$

By the voltage divider formula,  $V_o = \frac{\frac{9}{4}}{\frac{9}{4} + 1} \times 3 = \frac{9}{9+4} \times 3 = \frac{27}{13} \text{ V}$


Refer to this by  $V_o^{(b)}$ .

c) By superposition theorem,  $V_o = V_o^{(a)} + V_o^{(b)} = \frac{27}{13} + \frac{27}{13} = \frac{54}{13} \text{ V} \approx 4.154 \text{ V}$


a) When only  $4A$  is on:

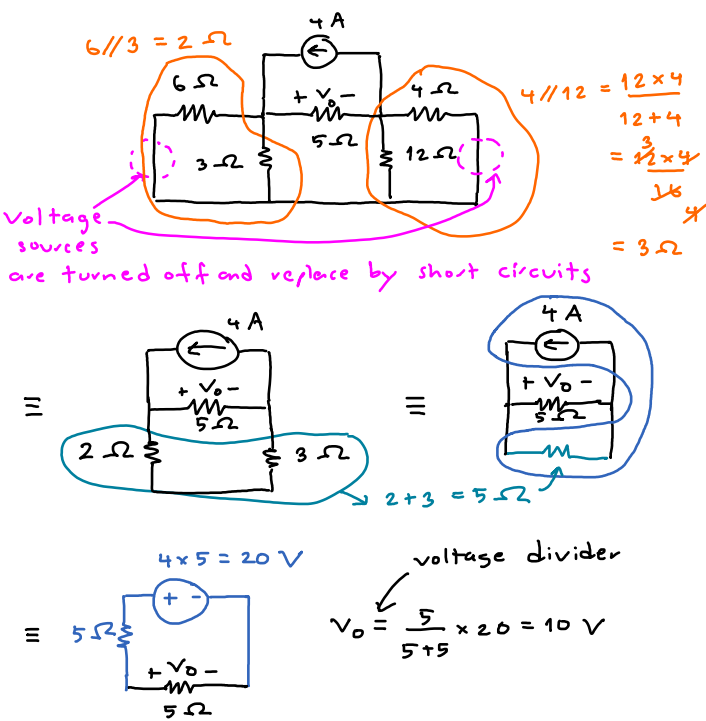

b) When only  $24V$  is on,

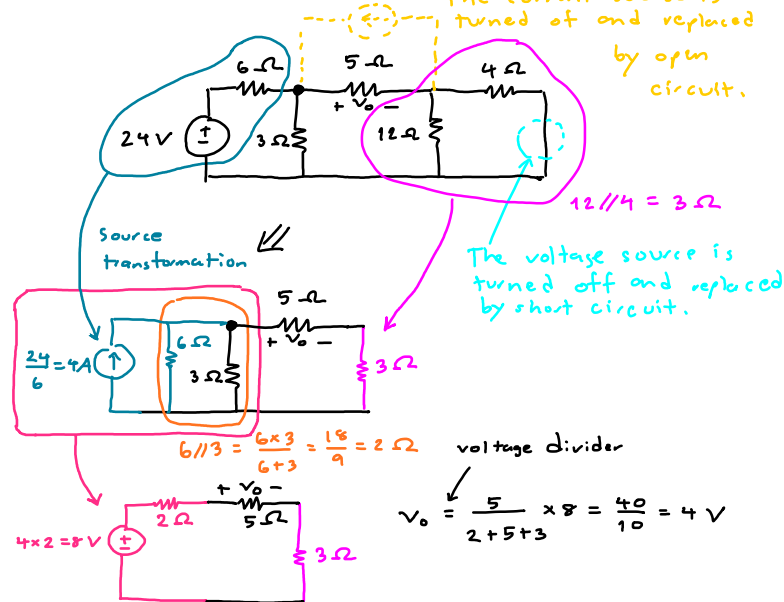

c) When only  $38V$  is on,

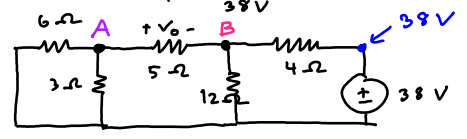

Here, let's try nodal analysis:

$$\begin{aligned}
 \text{KCL @ A: } & \frac{V_A}{6} + \frac{V_A}{3} + \frac{V_A - V_B}{5} = 0 \\
 \text{KCL @ B: } & \frac{V_B - V_A}{5} + \frac{V_B}{12} + \frac{V_B - 38}{4} = 0
 \end{aligned}
 \Rightarrow \begin{cases} V_A = \frac{57}{10} \\ V_B = \frac{397}{20} \end{cases}$$

$$\Rightarrow V_0 = V_A - V_B = \frac{57}{10} - \frac{397}{20} = -\frac{57}{4} V \approx -14.25 V$$

d) By superposition theorem,

$$V_0 = 10 + 4 + (-14.25) = -0.25 V = \boxed{-250 mV}$$


[Alexander and Sadiku, 2009, Q4.27]: Source Transformation; Two Voltage Sources and One Current Source Transformation; Two Voltage Sources and One Current Source

Monday, July 1, 2013 3:56 PM


In this class, when possible, we will try to solve any problem that requires the use of source transformation by successive applications of

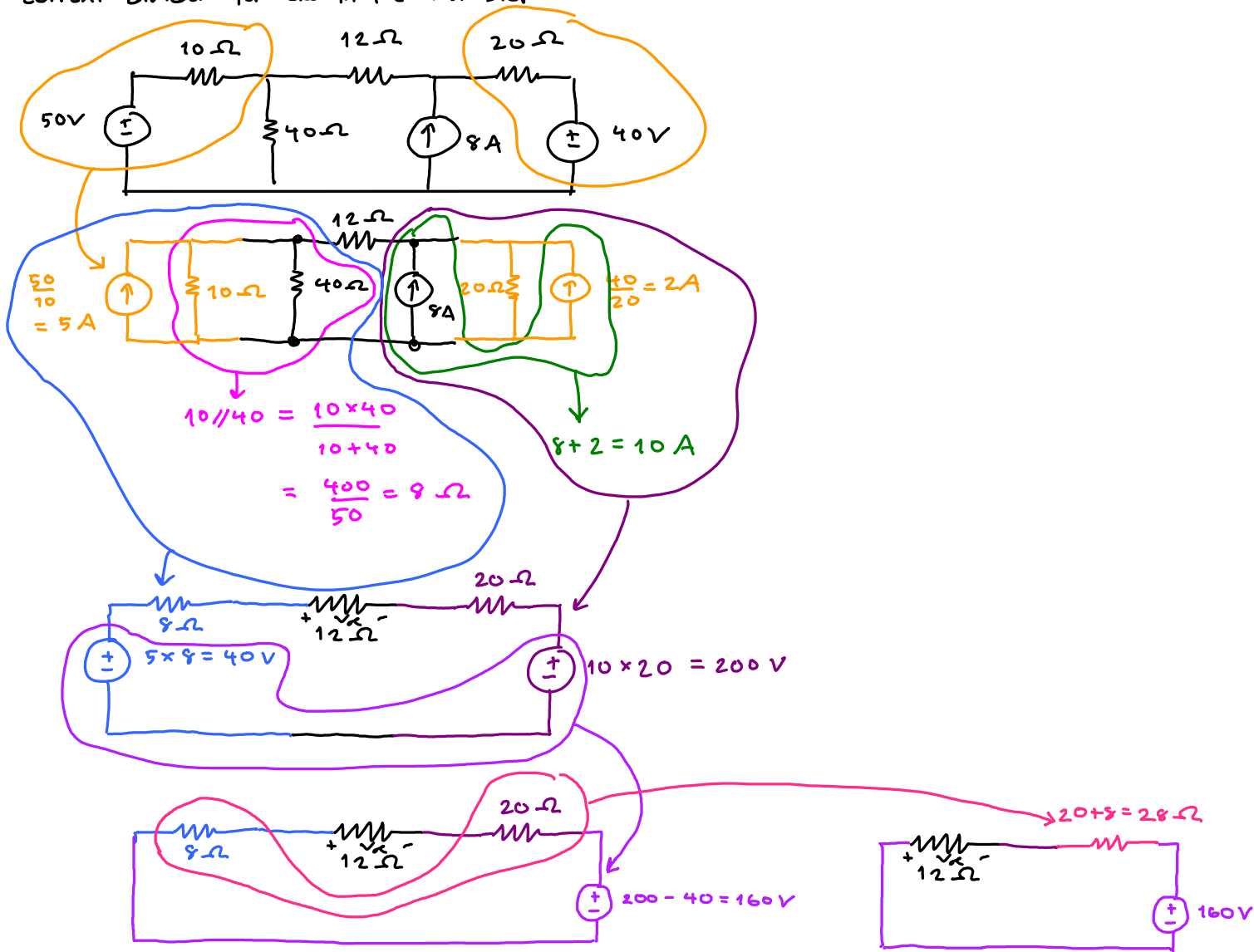- 1) source transformations
- 2) resistor combination(s) and/or source combination(s)

The voltage and/or the current of interest can be found by applying the voltage or current divider formula in the last step.



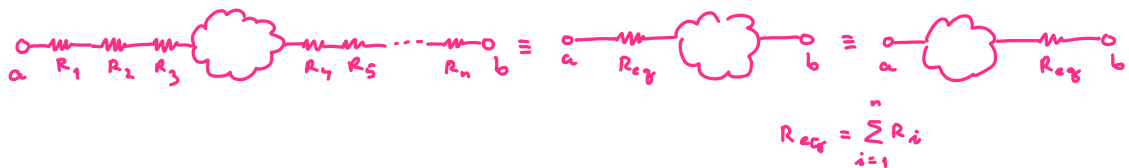
To see why we can combine the 8Ω and 20Ω, recall our generalization of the combination of resistors in series:



Here, terminals a-b are across the 12Ω. The 160V voltage source is the

$$\sum_{i=1}^n$$

Here, terminals a-b are across the  $12\ \Omega$ . The  $160\text{V}$  voltage source is the  in the generalization above. Therefore, although the  $8\ \Omega$  and  $20\ \Omega$  are not connected directly in series, they are "in series" from the point of view of terminals a-b.

Finally, by the voltage divider formulae,  $V_x = - \frac{12}{12+28} \times 160 = \boxed{-48\ \text{V}}$

[Alexander and Sadiku, 2009, Q4.22]: Source Transformation

Monday, July 1, 2013 4:02 PM

In this class, when possible, we will try to solve any problem that requires the use of source transformation by successive applications of

- 1) source transformations
- 2) resistor combinations and/or source combinations

The voltage and/or the current of interest can be found by applying the voltage or current divider formula in the last step.

