

Sirindhorn International Institute of Technology  
Thammasat University at Rangsit  
School of Information, Computer and Communication Technology

## ECS 203: Problem Set 5

**Semester/Year:** 2/2014

**Course Title:** Basic Electrical Engineering

**Instructor:** Asst. Prof. Dr. Prapun Suksompong ([prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th))

**Course Web Site:** <http://www2.siiit.tu.ac.th/prapun/ecs203/>

**Due date:** Feb 20, 5 PM

### Instructions

1. Solve all problems. (5 pt)
2. ONE sub-question will be graded (5 pt). Of course, you do not know which part will be selected; so you should work carefully on all of them.
3. Late submission will be heavily penalized.
4. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

### Questions

- 1) [Alexander and Sadiku, 2009, Q4.6] For the linear circuit shown in Figure 1, use linearity to complete the following table.

Experiment	$V_s$	$V_o$
1	12 V	4 V
2		16 V
3	1 V	
4		-2 V

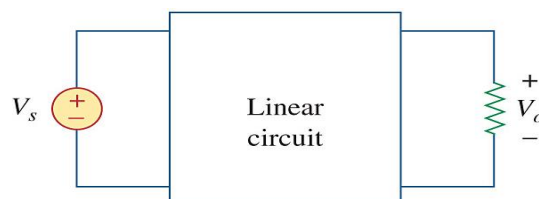


Figure 1

- 2) [Alexander and Sadiku, 2009, Q4.8] Using superposition, find  $V_o$  in the circuit of Figure 2.

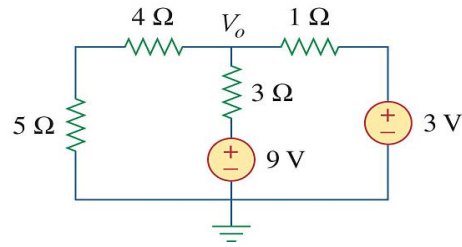


Figure 2

- 3) [Alexander and Sadiku, 2009, Q4.12] Determine  $v_o$  in the circuit in Figure 3 using the superposition principle.

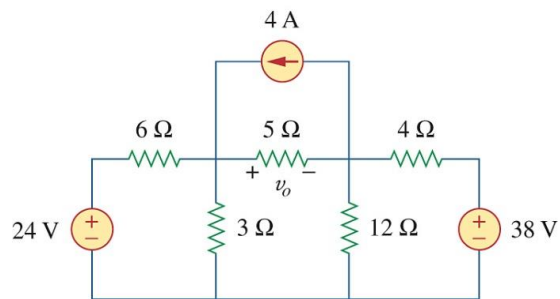


Figure 3

- 4) [Alexander and Sadiku, 2009, Q4.27] Apply **source transformation** to find  $v_x$  in the circuit of Figure 4.

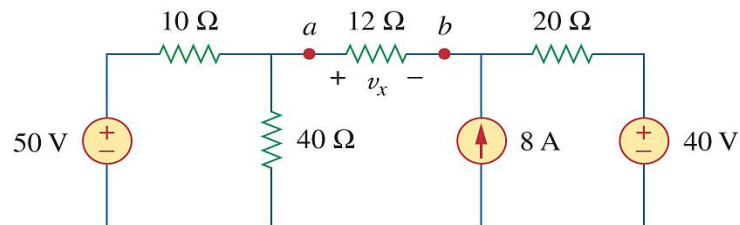


Figure 4

- 5) [Alexander and Sadiku, 2009, Q4.22] For the circuit in Figure 5, use **source transformation** to find  $i$ .

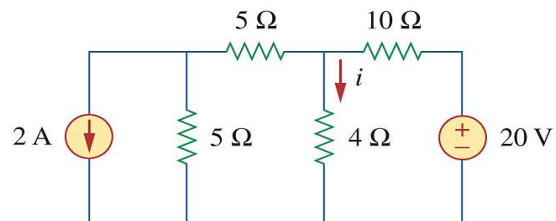


Figure 5