


In class, we have seen one important fact :

To maximize the power transfer to the resistive load, the load's resistance must be the same as R_{TH} from the thevenin equivalent circuit (wrt. the load's two terminals).

Under such load, the corresponding power delivered to the load is $\frac{V_{TH}^2}{4R_{TH}}$.


so, our first step is to find R_{TH} and V_{TH}

R_{TH} :

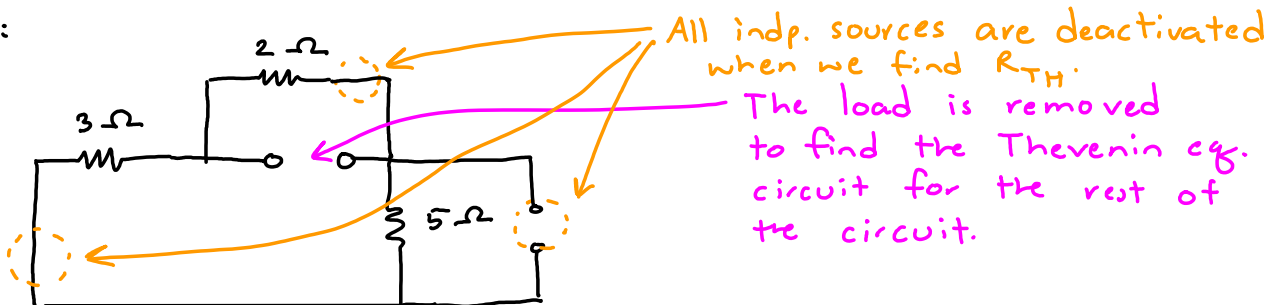


$$R_{TH} = 2 // (3 + 5) = 2 // 8 = \frac{2 \times 8}{10} = 1.6 \Omega$$

V_{TH} :

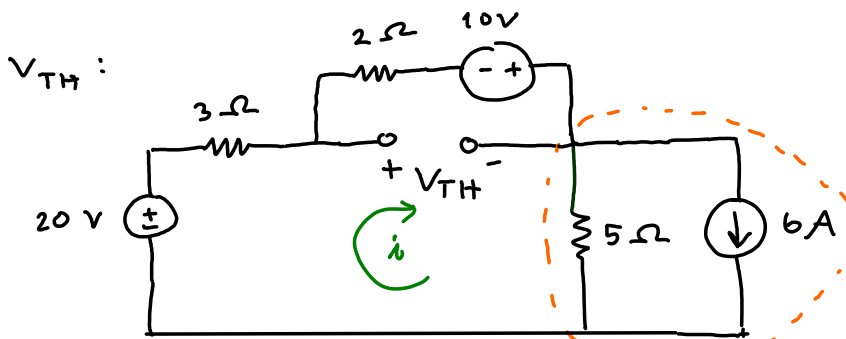

V_{TH} :

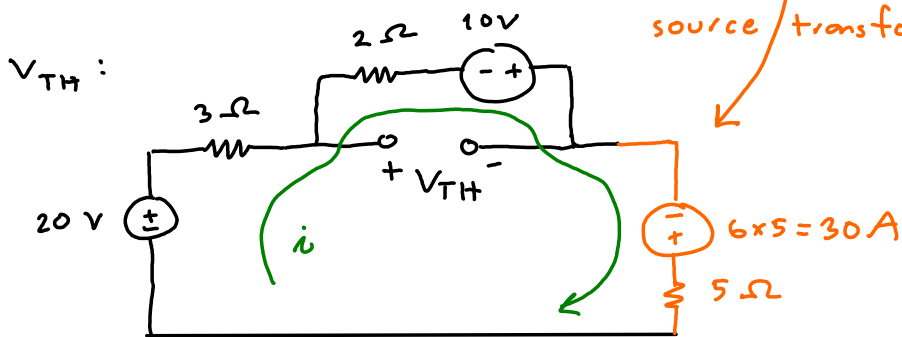

$$i = \frac{20 + 10 + 30}{3 + 2 + 5} = 6 A$$

To see this, use KVL around this single loop in the i direction (clockwise):

$$20 - 3i - 2i + 10 + 30 - 5i = 0$$

$$i = \frac{20 + 10 + 30}{3 + 2 + 5} = 6 \text{ A} \leftarrow$$

in the i direction (clockwise):

$$20 - 3i - 2i + 10 + 30 - 5i = 0$$


$$20 + 10 + 30 = (3 + 2 + 5)i$$

$$V_{TH} = -10 + 2 \times 6 = 2 \text{ V} \leftarrow$$


To see this, use KVL around the upper (virtual) loop:

$$-i \times 2 + 10 + V_{TH} = 0$$
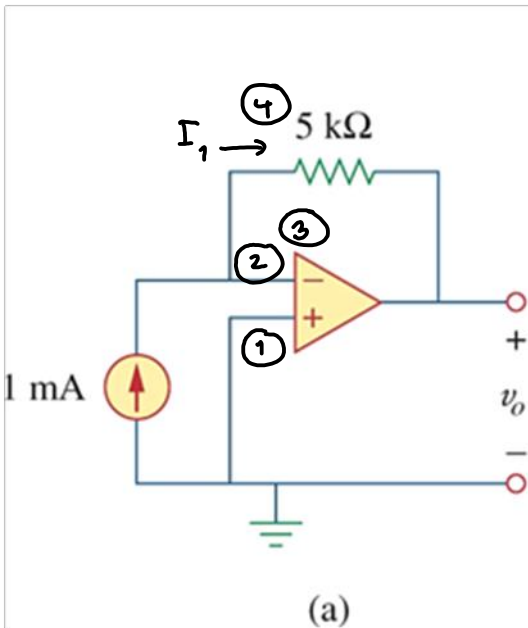
$$\text{So, max power} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{2^2}{4 \times 1.6} = \frac{10}{16} = \boxed{\frac{5}{8} \text{ W}} \approx 0.625 \text{ W}$$



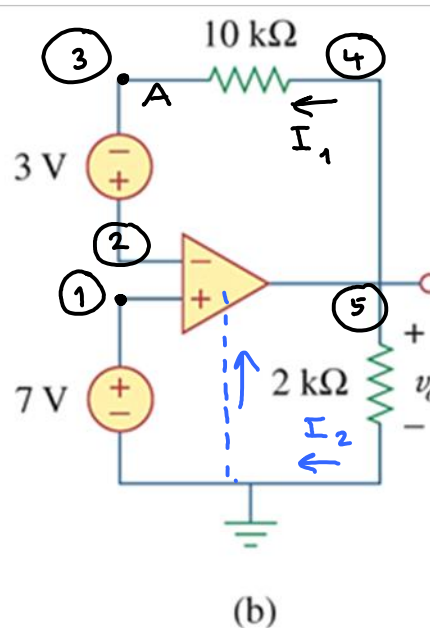- ① $v_+ = 0\text{ V}$ because it is connected to the ground.
- ② $v_- = v_+ = 0\text{ V}$ by Rule #2
- ③ $i_- = 0\text{ A}$ by Rule #1
- ④ $I_1 = 1\text{ mA}$ because $i_- = 0$.
- ⑤ $v_o = v_- - I_1 \times 5\text{ k}$
 $= 0 - 1\text{ mA} \times 5\text{ k}\Omega$
 $= \boxed{-5\text{ V}}$




- ① $v_+ = 7\text{ V}$.
- ② $v_- = v_+ = 7\text{ V}$ by Rule #2.
- ③ $v_- - v_A = 3\text{ V}$
 $v_A = v_- - 3\text{ V} = 7\text{ V} - 3\text{ V} = 4\text{ V}$
- ④ $I_1 = i_- = 0$ by Rule #1
- ⑤ $v_o = v_A + I_1 \times 10\text{ k} = v_A + 0 = v_A$
 $= \boxed{4\text{ V}}$

Note: It is tempting to say

$$I_2 \approx i_+ = 0 \text{ by Rule \#1 and hence } v_o = 0 + I_2 \times 2\text{ k}\Omega = 0 + 0 = 0$$

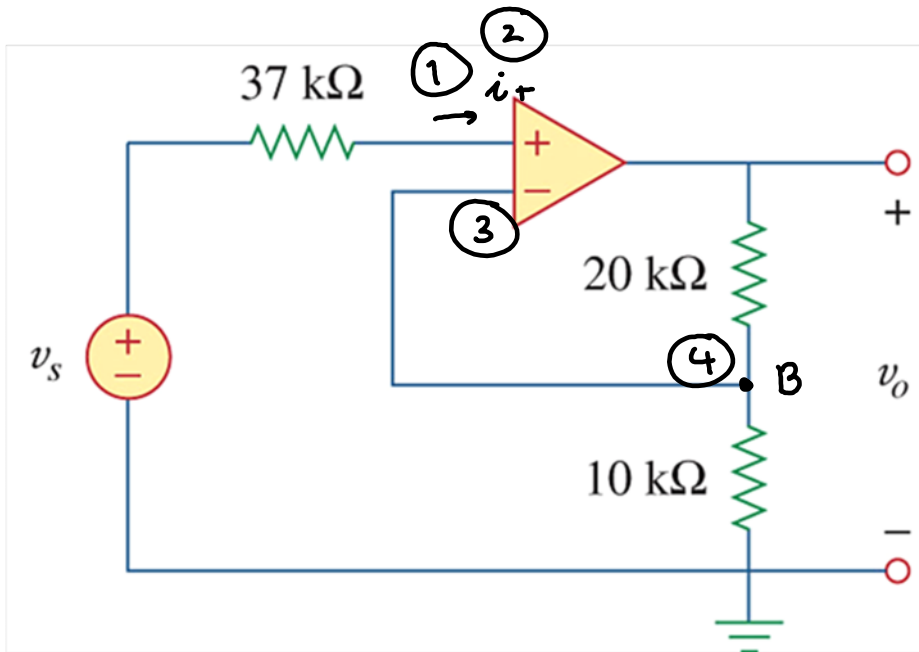This is not true because I_2 can still flow via the hidden connection into the op-amp.



- ① $i_+ = 0$ by Rule #1
- ② $v_+ = v_s - i_+ \times 37 \text{ k}\Omega = v_s - 0 = v_s$
- ③ $v_- = v_+ = v_s$ by Rule #2
- ④ KCL at B gives

$$\frac{v_B - v_o}{20 \text{ k}} + \overset{\downarrow}{i_-} + \frac{v_B}{10 \text{ k}} = 0$$

by Rule #1

$v_B = v_- = v_s$ by ③

$$\frac{v_B}{20 \text{ k}} + \frac{v_B}{10 \text{ k}} = \frac{v_o}{20 \text{ k}}$$

$$v_B + 2v_B = v_o$$

$$v_B = \frac{1}{3} v_o$$

$$\therefore v_o = \frac{1}{3} v_o$$

Alternatively, because $i_- = 0$, the relationship between v_B and v_o is given by voltage divider formula

$$v_B = \frac{10 \text{ k}}{20 \text{ k} + 10 \text{ k}} v_o$$


\therefore

$$v_B = \frac{1}{3} v_0$$

$$v_D = \frac{1}{3} v_0$$

$$\frac{v_0}{v_s} = 3$$

$$v_B = \frac{10k}{20k+10k} v_0$$

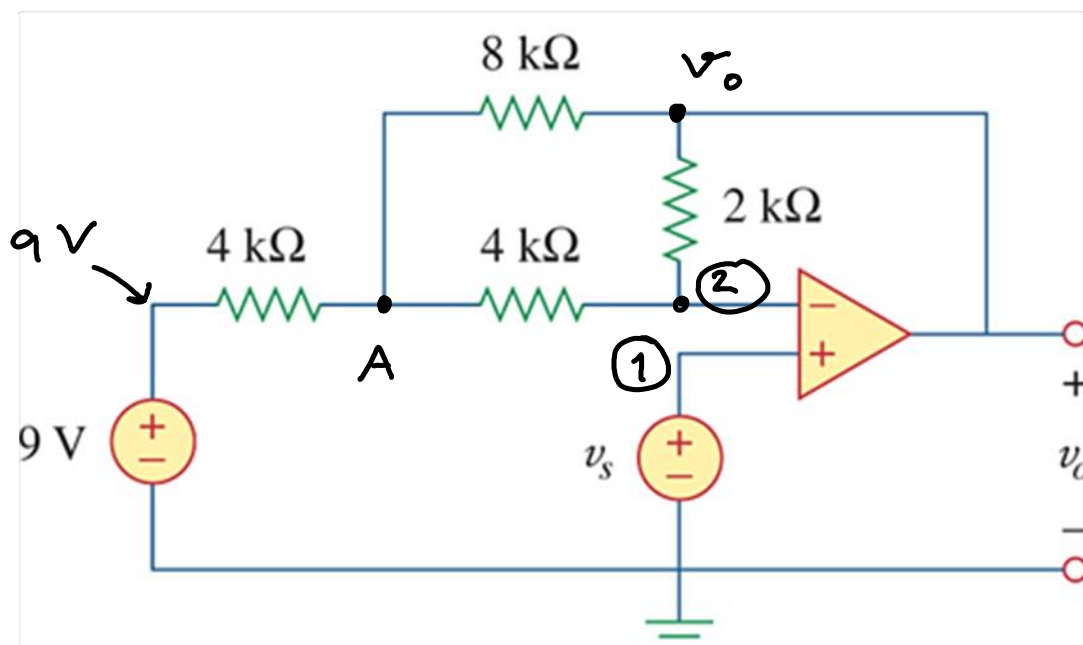

① $v_+ = v_-$

② $v_- = v_+ = v_-$ by Rule #2.

③ At A $\frac{v_A - 9}{4} + \frac{v_A - v_o}{8} + \frac{v_A - v_s}{4} = 0$

At (-) $\frac{v_- - v_A}{4} + \frac{v_- - v_o}{2} = 0$

$\Rightarrow v_A = \frac{7}{11} v_-$

$v_o = \frac{13}{11} v_- - \frac{18}{11}$

If $v_- = 0$, we have

$v_o = -\frac{18}{11} \text{ V}$

[Alexander and Sadiku, 2009, Q5.37]

Monday, July 1, 2013 4:02 PM

$$v_o = - \left(\frac{30}{10} \times 1 + \frac{30}{20} \times 2 + \frac{30}{30} \times (-3) \right) = \boxed{-3V}$$

(This is a summing amplifier.)