

ECS 203: Problem Set 8

Semester/Year: 2/2014

Course Title: Basic Electrical Engineering

Instructor: Asst. Prof. Dr. Prapun Suksompong (prapun@siit.tu.ac.th)

Course Web Site: <http://www2.siiit.tu.ac.th/prapun/ecs203/>

Due date: March 27

Questions

- 1) [Alexander and Sadiku, 2009, Q5.41] An averaging amplifier is a summing amplifier that provides an output equal to the average of the inputs. By using proper input and feedback resistor values, one can get

$$-v_o = \frac{1}{4}(v_1 + v_2 + v_3 + v_4)$$

Using a feedback resistor of 10 k Ω , **design** an averaging amplifier with four inputs.

- 2) [Alexander and Sadiku, 2009, Q5.47] The circuit in Figure 1 is for a difference amplifier. Find v_o given that $v_1 = 1\text{V}$ and $v_2 = 2\text{V}$

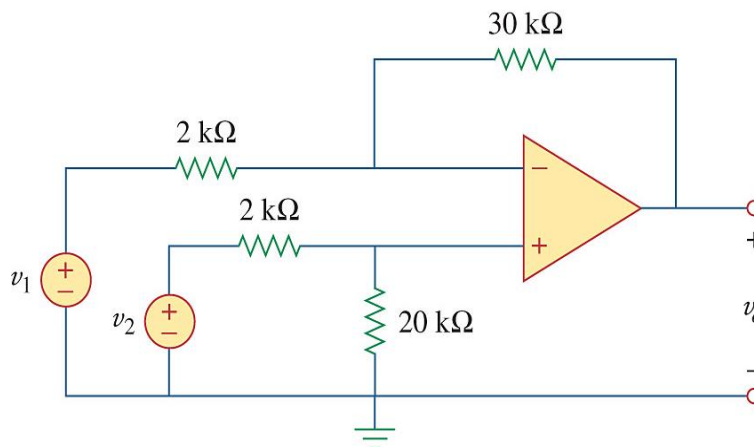


Figure 1

- 3) [Alexander and Sadiku, 2009, Q5.29] Determine the voltage gain v_o/v_i of the op amp circuit in Figure 2.

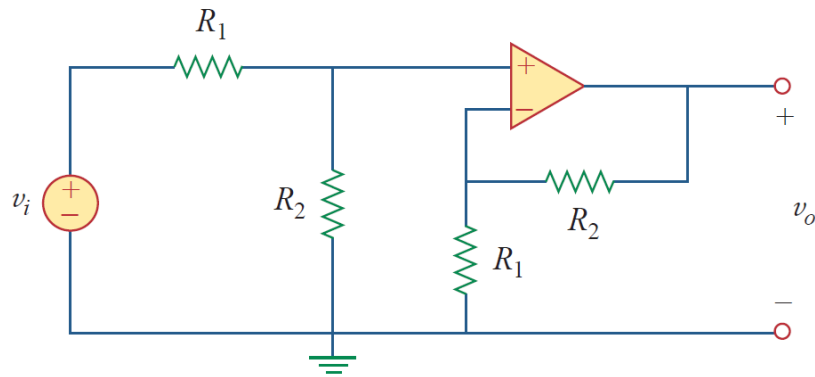


Figure 2

- 4) Use superposition theorem to derive the relation $v_o = -Av_1 + \frac{1+A}{1+B}v_2$ for the difference amplifier on page 70 of the lecture note.
- 5) [Alexander and Sadiku, 2009, Q5.57] Find v_o in the op amp circuit of Figure 3.

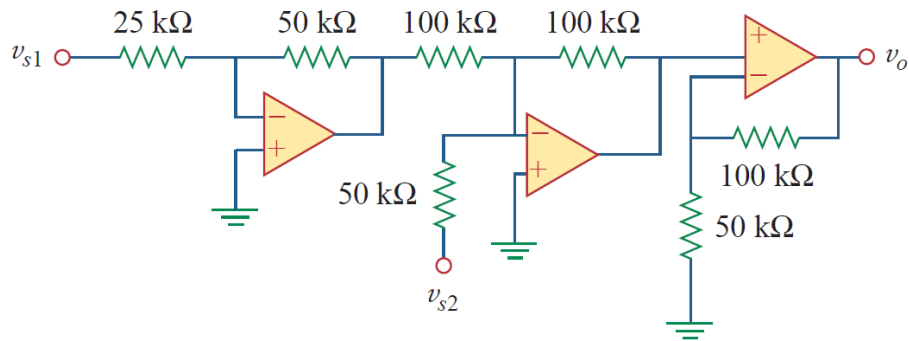


Figure 3

- 6) [Alexander and Sadiku, 2009, Q5.49] Design a circuit to amplify the difference between two inputs by 2.
- Use only one op amp.
 - Use exactly two op amps.