
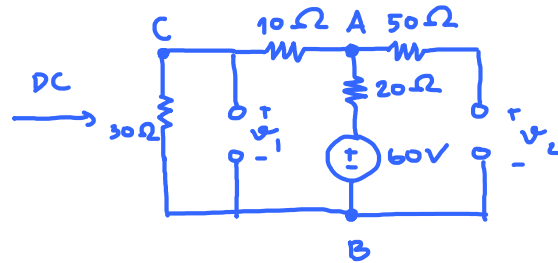


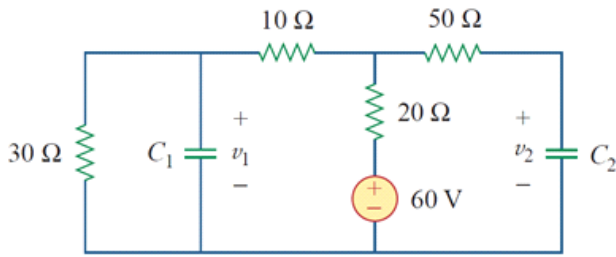Q1 [Alexander and Sadiku, 2009, Q6.13]

Monday, August 12, 2013 9:24 PM

Under DC conditions, capacitors become open circuits.




Note that the hanging branches created by the open circuits at the capacitor locations change the circuit to only one loop.

Method 1:

The current I in this loop is given by
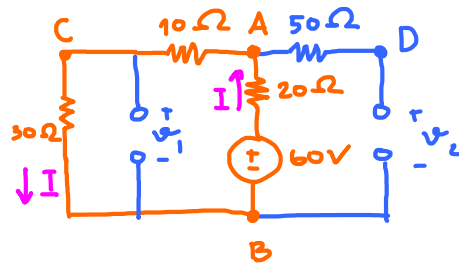
$$\frac{60}{30+10+20} = \frac{60}{60} = 1 \text{ A}$$



Observe that $v_1 = v_C - v_B =$ the voltage across the 30Ω resistor

$$= 30\Omega \times 1 \text{ A} = 30 \text{ V}$$

$$v_2 = v_D - v_B = v_A - v_B = 60 - I \times 20 = 60 - 20 = 40 \text{ V}$$

no current through the 50Ω
 \Rightarrow Therefore, $v_A = v_D$.


Method 2: Use voltage divider:

$$v_1 = \frac{30}{30+10+20} \times 60 = 30 \text{ V}$$

$$v_2 = \frac{10+30}{10+30+20} \times 60 = 40 \text{ V}$$

Method 3: Use nodal analysis:

At C:

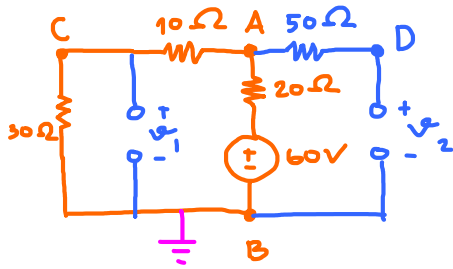

At C:

$$\frac{V_C}{30} + \frac{V_C - V_A}{10} = 0 \Rightarrow V_C + 3V_C - 3V_A = 0 \Rightarrow V_C = \frac{3}{4} V_A$$

At D:

$$\frac{V_D - V_A}{50} + 0 = 0 \Rightarrow V_D = V_A$$

At A:

$$\frac{V_A - V_C}{10} + \frac{V_A - 60}{20} + \frac{V_A - V_D}{50} = 0 \Rightarrow 2V_A - 2V_C + V_A - 60 = 0$$

$$3V_A - 2V_C = 60$$

$$3V_A - 2 \cdot \frac{3}{4} V_A = 60 \Rightarrow \frac{3}{2} V_A = 60 \Rightarrow V_A = 40V$$

$$V_C = \frac{3}{4} \times 40 = 30V$$

$$V_1 = V_C = 30V$$

$$V_2 = V_D = V_A = 40V$$


Capacitor Combination

Monday, August 12, 2013 9:20 PM

A couple of exercises in this HW deal with capacitor combination. To simplify our notation, we will use

series (C_1, C_2, \dots, C_n)

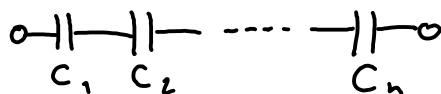
to mean the combined value of C_1, C_2, \dots, C_n when they are all connected in series:



We will use

parallel (C_1, C_2, \dots, C_n)

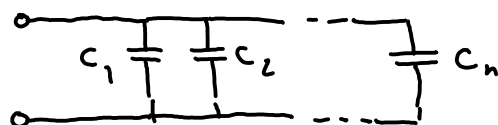to mean the combined value of C_1, C_2, \dots, C_n when they are all connected in parallel:



We know that $\text{series}(C_1, \dots, C_n) = \left(\frac{1}{C_1} + \dots + \frac{1}{C_n}\right)^{-1}$





$\text{parallel}(C_1, \dots, C_n) = C_1 + \dots + C_n$

Note that we avoid using "||" to denote parallel combination for capacitors, because it has been used for parallel combination of resistors which corresponds to different formula:

$$R_1 \parallel R_2 = \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1}$$

Q2 [Alexander and Sadiku, 2009, Q6.19]

Monday, August 12, 2013 9:23 PM

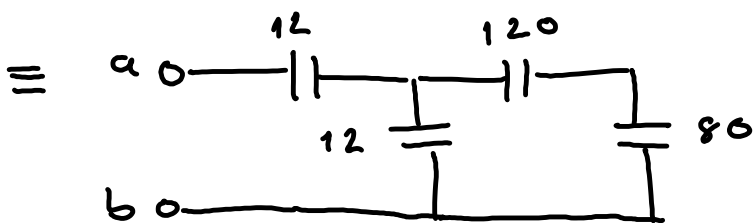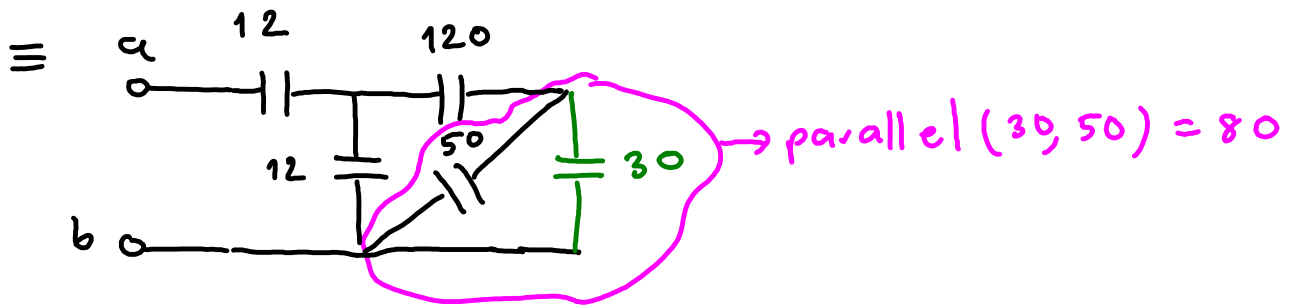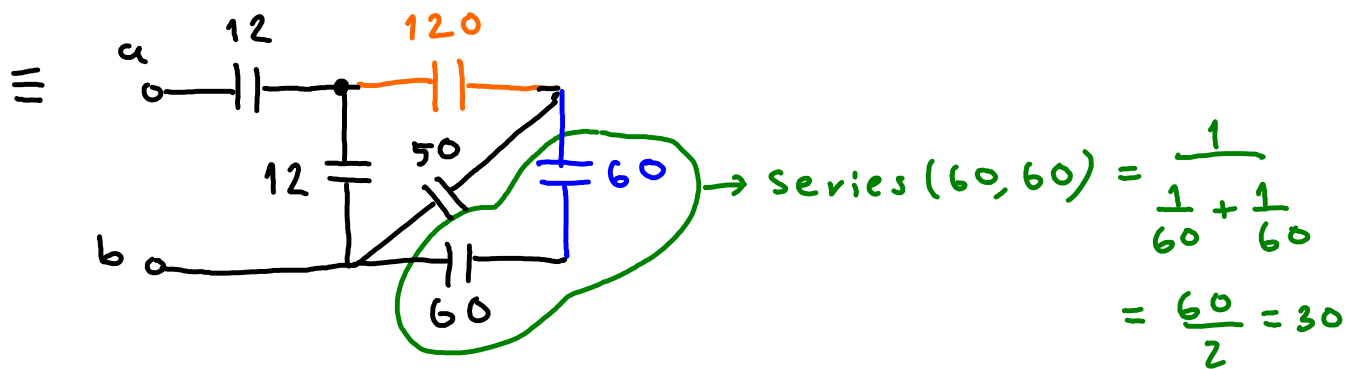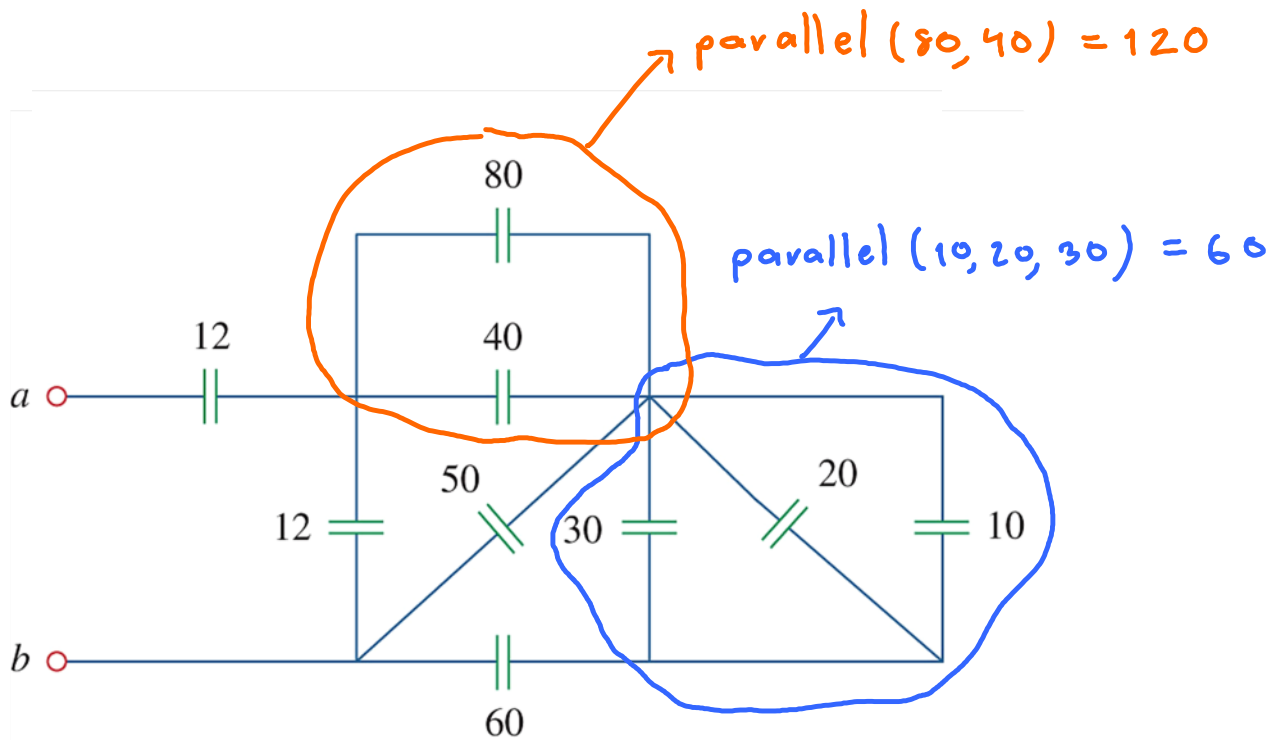

At this point I'm too lazy to draw more pictures

At this point, I'm too lazy to draw more pictures. Our simplified combination above is easy enough to be represented in a one-line expression:

$$C_{ab} = \text{series} (12, \text{parallel} (12, \text{series} (120, 80)))$$

$$\frac{120 \times 80}{120 + 80} = \frac{120 \times 80}{200} = 48$$

$$48 + 12 = 60$$


$$\frac{60 \times 12}{60 + 12} = \frac{60 \times 12}{72} = 10$$

$$= 10 \mu\text{F}$$

↑ don't forget the unit!!

Q3 [Alexander and Sadiku, 2009, Q6.20]


Monday, August 12, 2013 9:24 PM

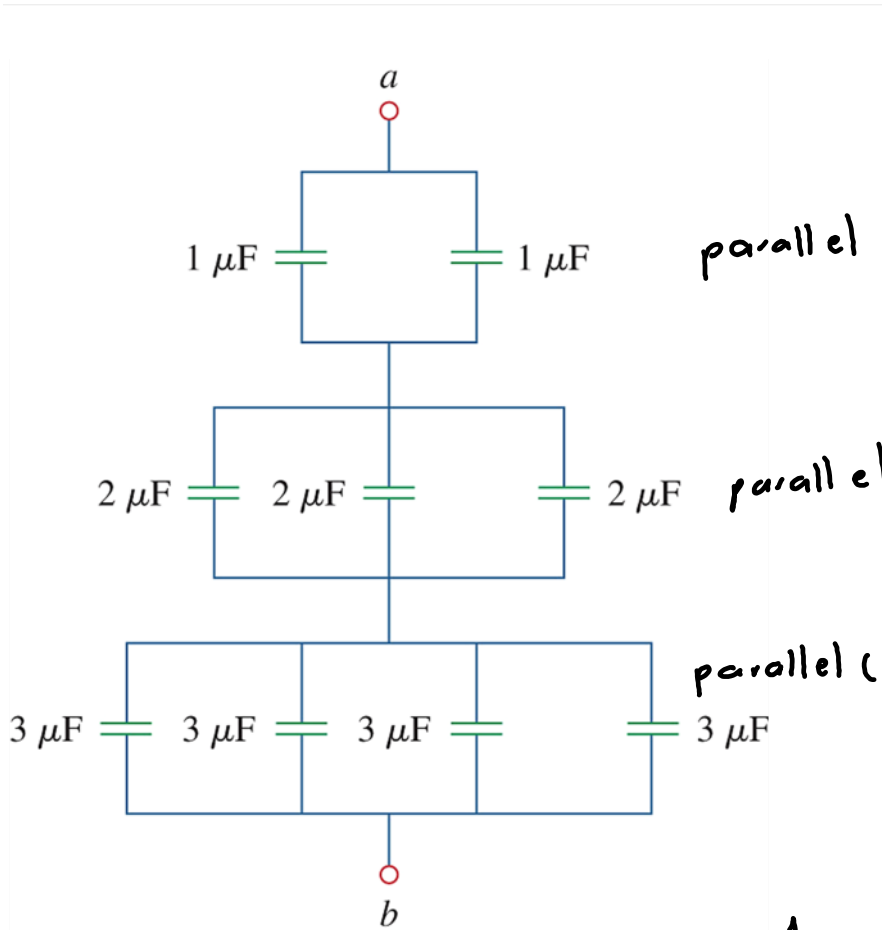

parallel (1, 1) = 2

parallel (2, 2, 2) = 6

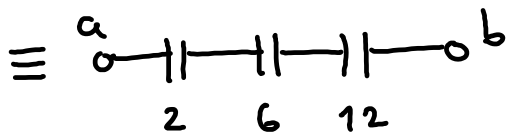
parallel (3, 3, 3, 3) = $3 \times 4 = 12$




$$C_{ab} = \frac{1}{\frac{1}{2} + \frac{1}{6} + \frac{1}{12}} = \frac{2}{1 + \frac{1}{3} + \frac{1}{6}} = \frac{4}{3} \mu\text{F}$$

Q4 [Alexander and Sadiku, 2009, Q6.46]

Monday, August 12, 2013 9:24 PM

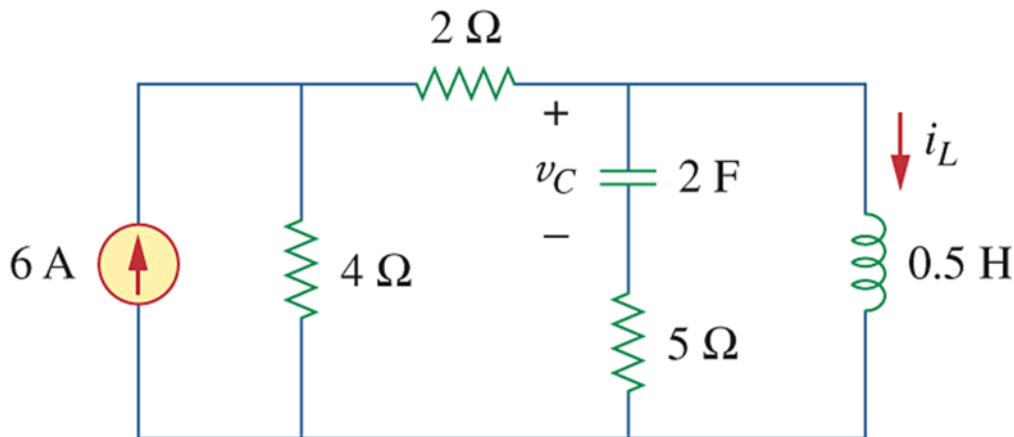

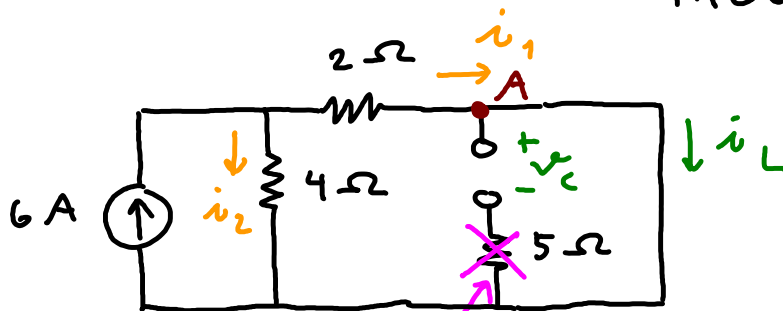Under DC conditions, capacitor \rightarrow open circuit
 inductor \rightarrow short circuit



No current through this resistor because of the open connection at the capacitor.

By current divider formula, $i_1 = 4A$
 $i_2 = 2A$

$$i_L = i_1 = 4A$$

$$v_C = v_A = 0V$$

↑
no current through the

(There is a short connection from the top to the bottom of the circuit)

through the
 $5\text{-}\Omega$ resistor

The energy stored in the capacitor is $w_c = \frac{1}{2} C v_c^2 = 0\text{ J}$



The energy stored in the inductor is $w_L = \frac{1}{2} L i_L^2$
 $= \frac{1}{2} \times \frac{1}{2} \times 4^2 = 4\text{ J}$

$$v_c = 0\text{ V} \quad w_c = 0\text{ J}$$

$$i_L = 4\text{ A} \quad w_L = 4\text{ J}$$

Q5 [Alexander and Sadiku, 2009, Q6.49]

Monday, August 12, 2013 9:24 PM

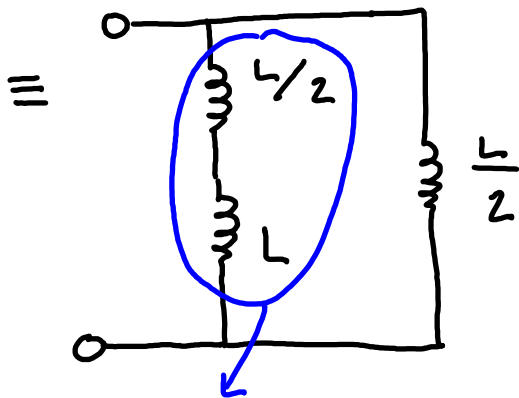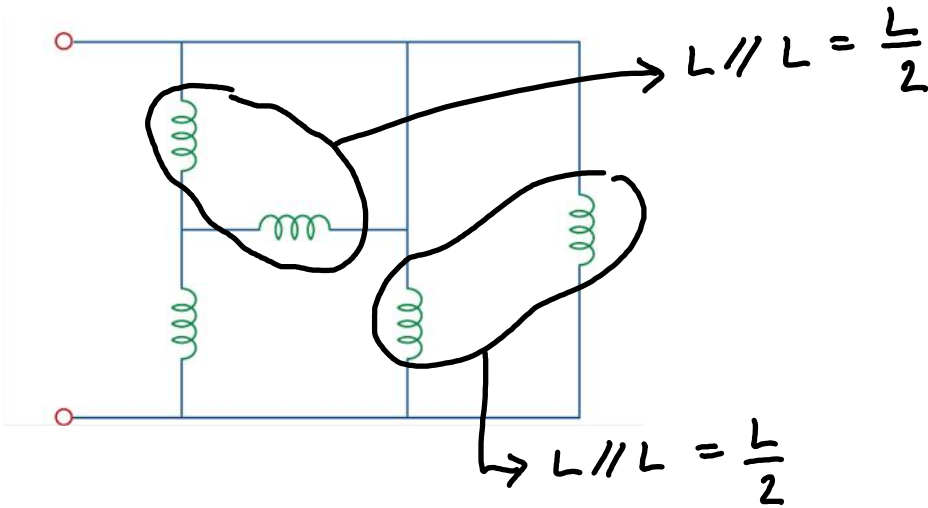

$$\frac{L}{2} + L = \frac{3L}{2}$$

$$\begin{aligned} L_{eq} &= \frac{3L}{2} // \frac{L}{2} \\ &= \frac{L}{2} (3 // 1) \\ &= \frac{L}{2} \frac{3}{4} = \frac{3L}{8} \end{aligned}$$

When $L = 10$,

$$L_{eq} = \frac{3 \times 10}{8} = 3.75 \text{ H}$$