

ECS 203: Problem Set 9

Semester/Year: 2/2014

Course Title: Basic Electrical Engineering

Instructor: Asst. Prof. Dr. Prapun Suksompong (prapun@siit.tu.ac.th)

Course Web Site: <http://www2.siiit.tu.ac.th/prapun/ecs203/>

Due date: April 3

Questions

- 1) [Alexander and Sadiku, 2009, Q6.13] Find the voltage across the capacitors in the circuit of Fig. 6.49 under dc conditions.

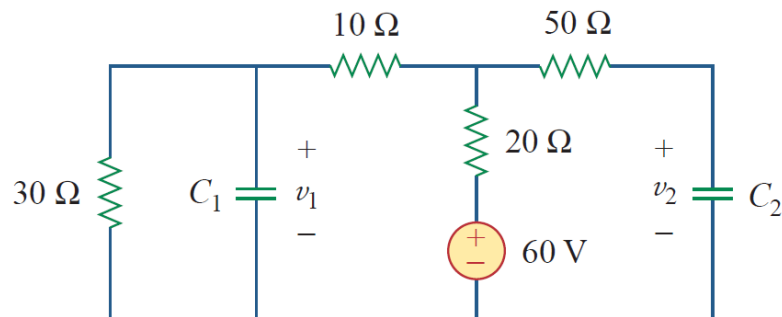


Figure 1

- 2) [Alexander and Sadiku, 2009, Q6.19] Find the equivalent capacitance between terminals a and b in the circuit of Figure 2. All capacitances are in μF .

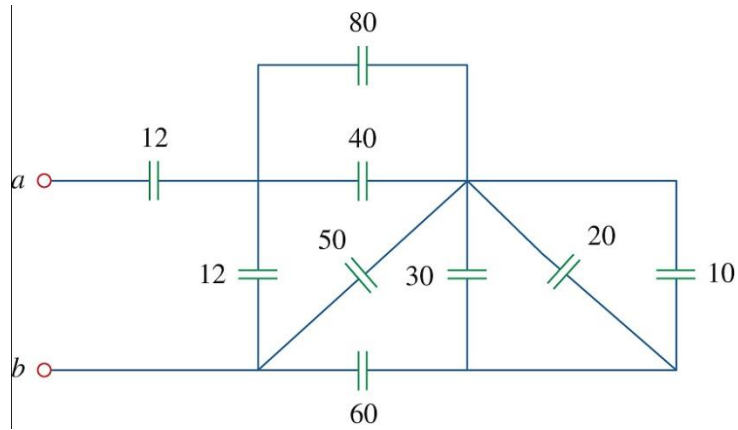


Figure 2

- 3) [Alexander and Sadiku, 2009, Q6.20] Find the equivalent capacitance at terminals a-b of the circuit in Figure 3.

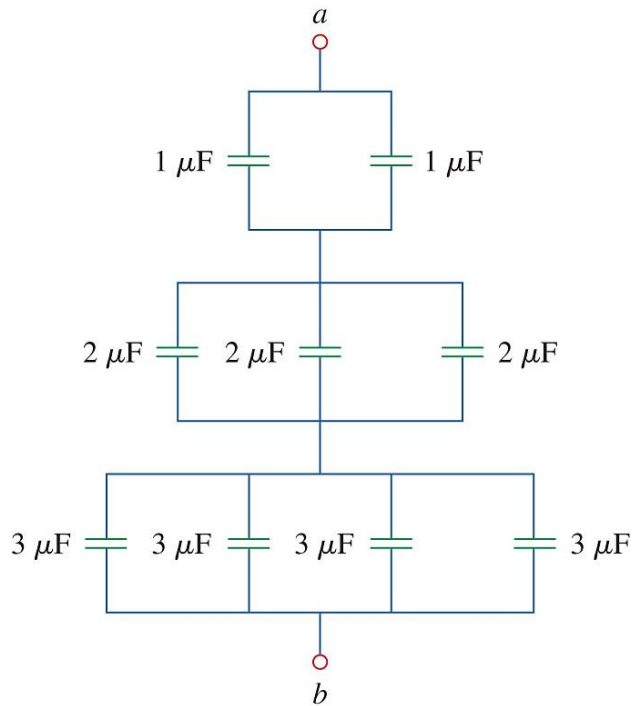


Figure 3

- 4) [Alexander and Sadiku, 2009, Q6.46] Find v_C , i_L , and the energy stored in the capacitor and inductor in the circuit of Figure 4 under dc, steady-state, conditions.

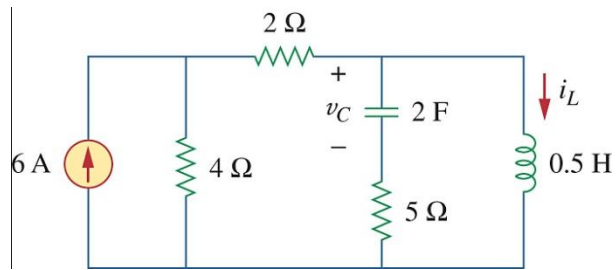


Figure 4

- 5) [Alexander and Sadiku, 2009, Q6.49] Find the equivalent inductance of the circuit in Figure 5. Assume all inductors are 10 mH.

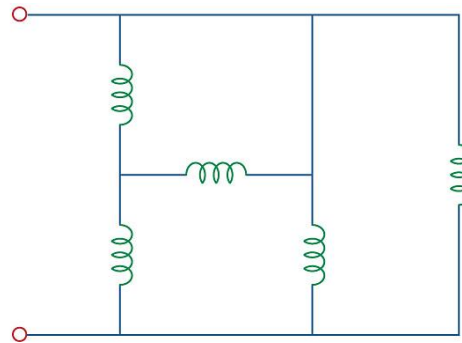


Figure 5