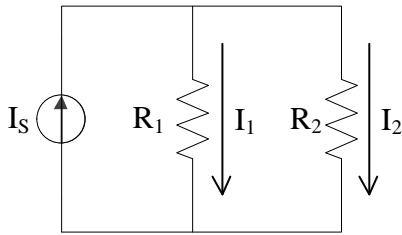


ECS 203 2014: Quiz 1 solution

Instructions

- i. Separate into groups of no more than three persons.
 - ii. Only one submission is needed for each group. Late submission will not be accepted.
 - iii. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.
 - iv. **Do not panic.**
1. Find I_1 when $I_s = 10$ A, $R_1 = 3$ k Ω and $R_2 = 2$ k Ω .


Name	ID
Prapon	




current divider formula

$$I_1 = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} I_s = \frac{R_2}{R_1 + R_2} I_s = \frac{2k}{3k + 2k} \times 10 = \frac{2}{5} \times 10 = 4 \text{ A}$$

2. Consider the circuit below.

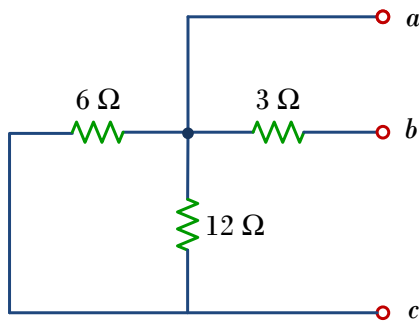

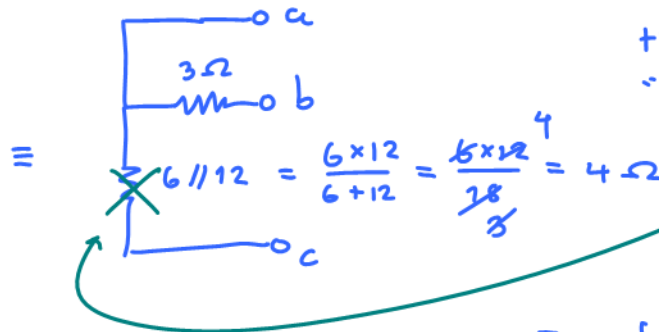
- a. Find the equivalent resistance with respect to terminals a-b



Wrt. terminals a-b, the 4 Ω is a "hanging" branch. So, we can ignore it. Then, only the 3 Ω resistor is left.

Therefore, $R_{eq} = 3\Omega$.

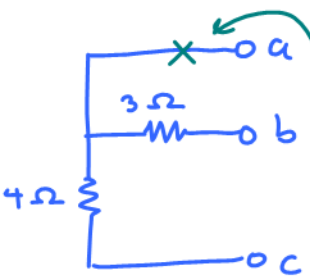
- b. Find the equivalent resistance with respect to terminals b-c



wrt. terminals b-c, the connection to a is simply a "hanging" line.

(If we put a current source across terminals b-c, there won't be any current going up to "a" because there is no where the current can go after that)

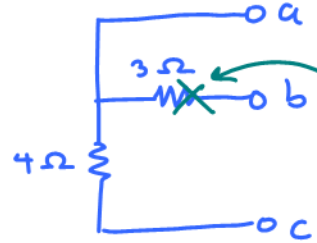- c. Find the equivalent resistance with respect to terminals a-c



wrt. terminals a-c, the 3 Ω is a "hanging" branch. So, we can ignore it. Then, only the 4 Ω resistor is left.

Therefore, $R_{eq} = 4\Omega$

So, 3 Ω and 4 Ω are actually in series and

$R_{eq} = 3 + 4 = 7\Omega$


Quiz 1

Note that $k\Omega$ is used instead of Ω .
(too small)

1

Quiz 1 Solution


$$R_{bc} \approx 7 k\Omega$$

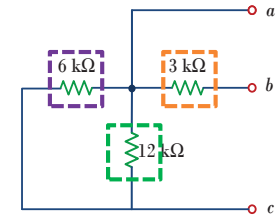

3

Quiz 1 Solution


$$R_{ab} \approx 3 k\Omega$$

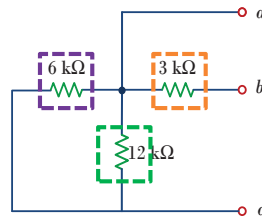

2

Quiz 1 Solution

$$R_{ac} \approx 4 k\Omega$$

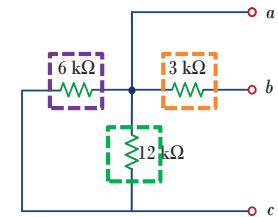

4