

# ECS 203 2014: Quiz 2 Solution


## Instructions

- i. Separate into groups of no more than three persons. Make sure the group members are not exactly the same as any of your earlier groups.
- ii. Only one submission is needed for each group. Late submission will not be accepted.
- iii. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

Name	ID
Prapun	555

For the circuit below, suppose  $i_s = 15A$ .

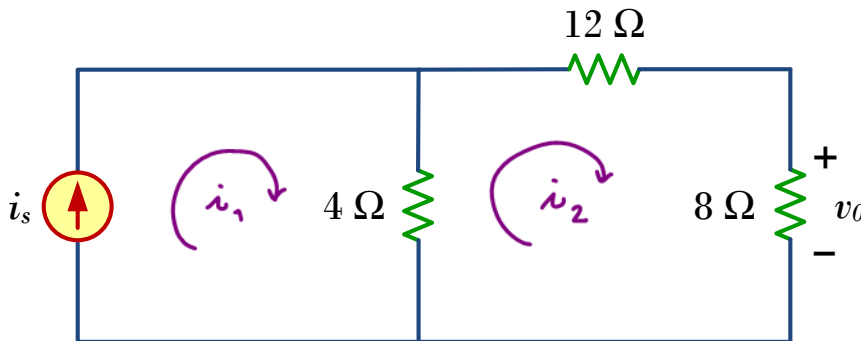- a. Find all mesh currents.
- b. Find  $v_0$



From mesh ①,  
 $i_1 = i_s = 15 A$

From mesh ②,

$$-(i_2 - i_1) \times 4 - i_2 \times 12 - i_2 \times 8 = 0$$

$$4 i_1 = i_2 \underbrace{(4 + 12 + 8)}_{24}$$

$$i_2 = \frac{4}{24} i_1 = \frac{5}{6} \times 15 = 2.5 A$$

(a)  $i_1 = 15 A$   
 $i_2 = 2.5 A$

(b) From Ohm's law,  $v_0 = +i_2 \times 8 = \frac{5}{2} \times 8 = 5 \times 4 = 20 V$

↑  
direction of  $i_2$  conforms with the passive sign convention when considered with the polarity of  $v_0$ .