

Instructions

- i. Separate into groups of no more than three persons. Make sure the group members are not exactly the same as any of your earlier groups.
- ii. Only one submission is needed for each group. Late submission will not be accepted.
- iii. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

| Name | ID |
|--------|-----|
| Prapun | 555 |
| | |
| | |

Find the voltage v under dc condition in each of the following circuits.

(a)

under dc condition, capacitor becomes an open circuit. This same reasoning is applied in all parts.

dc \Rightarrow

Note that v is the same as the voltage across the $5k\Omega$ resistor. By the voltage divider formula: $v = \frac{5k}{5k+3k} \times 24 = 15V$

(b)

Here, note that the open circuit prevents any current to flow through the 1Ω resistor.

dc \Rightarrow

Therefore, there is no voltage drop across the 1Ω resistor and hence v is the same as the voltage across the 9Ω resistor. Furthermore, since there is no current through the 1Ω resistor, it is simply a hanging branch which can be eliminated from our consideration. By the voltage divider formula,

$v =$ voltage across the 9Ω resistor $= \frac{9}{9+3} \times 20 = \frac{9}{12} \times 20 = 15V$

(c)

Method 1: Mesh analysis: There is only one mesh. Applying KVL gives $10 - i \times 2 - i \times 6 + 5 = 0$. This implies $i = \frac{15}{8} A$. So, $v = 10 - \frac{15 \times 2}{8} = \frac{25}{4} = 6.25 V$

Method 2: Nodal analysis: KCL @ A gives $3 \times \frac{V_A - 10}{2} + \frac{V_A - (-5)}{6} = 0 \Rightarrow V_A = \frac{25}{4}$. Note that $v = V_A$.