

Basic Elec. Engr. Lab

ECS 204

Asst. Prof. Dr. Prapun Suksompong


prapun@siit.tu.ac.th



Lab 2


- Thevenin's and Norton's Theorems
- New toy: Potentiometer
- Building a “fake” current source

Lab 2: Circuit under consideration

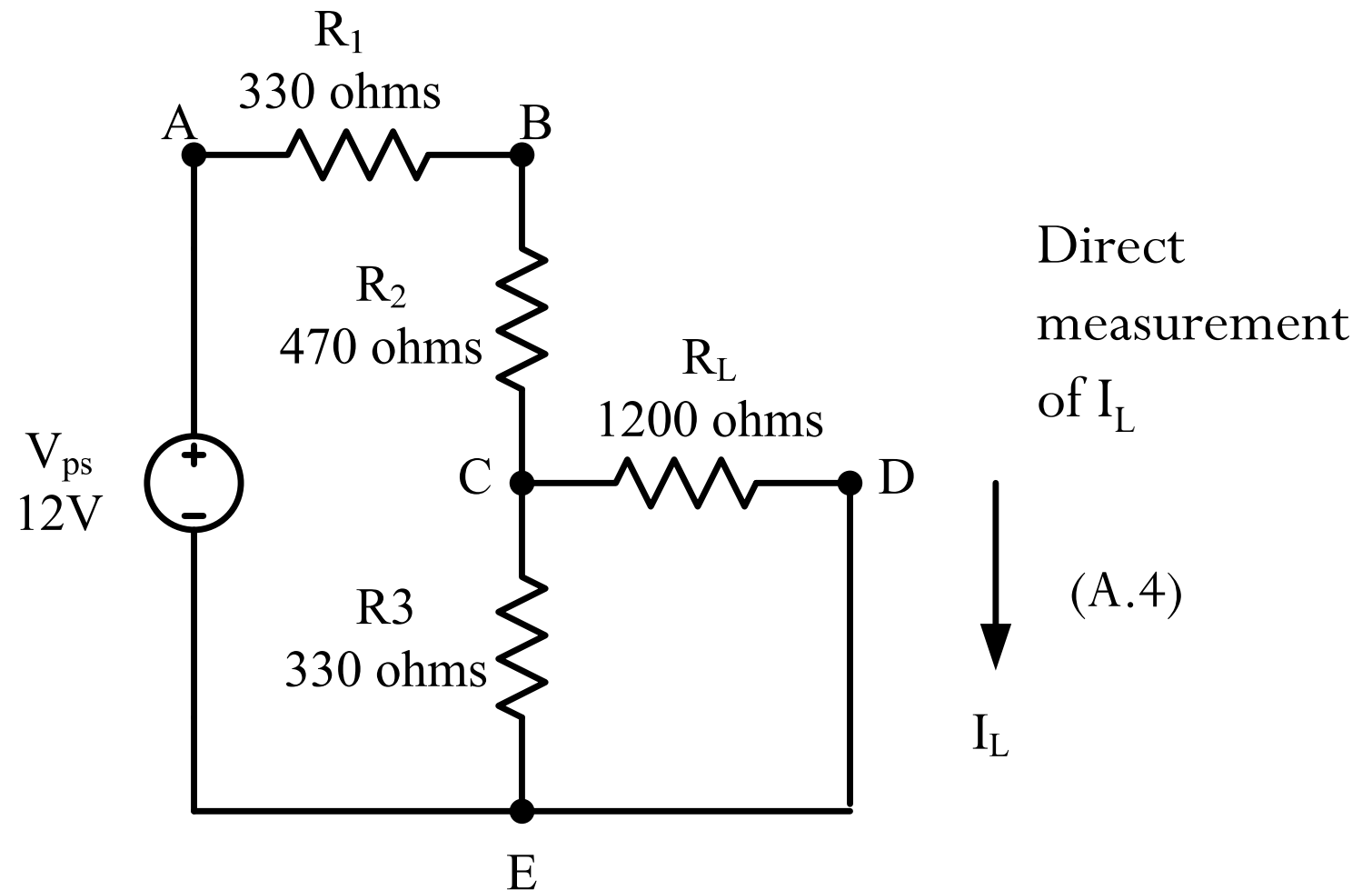


Outline of the lab

Part A (Thevenin Eq.)

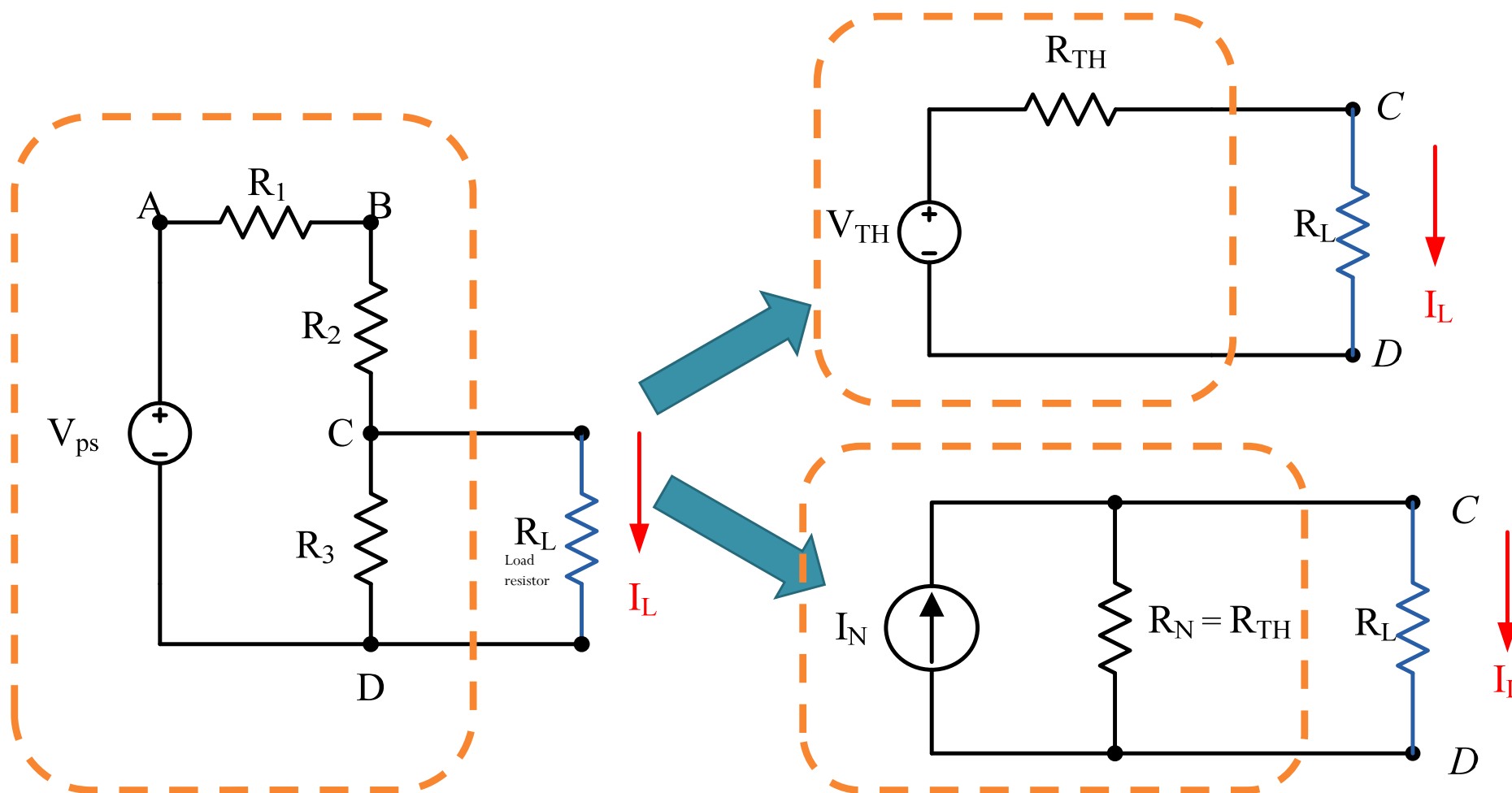


Part B (Norton Eq.)

Part A: Thevenin Equivalent (1)

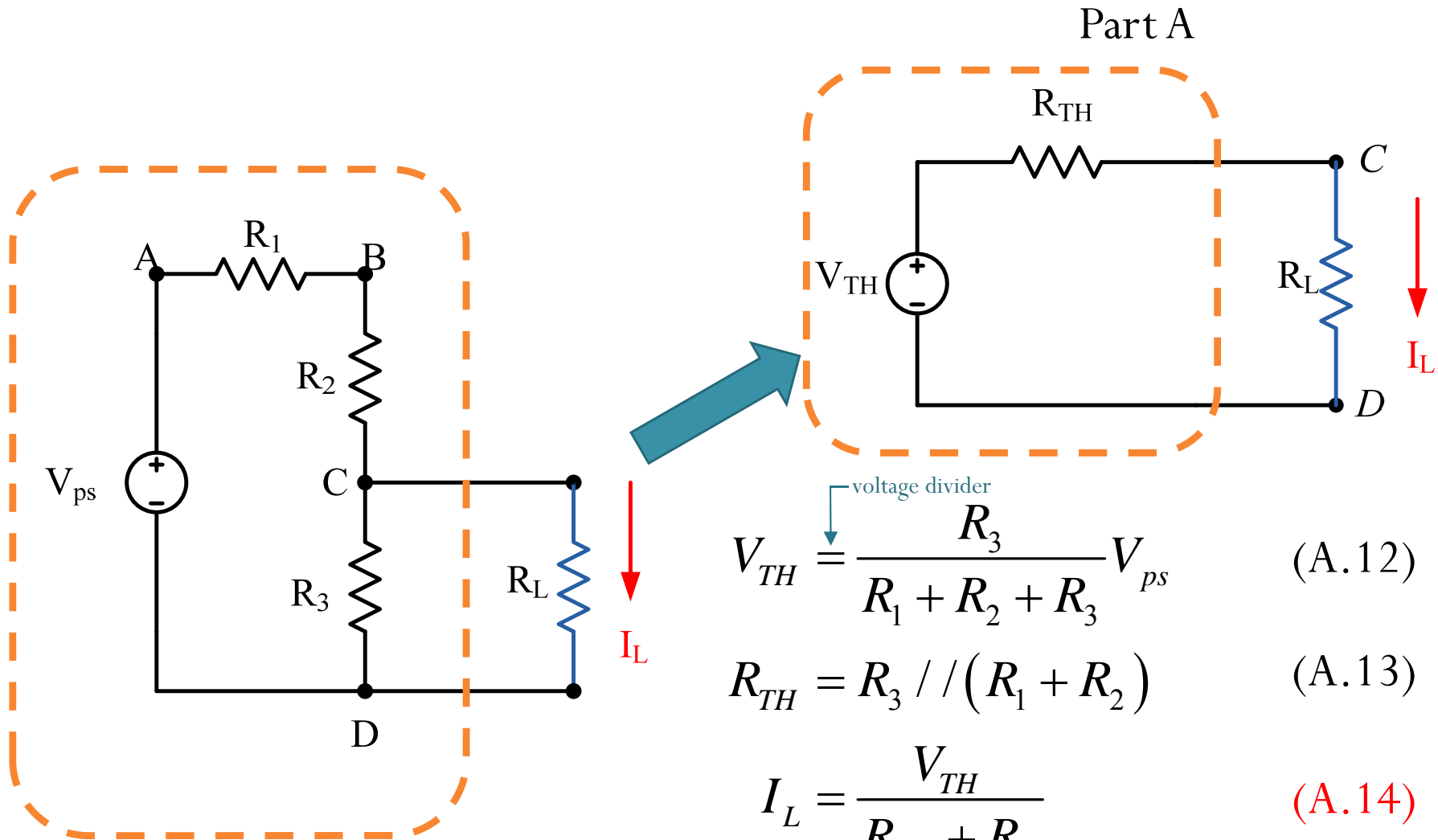

Part A: Thevenin Equivalent (2)


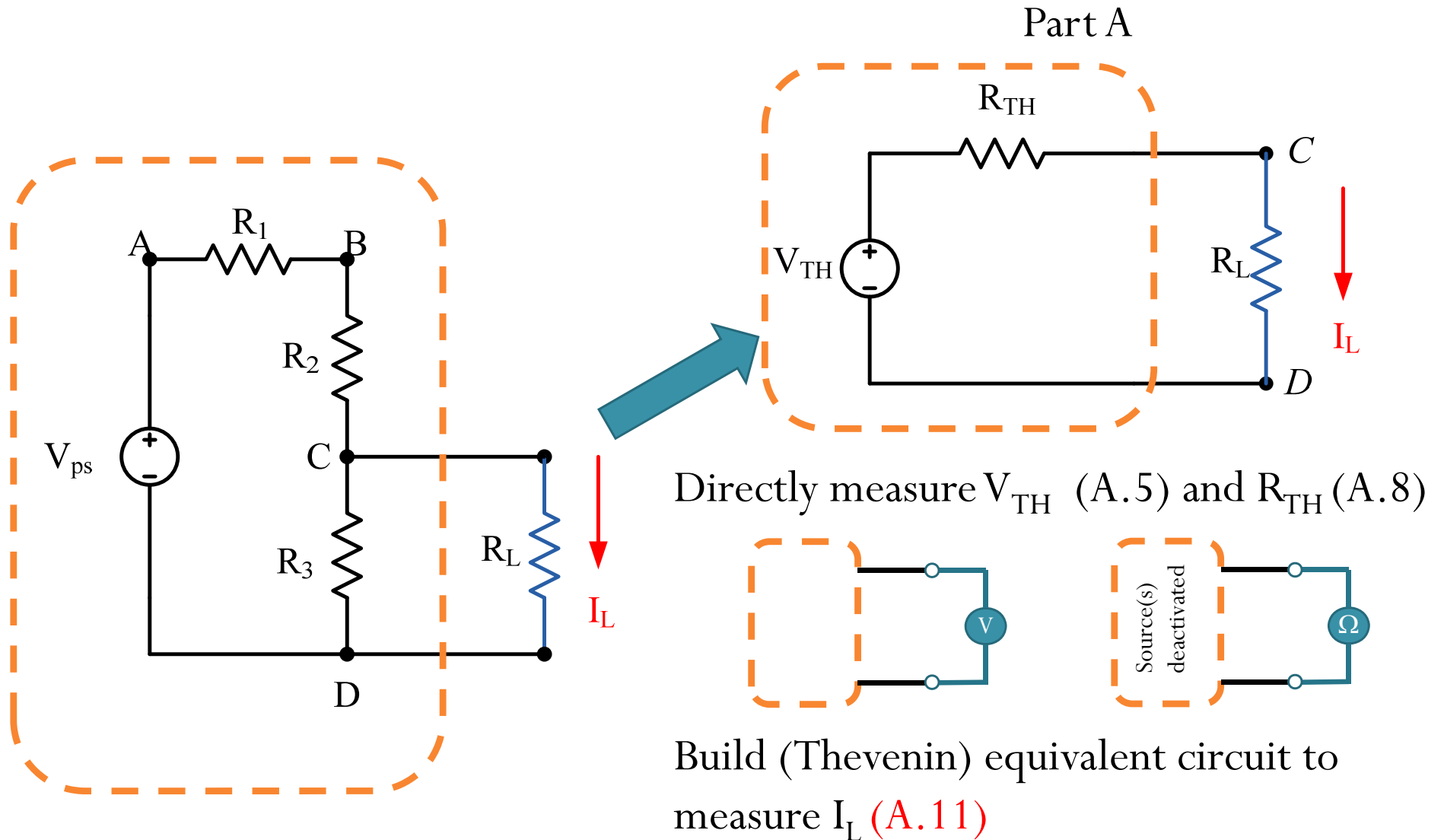


Part B: Norton Equivalent (1)

$$R_N = R_{TH}$$


$$I_N = \frac{V_{ps}}{R_1 + R_2} \quad (\text{B.6})$$
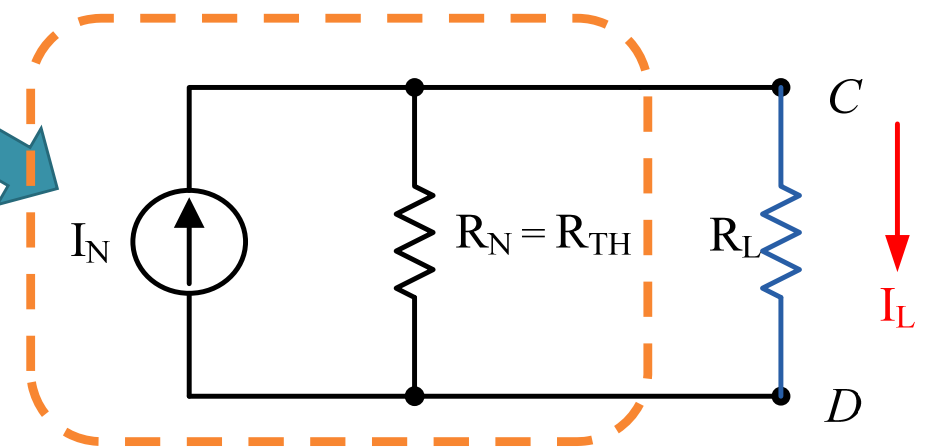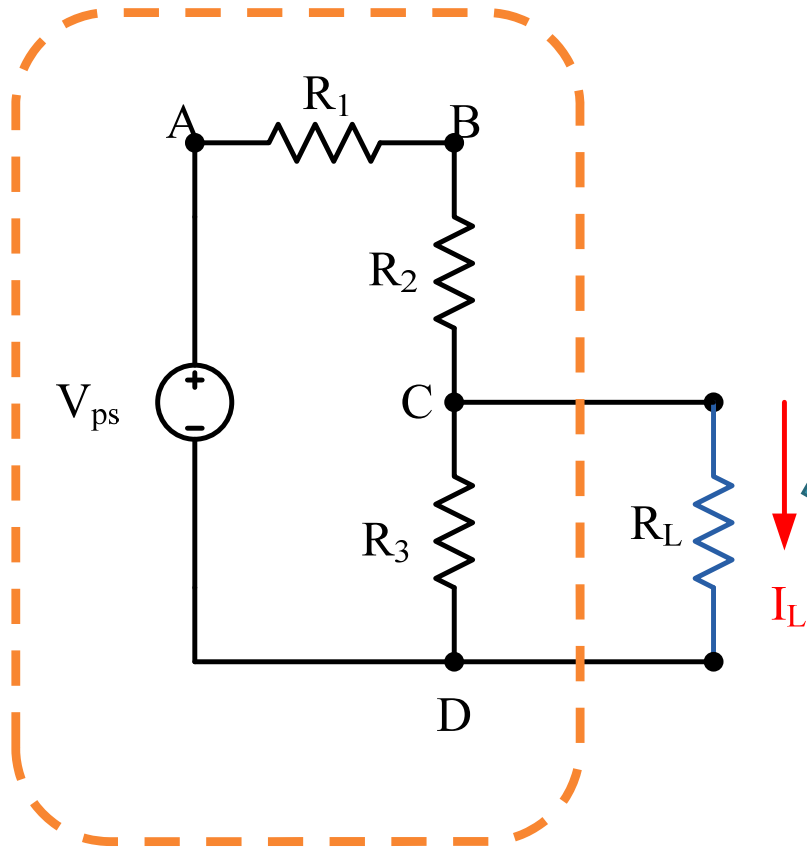
$$I_L = \frac{R_N}{R_L + R_N} I_N \quad (\text{B.7})$$




Part B


Part B: Norton Equivalent (2)

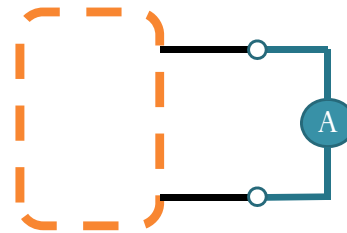

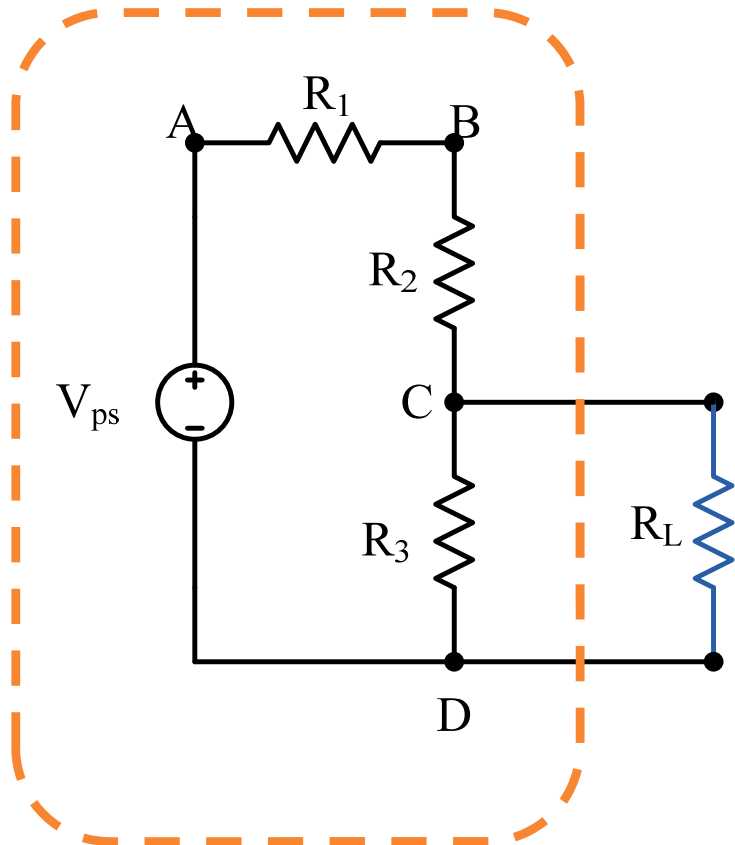Note that the ammeter itself acts as a short circuit.




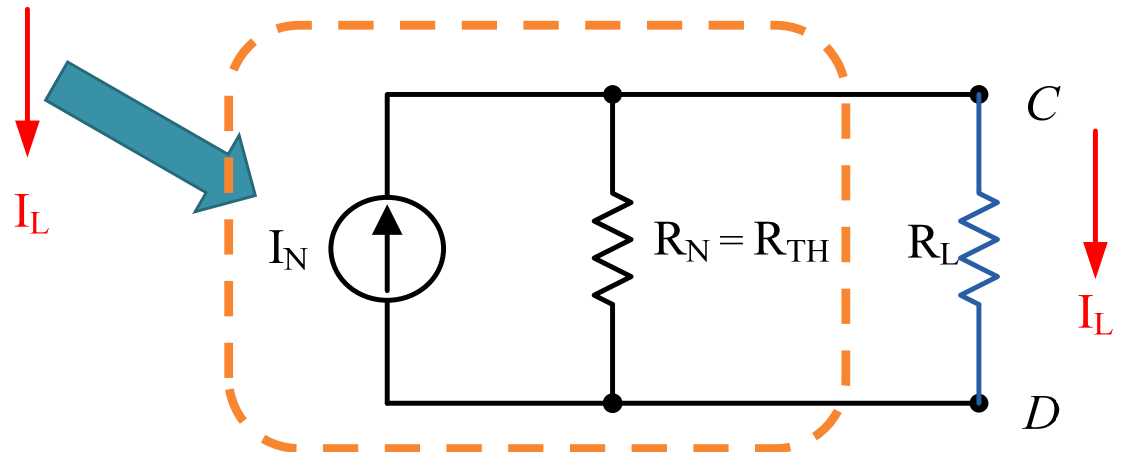Directly measure I_N (B.2)
Build (Norton) equivalent circuit to measure I_L (B.5)




Part B

Lab 2: Summary



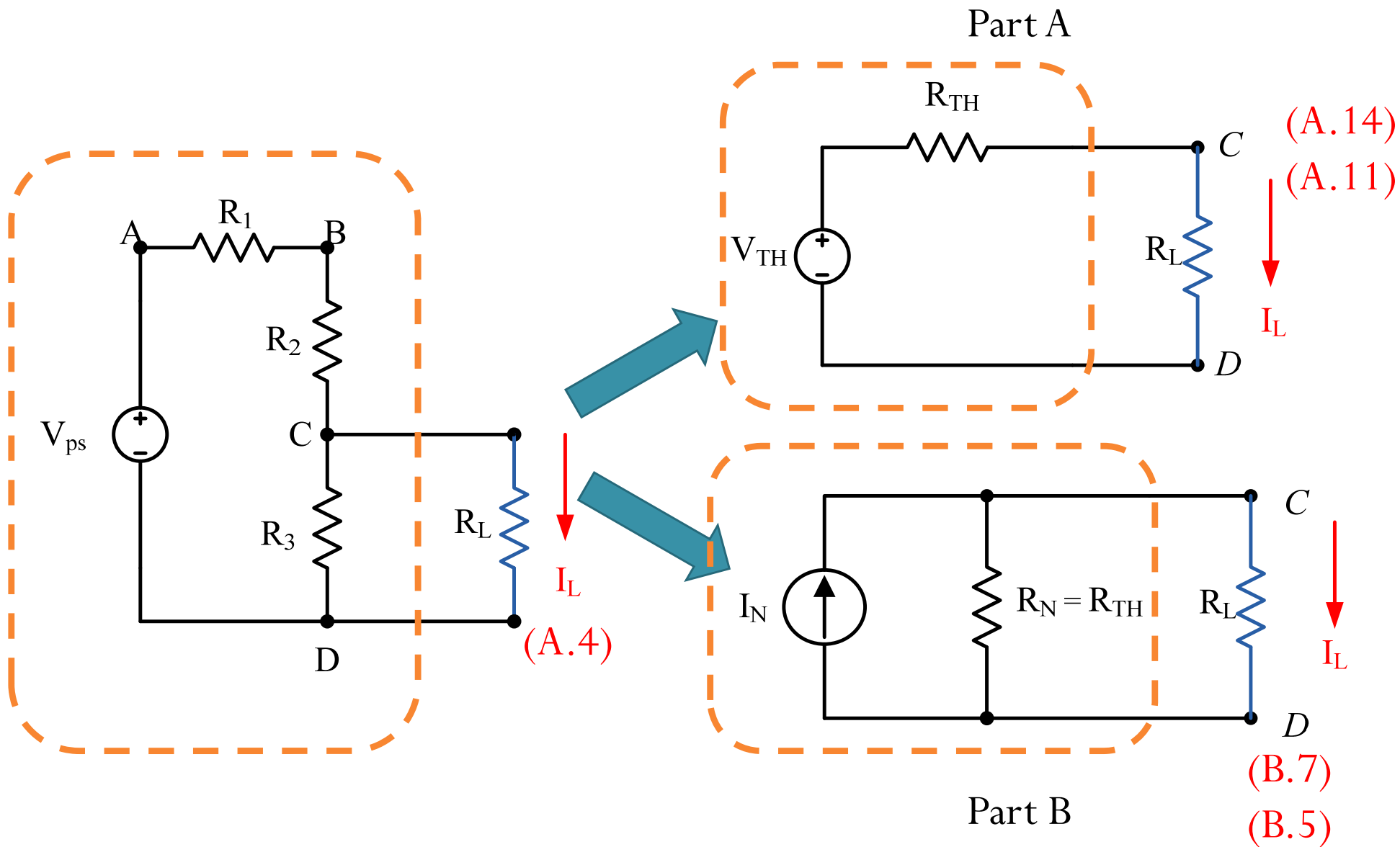


Lab 2: Summary

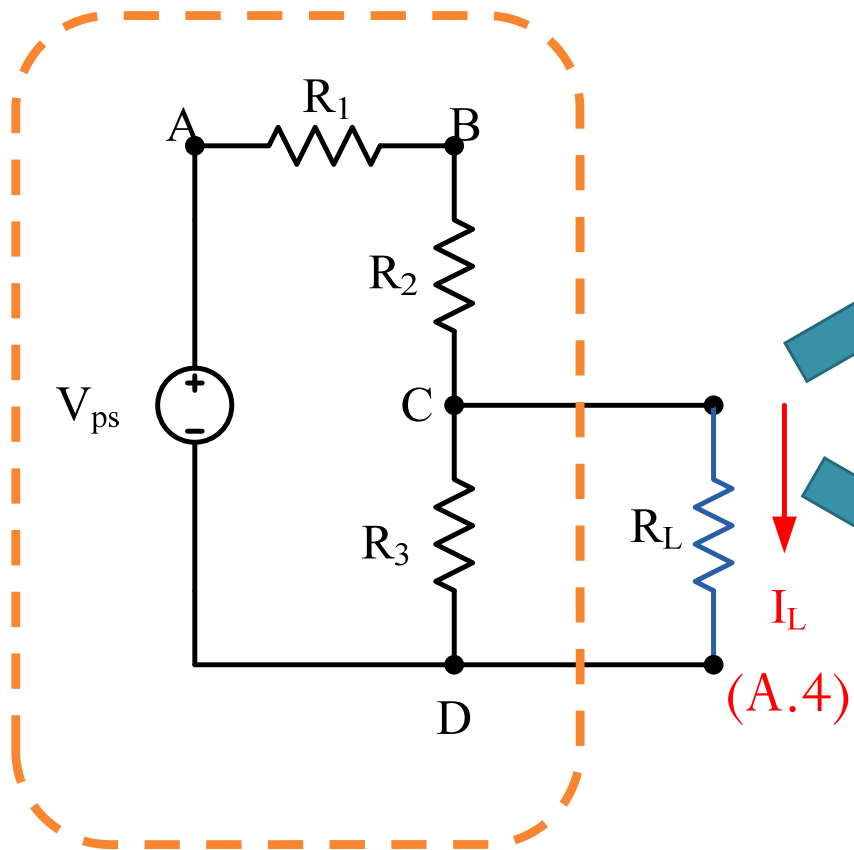

Need resistor whose value can be adjusted arbitrarily

Part A

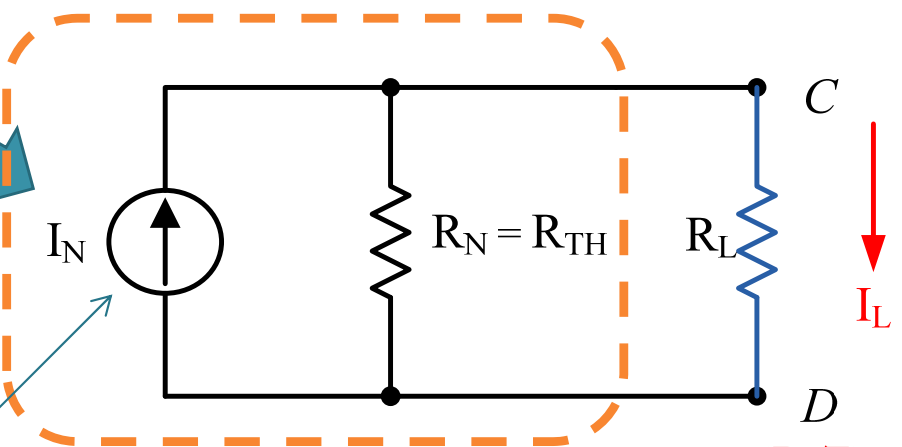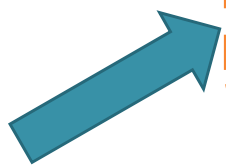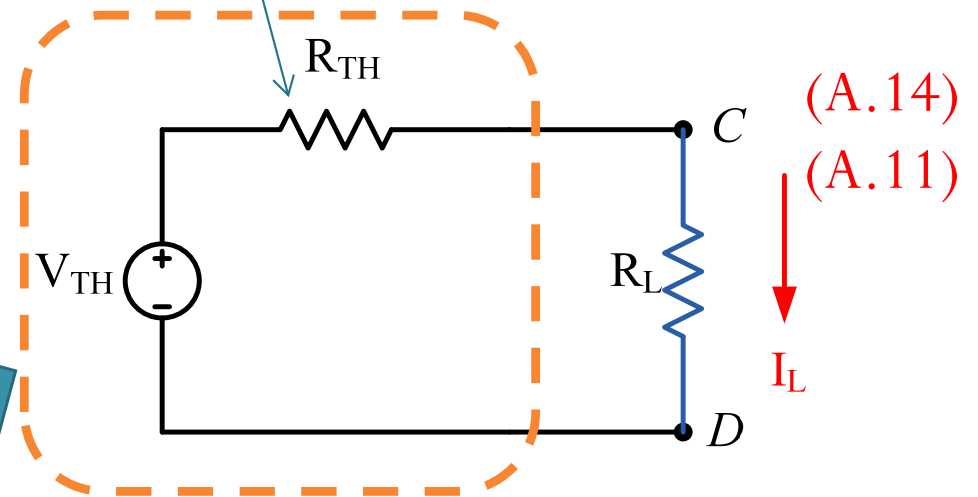

Need current source


Part B

Potentiometer (Pot)



Pot as a variable resistor

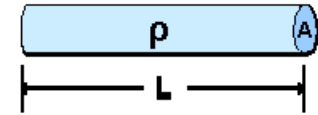- Manually adjustable resistor
- Three terminals
- The resistance between the middle terminal and either of the two sides depends on the position of the wiper.





$$R = \rho \times L / A$$

ρ = Resistivity

L = Length

A = Cross-sectional area

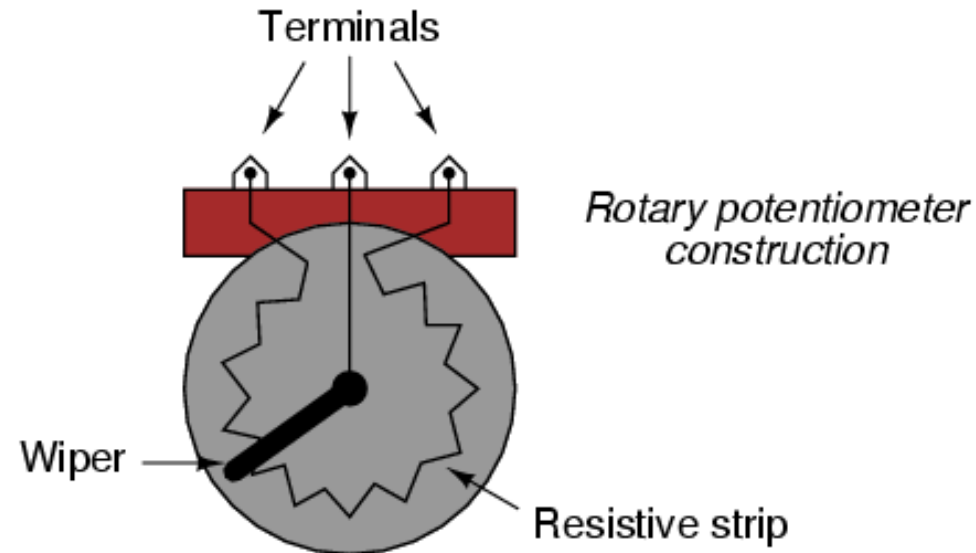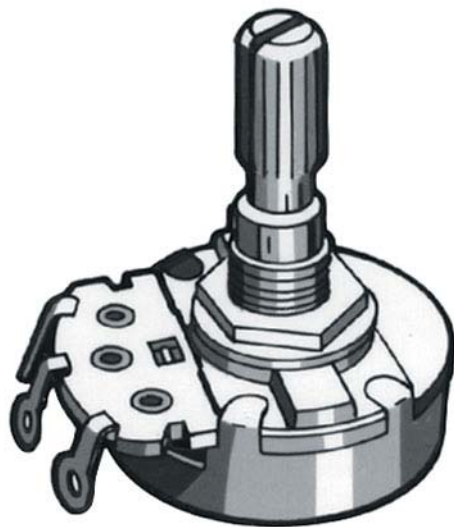

Current source

- We do not have current source.
 - Again, it is meaningless to connect an ammeter directly across the power supply. This will NOT give you the amount of current produced by the power supply.
- We use a voltage source (power supply) to give the specified amount of current.

