

Basic Elec. Engr. Lab

ECS 204

Asst. Prof. Dr. Prapun Suksompong

prapun@siit.tu.ac.th




Lab 3


- Superposition Theorem (Part A)
- Maximum Power Transfer (Part B)

Part A


A.(a)

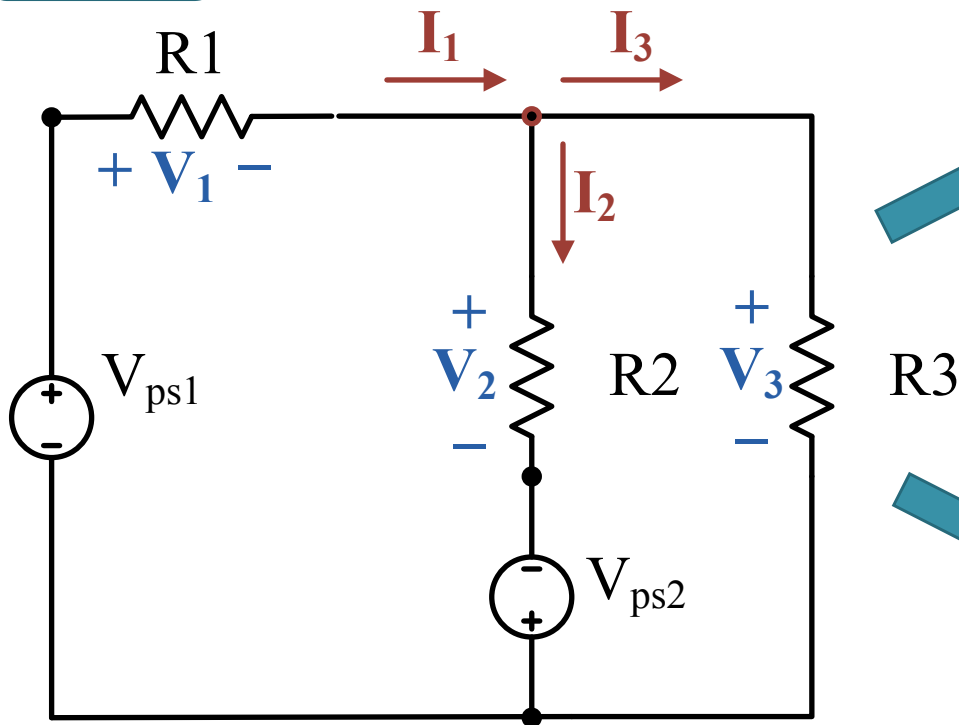


A.(b)

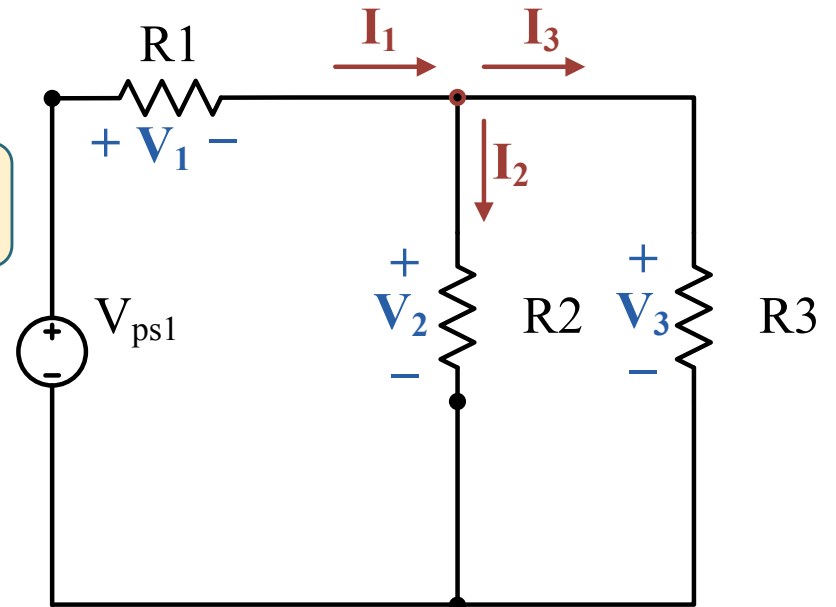

A.(c)

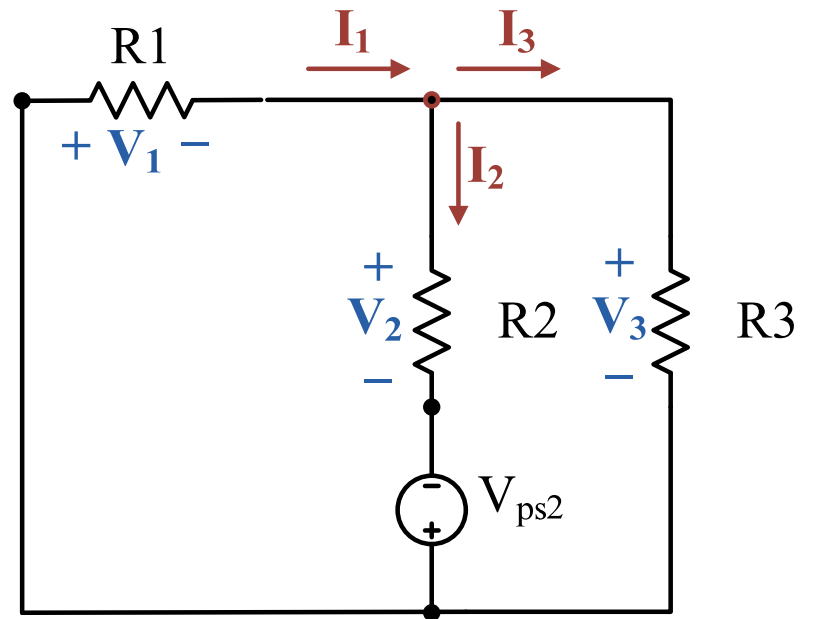

A.(b)

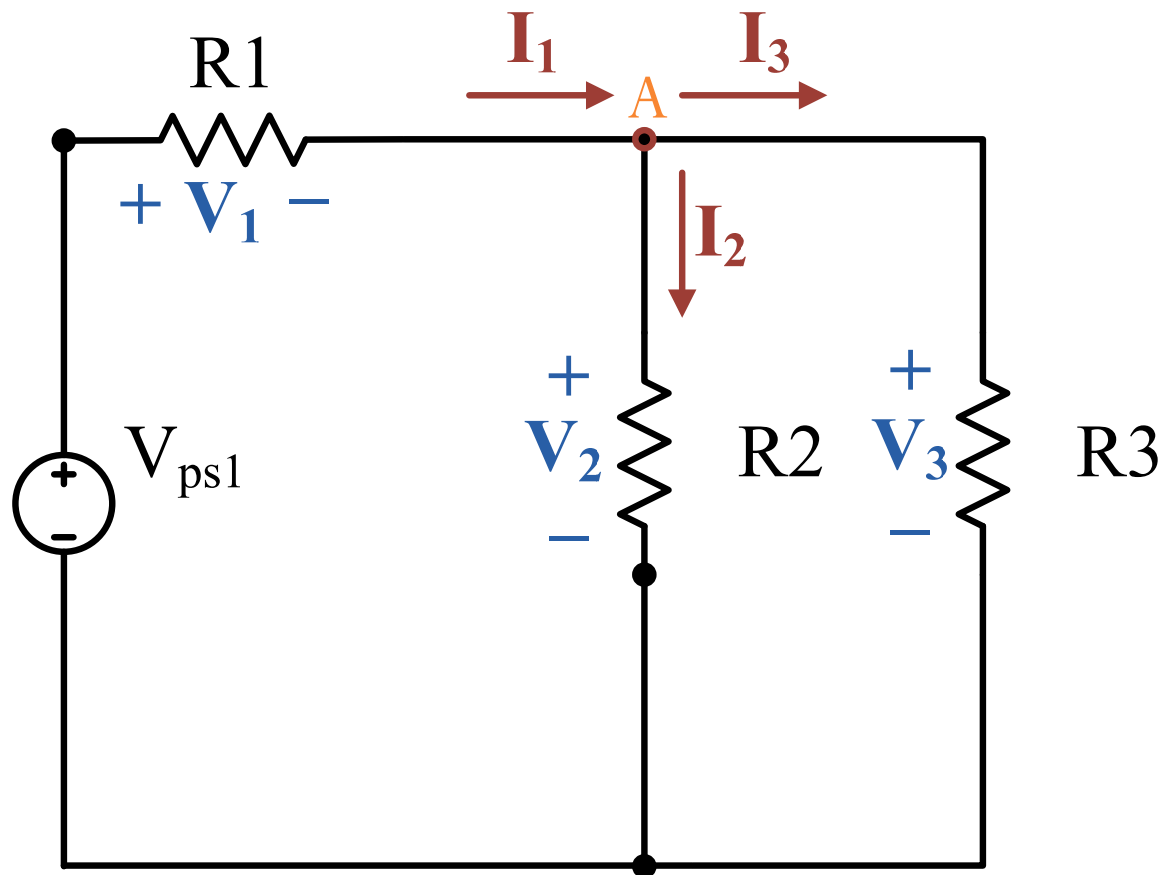

Voltage divider

$$V_A^{(b)} = \frac{R_2 // R_3}{R_1 + (R_2 // R_3)} V_{ps1}$$

$$V_1^{(b)} = V_{ps1} - V_A$$

$$V_2^{(b)} = V_A$$


$$V_3^{(b)} = V_A$$

$$I_1^{(b)} = \frac{V_1}{R_1}$$

$$I_2^{(b)} = \frac{V_2}{R_2}$$

$$I_3^{(b)} = \frac{V_3}{R_3}$$

A.(c)

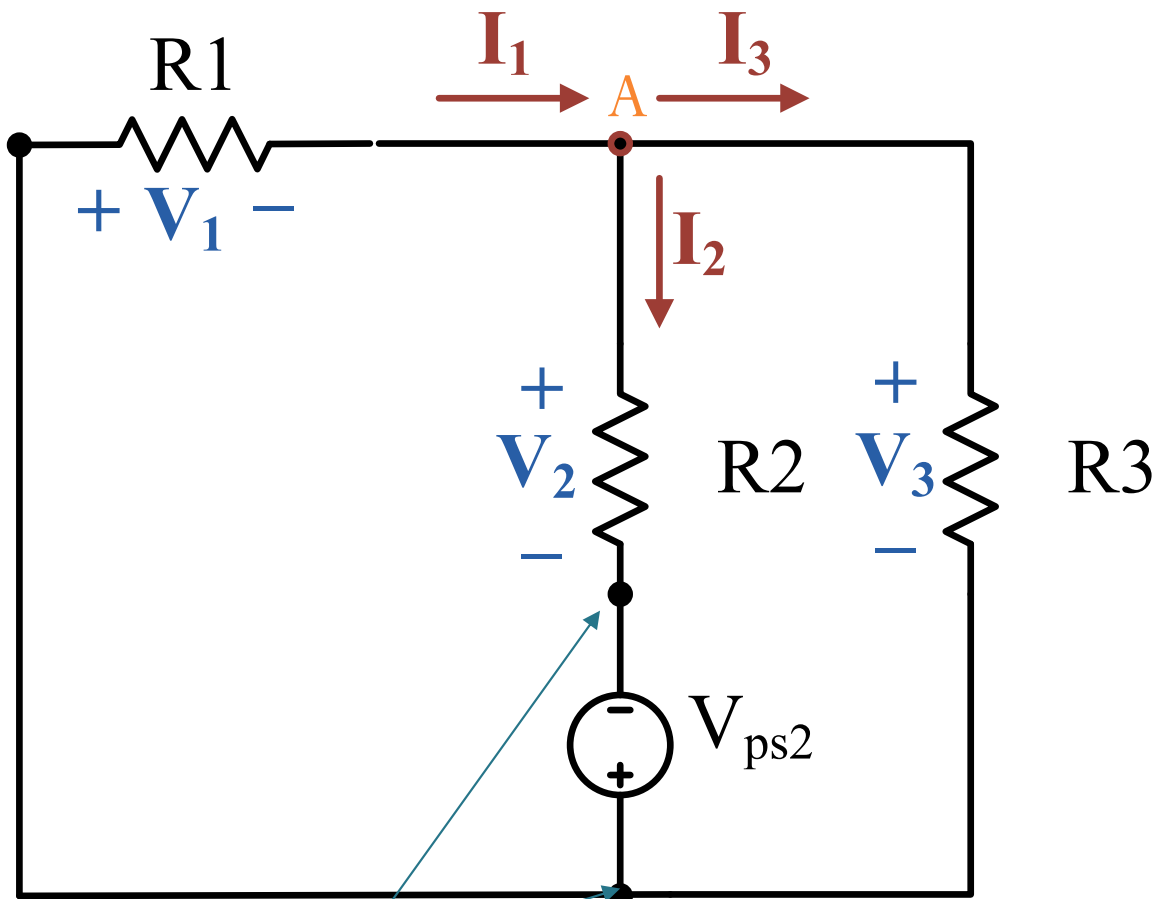

Voltage divider

$$V_A^{(c)} = \frac{R_1 // R_3}{R_2 + (R_1 // R_3)} \times (-V_{ps2})$$

$$V_1^{(c)} = -V_A$$

$$V_2^{(c)} = V_A - (-V_{ps2})$$

$$V_3^{(c)} = V_A$$



$$I_1^{(c)} = \frac{V_1}{R_1}$$

$$I_2^{(c)} = \frac{V_2}{R_2}$$

$$I_3^{(b)} = \frac{V_3}{R_3}$$

These two nodes are not the same. Resistor R2 and R3 are not in parallel.

A.a

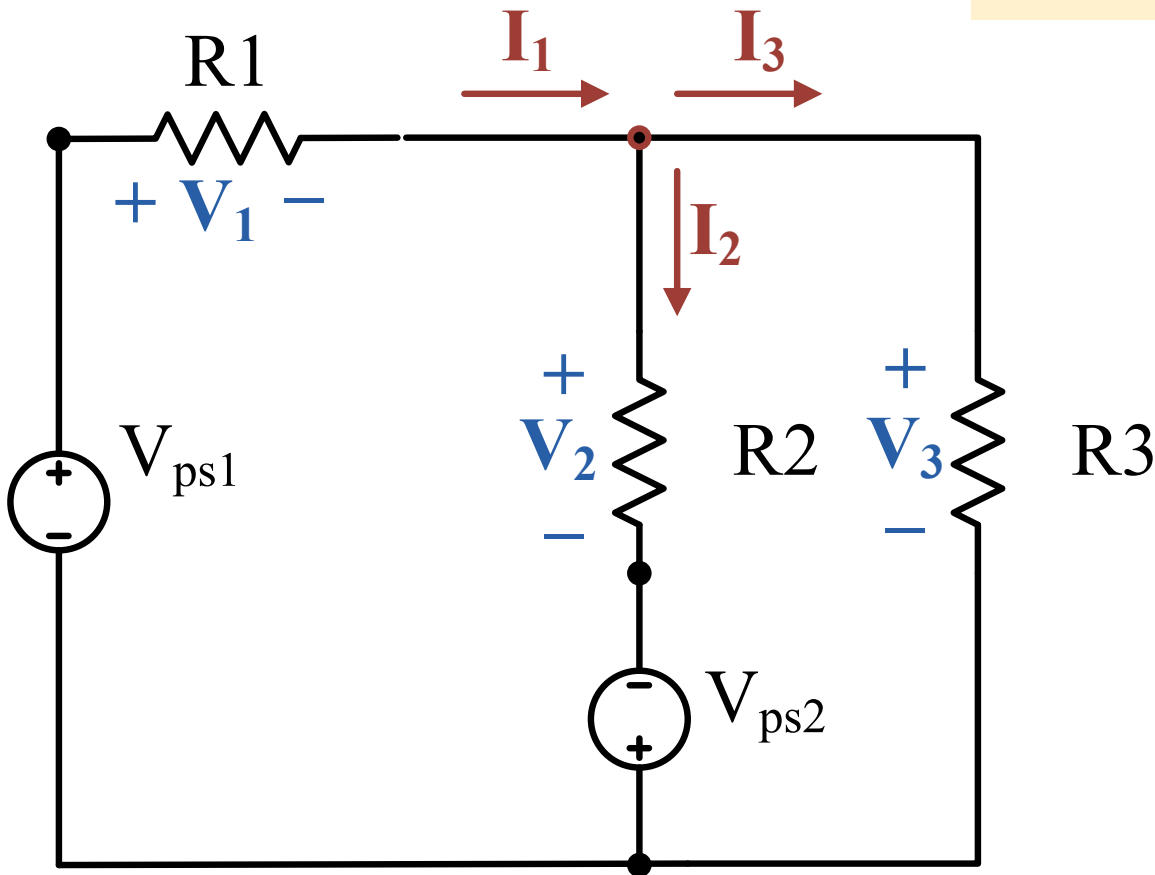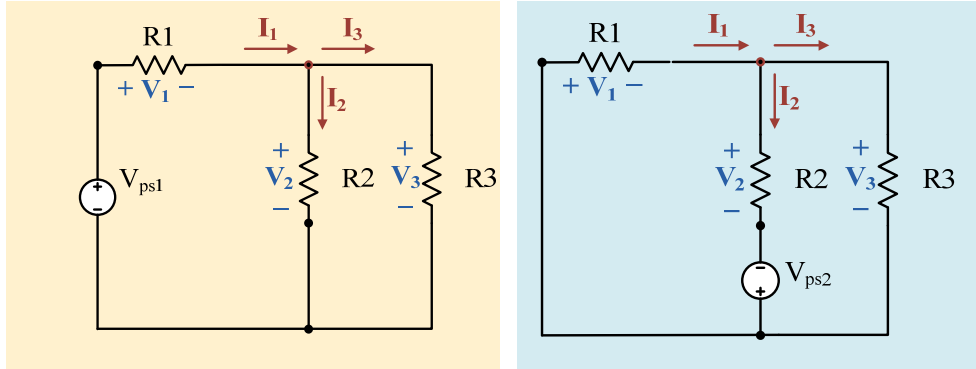


$$\begin{aligned}
 V_1^{(a)} &= V_1^{(b)} + V_1^{(c)} \\
 V_2^{(a)} &= V_2^{(b)} + V_2^{(c)} \\
 V_3^{(a)} &= V_3^{(b)} + V_3^{(c)} \\
 I_1^{(a)} &= I_1^{(b)} + I_1^{(c)} \\
 I_2^{(a)} &= I_2^{(b)} + I_2^{(c)} \\
 I_3^{(a)} &= I_3^{(b)} + I_3^{(c)}
 \end{aligned}$$

Remark: Some of these values will be negative!!

Multiple voltage sources

V_{ps2}



V_{ps1}

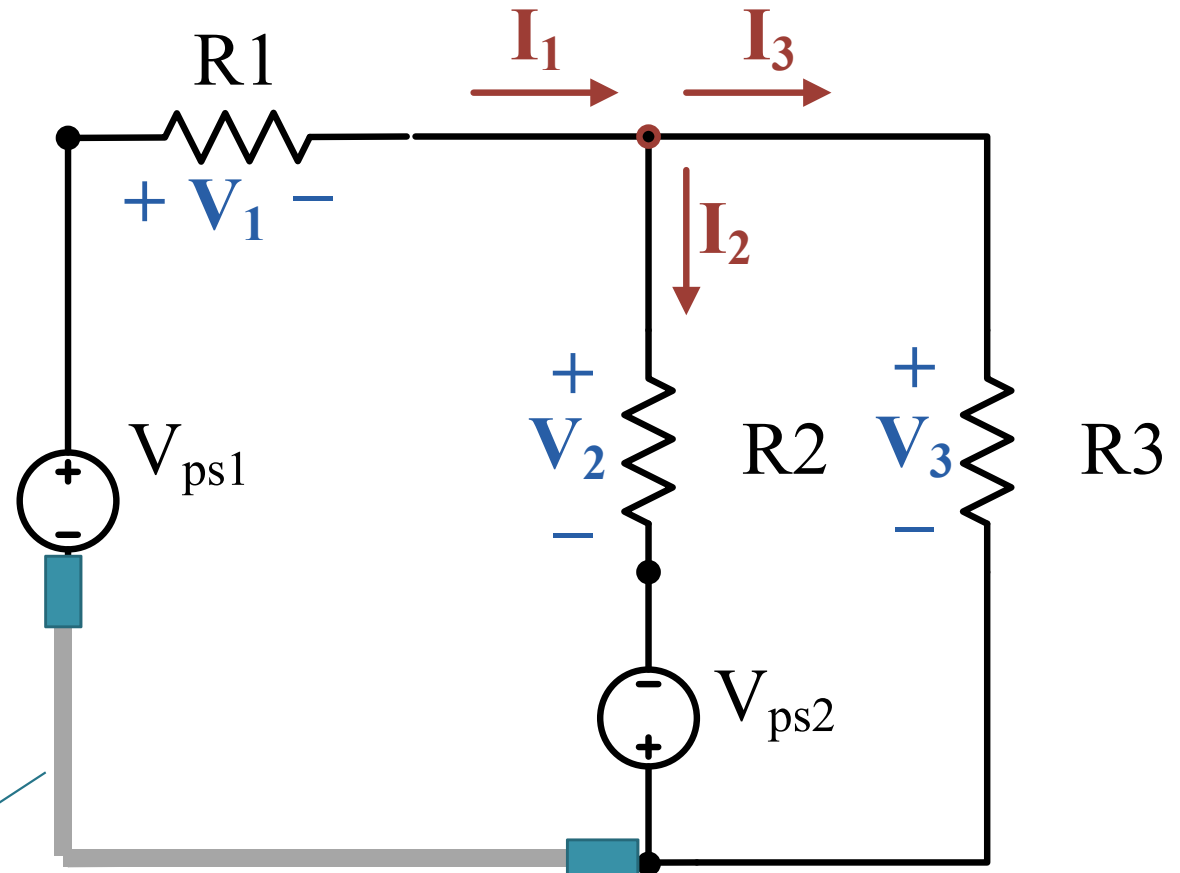

This connection can use the small connector.

Note that it is the “-” (black) terminal of V_{ps1} that is connected to the “+” (red) terminal of V_{ps2} .

Multiple voltage sources

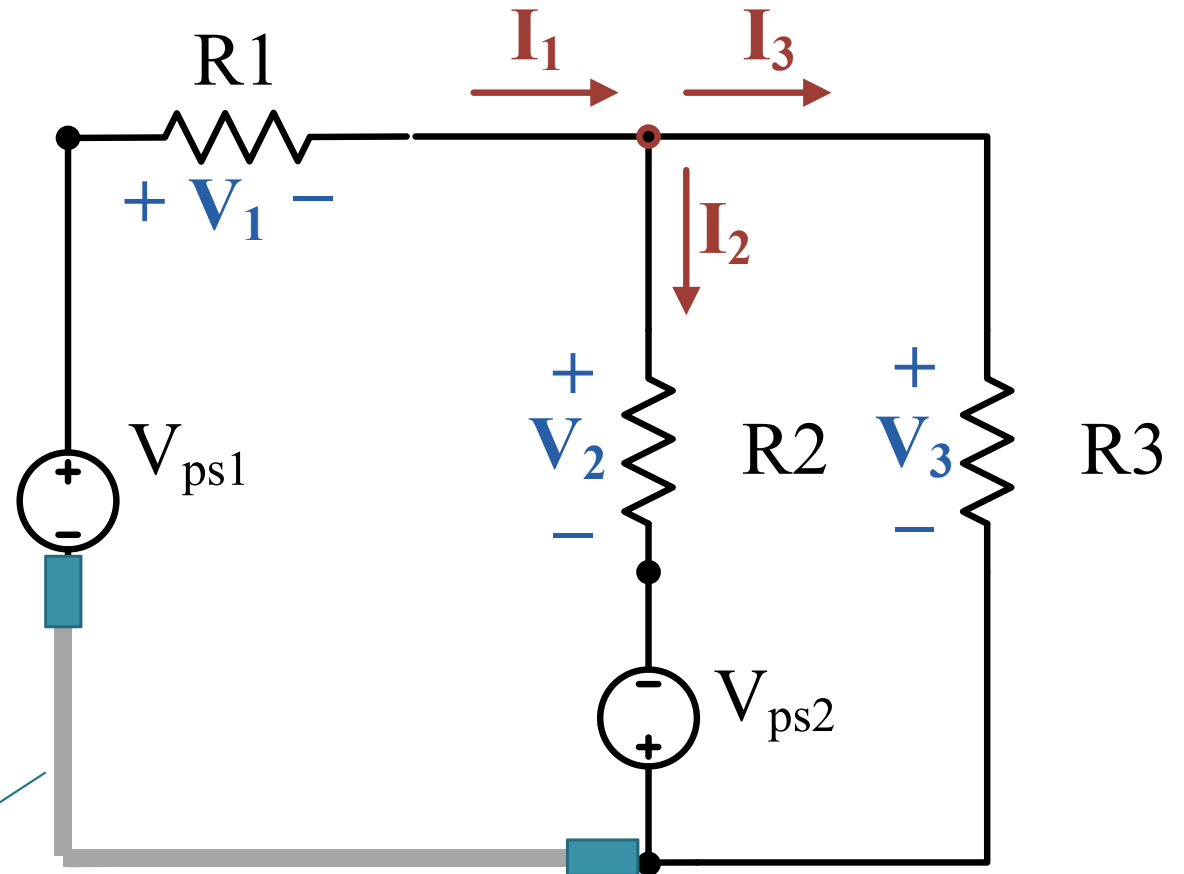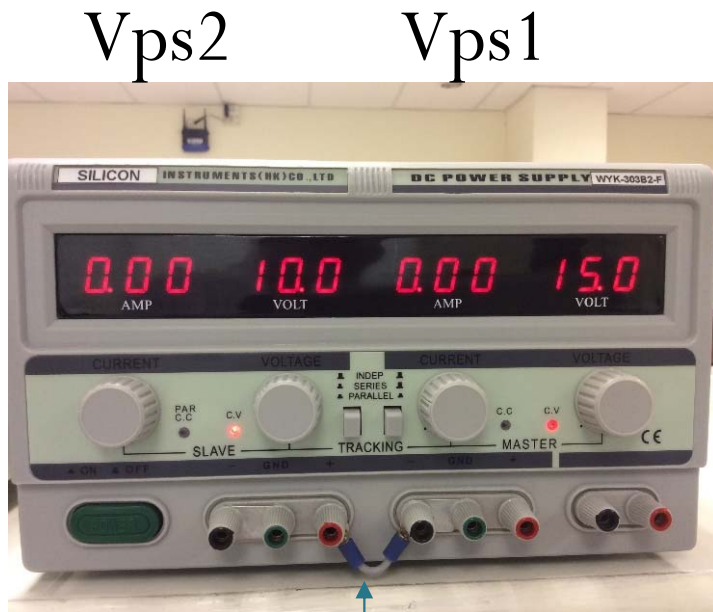


This connection can use the small connector.

Note that it is the “-” (black) terminal of V_{ps1} that is connected to the “+” (red) terminal of V_{ps2} .

$$P_L = \frac{V_L^2}{R_L}$$

Part B

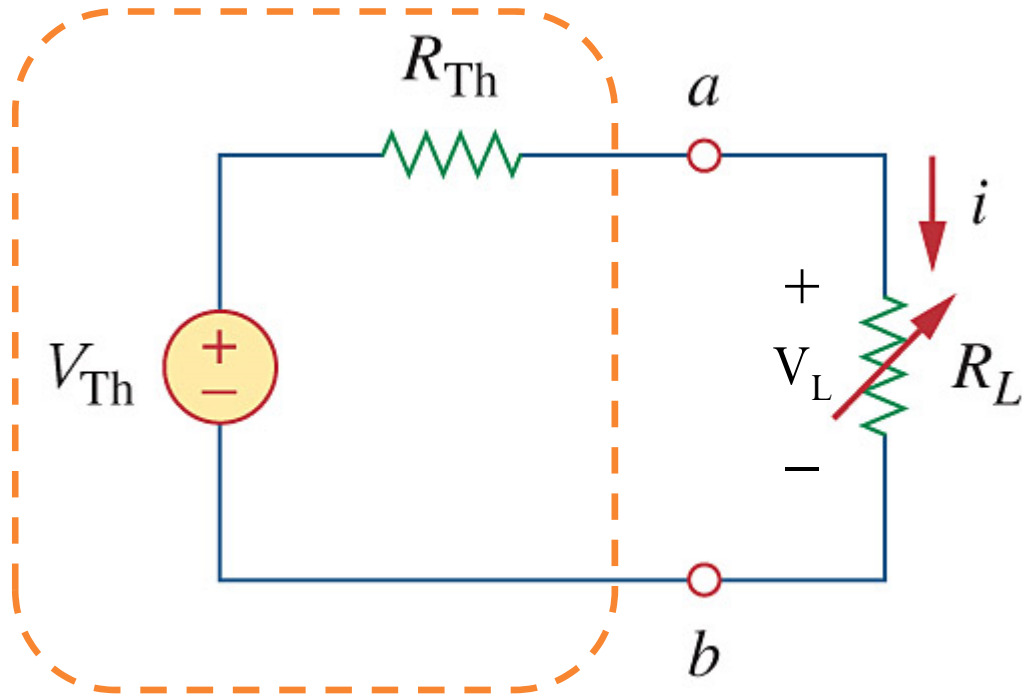

| $R_C = \underline{\hspace{2cm}} \Omega$ | | $V_{PS1} = \underline{\hspace{2cm}} V$ | |
|---|-----------|--|--|
| $R_L (\Omega)$ | $V_L (V)$ | Calculated P_L (mW) | |
| 0 | | | |
| 300 | | | |
| 600 | | | |
| 900 | | | |
| 950 | | | |
| 1000 | | | |
| 1050 | | | |
| 1100 | | | |
| 1400 | | | |
| 1700 | | | |
| 2000 | | | |

You may have to combine the potentiometer (in series) with some regular resistor to produce the desired resistance value.

