



COURSE : ECS 204 Basic Electrical Engineering Lab
INSTRUCTOR : Asst. Prof. Dr. Prapun Suksompong (prapun@siit.tu.ac.th)
WEB SITE : <http://www2.siiit.tu.ac.th/prapun/ecs204/>
EXPERIMENT : 06 Diodes and Rectifiers

I. OBJECTIVES

1. To study diodes and their applications to half-wave and full-wave rectifiers.
2. To study the use of capacitors as low-pass filters for ripple removal in rectifier circuits.

II. BASIC INFORMATION

II.1 Junction Diode

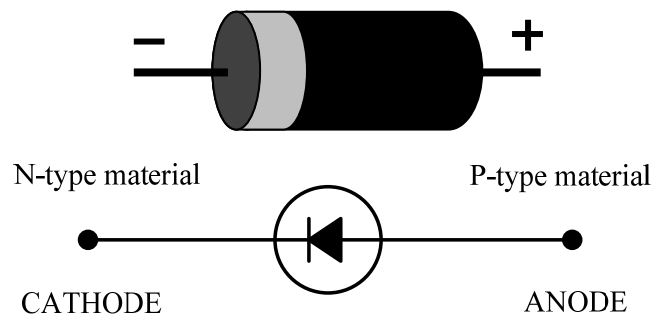


Figure 6-1: Circuit symbol for a semiconductor diode

1. A **junction diode** shown in Figure 6-1 has unidirectional current characteristics; that is, it will permit current to flow through in one direction (when forward-biased), but not the other (reverse-biased). Connection with the negative battery terminal to the N-type and the positive battery terminal to the P-type silicon is called **forward bias**, and results in a flow of current. Connection with the negative battery terminal to the P-type and the positive battery terminal to the N-type is called **reverse bias**. The “**turn-on**” or

“**threshold**” voltage is 0.7 V for a silicon junction diode and 0.3 V for a germanium diode. Once this potential is applied across the diode, it will conduct appreciably.

2. A junction diode can be tested using an ohmmeter. The meter reads the current that the device allows as determined by the voltage applied from the meter. By the Ohm’s law, the current reading is then translated into a resistance measurement. When the ohmmeter leads are connected to the diode such that it is forward-biased, high current flows, indicating a low resistance. Reversing the ohmmeter leads causes reverse-biasing to the diode. This prevents the current flow, and thus gives a high resistance reading.
3. The nonlinear characteristic of an ideal diode is illustrated in Figure 6-2. When the source voltage v_i is positive, i_D is positive and the ideal diode becomes a short circuit ($v_D = 0$). When v_i is negative, i_D is zero and the ideal diode becomes an open circuit ($v_D = v_i$). The diode can be thought of as a switch controlled by the polarity of the source voltage. The switch is closed for positive source voltages and open for negative source voltages. In practice, however, v_D is not 0 but $v_D = 0.7$ V for a silicon diode.

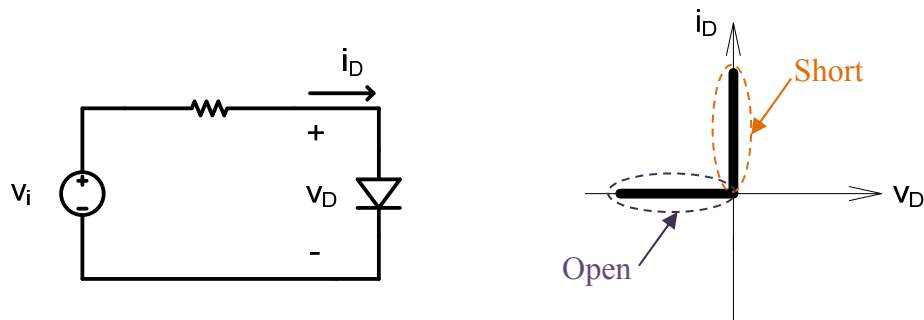


Figure 6-2: The ideal diode and v - i characteristic.

II.2 Rectifier

1. **Rectifiers** convert an ac voltage to a dc voltage. Applications of rectifiers are in both low power instrumentations and those involve higher power, such as dc power supplies.

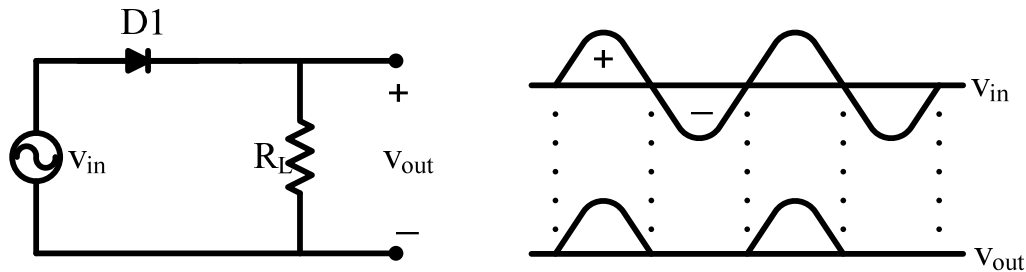


Figure 6-3-1: Diode half-wave rectifier and rectifier waveforms.

2. Figure 6-3-1 shows a **half-wave rectifier** circuit. The output of a half-wave rectifier is positive or zero depending on whether the input is positive or negative, respectively, as shown in Figure 6-3-1.

When the sinusoidal input voltage is positive, the diode is forward biased and therefore the diode conducts. When the sinusoidal input voltage is negative, the diode is reverse biased and no current flow through the diode. The current through the resistor in series with the diode is therefore zero. Hence the voltage across the resistor is zero.

3. For the half-wave rectifier shown in Figure 6-3-1, the average of the input voltage V_{in} is zero. The average value of the output voltage is

$$\frac{1}{2\pi} \int_0^{\pi} A \sin x dx = \frac{1}{2\pi} (2A) = \frac{A}{\pi}$$

where A is the peak input voltage. For example, if we use $13 V_{rms}$ input voltage, then

$$A \approx 13\sqrt{2} \approx 19 V_p,$$

the average value of the output voltage is $\frac{13\sqrt{2}}{\pi} \approx 6 V$.

These average values can be measured by the DMM in DC mode. In particular, Suppose a periodic signal $x(t)$ with period T is fed into DMM. In DC mode, the DMM will measure the average value which is

$$\frac{1}{T} \int_0^T x(t) dt$$

Remark: It is useful to remember that

the average of $\sin x$ is 0, the average of $\sin^2 x$ is $1/2$, and the average of $|\sin x|$ is $2/\pi$.

4. In this experiment, the input of the half-wave rectifier is a 220/(12-0-12) center-tapped transformer as shown in Figure 6-3-2.

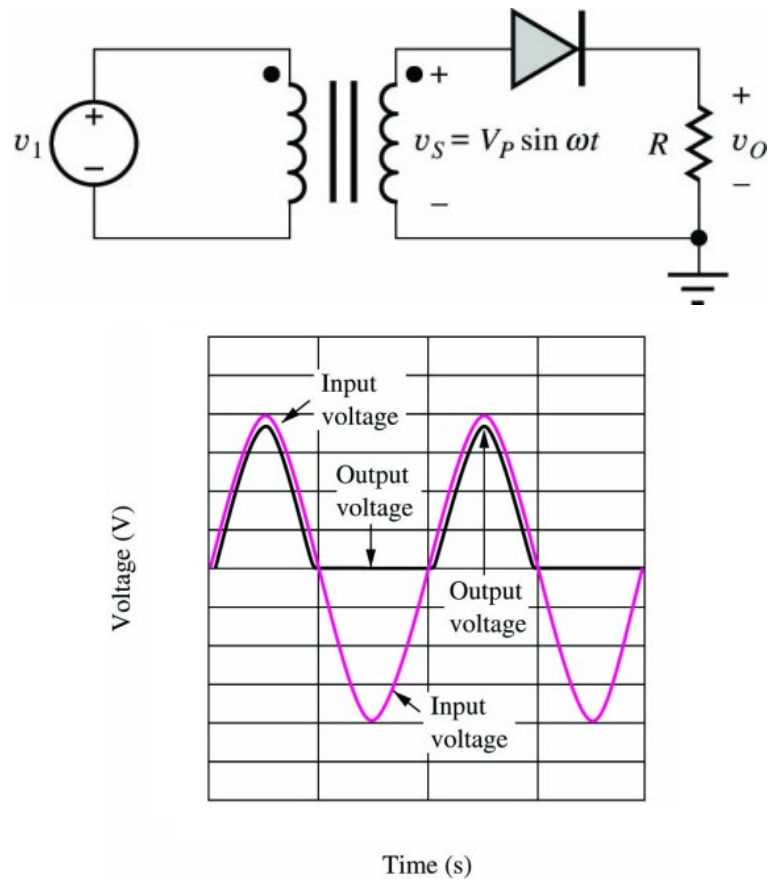


Figure 6-3-2: A half-wave rectifier and its output waveforms when the input is a 220/(12-0-12) center-tapped transformer

5. Figure 6-3-3 shows a **full-wave rectifier** using two diodes. The direction of the current flowing in the load resistor produces the positive output voltage, in both positive and negative input voltage.

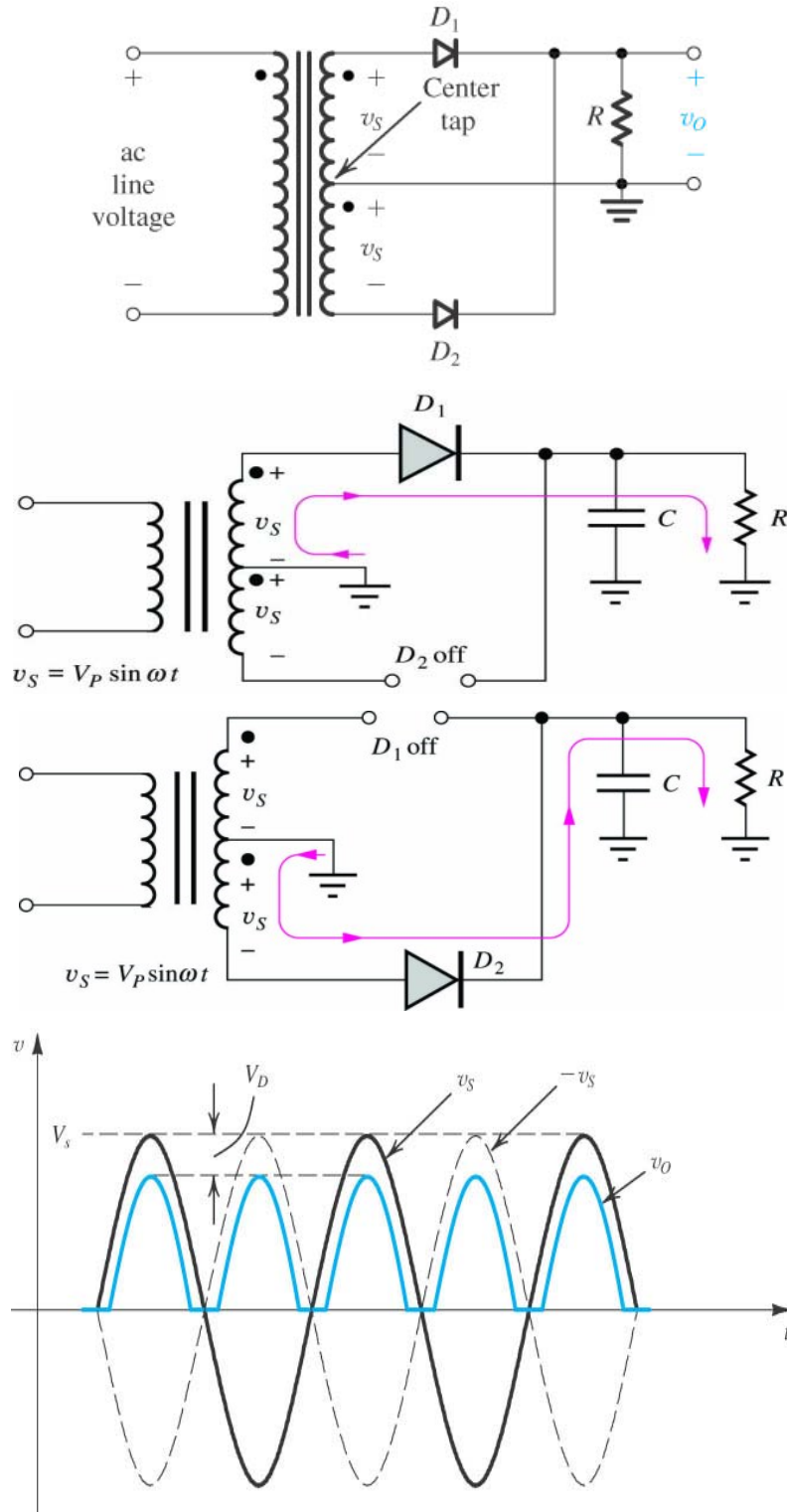


Figure 6-3-3: A full-wave rectifier and its output waveforms.

6. Figure 6-3-4 shows a **full-wave bridge rectifier** using four diodes.

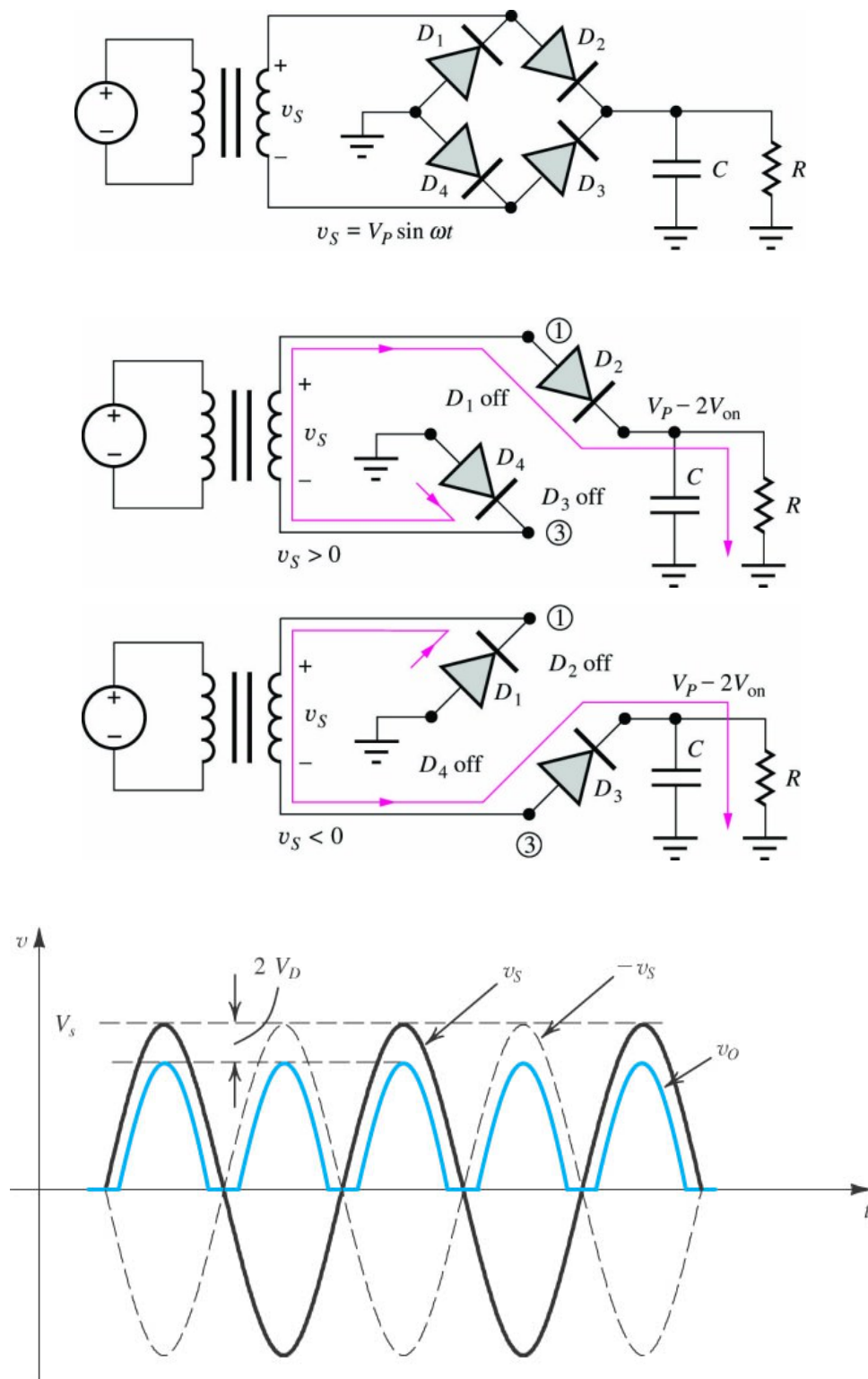


Figure 6-3-4: A full-wave bridge rectifier and its output waveforms.

7. The output of the rectifier contains considerable voltage variation called a **ripple**. A low-pass filter is usually required to remove the ripple. The simplest low-pass filter can be constructed using a **large capacitor** connected across the output of the rectifier, in parallel with the load resistor as shown in Figures 6-3-3 and 6-3-4. Figure 6-4 shows the output waveforms with ripples.

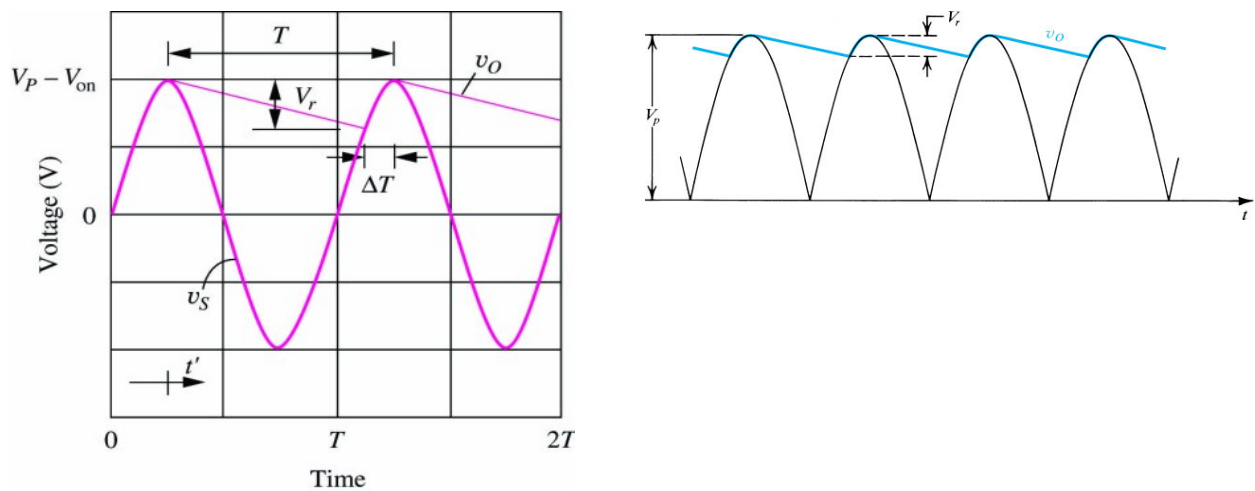


Figure 6-4: Output waveforms with ripples.

8. The polarity of the **electrolytic capacitor** is almost always indicated by a printed band. The lead nearest to that band is the cathode lead (-). Additionally, the positive lead is usually longer.

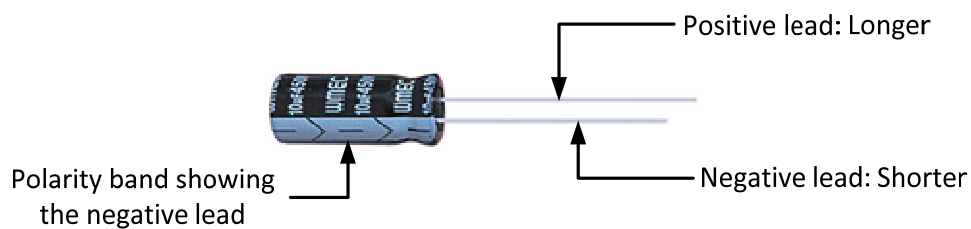


Figure 6-5: Electrolytic Capacitor

Caution: Most electrolytic capacitors are polarized. Hook them up the wrong way and at best, you'll block the signal passing through. At worst (for higher voltage applications) they'll explode.

9. A center tapped transformer is shown in Figure 6-6. The label '220/(12-0-12)' is represented in **rms** values. This means that when input (primary) voltage is approximately 220 V_{rms} , and the center output terminal is grounded, the output (secondary) voltages of the two side terminals will be approximately 12 V_{rms} and 12 V_{rms} (with opposite polarity).

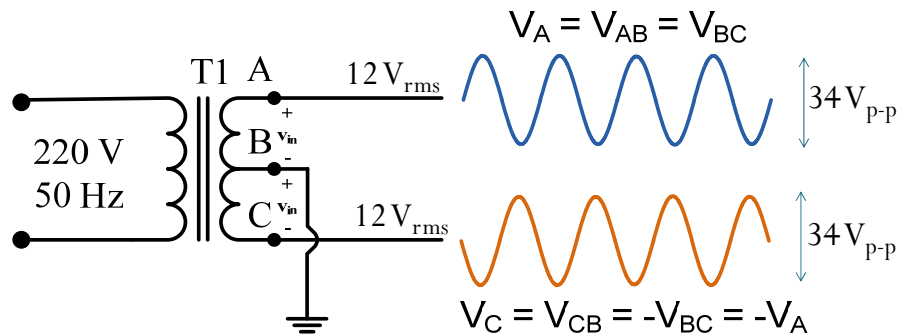


Figure 6-6: A Centre-Tapped Transformer

III. MATERIALS REQUIRED

Power supply: 240-V 50-Hz source¹

Equipment: Oscilloscope, Multi-meter.

Resistors: 1 k Ω , 2.7 k Ω , 5.6 k Ω , and 10 k Ω .

Capacitors: 100- μ F 50-V

Diodes: Four solid state diodes 1N4001

Power transformer with center tapped secondary, 220/(12-0-12).

IV. PROCEDURE

Warning:

This experiment use high voltage. Great care is needed to avoid direct contact to the transformer. Damage on any equipment, devices, or any part of your body is subject to punishment.

¹ Note that the rms output voltage from the electrical outlet is 240 V_{rms} instead of 220 V_{rms} . Therefore, the output voltages of the transformer will be higher 12 V_{rms} .

Part A: Half-wave and full-wave rectifiers.

1. Connect a half-wave rectifier circuit shown in Figure 6-7.

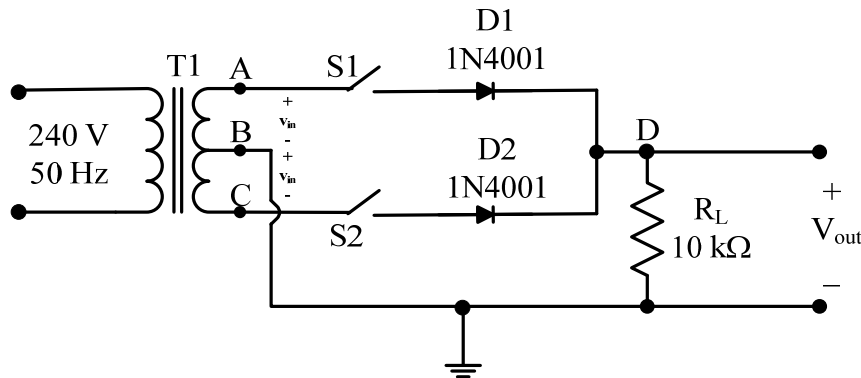


Figure 6-7: A half-wave and full-wave rectifier circuit.

2. Close the switch S1 and open the switch S2. This means that node 'A' is connected to the anode of D1, and node 'C' is not connected to the anode of D2.
3. Use the oscilloscope in DC mode. Measure the peak-to-peak voltage values and observe the waveforms of v_{in} (connect Channel 1 to node 'A'² with respect to³ node 'B') and V_{out} (connect Channel 2 to node 'D' with respect to node 'B'). Record the results in Table 6-1. Do not forget to indicate where the ground level of the voltage is.
Remark: Because B is connected to the ground and the transformer is center-tapped, we know that $v_C = -v_A$.
4. With a DMM (**in DC mode**), measure and record the DC voltage of V_{in} and V_{out} in Table 6-1.
5. Open S1 and close S2. Then repeat steps 3 and 4.⁴
6. Close S1 and S2. Then repeat steps 3 and 4.

² Note that node 'A' is on the transformer not the diode.

³ "Connect Channel 1 to node A with respect to node B" means "attach the probe tip to node A and the ground clip to node B".

⁴ Remark: To view v_{in} for this case, it may be tempting to move Channel 1 of the oscilloscope from AB to BC. However, this will separate the two probe grounds of the oscilloscope to two different places (which will cause trouble.) Therefore, we keep Channel 1 of the oscilloscope at output terminal A of the transformer as in step 3. It is also tempting to view v_C directly by moving Channel 1 to node 'C'. However, on the oscilloscope, your v_C will look exactly the same as v_A instead of having opposite polarity. This is because the triggering operation of the oscilloscope (which shifts the signal such that it is not aligned with the original $v_{in} = v_A$ anymore). Moreover, because the signal is shifted, you can not compare the phase of v_{out} with the original v_{in} . If you have to look at v_C , it is possible to use Channel 2 (while leaving Channel 1 connected to terminal A so that the oscilloscope is triggered at the same place) to view v_C and then move Channel 2 to the output to view v_{out} .

Part B: Effects of a filter capacitor on the output of full-wave rectifier.

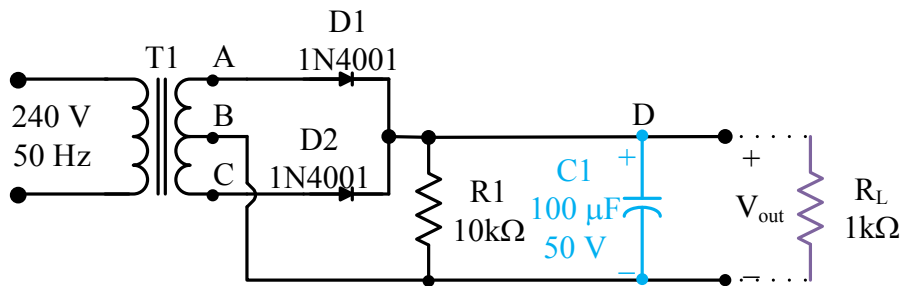


Figure 6-8: A full-wave rectifier with capacitor filter.

1. Connect the circuit of Figure 6-8 **without** the load R_L . Note, again, that capacitor C_1 has +/- polarity, and its terminals must be connected correctly.
2. Use the DMM to measure V_{out} , the average (dc) output voltage across R_1 , and record the result in Table 6-2.
3. Set the oscilloscope in DC mode. Connect Channel 1 to node A with respect to node B and connect Channel 2 to node D with respect to node B.
4. On channel 2, observe, measure, and record **the ripple waveform** and its peak-to-peak voltage in Table 6-2. Note that it may be easier to find the peak-to-peak voltage of the ripple when the oscilloscope is in AC mode.
5. Connect a 1 k Ω load resistor (R_L).
6. Repeat steps 2 to 4.

Part C: Bridge rectifier.

1. Connect a full-wave bridge rectifier as shown in Figure 6-9. Note that one end of the transformer secondary is open.

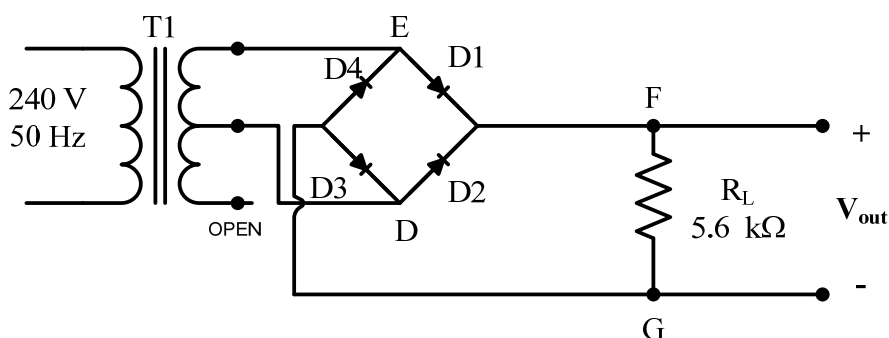
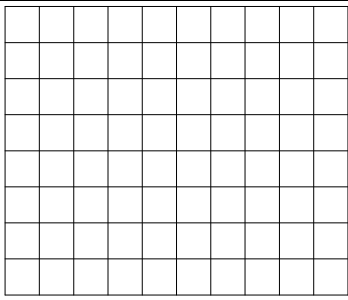
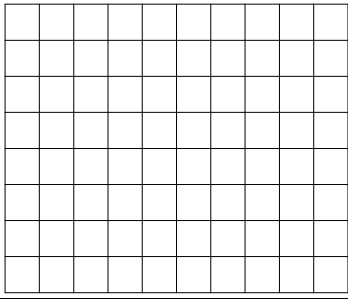
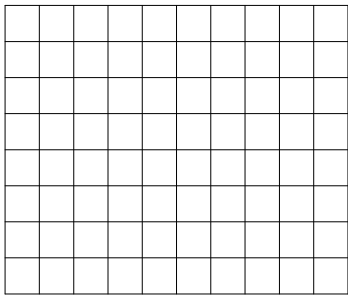
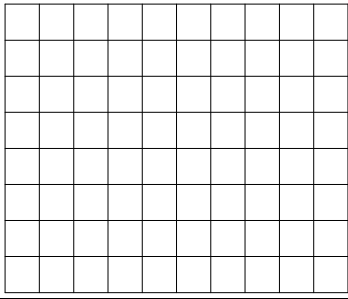
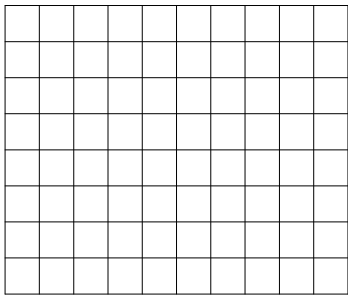


Figure 6-9: A bridge rectifier circuit.

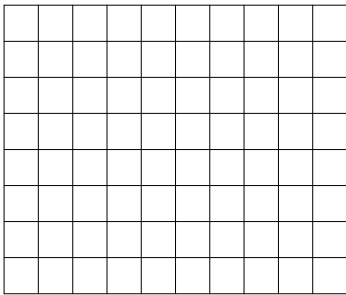
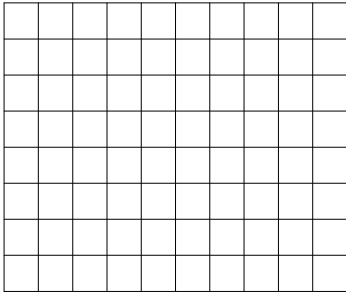
2. With the oscilloscope in DC mode, observe and draw the waveform of V_{out} (the output voltage across R_L) in Table 6-3.

TABLE 6-1: Half-wave and full-wave measurements.

<p>(A.3, A.4) V_{in} (A to B) close S1 open S2</p>		<p>V_{p-p} = _____ V_{DC} = _____ volts/div = _____ Time/div = _____</p>
<p>(A.3, A.4) V_{out} close S1 open S2</p>		<p>V_{p-p} = _____ V_{DC} = _____ volts/div = _____ Time/div = _____</p>
<p>(A.5) V_{in} (A to B) close S2 open S1</p>		<p>V_{p-p} = _____ V_{DC} = _____ volts/div = _____ Time/div = _____</p>
<p>(A.5) V_{out} close S2 open S1</p>		<p>V_{p-p} = _____ V_{DC} = _____ volts/div = _____ Time/div = _____</p>
<p>(A.6) V_{out}(full-wave) close S1 close S2</p>		<p>V_{p-p} = _____ V_{DC} = _____ volts/div = _____ Time/div = _____</p>

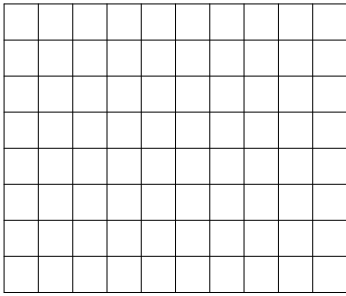
TA's Signature: _____

TABLE 6-2. Capacitive Filter.

Load [Ohms]	Ripple Waveform	
No load		Average $V_{out} =$ _____ $V_{p-p} =$ _____ volts/div = _____ Time/div = _____
1 k Ω		Average $V_{out} =$ _____ $V_{p-p} =$ _____ volts/div = _____ Time/div = _____

TA's Signature: _____


TABLE 6-3. Bridge rectifier output

	volts/div = _____ Time/div = _____
---	---------------------------------------

TA's Signature: _____

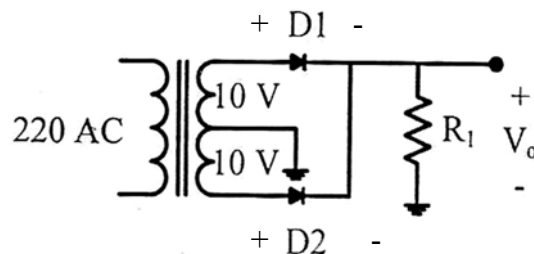V. QUESTIONS

- The most common materials used to manufacture diodes are:
 - Silicon and Germanium
 - Silicon and Gallium Arsenide
 - None of the above.
 - Silicon and Selenium
 - Silicon and Cuprous Oxide
- Diodes have two terminals, called:
 - Positive and negative
 - Source and drain
 - None of the above.
 - Bar and triangle
 - Emitter and collector
- The typical voltage drop on a silicon diode is:
 - 0.15 V
 - 0.5 V
 - None of the above.
 - 0.3 V
 - 0.6 V to 0.7 V
- If values of voltage which are shown below measure from DMM, what are the voltages peak across R_1 , D_1 and D_2 ?



- 10 V, 10 V and 10 V
- 10 V, 20 V and 20 V
- 14.14 V, 14.14V and 14.14V
- 14.14V, 28.28V and 28.28V
- None of the above.

Do not forget to justify your answer.