

Basic Elec. Engr. Lab

ECS 204

Asst. Prof. Dr. Prapun Suksompong


prapun@siit.tu.ac.th




Lab 8

- Operational amplifier
- V2I and I2V Converters
- Inverting Integrator

V2I and I2V Converters

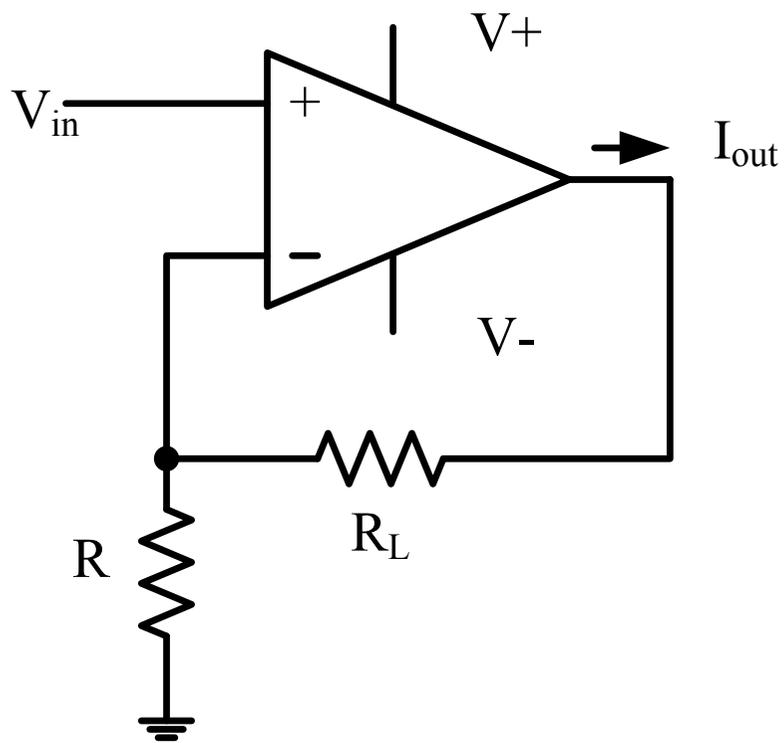


V2I Converter

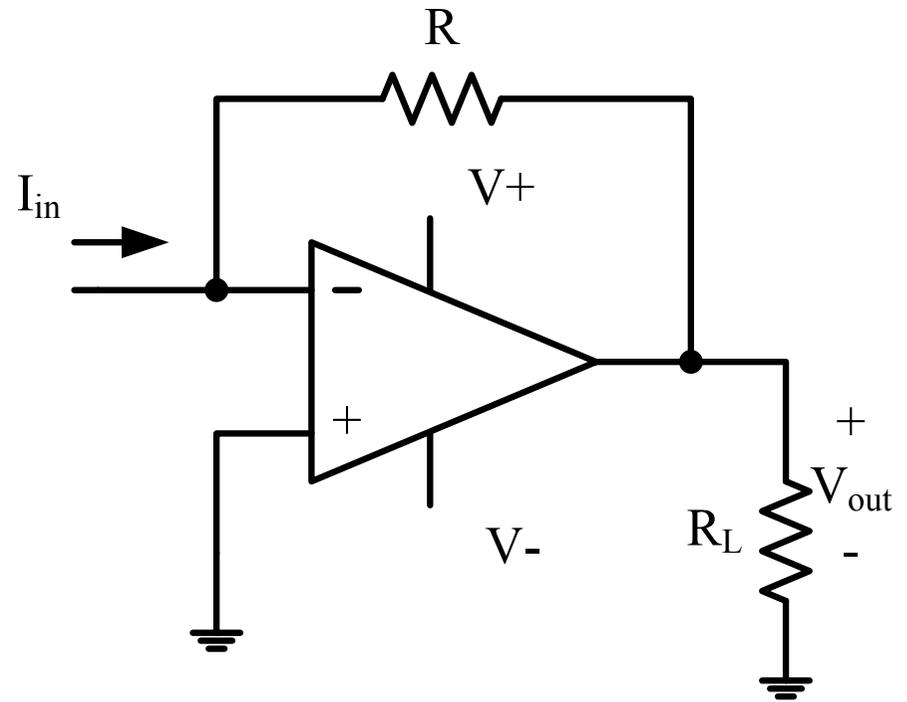


I2V Converter

V2I and I2V Converters


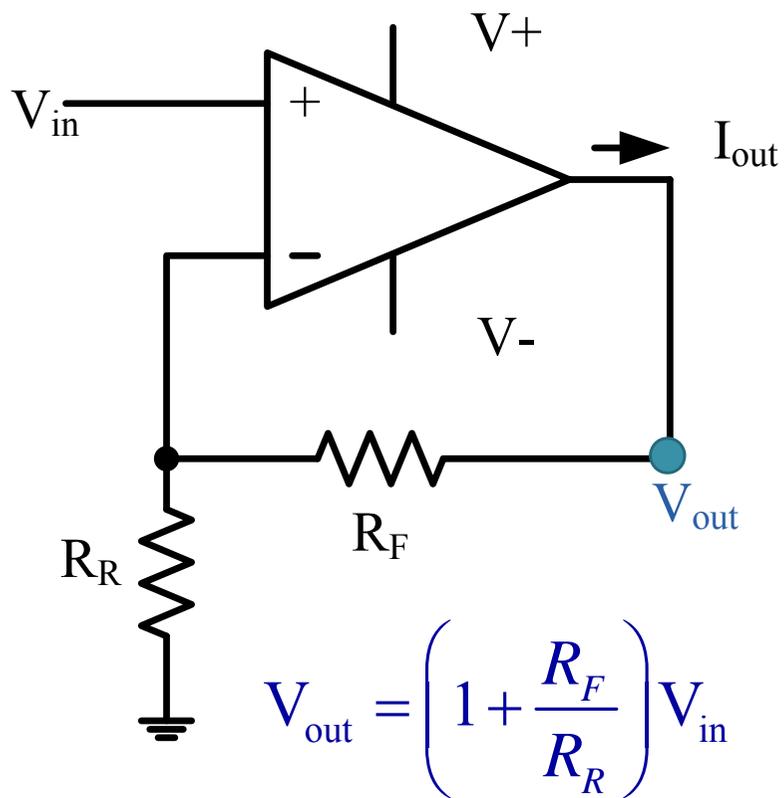


Non-inverting Amplifier

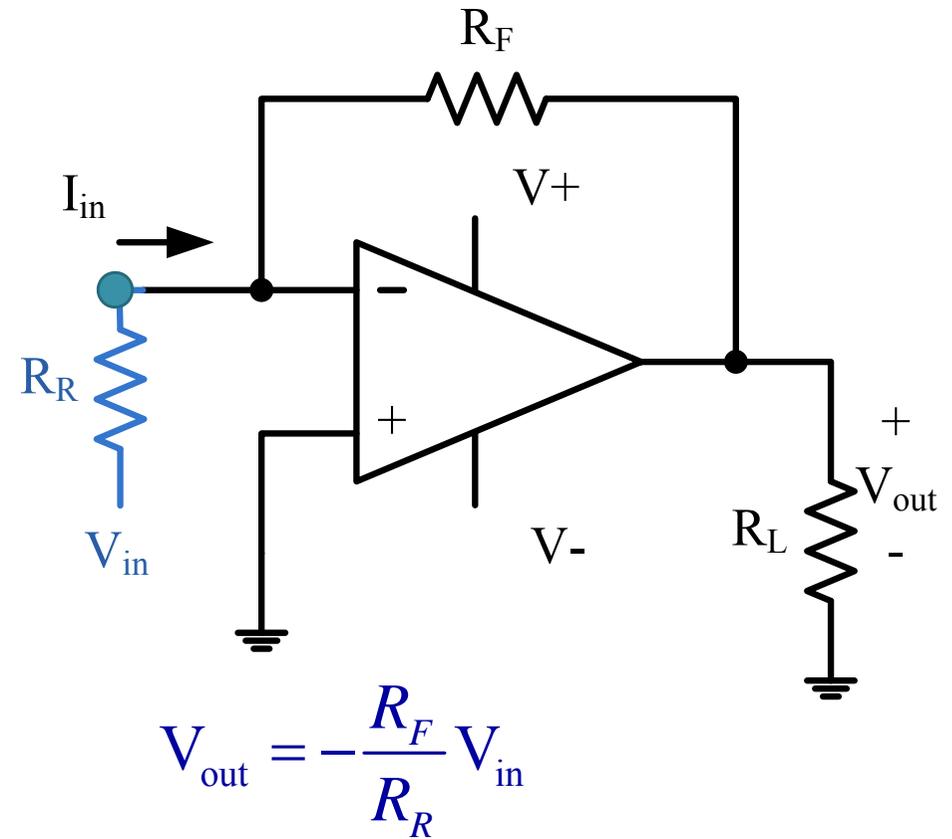


Inverting Amplifier

V2I and I2V Converters

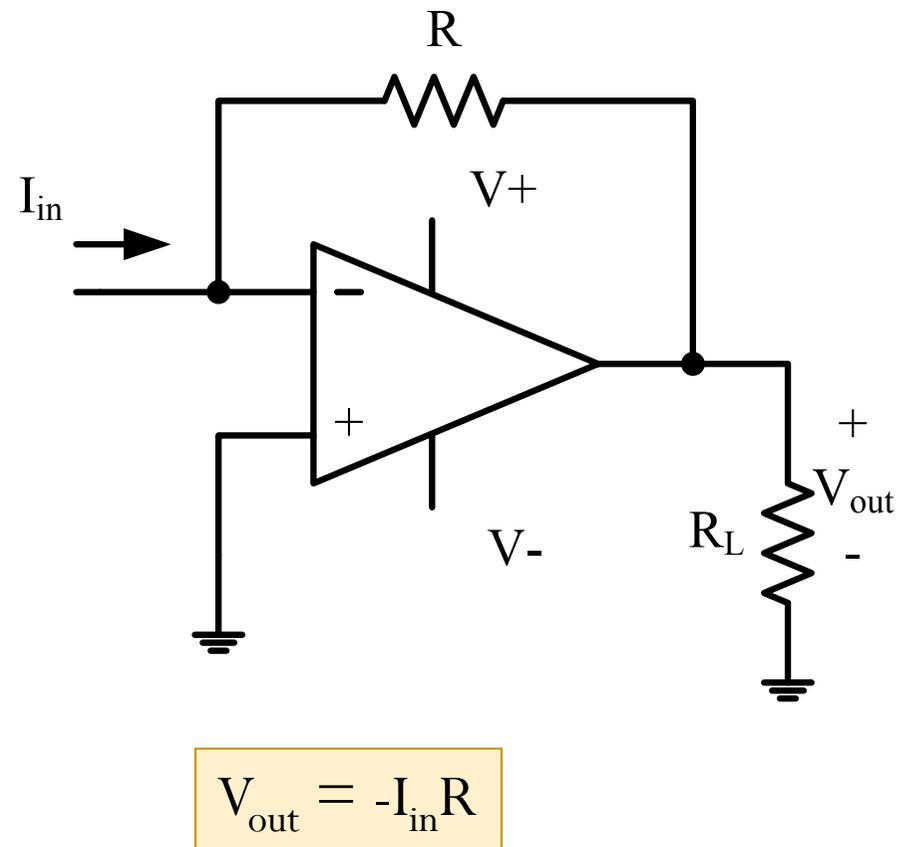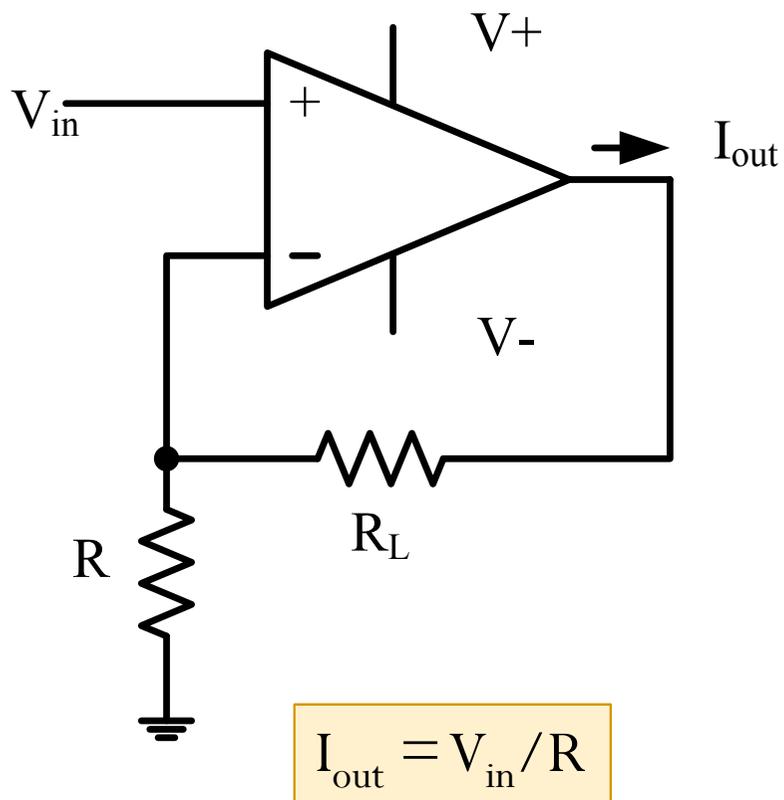


These relations hold regardless of the value of R_L .

A: Voltage-to-current converter

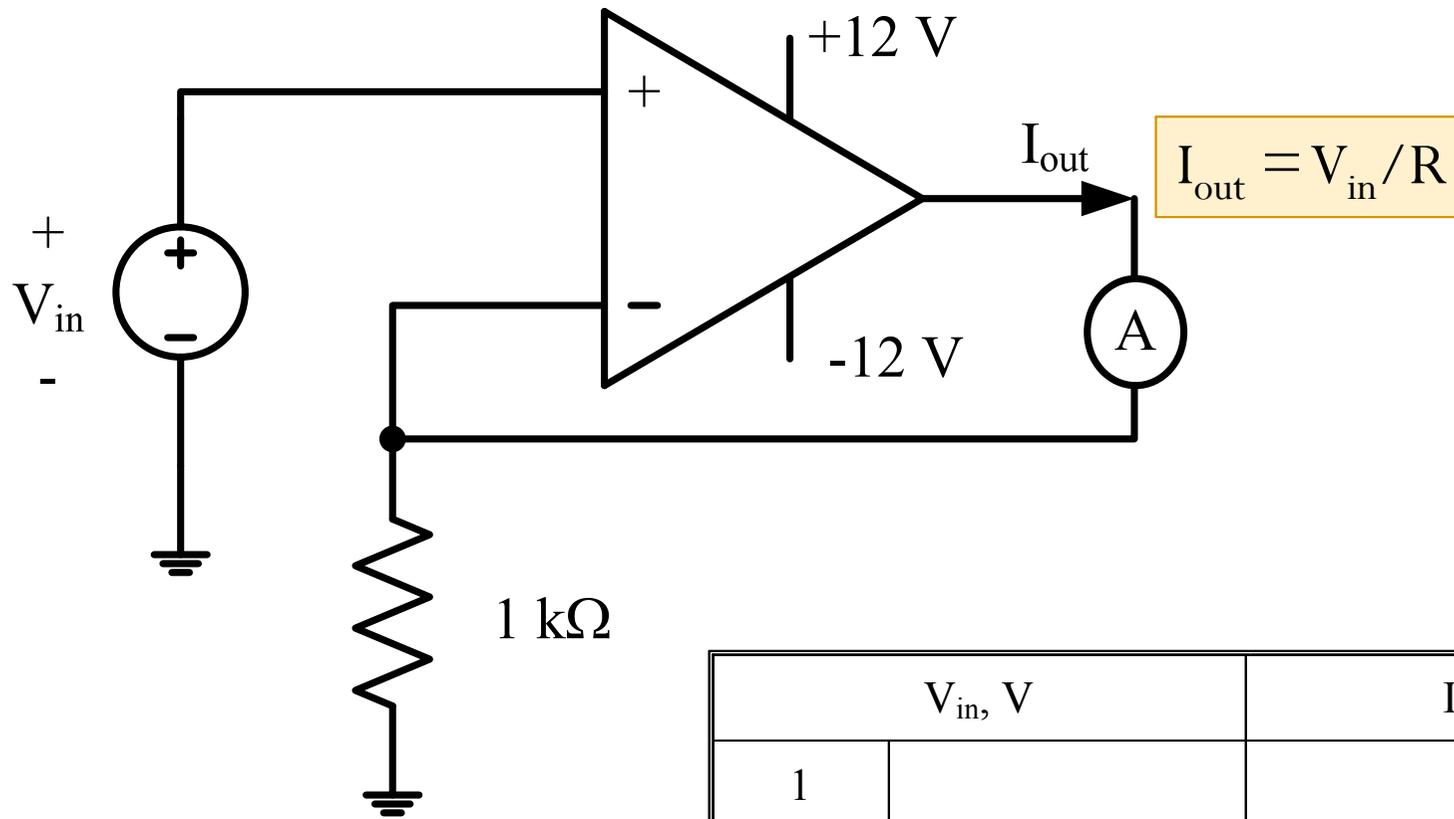


	V_{in}, V	I_{out}, mA
1		
3		
6		
10		

B: Current-to-voltage converter

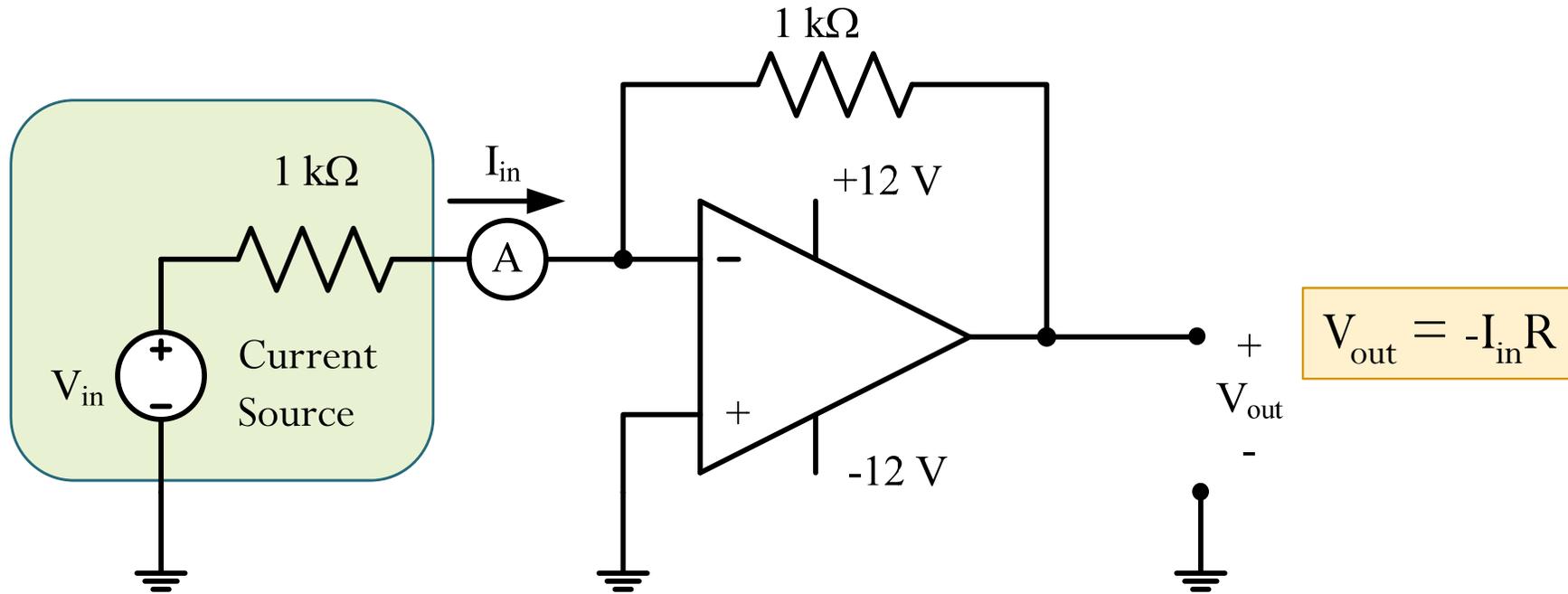

	$I_{in}, \text{ mA}$	$V_{out}, \text{ V}$
1		
3		
6		
10		

Part C: Inverting Integrator

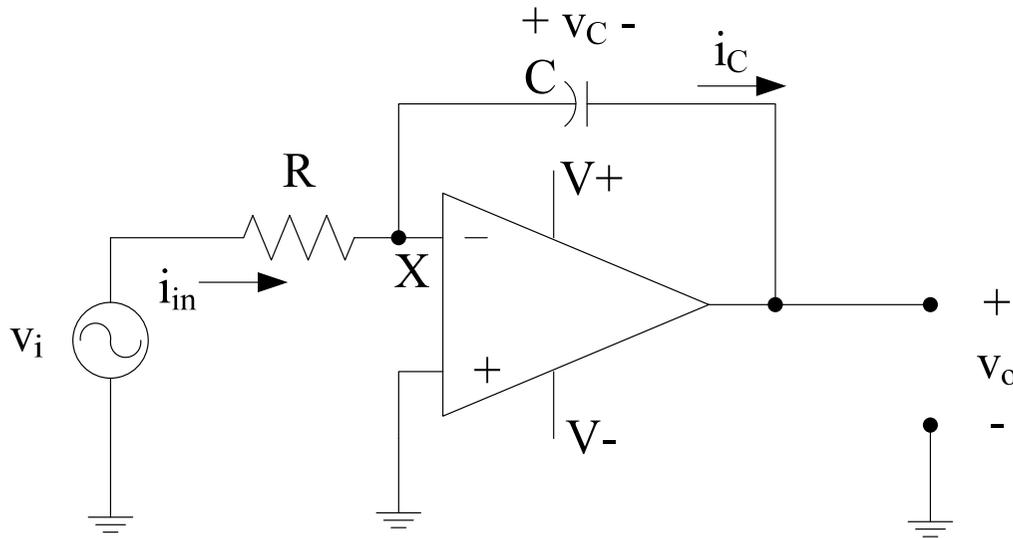


$$i_i(t) = i_c(t)$$


$$\frac{v_i(t)}{R} = -C \frac{d}{dt} v_o(t)$$

$$v_o(t) = v_o(0) - \frac{1}{RC} \int_0^t v_i(t) dt$$

As a Ramp Generator...

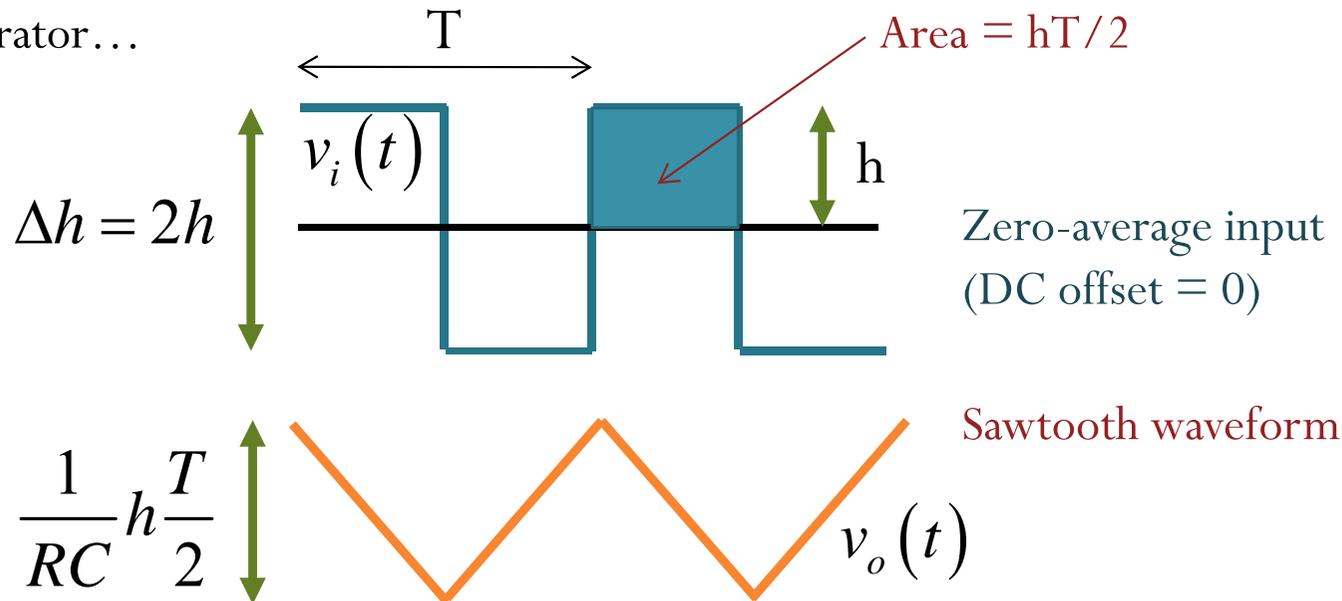

Inverting Integrator (2)

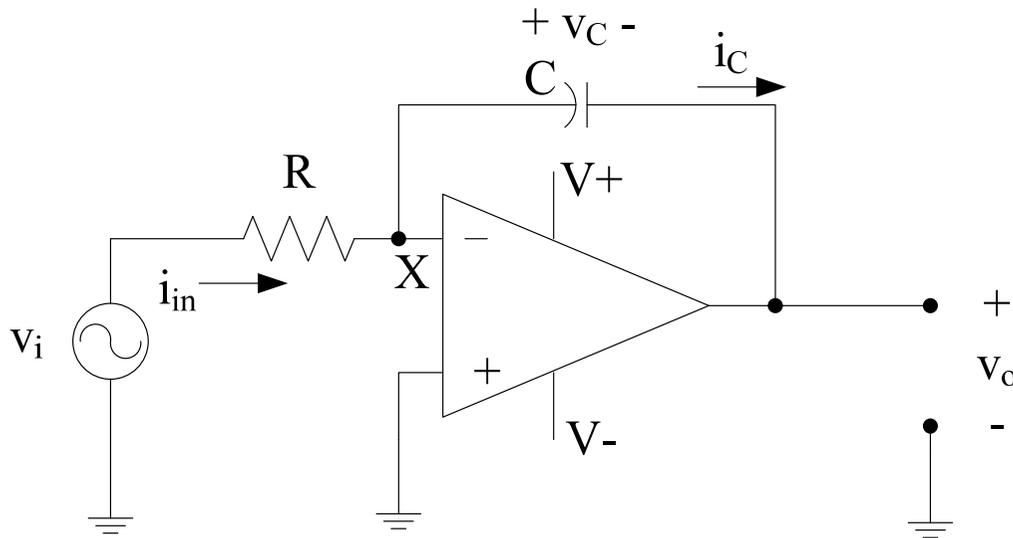


- An input with nonzero mean (DC offset) can saturate the op amp.


$$i_i(t) = i_c(t)$$

$$\frac{v_i(t)}{R} = -C \frac{d}{dt} v_o(t)$$
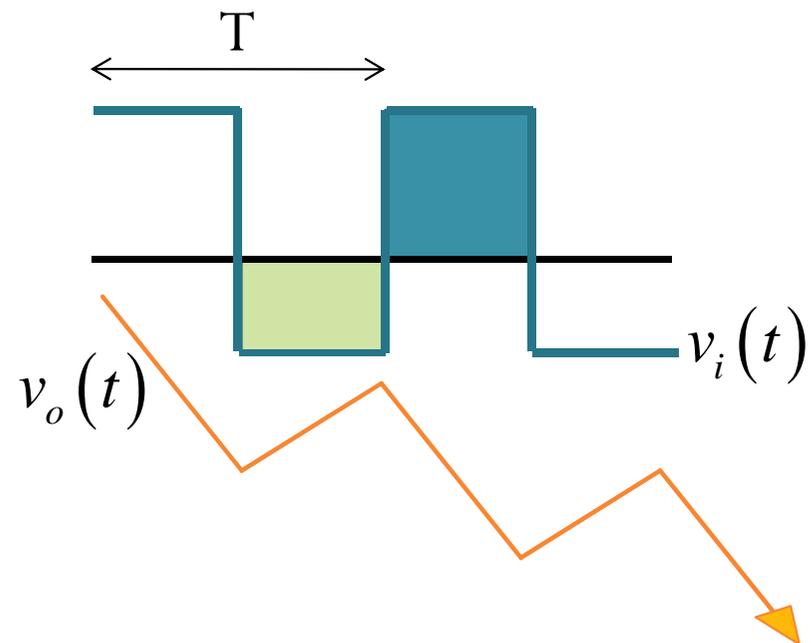
$$v_o(t) = v_o(0) - \frac{1}{RC} \int_0^t v_i(t) dt$$



Inverting Integrator: AC SS Analysis

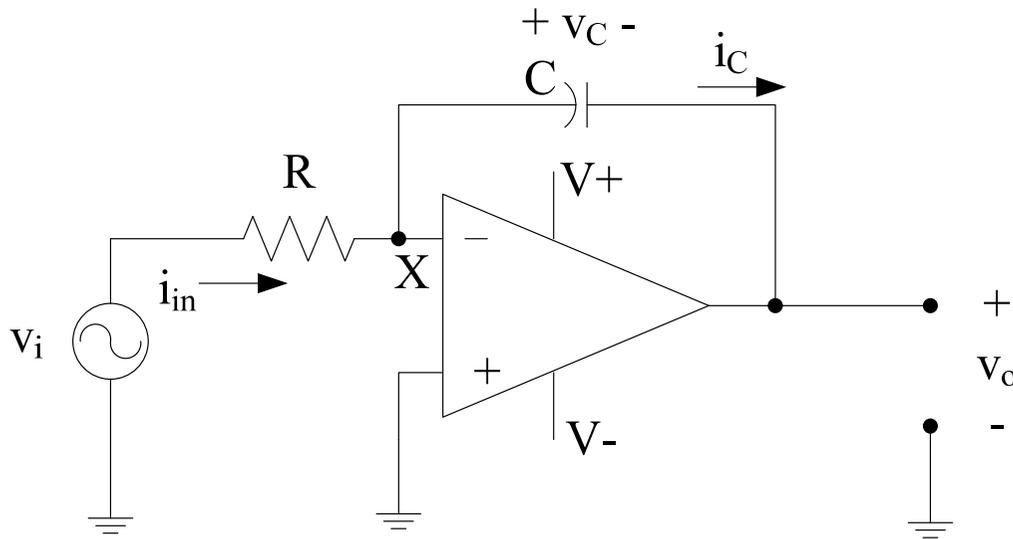


$$\begin{aligned} V_o &= -\left(\frac{Z_C}{R}\right)V_i \\ &= -\left(\frac{V_i}{R}\right) \times \frac{1}{j\omega C} \end{aligned}$$

- The gain at $f = 0$ is unbounded.
- Act like an **active low pass filter**, passing low frequency signals while attenuating the high frequencies.

(w/ DC Gain Control)

Inverting Integrator w/ Shunt Resistor

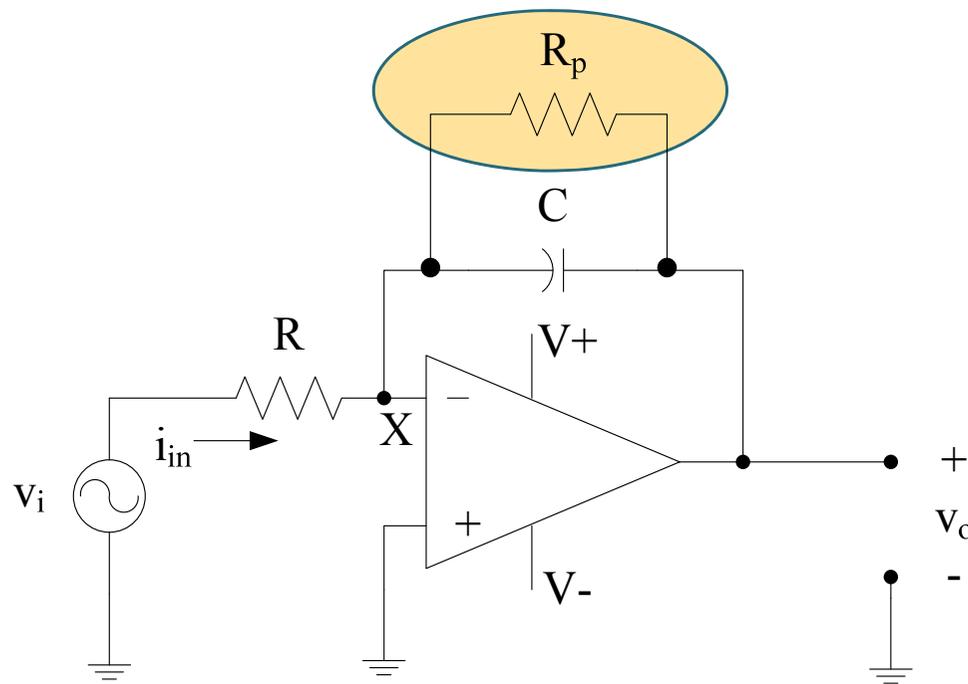
- In practical circuit, a large resistor R_p is usually shunted across the capacitor



$$\begin{aligned} V_o &= - \left(\frac{Z_C // R_p}{R} \right) V_i \\ &= - \left(\frac{V_i}{R} \right) \times \frac{R_p}{j\omega R_p C + 1} \end{aligned}$$


- Observe that at $f = 0$, the gain is finite.

Inverting Integrator w/ Shunt Resistor

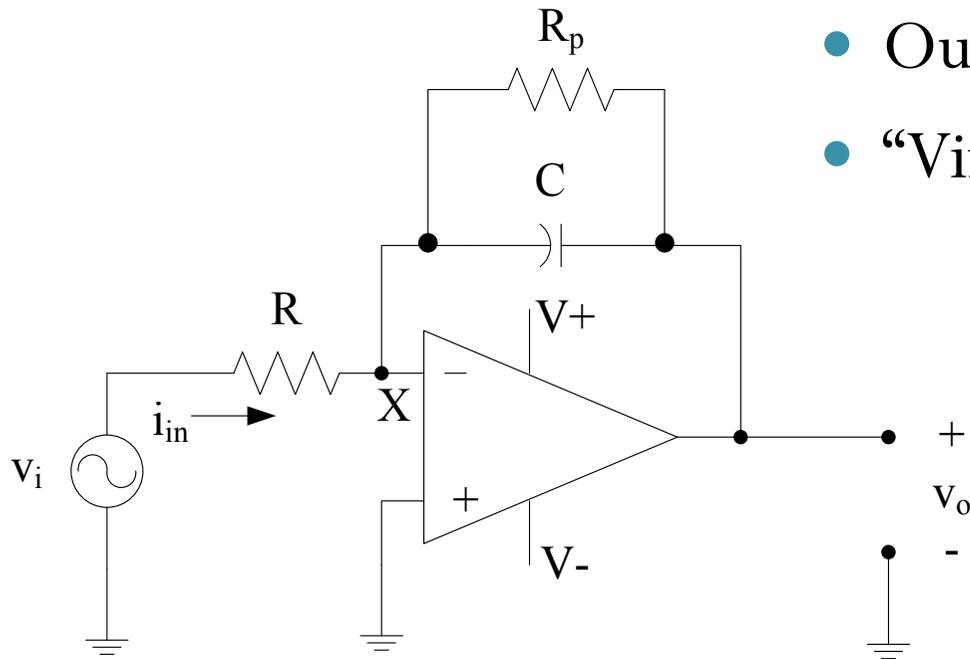

- Output is not triangular.
- “Virtually triangular” if $R_p C \gg \frac{T}{2}$
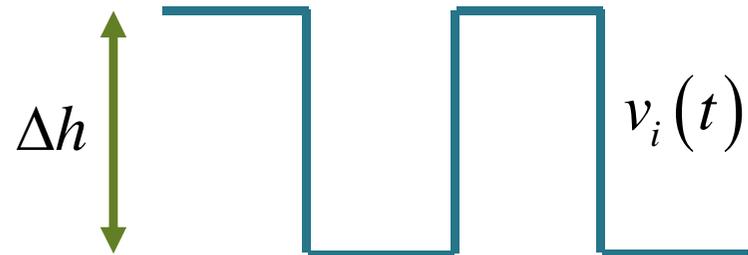
$$R_p \gg \frac{1}{2fC} \quad C \gg \frac{1}{2fR_p}$$



$$r = \exp\left(-\frac{1}{2fR_p C}\right) \quad \tau = R_p C$$