

Basic Elec. Engr. Lab

ECS 204

Asst. Prof. Dr. Prapun Suksompong


prapun@siit.tu.ac.th




Lab 2

- Thevenin's and Norton's Theorems
- New toy: Potentiometer
- Building a “fake” current source

Lab 2: Circuit under consideration


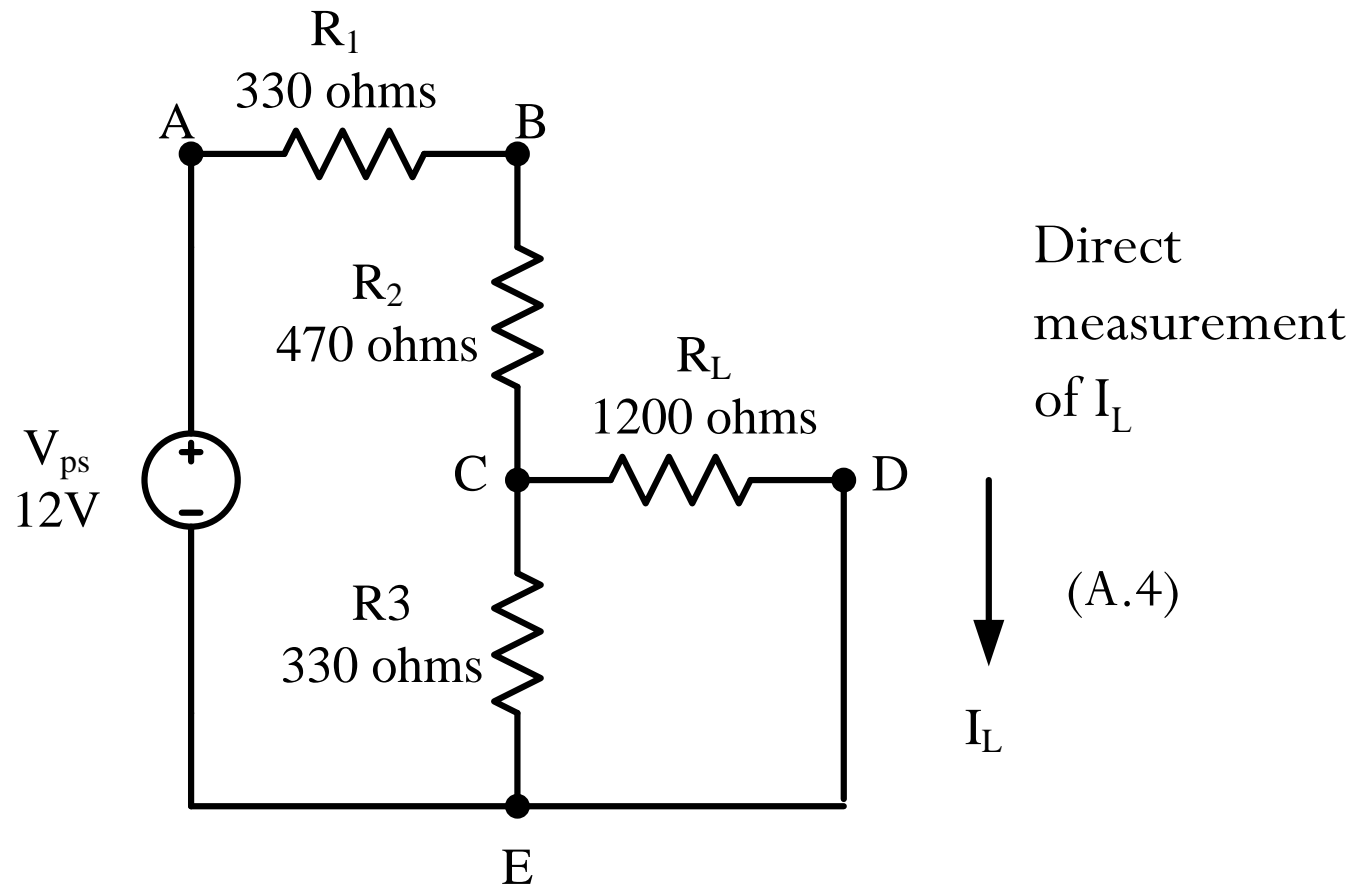


Outline of the lab

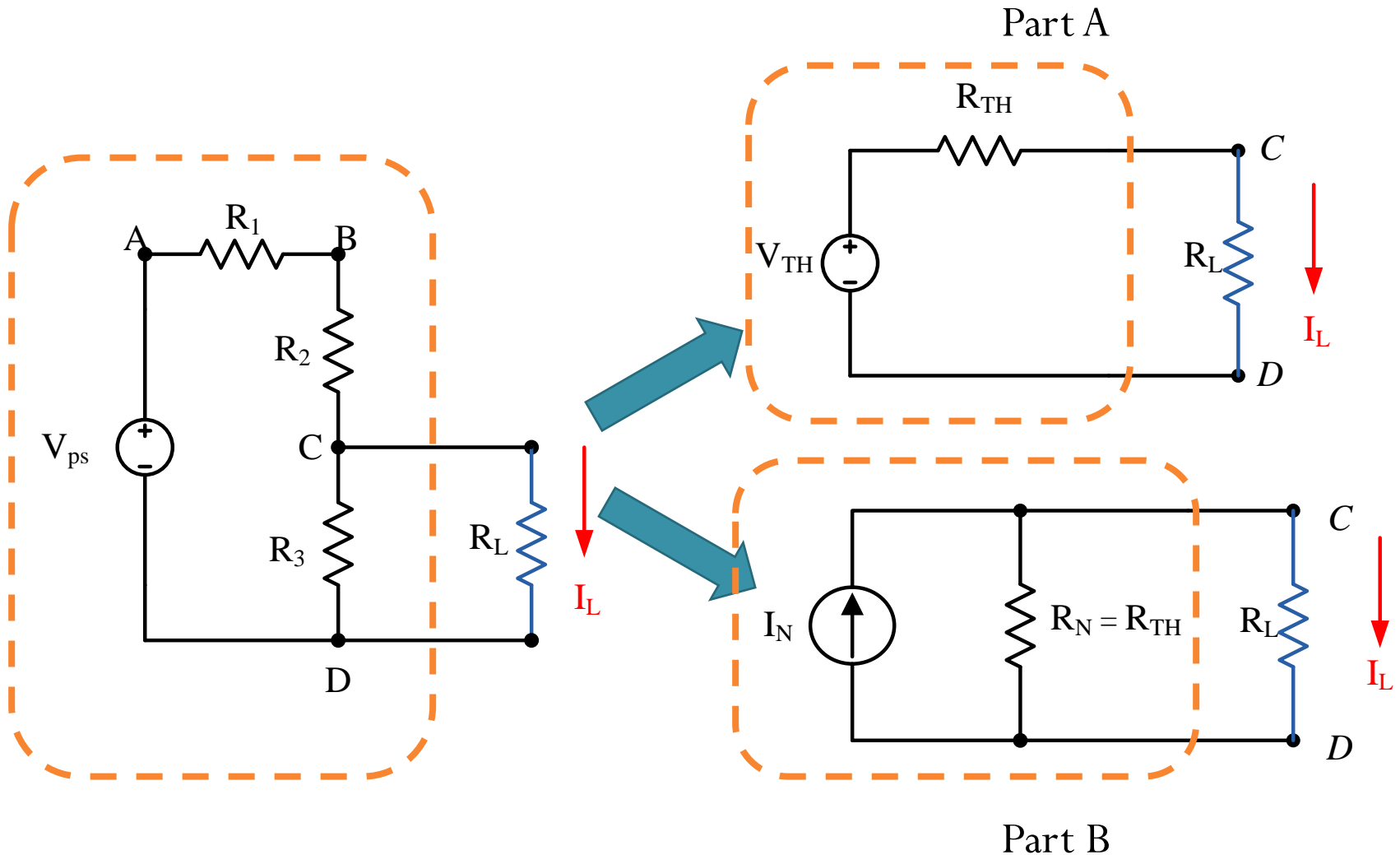

Part A: Thevenin Equivalent (1)

Part A

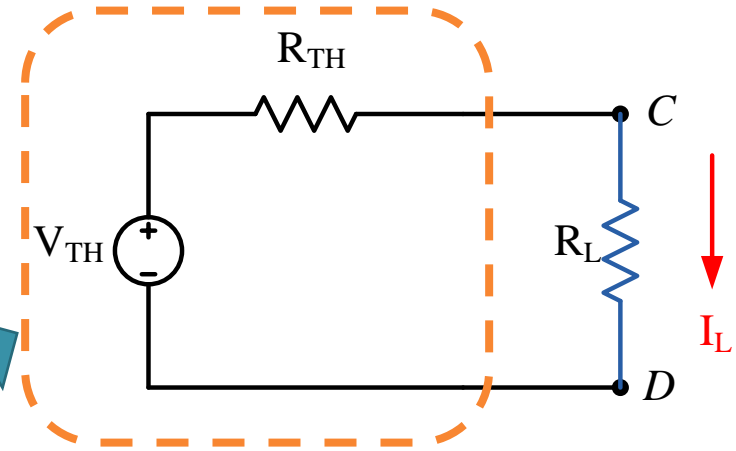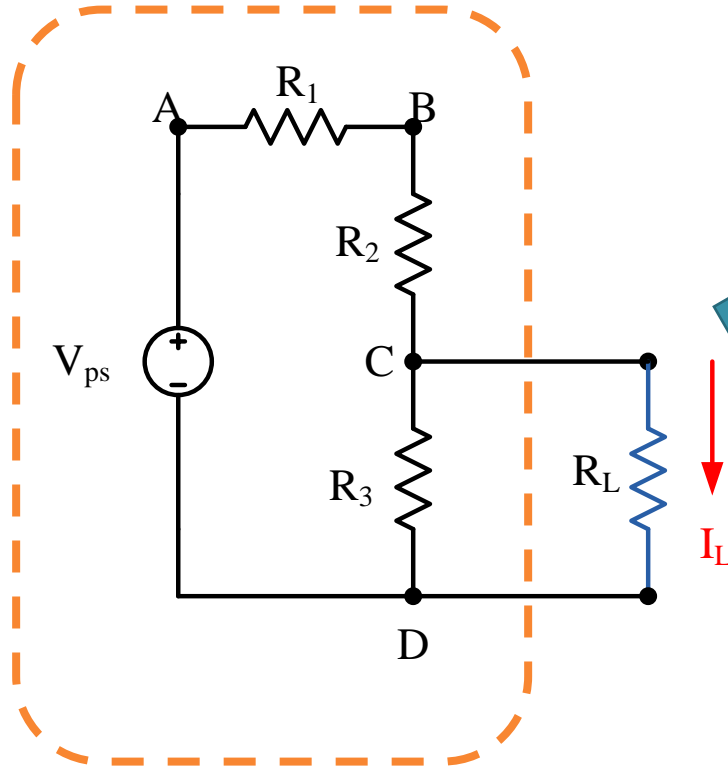



$$V_{TH} = \frac{R_3}{R_1 + R_2 + R_3} V_{ps} \quad (\text{A.12})$$

$$R_{TH} = R_3 // (R_1 + R_2) \quad (\text{A.13})$$



$$I_L = \frac{V_{TH}}{R_{TH} + R_L} \quad (\text{A.14})$$

Part A: Thevenin Equivalent (2)


Part A

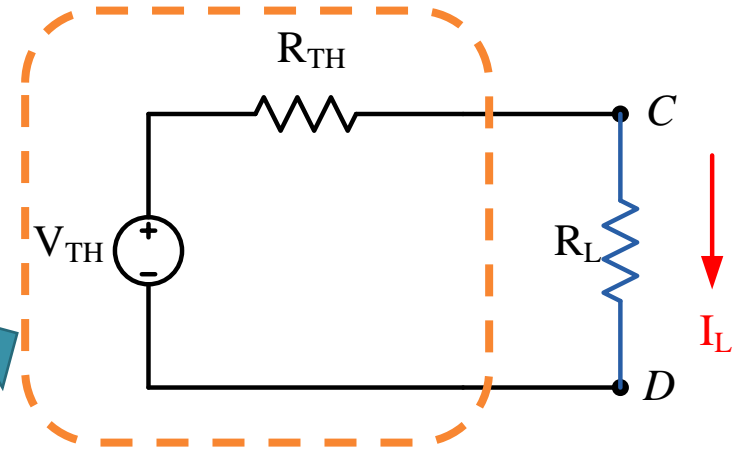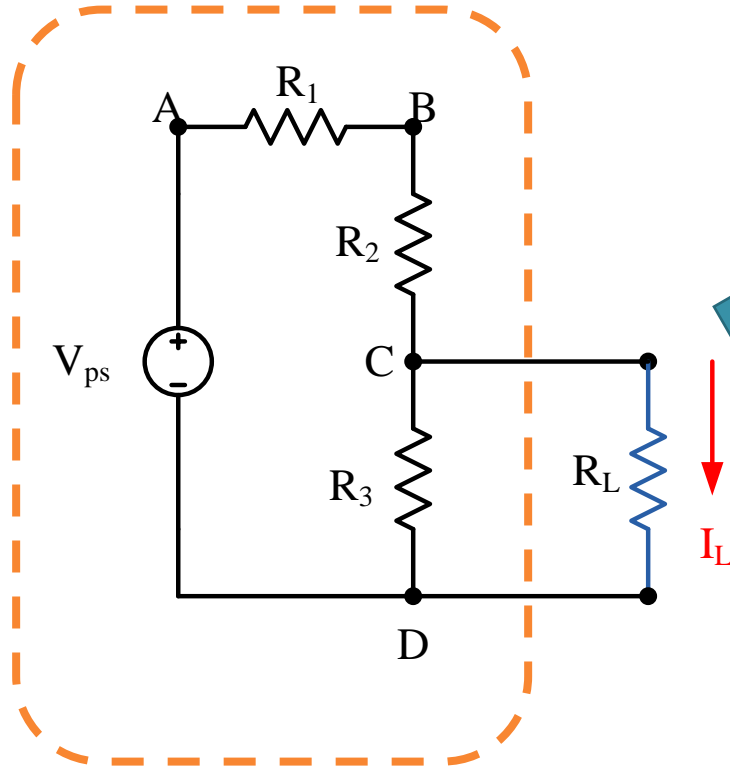

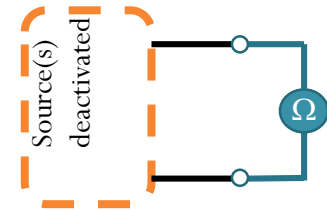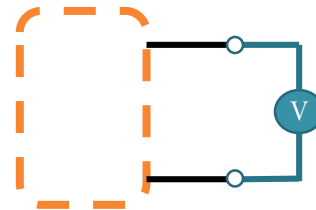Directly measure V_{TH} (A.5) and R_{TH} (A.8)
Build simplified circuit to measure I_L (A.11)




Part B: Norton Equivalent

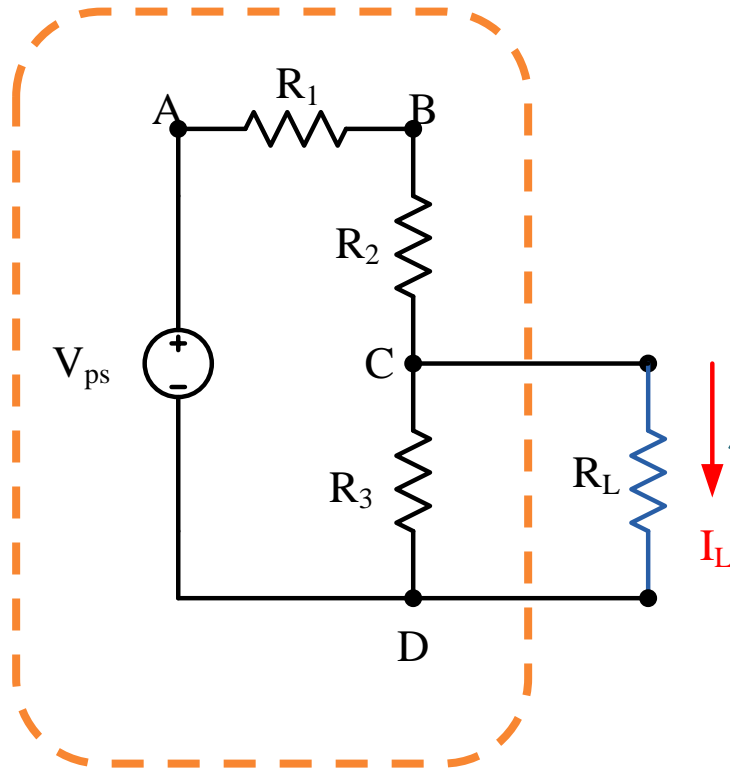

$$R_N = R_{TH}$$



$$I_N = \frac{V_{ps}}{R_1 + R_2} \quad (\text{B.6})$$
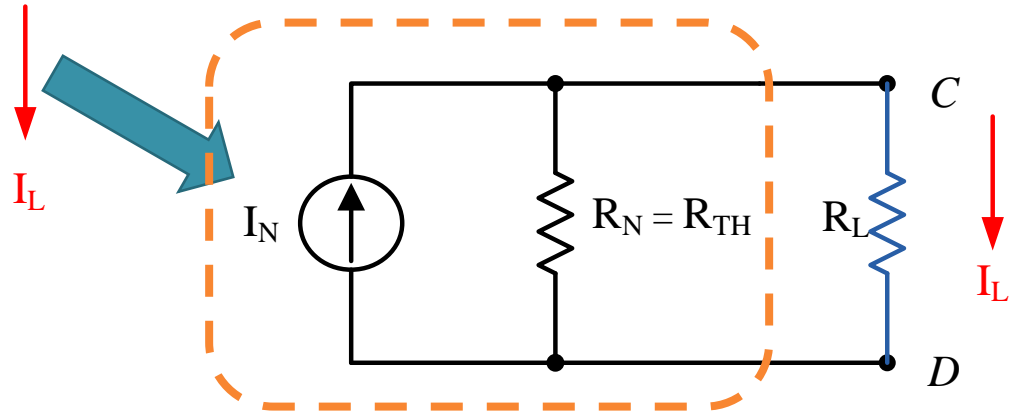
$$I_L = \frac{R_N}{R_L + R_N} I_N \quad (\text{B.7})$$




Part B

Part B: Norton Equivalent

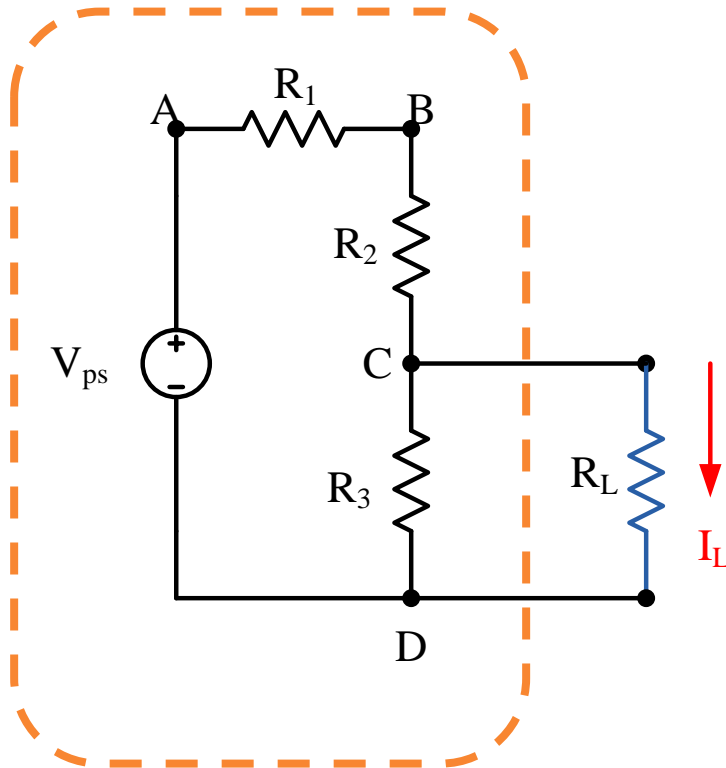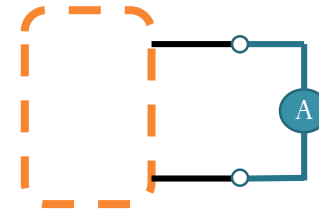


Directly measure I_N (B.2)

Build simplified circuit to measure I_L (B.5)


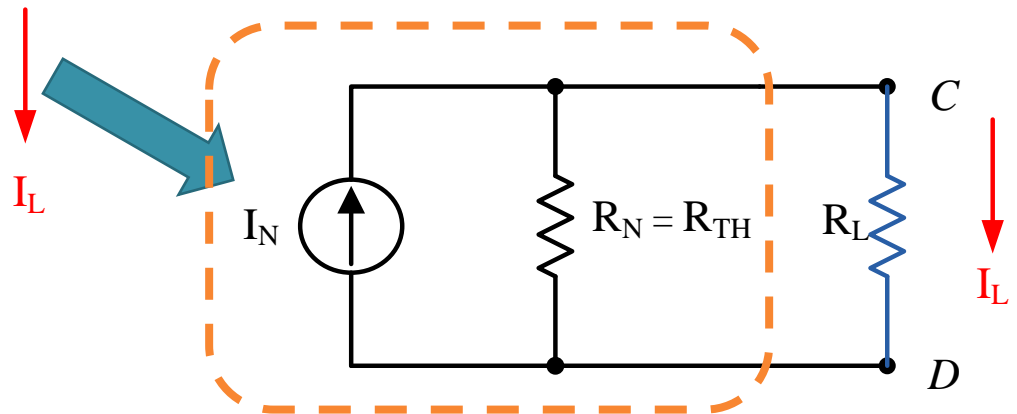


Lab 2: Summary

Part A



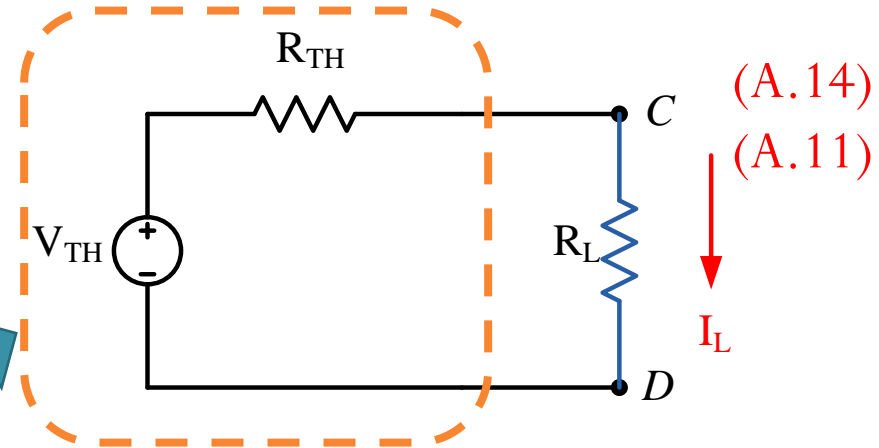


Part B

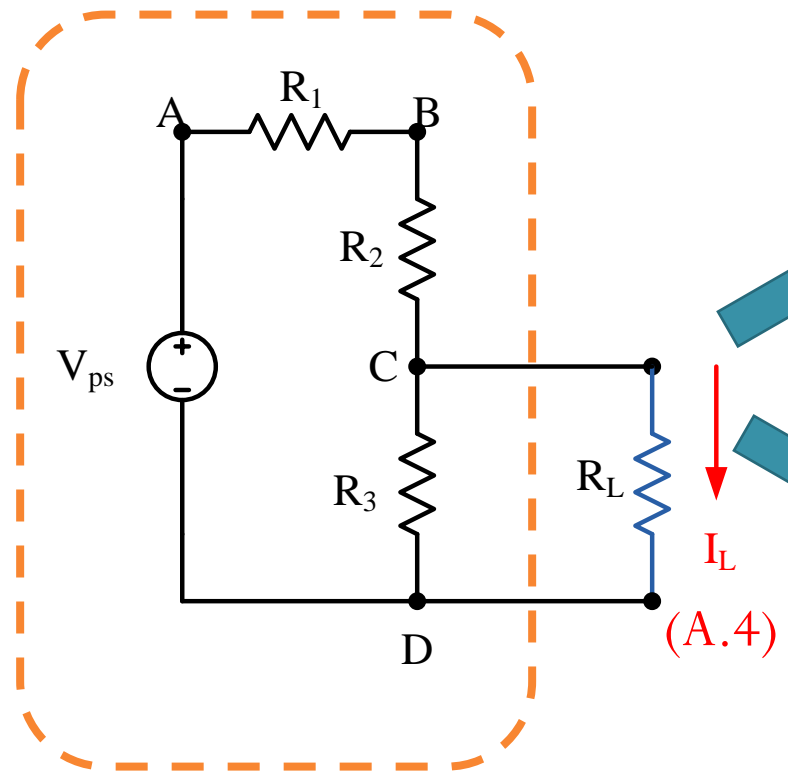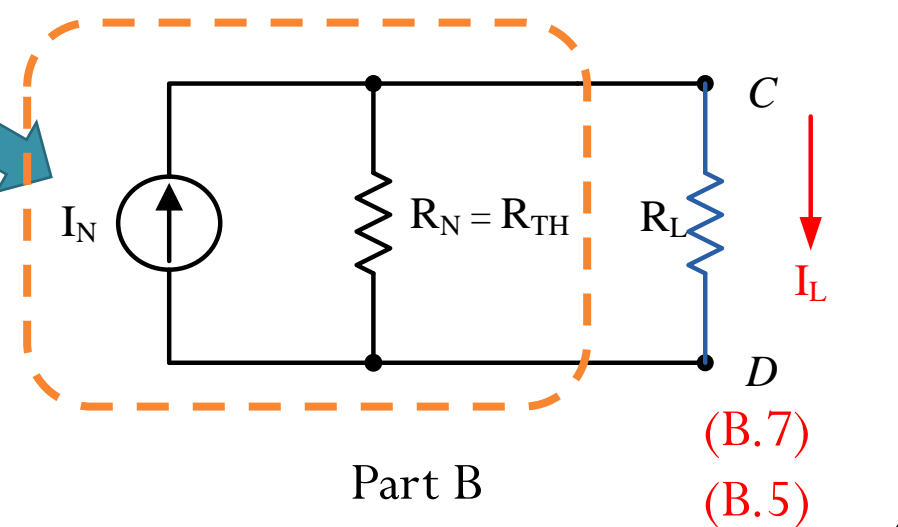

Lab 2: Summary

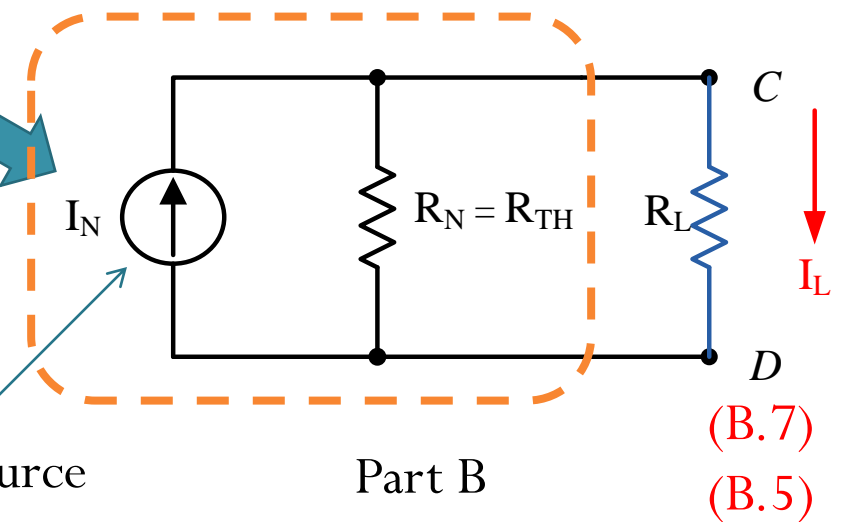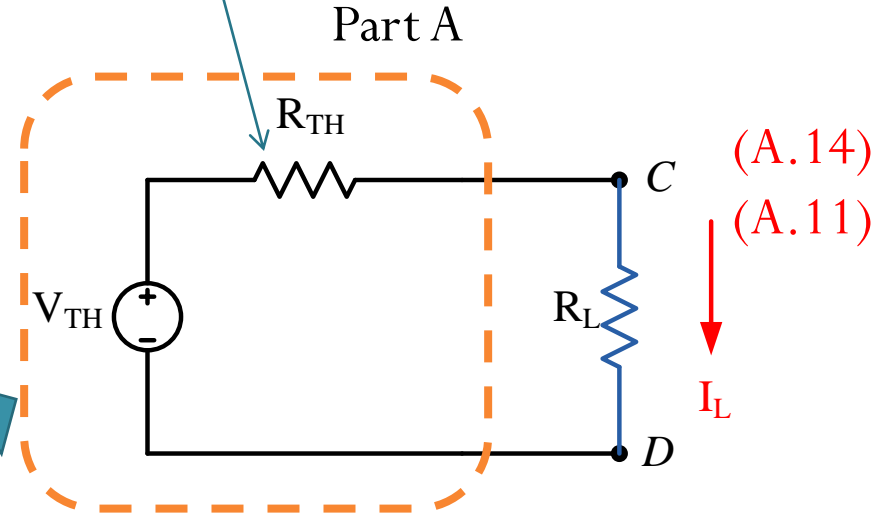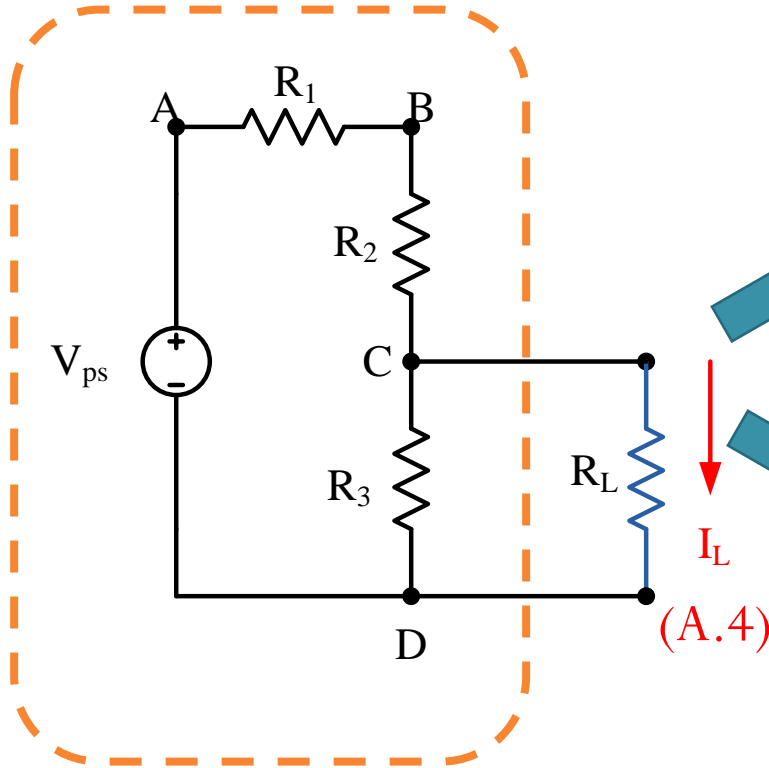Need resistor whose value can be adjusted arbitrarily




Need current source

Potentiometer (Pot)





Pot as a variable resistor

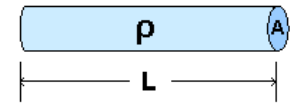- Manually adjustable resistor
- Three terminals
- The resistance between the middle terminal and either of the two sides depends on the position of the wiper.



$$R = \rho \times L / A$$

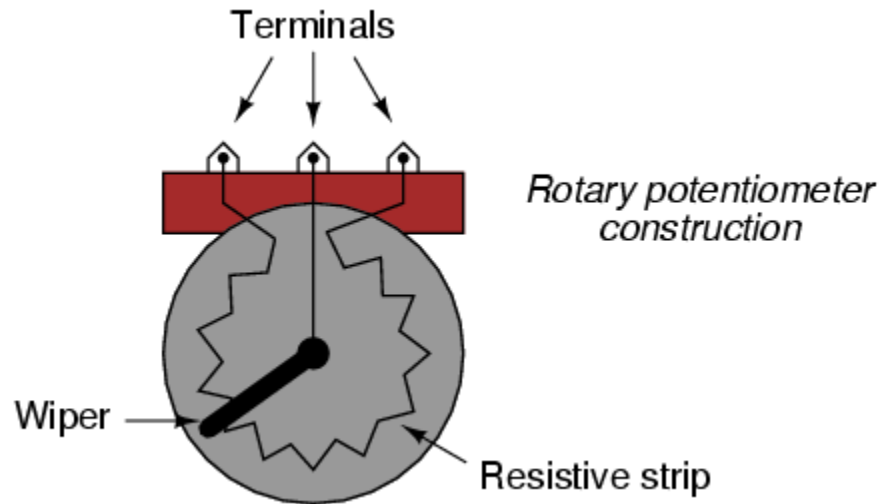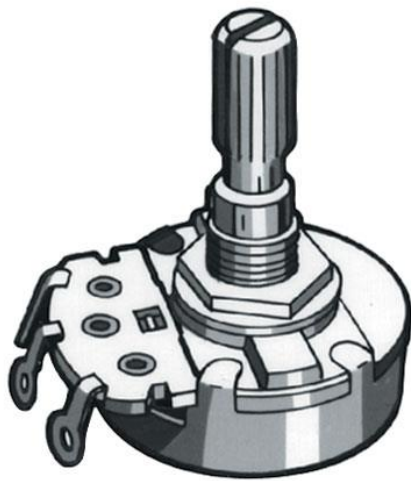ρ = Resistivity
 L = Length
 A = Cross-sectional area



Current source

- We do not have current source.
 - Again, it is meaningless to connect an ammeter directly across the power supply. This will NOT give you the amount of current produced by the power supply.
- We use a voltage source (power supply) to give the specified amount of current.

