

Sirindhorn International Institute of Technology  
Thammasat University at Rangsit  
School of Information, Computer and Communication Technology

---

<b>COURSE</b>	: ECS 204 Basic Electrical Engineering Lab
<b>INSTRUCTOR</b>	: Asst. Prof. Dr. Prapun Suksompong (prapun@siit.tu.ac.th)
<b>WEB SITE</b>	: <a href="http://www2.siit.tu.ac.th/prapun/ecs204/">http://www2.siit.tu.ac.th/prapun/ecs204/</a>
<b>EXPERIMENT</b>	: 03 Network Theorems II: Superposition & Maximum Power Transfer

---

## I. OBJECTIVES

1. To verify the superposition principle in resistive circuits.
2. To verify the condition of maximum power transfer for a resistive load.

## II. BASIC INFORMATION

### 1. Superposition principle

In any *linear* circuit containing several independent sources, the voltage across or the current flowing through any element can be computed by adding algebraically all the individual voltages or currents caused by each independent source acting alone, with all other independent sources **deactivated**. This is known as **superposition principle**. Steps in applying superposition principle may be summarized as follows.


Step 0: Consider one voltage or current source at a time.

Step 1: Replace the other voltage or current sources with short circuits (zero resistance) or open circuits (infinite resistance), respectively.


Step 2: Determine the particular current or voltage that we want to know as if there were only one source in the circuit—the one which is left activated in Step 1.

Step 3: Take the next source in the circuit, and repeat Steps 1 and 2 for each source.


Step 4: To find the actual current or voltage, add the currents or voltages due to individual sources.

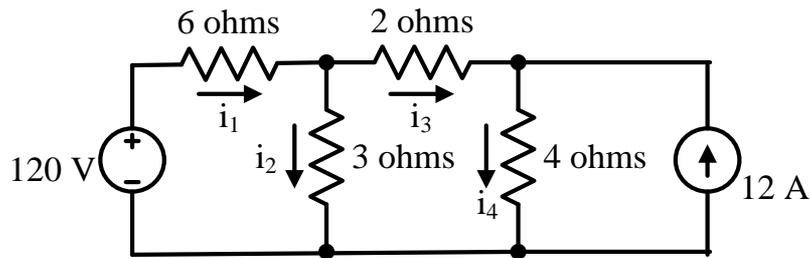

**Figure 3-1(a):** Circuit to illustrate superposition technique.

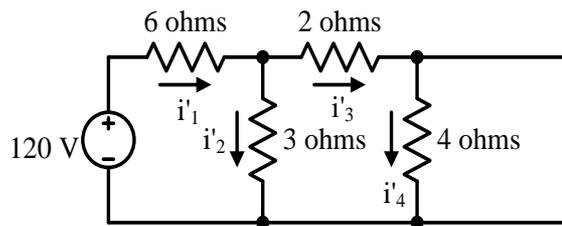

**Figure 3-1(b):** Circuit in Figure 3-1(a) with the current source deactivated (replaced by an open circuit).

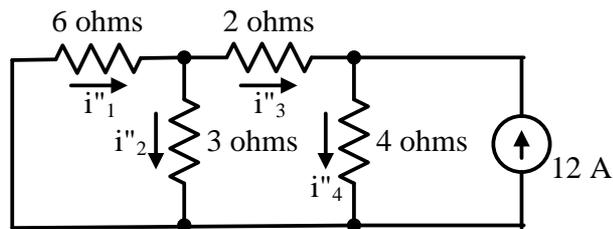

**Figure 3-1(c):** Circuit in Figure 3-1(a) with the voltage source deactivated (replaced by a short circuit).

From Figure 3-1, the four current values can be determined using superposition principle as follows:

$$i_1 = i'_1 + i''_1$$

$$i_2 = i'_2 + i''_2$$


$$i_3 = i'_3 + i''_3$$

$$i_4 = i'_4 + i''_4$$

## 2. Maximum power transfer

In many circumstances, it is desirable to obtain the maximum possible power that a given source can deliver to a load. For a *resistive circuit* connected with a load  $R_L$  across its two terminals, the condition for maximum power transfer to  $R_L$  is that  $R_L = R_{TH}$ , where  $R_{TH}$  is the Thevenin resistance of the circuit with respect to the two terminals. To see why this fact holds, recall that the original resistive circuit can be replaced by its Thevenin equivalent circuit as shown in Figure 3-2. The power  $p$  dissipated in  $R_L$  can then be expressed as a function of three circuit parameters:  $V_{TH}$ ,  $R_{TH}$ , and  $R_L$ :

$$p = i^2 R_L \text{ where } i = \frac{V_{th}}{R_{th} + R_L}.$$

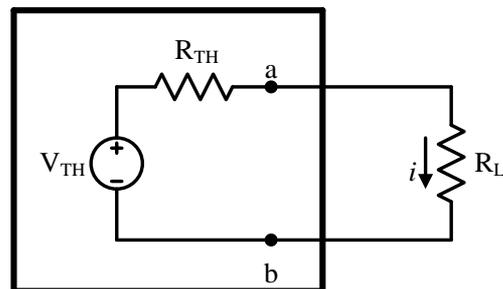

**Figure 3-2:** A circuit used to determine the value of  $R_L$  for maximum power transfer.

To find the value of  $R_L$  that maximizes the power, elementary calculus says we should solve for the value of  $R_L$  when  $dp/dR_L$  equals zero. The derivative of  $p$  is given by

$$\begin{aligned} \frac{dp}{dR_L} &= 2i \frac{di}{dR_L} R_L + i^2 = 2 \frac{V_{th}}{R_{th} + R_L} \left( -\frac{V_{th}}{(R_{th} + R_L)^2} \right) + \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 \\ &= \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 \left( -\frac{2R_L}{R_{th} + R_L} + 1 \right). \end{aligned}$$

The value of  $R_L$  which makes  $\frac{dp}{dR_L} = 0$  is

$$R_L = R_{TH}.$$

Thus, the maximum power transfer occurs when the load resistance  $R_L$  equals the Thevenin resistance  $R_{TH}$ . As a consequence, the maximum power transferred to  $R_L$  equals to


$$P_{\max} = \left( \frac{V_{th}}{R_{th} + R_{th}} \right)^2 R_{th} = \frac{V_{th}^2}{4R_{th}}$$

## II. MATERIALS REQUIRED

- DC power supplies
- Multi-meters
- Resistors (1/4-W):  
820- $\Omega$ , 1-k $\Omega$ , 1.2-k $\Omega$ , 2.2-k $\Omega$ , and a potentiometer (variable resistor).

## IV. PROCEDURE

**Caution: Watch out for the signs of the current and voltage.**

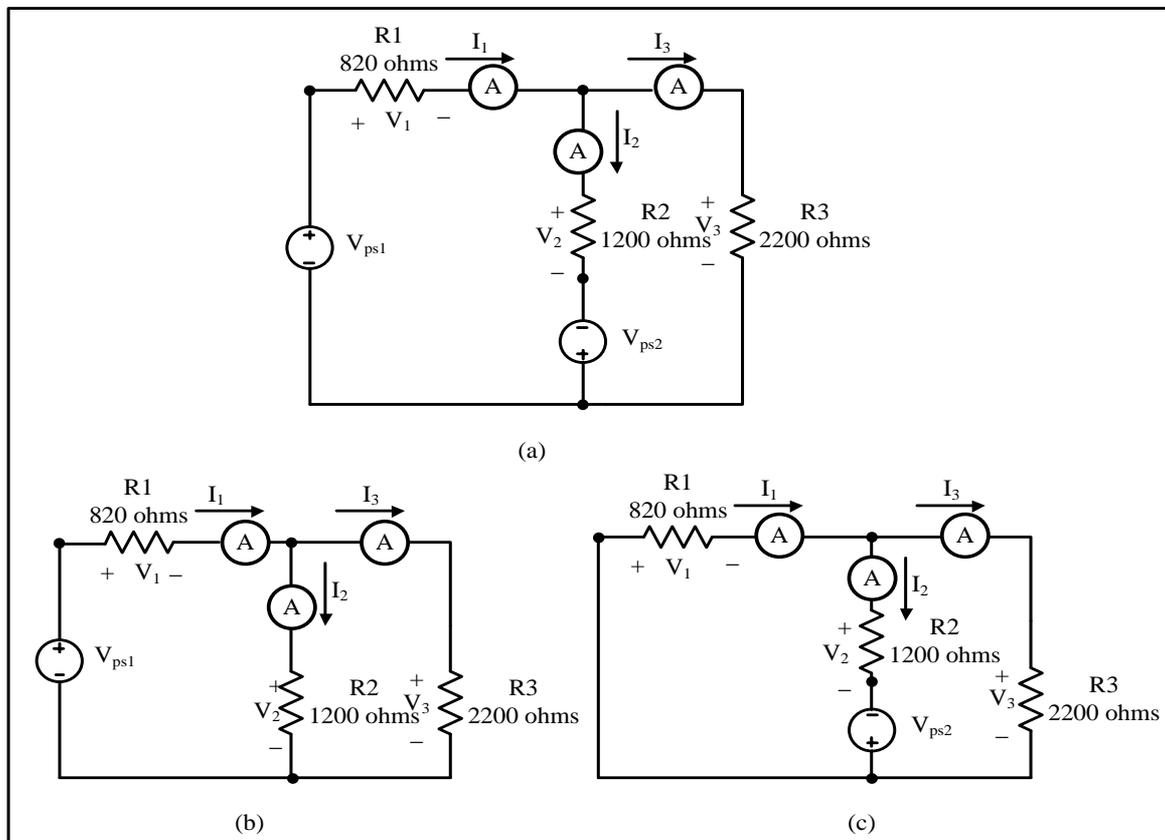


**Figure 3-3:** Circuit to verify superposition principle: (a) original circuit, (b) modified circuit with  $V_{ps1}$  only, and (c) modified circuit with  $V_{ps2}$  only.

### Part A: Superposition principle

1. Figure 3-3(a) shows the circuit under consideration. Let  $R_1 = 820 \Omega$ ,  $R_2 = 1.2 \text{ k}\Omega$ , and  $R_3 = 2.2 \text{ k}\Omega$ . Use a DMM to measure the resistance of each resistor, and record the values in Table 3-1.
2. Turn on the power supply, and adjust its voltage to 15 V. Use this voltage as  $V_{PS1}$ , and connect the circuit shown in Figure 3-3(b).
3. Measure the currents  $I_1$ ,  $I_2$ ,  $I_3$ , and the voltages  $V_1$ ,  $V_2$ ,  $V_3$ . Record the results in Table 3-1.
4. Adjust *another* output of the power supply to 10 V. Use this voltage as  $V_{PS2}$ , and connect the circuit in Figure 3-3(c). Measure  $I_1$ ,  $I_2$ ,  $I_3$ ,  $V_1$ ,  $V_2$ , and  $V_3$ . Record the results in Table 3-2.
5. With  $V_{PS1} = 15 \text{ V}$  and  $V_{PS2} = 10 \text{ V}$ , connect the circuit given in Figure 3-3(a). Measure  $I_1$ ,  $I_2$ ,  $I_3$ ,  $V_1$ ,  $V_2$ , and  $V_3$ , and record the values in Table 3-3.
6. Turn the power supply off. Use the measured values of  $R_1$ ,  $R_2$ ,  $R_3$ ,  $V_{PS1}$ , and  $V_{PS2}$  to calculate  $I_1$ ,  $I_2$ ,  $I_3$ ,  $V_1$ ,  $V_2$ , and  $V_3$  by superposition principle. Record the calculated values in Table 3-3, and show the procedure of your analysis in the report.

### Part B: Maximum power transfer

1. Let  $R_C = 1 \text{ k}\Omega$ . Measure the exact value of  $R_C$  from the actual resistor and record the value in Table 3-4.
2. Turn on the power supply, and adjust the voltage  $V_{PS}$  to 10 V.
3. With a DMM connected directly across  $R_L$  (potentiometer), adjust  $R_L$  until  $R_L = 0 \Omega$ . (You will *not* be able to get  $0 \Omega$  from the potentiometer. Simply use the lowest value that you can make it be.) Record the exact resistance value in Table 3-4.
4. Connect the circuit in Figure 3-4.

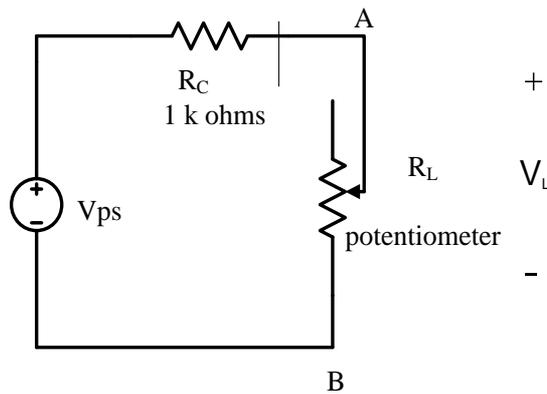

**Figure 3-4:** A circuit for verifying the maximum power transfer condition.

5. Measure  $V_L$  (the voltage across  $R_L$ ), and record the value in Table 3-4.
6. Disconnect  $R_L$  from the circuit.
7. Repeat Steps 3 through 6 for the values of  $R_L$  given in Table 3-4.
8. Calculate  $P_L$ , the power absorbed by the load  $R_L$ , for each value of  $R_L$ , and record the result in Table 3-4

Hint:  $P_L = \frac{V_L^2}{R_L}$ .

In the report, plot  $P_L$  as a function of  $R_L$ . Where does the maximum value of  $P_L$  occur?

**Table 3-1:**  $V_{PS1} =$  \_\_\_\_\_ (A.2) acting alone.

(A.1) Measured resistance:  $R1 =$  \_\_\_\_\_  $R2 =$  \_\_\_\_\_  $R3 =$  \_\_\_\_\_

A.3 {

Current	Voltage
$I_1:$	$V_1:$
$I_2:$	$V_2:$
$I_3:$	$V_3:$

TA Signature:

**Table 3-2:**  $V_{PS2} =$  \_\_\_\_\_ (A.4) acting alone.

A.4 {

Current	Voltage
$I_1:$	$V_1:$
$I_2:$	$V_2:$
$I_3:$	$V_3:$

TA Signature:

**Table 3-3: Superposition principle**

$V_{PS1} =$  \_\_\_\_\_ and  $V_{PS2} =$  \_\_\_\_\_ acting together.

Measured values (A.5)				Calculated values (A.6)											
				$V_{PS1}$ Only				$V_{PS2}$ Only				$V_{PS1}$ and $V_{PS2}$ together			
Current (mA)		Voltage (V)		Current (mA)		Voltage (V)		Current (mA)		Voltage (V)		Current (mA)		Voltage (V)	
$I_1$		$V_1$		$I_1$		$V_1$		$I_1$		$V_1$		$I_1$		$V_1$	
$I_2$		$V_2$		$I_2$		$V_2$		$I_2$		$V_2$		$I_2$		$V_2$	
$I_3$		$V_3$		$I_3$		$V_3$		$I_3$		$V_3$		$I_3$		$V_3$	

TA Signature:

**Table 3-4: Maximum power transfer**


$R_C = \text{_____} \Omega$ $V_{PS1} = \text{_____} V$			
	$R_L(\Omega)$	$V_L(V)$	Calculated $P_L(mW)$
0			
300			
600			
900			
950			
1000			
1050			
1100			
1400			
1700			
2000			

TA Signature: \_\_\_\_\_

## QUESTIONS

- Assume that  $R_3$  is the load of the whole circuit in Figure 3-3(a). Find the value of  $R_3$  for maximum power transfer, where  $R_1 = 820 \Omega$  and  $R_2 = 1.2 \text{ k}\Omega$  as given in the figure. (Do not use the measured value.) Also determine the maximum power that can be transferred to  $R_3$ .
- If the polarity of the power supply  $V_{ps2}$  in Figure 3-3 (a) is reversed, then
 

$I_1 =$ _____ mA	$V_1 =$ _____ V
$I_2 =$ _____ mA	$V_2 =$ _____ V
$I_3 =$ _____ mA	$V_3 =$ _____ V
- Consider the circuits in Figure 3-5.

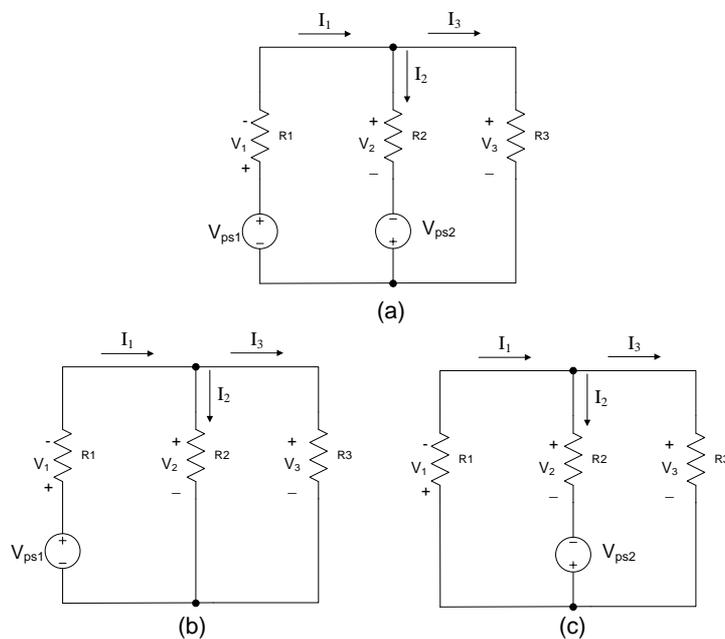

**Figure 3-5:** Circuits to verify superposition theorem in lab 03: (a) original circuit, (b) modified circuit with  $V_{ps1}$  only, and (c) modified circuit with  $V_{ps2}$  only.

Complete the following table:

$V_{ps1}$ Only (Fig. 1b)				$V_{ps2}$ Only (Fig. 1c)				$V_{ps1}$ and $V_{ps2}$ together (Fig. 1a)			
$I_1$	2 A	$V_1$	20 V	$I_1$		$V_1$		$I_1$		$V_1$	
$I_2$	1 A	$V_2$	20 V	$I_2$	9 A	$V_2$		$I_2$		$V_2$	
$I_3$		$V_3$		$I_3$		$V_3$		$I_3$		$V_3$	