

Basic Elec. Engr. Lab

ECS 204

Asst. Prof. Dr. Prapun Suksompong

prapun@siit.tu.ac.th




Lab 7 & 8

- Operational amplifier
- Inverting amplifier
- Summing Amplifier
- Inverting Integrator


Op-Amp 741

- **OP**erational **AMPL**ifier

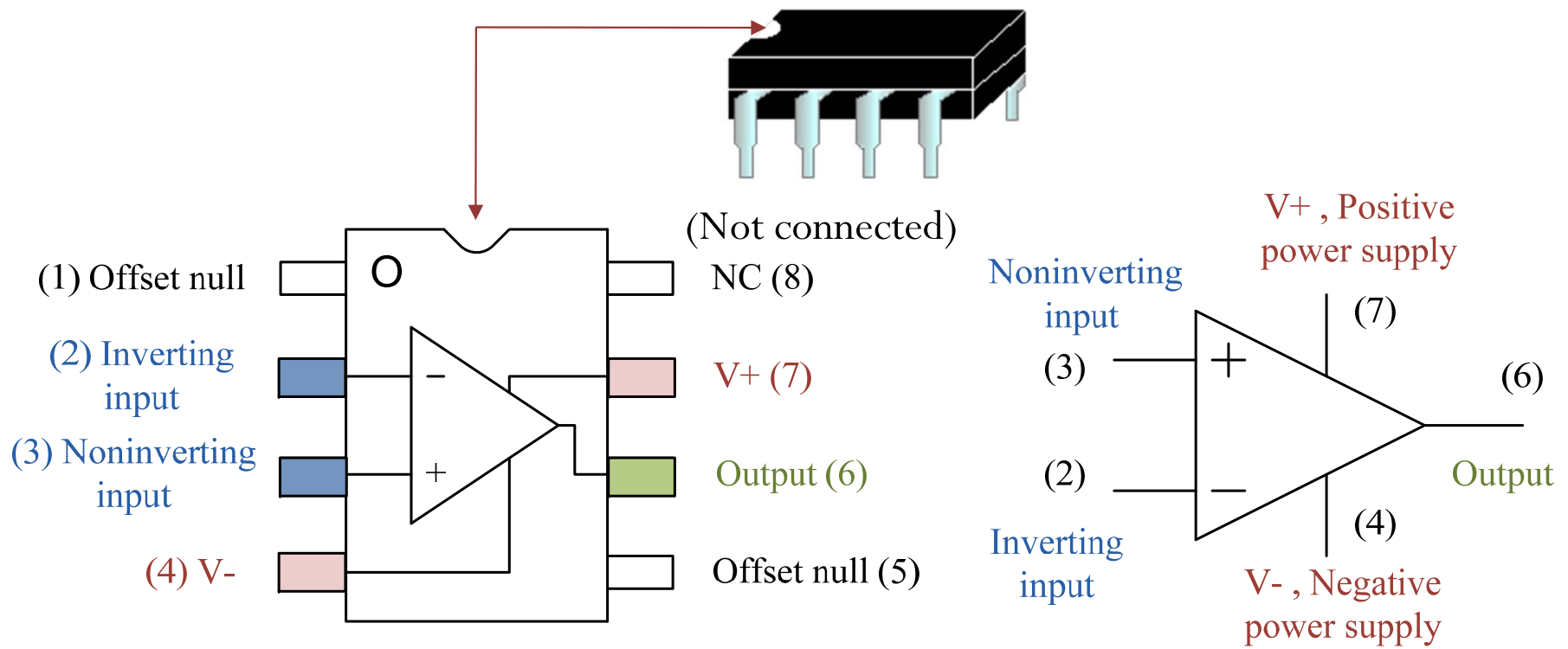



Placing op amps on the proto-board

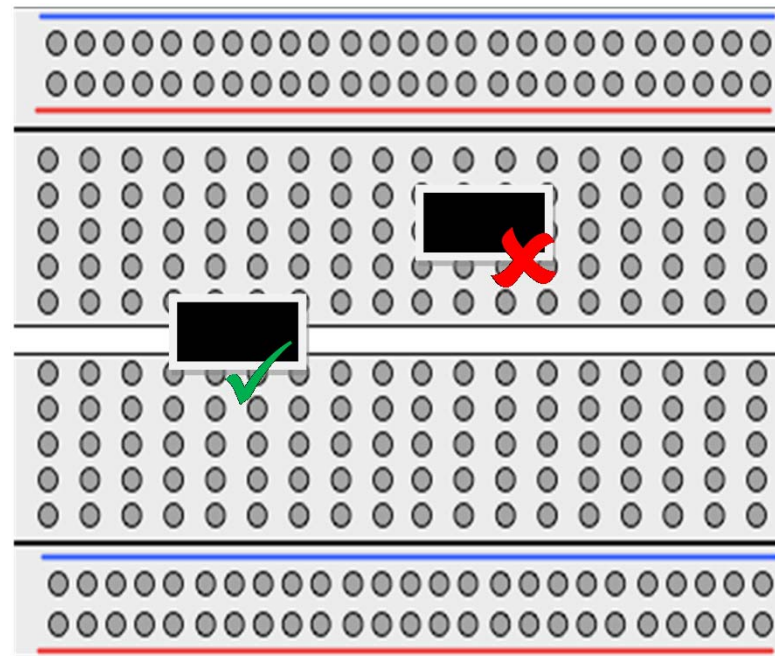- Plug in op amp chips so that they straddle the troughs on the proto board.
- In this way, each pin is connected to a different hole set.




Powering the op amp

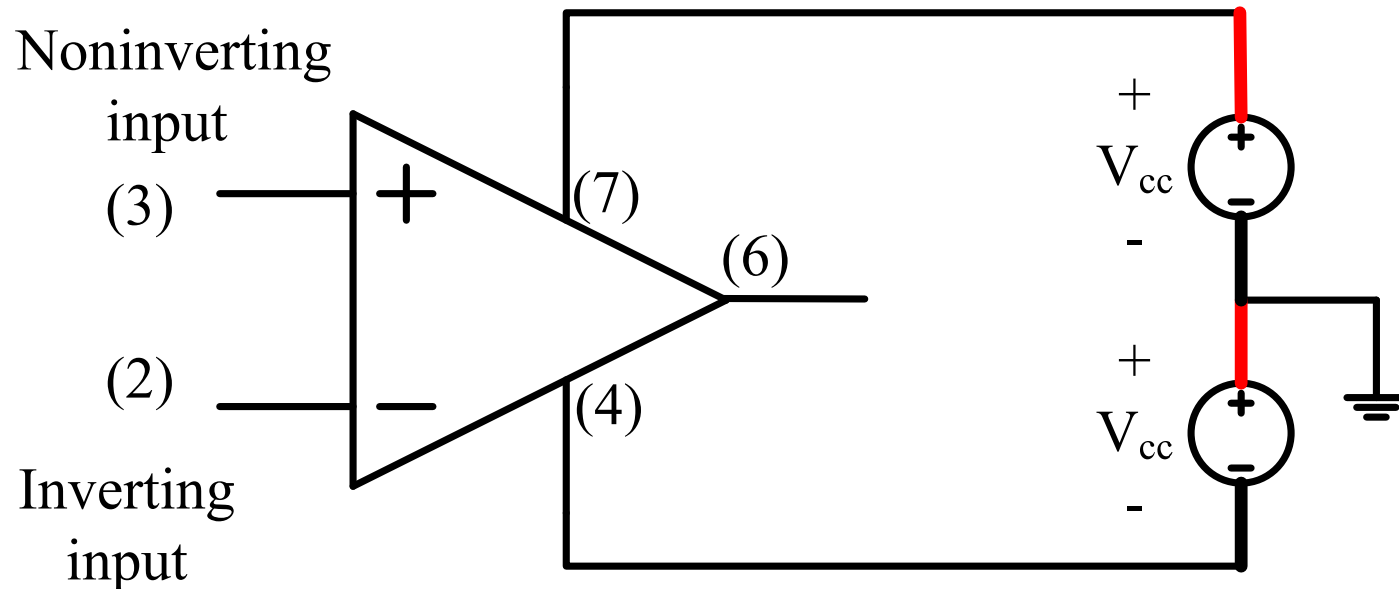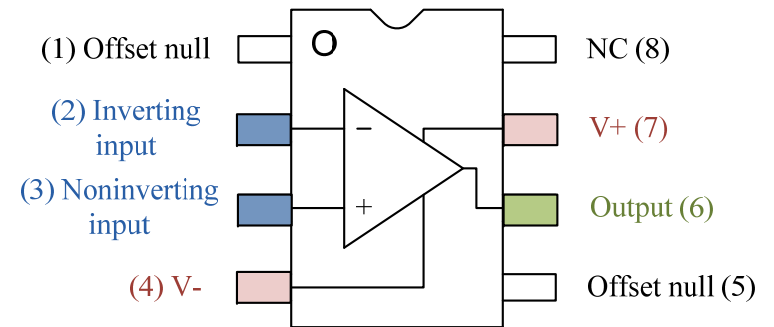- The op amp must be powered by voltage supplies.
- These supplies are often ignored in op amp circuit diagrams for the sake of simplicity.




Part A: Inverting Amplifier

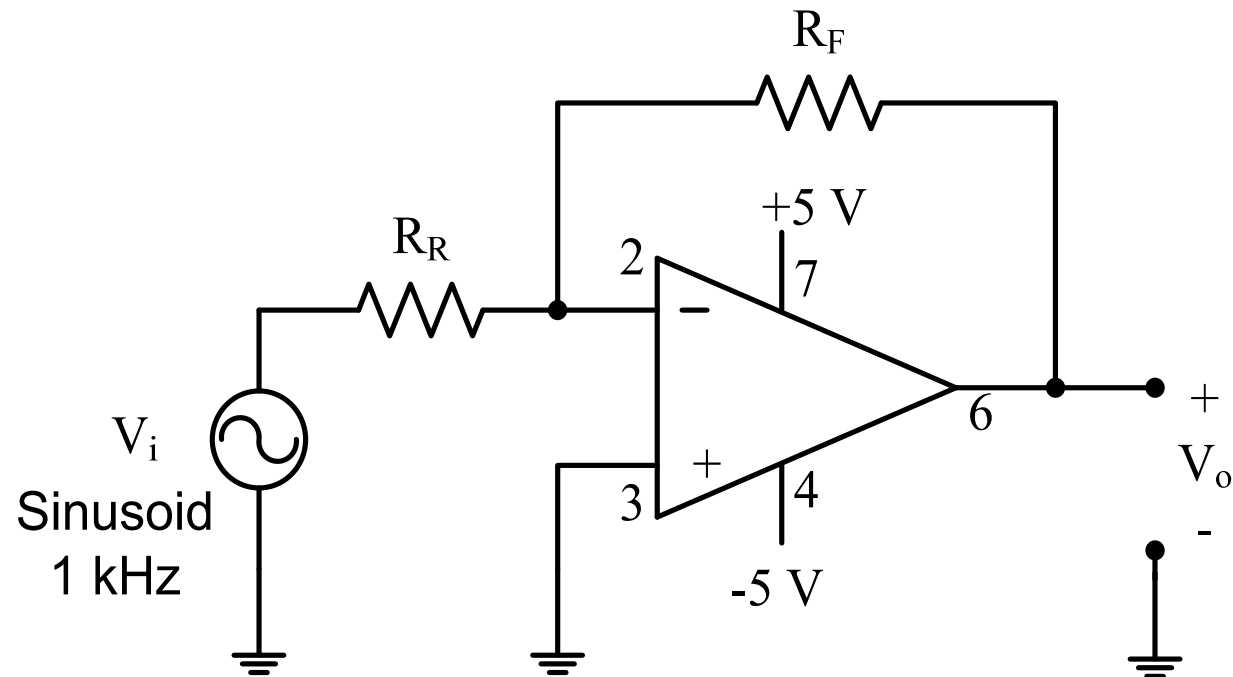

$$V_o = -\frac{R_F}{R_R} V_i.$$


Part A: Inverting Amplifier

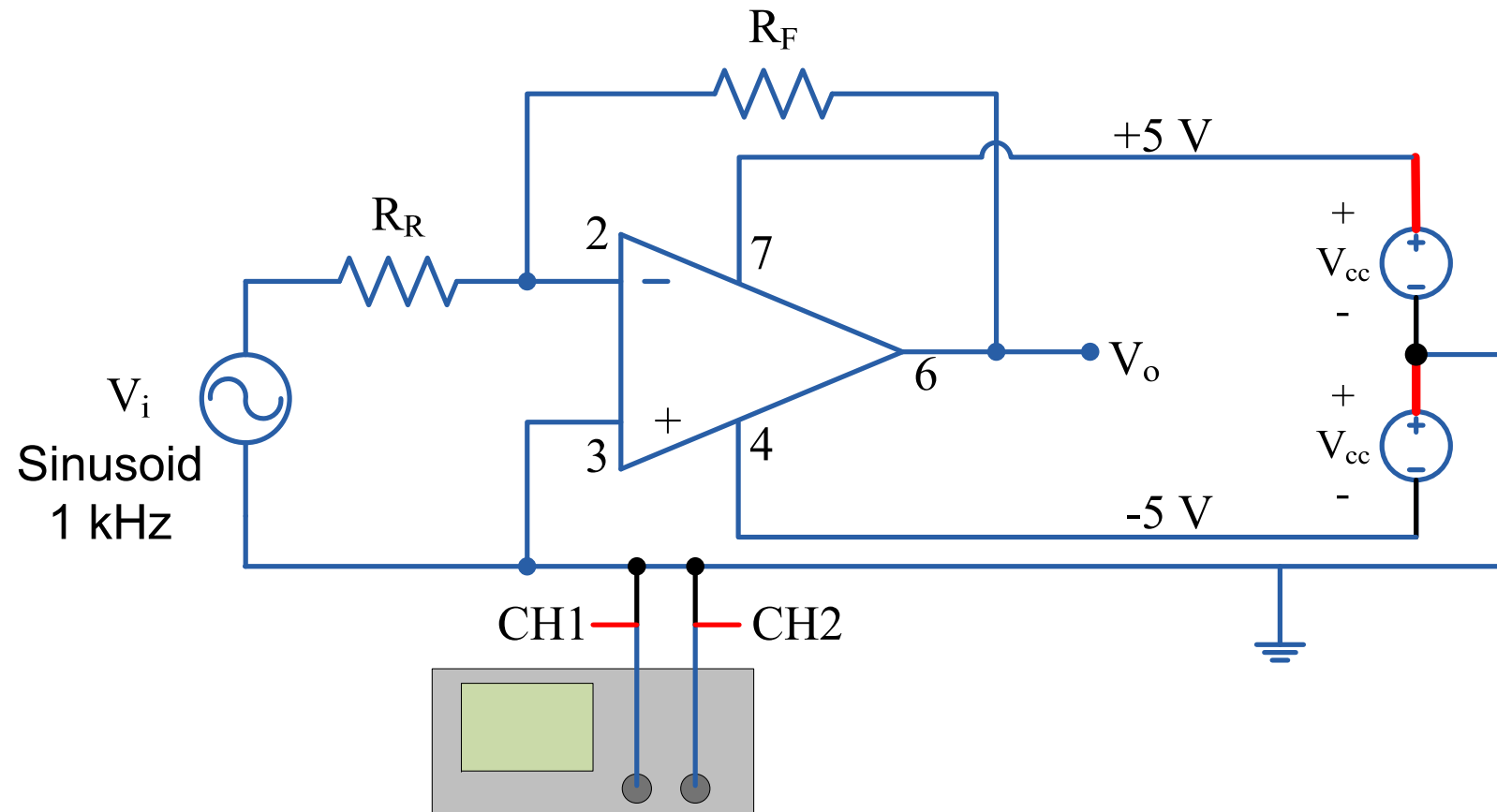

$$V_o = -\frac{R_F}{R_R} V_i$$

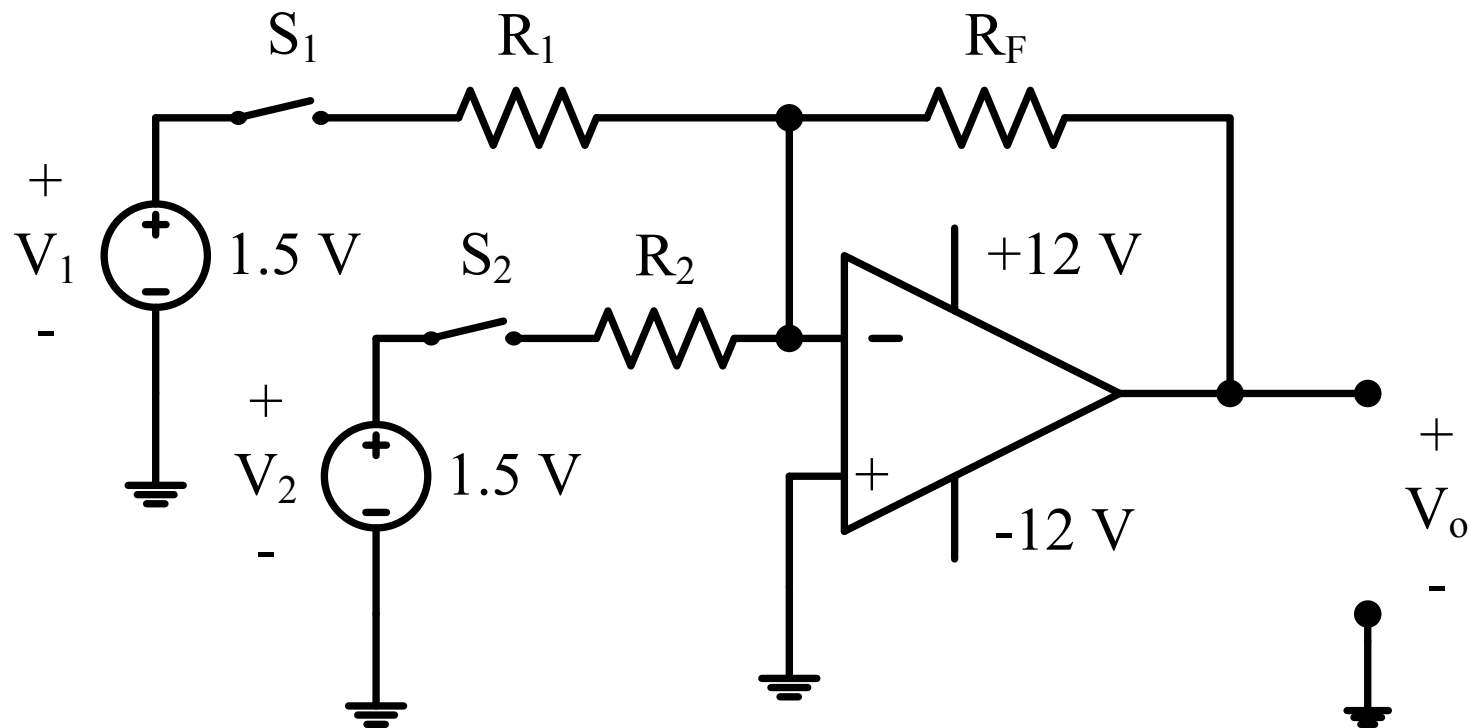
Part b: Summing Amplifier

- Note that you will **need 4 DC Voltage Sources** in this part.



$$V_0 = -\left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2\right).$$

Part C: Inverting Integrator

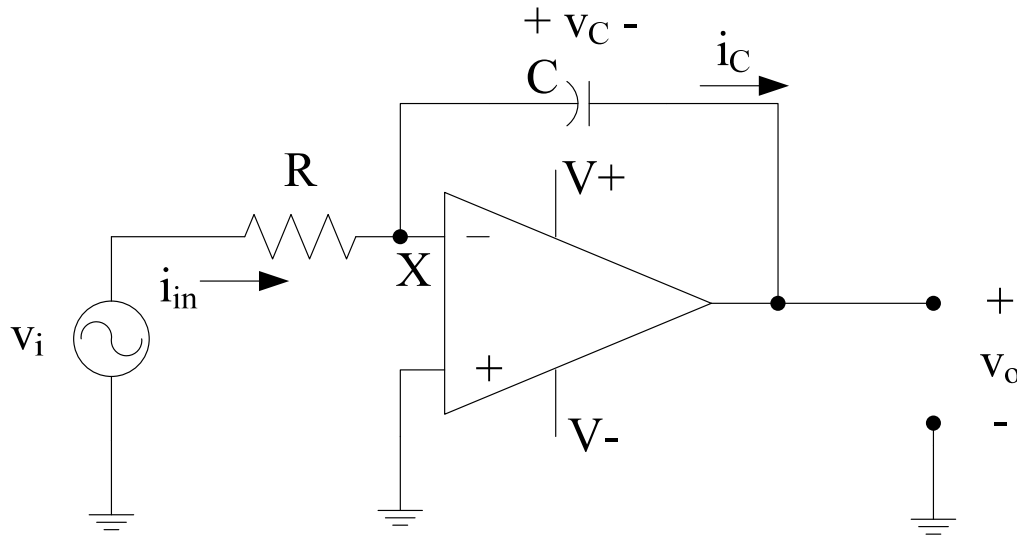


$$i_i(t) = i_c(t)$$


$$\frac{v_i(t)}{R} = -C \frac{d}{dt} v_o(t)$$

$$v_o(t) = v_o(0) - \frac{1}{RC} \int_0^t v_i(t) dt$$

As a Ramp Generator...

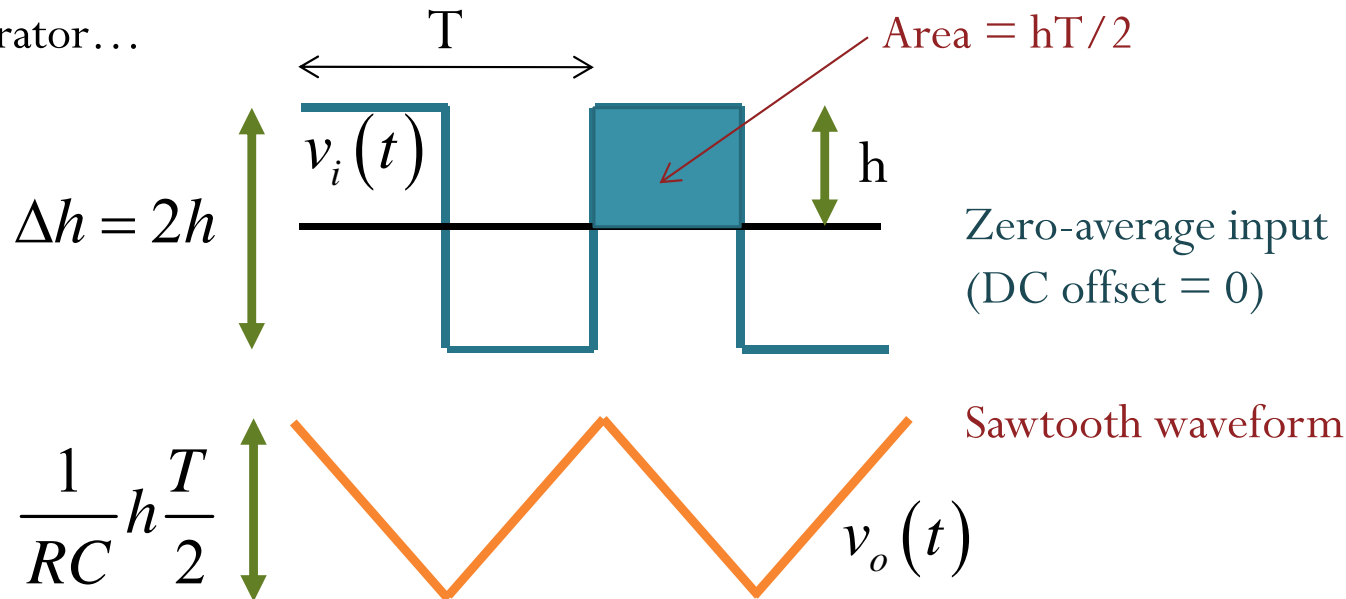

Inverting Integrator (2)

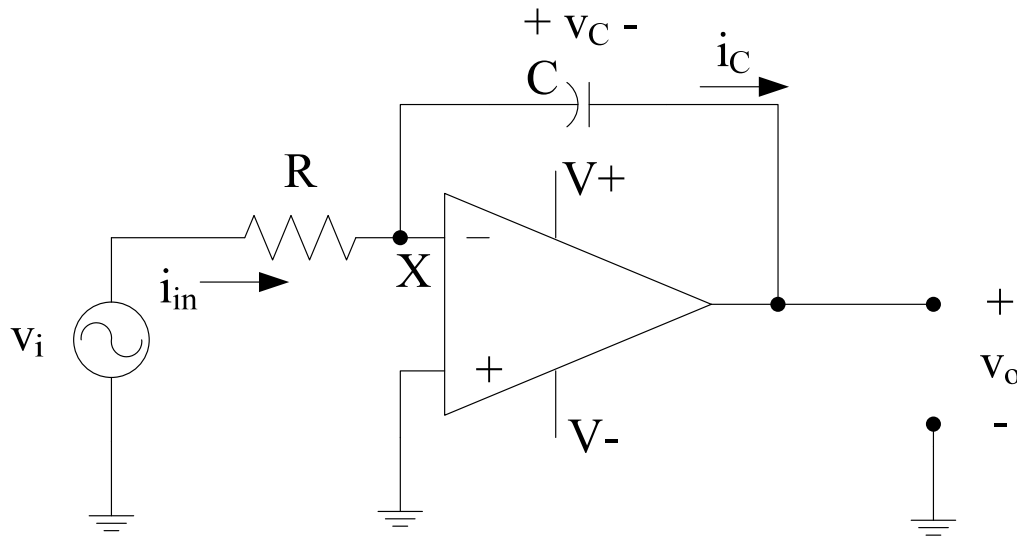


- An input with nonzero mean (DC offset) can saturate the op amp.


$$i_i(t) = i_c(t)$$

$$\frac{v_i(t)}{R} = -C \frac{d}{dt} v_o(t)$$
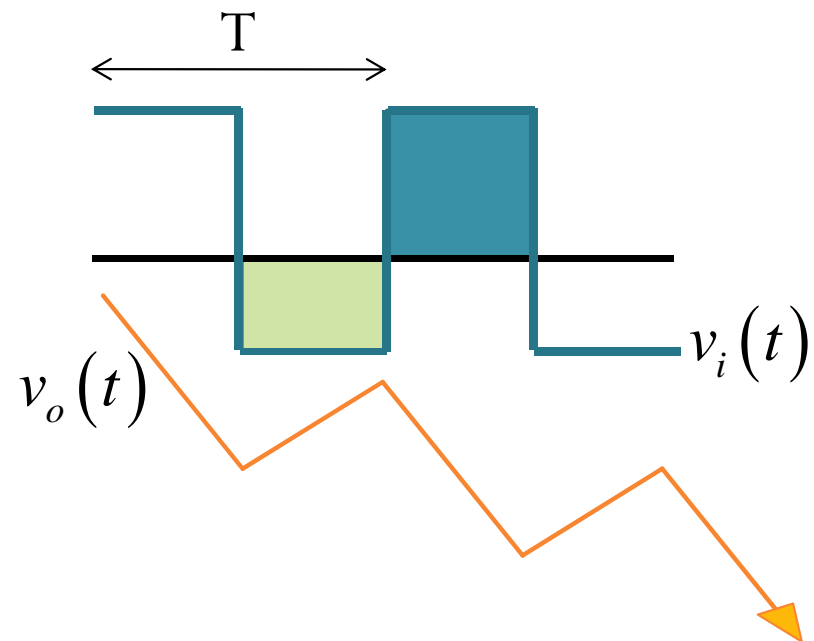
$$v_o(t) = v_o(0) - \frac{1}{RC} \int_0^t v_i(t) dt$$



Inverting Integrator: AC SS Analysis

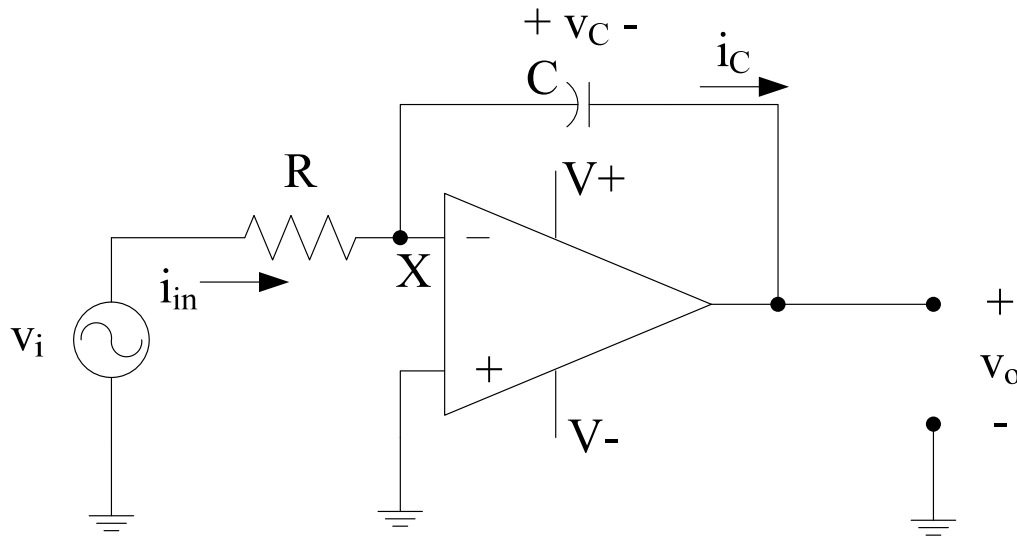


$$\begin{aligned} V_o &= -\left(\frac{Z_C}{R}\right)V_i \\ &= -\left(\frac{V_i}{R}\right)\times\frac{1}{j\omega C} \end{aligned}$$

- The gain at $f = 0$ is unbounded.
- Act like an **active low pass filter**, passing low frequency signals while attenuating the high frequencies.

(w/ DC Gain Control)

Inverting Integrator w/ Shunt Resistor

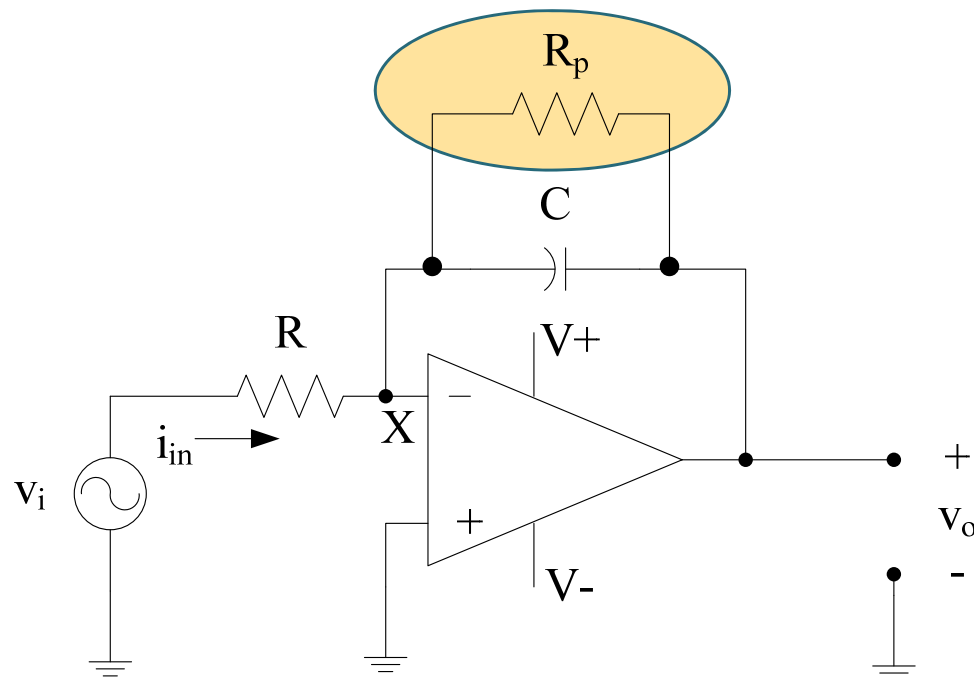
- In practical circuit, a large resistor R_p is usually shunted across the capacitor



$$\begin{aligned} V_o &= -\left(\frac{Z_C // R_p}{R}\right)V_i \\ &= -\left(\frac{V_i}{R}\right) \times \frac{R_p}{j\omega R_p C + 1} \end{aligned}$$


- Observe that at $f = 0$, the gain is finite.

Inverting Integrator w/ Shunt Resistor

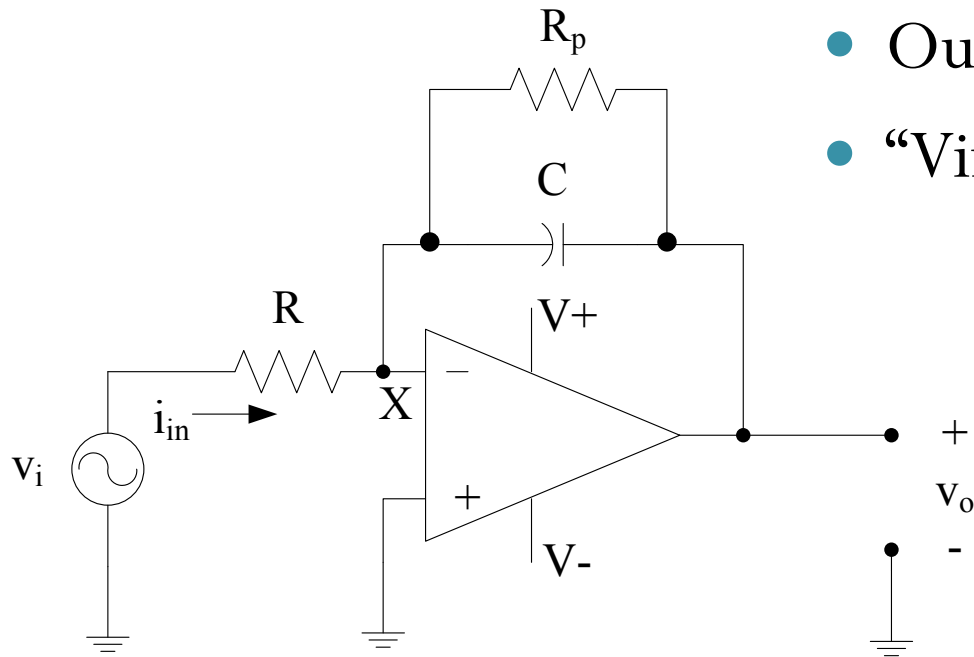

- Output is not triangular.
- “Virtually triangular” if $R_p C \gg \frac{T}{2}$
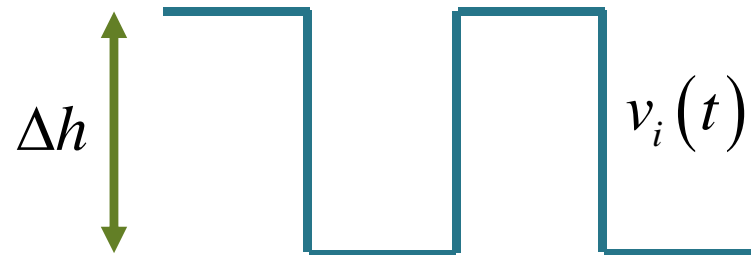
$$R_p \gg \frac{1}{2fC} \quad C \gg \frac{1}{2fR_p}$$



$$r = \exp\left(-\frac{1}{2fR_p C}\right) \quad \tau = R_p C$$