

Practice Problems for the Final Examination

COURSE : ECS204 Basic Electrical Engineering Laboratory

INSTRUCTOR: Asst. Prof. Dr. Prapun Suksompong

PLACE : BKD 3502

Name		ID	
Time	<input type="checkbox"/> group a: 9:30 – 10:30 AM <input type="checkbox"/> group b: 10:40 – 11:40 AM <input type="checkbox"/> group c: 1:30 – 2:30 PM <input type="checkbox"/> group d: 2:40 – 3:40 PM	Bench#	

Instructions:

1. This document contains **practice problems for the final examination**.
2. Date of the actual exam: **April 27, 2015**.
3. **Read these instructions and the questions carefully.**
4. Closed book. Closed notes. **No calculator.**
5. You may use any equipment available on your workbench to solve your questions or verify your answers.
6. For this practice session, you do not need any TA signature. However, for the actual exam, for the problems that ask for TA's signatures, lack of the signature(s) means no credit for the whole part. Request the TA to sign you answer again if you decide to change your answer later.
7. Allocate your time wisely. Some easy questions give many points.
8. When not explicitly stated/defined, all notations and definitions follow ones given in the lab manuals and slides.
9. **Units** are important.
10. When possible, record *at least two decimal places* from the DMM. Do not write 12 mA when you see 12.00 mA on the DMM's display.
11. On the actual exam, do not forget to write your **first name and the last three digits of your ID** on each page of your examination paper, starting from page 2.
12. For the actual exam,
 - a. the TAs will not help you debug your circuit.
 - b. arrive at least 10 minutes early
 - c. do not leave the exam room until the end of the allotted time.
13. Do not cheat. The use of communication devices including mobile phones is prohibited in the examination room.
14. Organize items on your desk/bench before you leave the exam room.
15. Do not panic.

Printed on: April 16, 2015

Sec 1		Sec 2	
5422780759	a	5422800680	d
5622780153	b	5622770659	c
5622780427	b	5622770733	d
5622780609	b	5622772093	d
5622781359	b	5622780237	c
5622781565	b	5622780260	c
5622790129	a	5622780310	d
5622790194	b	5622780344	c
5622790244	a	5622780526	d
5622790251	b	5622780799	c
5622790301	b	5622780856	d
5622790566	a	5622780898	c
5622791192	a	5622780906	c
5622791812	b	5622781003	c
5622791838	a	5622781227	c
5622791846	a	5622781615	c
5622792182	b	5622781748	d
5622792281	a	5622782019	d
5622792349	b	5622790582	c
5622792604	a	5622790723	d
5622792950	b	5622790731	d
5622793172	a	5622791424	d
5622793826	a	5622791549	c
5622795012	a	5622791580	d
5622795137	a	5622792067	c
5622795319	b	5622792315	c
5622795459	b	5622792331	c
5622795483	a	5622792455	c
5622795681	b	5622792497	d
5622795723	b	5622792521	d
5622800100	a	5622792539	d
5622800118	a	5622793040	d
5622800472	a	5622793313	d
		5622793578	c
		5622793800	c
		5622794923	d

Basic Information

The following table might be useful for reading resistor code:

Black	Brown	Red	Orange	Yellow	Green	Blue	Violet	Grey	White
0	1	2	3	4	5	6	7	8	9

The pin details of op amp 741 are shown in Figure 1 below.

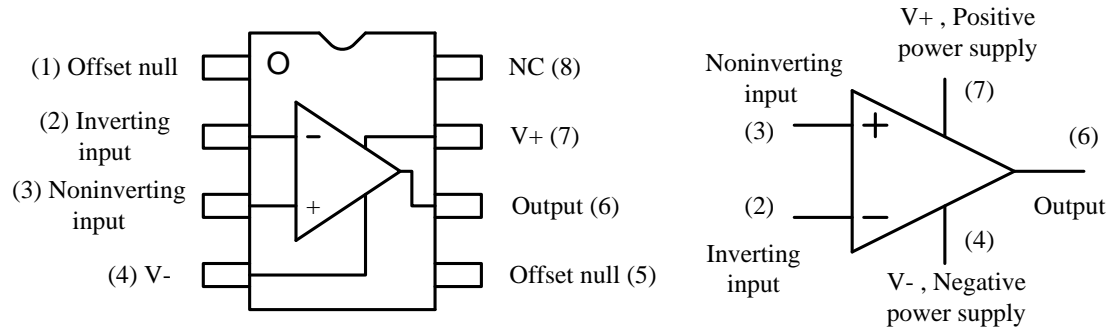


Figure 1

Reminders:

1. V_{DC} = measured voltage value using the DMM in DC mode.
2. V_{AC} = measured voltage value using the DMM in AC mode.
3. $V_{RMS} = \sqrt{v^2(t)} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt}$ for periodic waveform $v(t)$ with period T

Name _____ ID _____

Model number of your DMM: _____

Model number of your Oscilloscope: _____

Problem 0

Display the calibration signal of the oscilloscope on both channel 1 and channel 2 of the oscilloscope. The ground levels of both channels should be in the middle of the screen.


Problem 1

Use the function generator to generate a 3 V_{p-p} 2 kHz **square** waveform. Set the **DC offset** of the waveform to be 1 V. Display the waveform on channel 1 of the oscilloscope. Make sure that the scope is in **DC mode**.

Sketch the waveforms here. Indicate the ground level on your sketch as well.

Voltage/Division _____

Time/Division _____

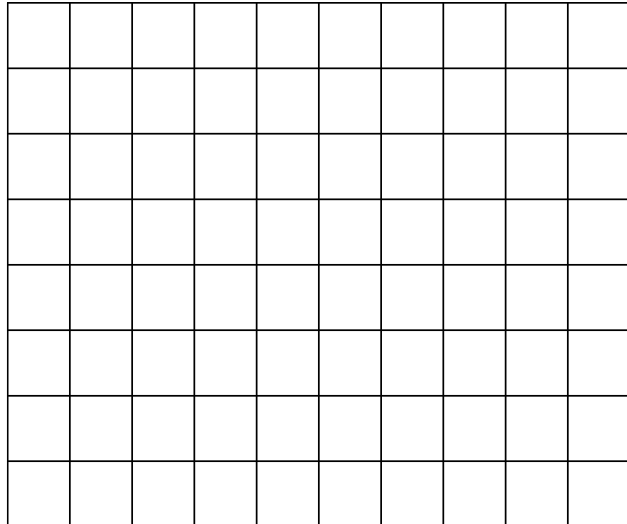

Measure V_{DC} and V_{AC} of this waveform.

V_{DC} = _____

V_{AC} = _____

Now, **change** the DC offset to 2 V.

Measure V_{DC} and V_{AC} of this waveform.

V_{DC} = _____

V_{AC} = _____

Problem 2

Connect the circuit as shown in Figure 2.

Use $R_1 = 1\text{ k}\Omega$
and $R_2 = 2\text{ k}\Omega$.

Measure the exact values of the resistance for R_1 and R_2 .

Record these values in the table here along with the corresponding color codes.

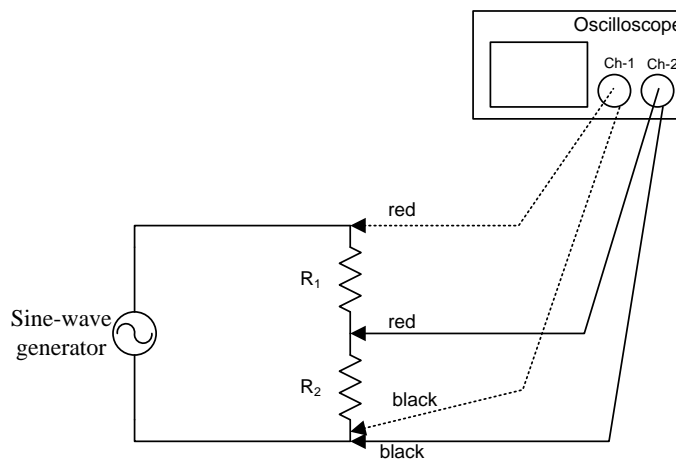


Figure 2


	Value	Color Code
R_1		
R_2		

Set the function generator to generate a 2 V_{p-p} 1 kHz **sinusoidal** waveform with **NO DC offset**.

a) Sketch the waveforms here. Make sure that you put appropriate labels (“Ch-1” or “Ch-2”) on your sketch. Indicate the ground level on your sketch as well.

Voltage/Division _____

Time/Division _____

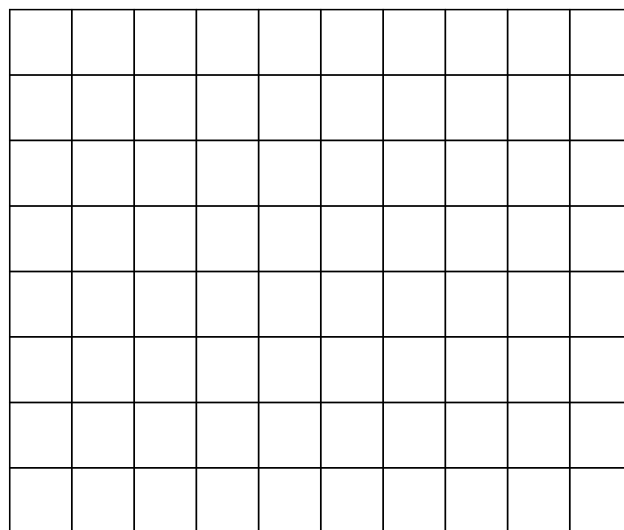

b) From the oscilloscope display, read the peak-to-peak voltage V_1 across R_1 , and the peak-to-peak voltage V_2 across R_2 .


V_1 (p-p) = _____ V_2 (p-p) = _____

c) Measure the rms current I_1 through the resistor R_1 .

I_1 (rms) = _____

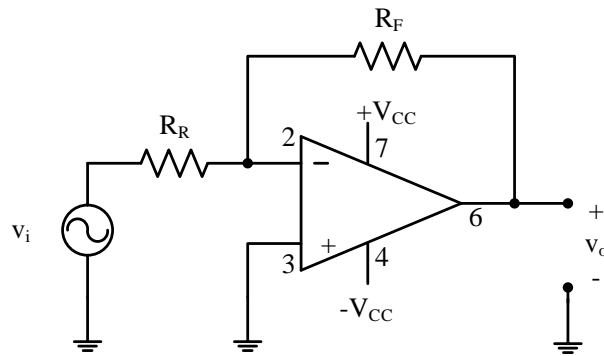Problem 3


Connect the circuit in the figure below. Channel 1 of the oscilloscope should display v_i and Channel 2 of the oscilloscope should display v_o .



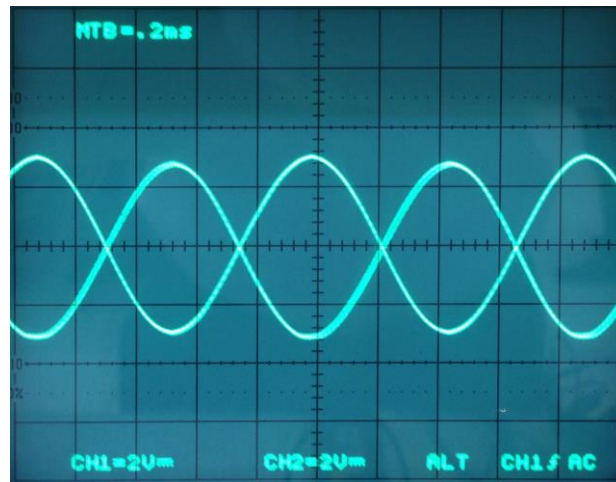
a. Select

- the resistance values R_F and R_R (which can be 5-k Ω , 10-k Ω , or 20-k Ω)
- the amplitude and frequency of the signal from the function generator
- the values of V_{CC} from the power supply
- the settings on the oscilloscope panel

so that your oscilloscope screen matches the photo below.



b. Repeat part (a) but now your screen should match the new photo below.

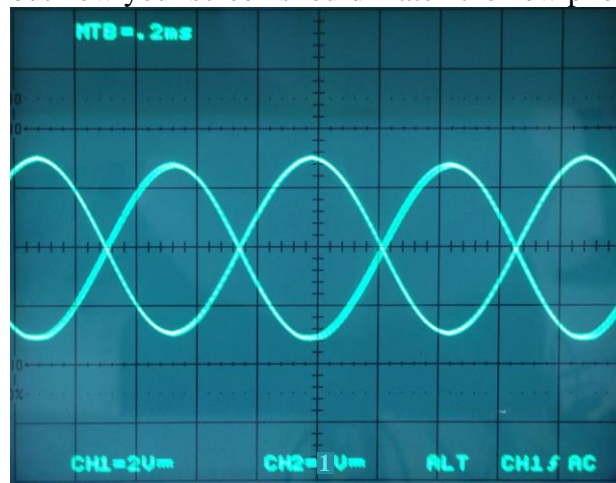


Problem 4

a) Use the function generator to generate a 1 V_{rms} 2 kHz **sinusoidal** waveform with **NO DC offset**. Display it on channel 1 of the oscilloscope. Make sure that the scope is in DC mode.

Sketch the waveform here. Indicate the ground level on your sketch as well.

Voltage/Division _____

Time/Division _____

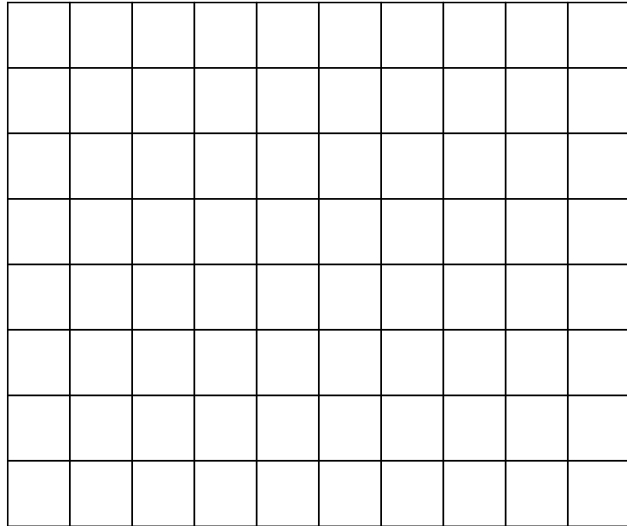

Record the exact rms value here: _____

Record the exact frequency here: _____

Find the peak-to-peak value of this signal: _____

For the rest of this problem, **DO NOT** adjust anything on the function generator. This means keep its OPEN-circuit voltage at 1 V_{rms} .

b) Connect the function generator output (with 1 V_{rms} OPEN-circuit voltage) across a 100Ω resistor. Measure the voltage (rms) across this resistor.

The exact resistance is _____.

The rms voltage across the resistor is _____. (Hint: Not 1.)

Display the voltage across the resistor on channel 1 of the oscilloscope. Make sure that the scope is in DC mode. Sketch the waveforms here. Indicate the ground level on your sketch as well.

Voltage/Division _____


Time/Division _____

c) Change the resistor to 50Ω . (If you can't find a 50Ω resistor, you can construct one using two 100Ω resistors.) Measure the voltage (rms) across this resistor.

The exact resistance is _____.

The rms voltage across the resistor is _____. (Hint: Not 1.)

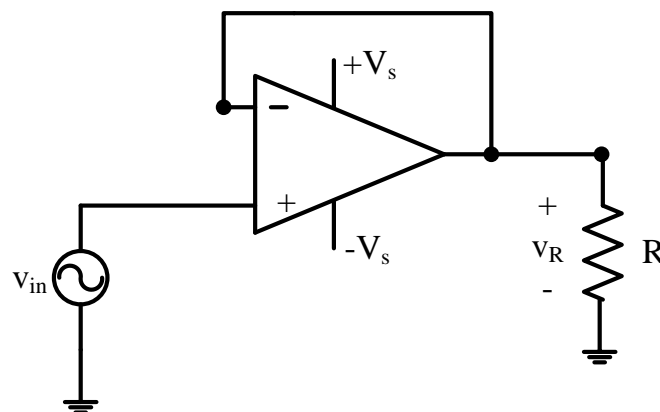d) Connect the circuit as shown in the figure below:



Use $V_S = 10\text{ V}$. The input v_{in} is again the 2 kHz sinusoidal waveform with 1 V_{rms} OPEN-circuit voltage from the function generator. Measure the rms voltage across R when R is 100Ω .

The exact resistance is _____.

The rms voltage across the resistor is _____.

e) Change the resistor to 50Ω . Measure the voltage (rms) across this resistor.

The exact resistance is _____.

The rms voltage across the resistor is _____.

f) Why does the voltages across the resistor change when there is no op amp?

Problem 5

a) Connect the circuit as shown in Figure 3. Adjust the function generator to generate a $2 V_{p-p}$ 2 kHz **sinusoidal** waveform with **NO DC offset**. Use $R = 3.3 k\Omega$.

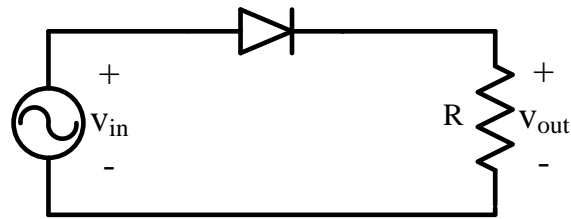



Figure 3

The exact value of R is _____.

Display the voltage v_{in} across the function generator on channel 1 of the oscilloscope. Display the voltage v_{out} across the resistor R on channel 2 of the oscilloscope. Make sure that the scope is in DC mode. Sketch the waveforms here. Make sure that you put appropriate labels (“Ch-1” or “Ch-2”) on your sketch. Indicate the ground level on your sketch as well.

Voltage/Division _____

Time/Division _____

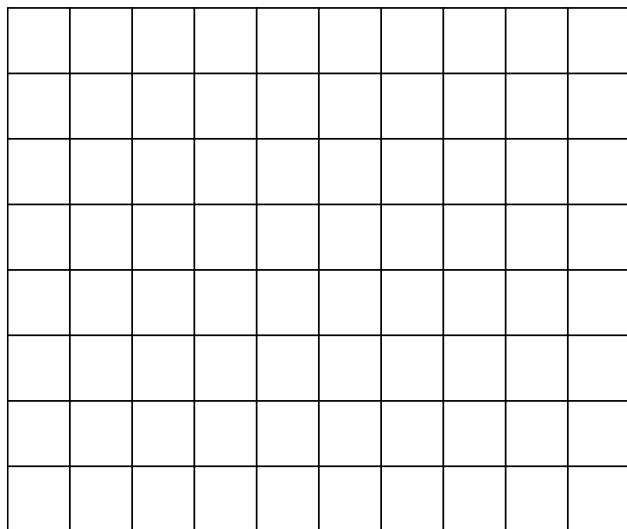

b) Describe the relationship between v_{in} and v_{out} .

c) Measure the peak-to-peak, V_{AC} , and DC (average) values of v_{in} and v_{out} .

	$V_{peak-to-peak}$	V_{AC}	V_{DC}
V_{in}			
V_{out}			