

# Basic Elec. Engr. Lab

ECS 204/210

**Dr. Prapun Sukksompong**

[prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th)

**Office Hours:**

**BKD 3601-7**

**Tuesday 15:00-16:00**


**Friday 14:00-16:00**

# Lab 2


- Thevenin's and Norton's Theorem
- New toy: Potentiometer
- Building a “fake” current source

# Thevenin's and Norton's Theorem

# Lab 2: Circuit under consideration


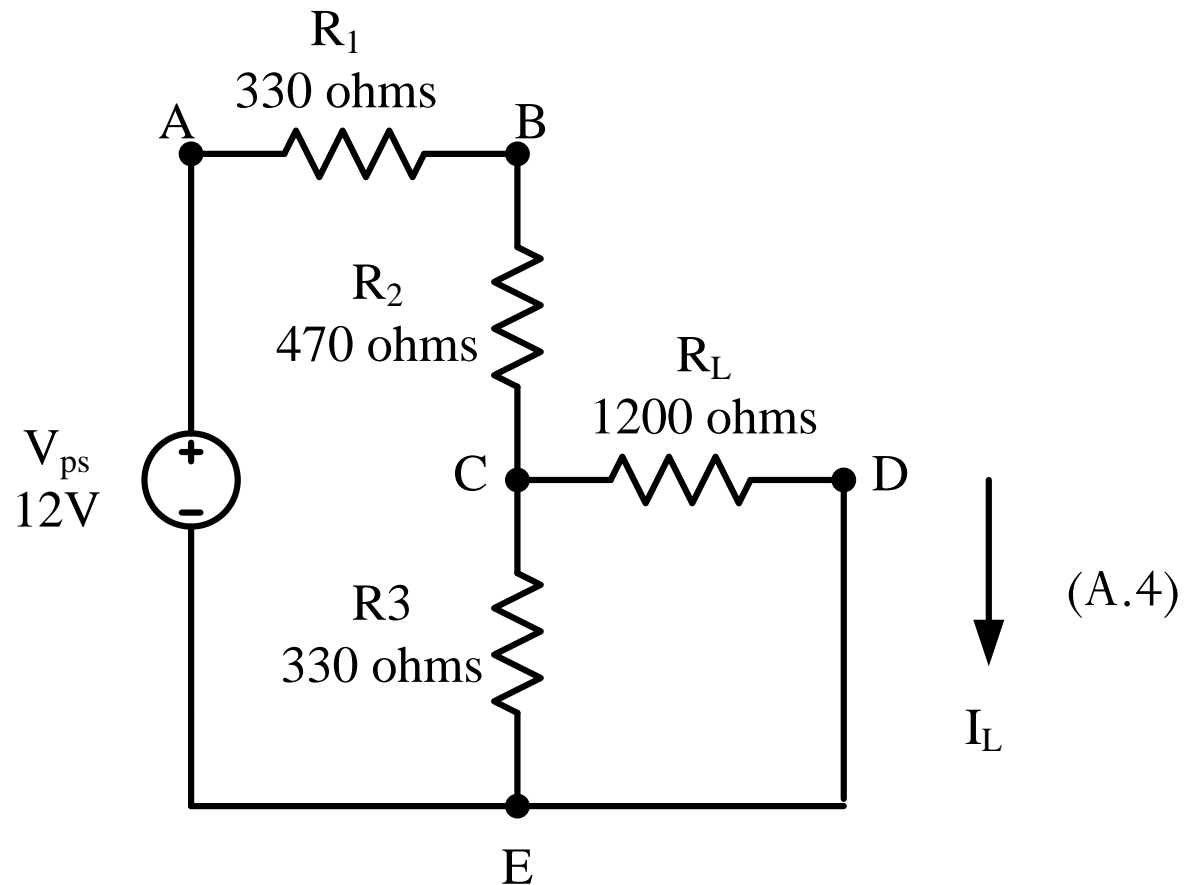


# Outline of the lab

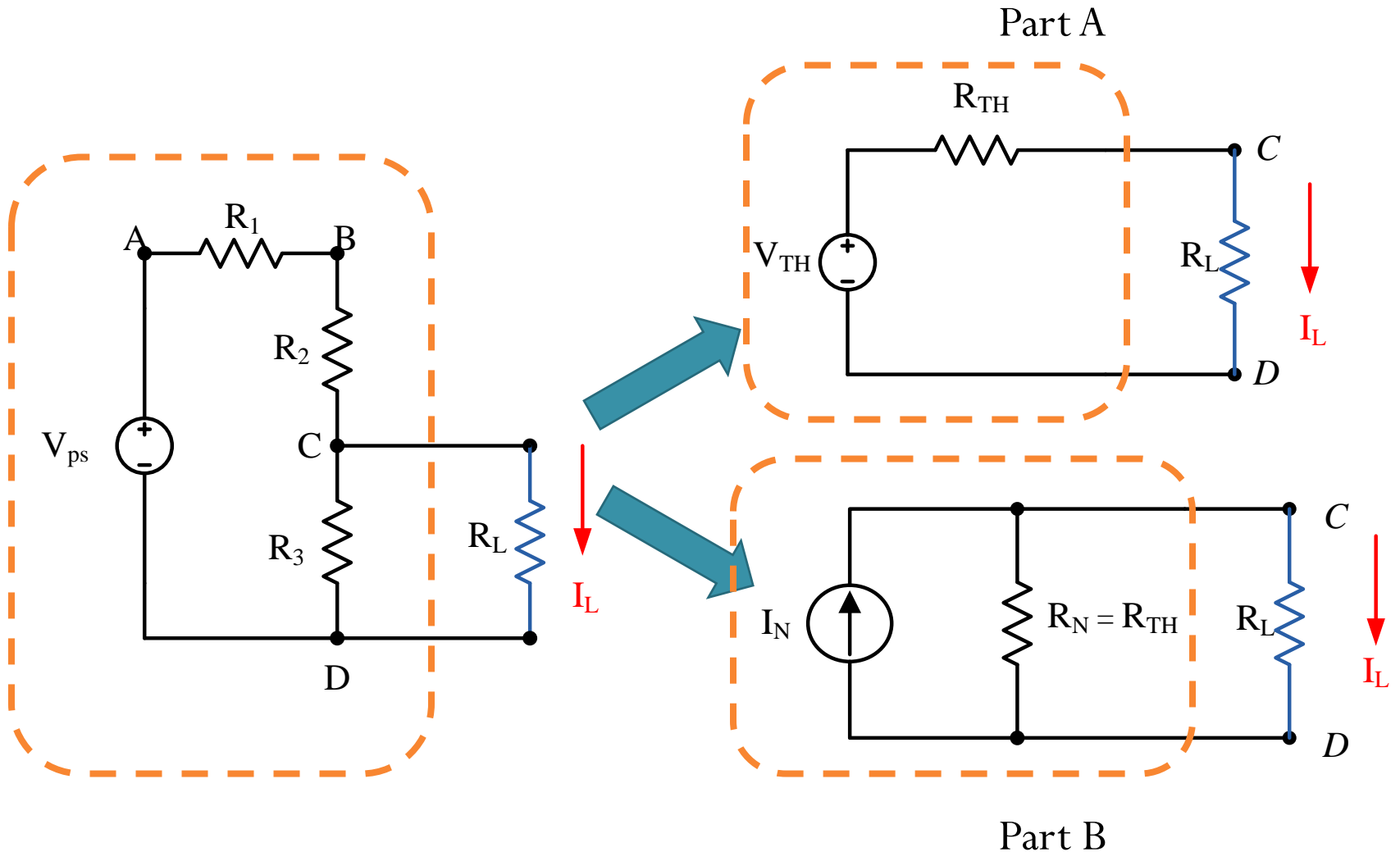

# Part A: Thevenin Equivalent (1)

Part A

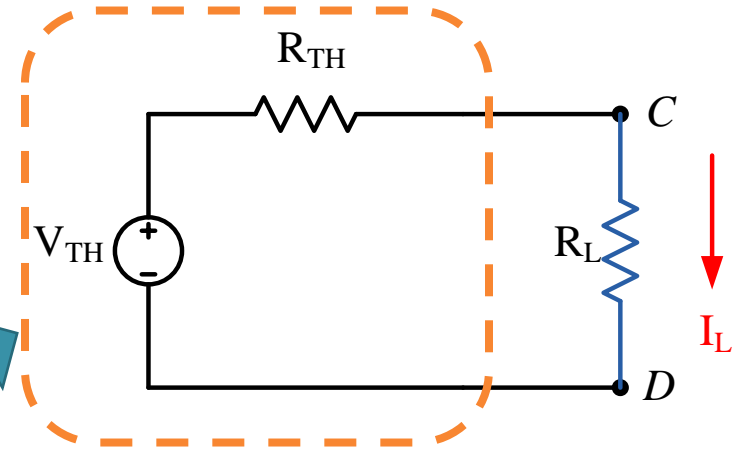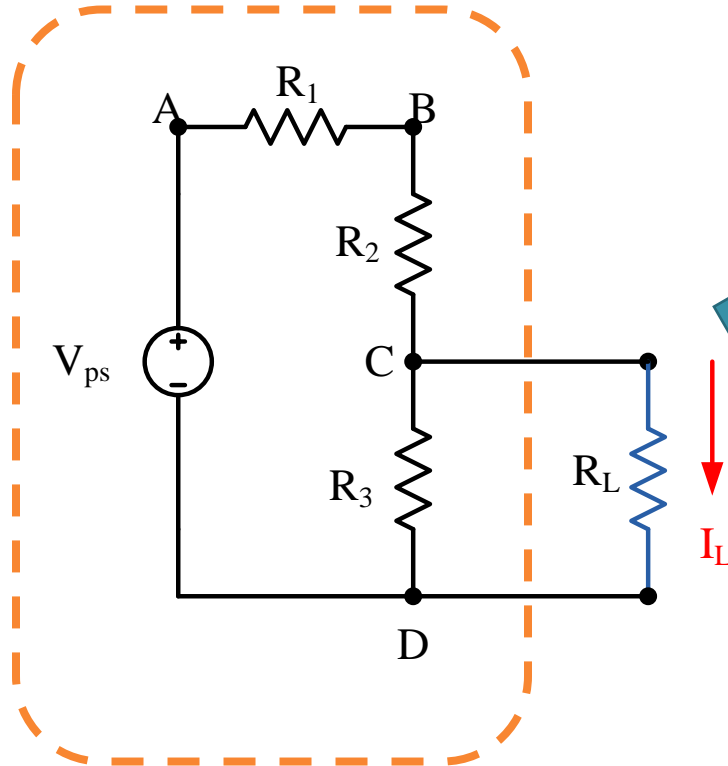



$$V_{TH} = \frac{R_3}{R_1 + R_2 + R_3} V_{ps} \quad (\text{A.12})$$

$$R_{TH} = R_3 // (R_1 + R_2) \quad (\text{A.13})$$

$$I_L = \frac{V_{TH}}{R_{TH} + R_L} \quad (\text{A.14})$$


# Part A: Thevenin Equivalent (2)

Part A

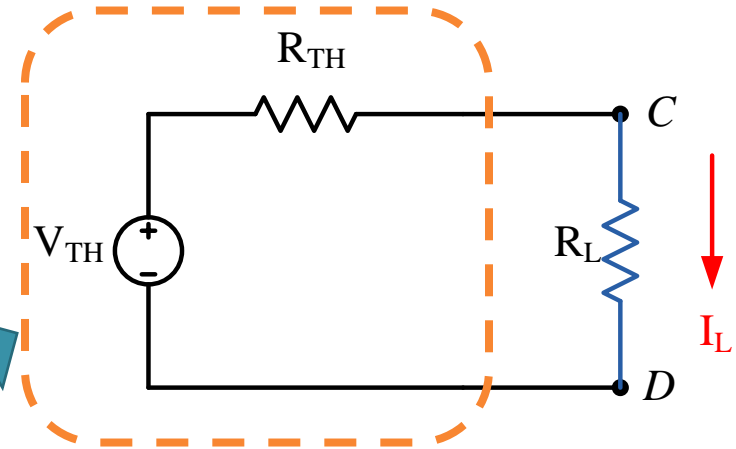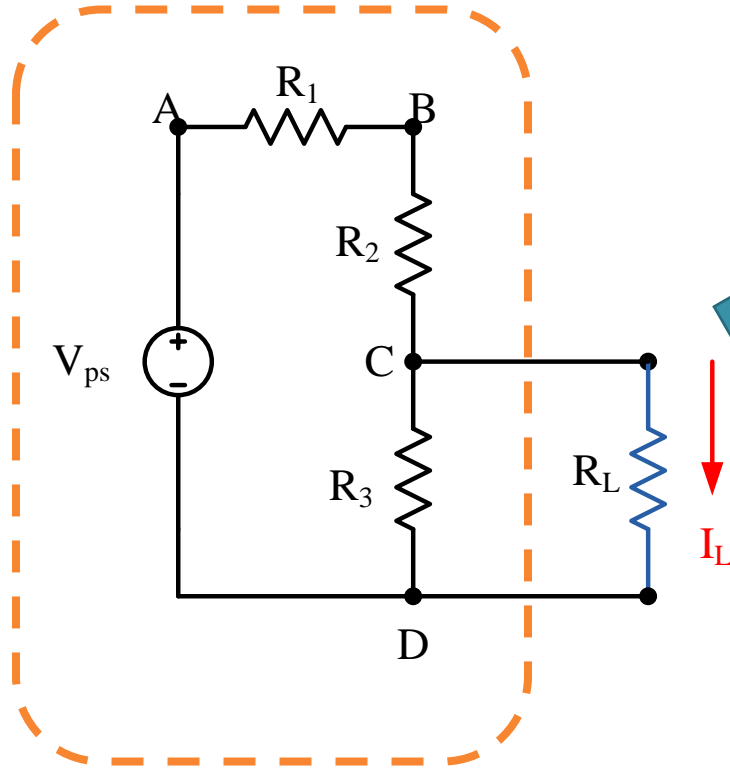

Directly measure  $V_{TH}$  (A.5) and  $R_{TH}$  (A.8)  
Build simplified circuit to measure  $I_L$   
(A.11)


# Part B: Norton Equivalent

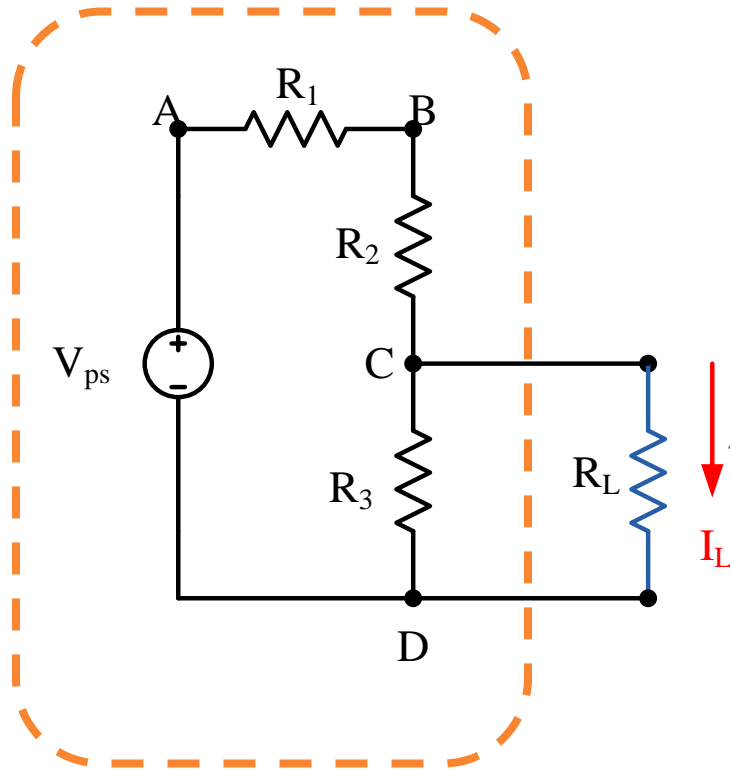

$$R_N = R_{TH}$$

$$I_N = \frac{V_{ps}}{R_1 + R_2} \quad (\text{B.6})$$

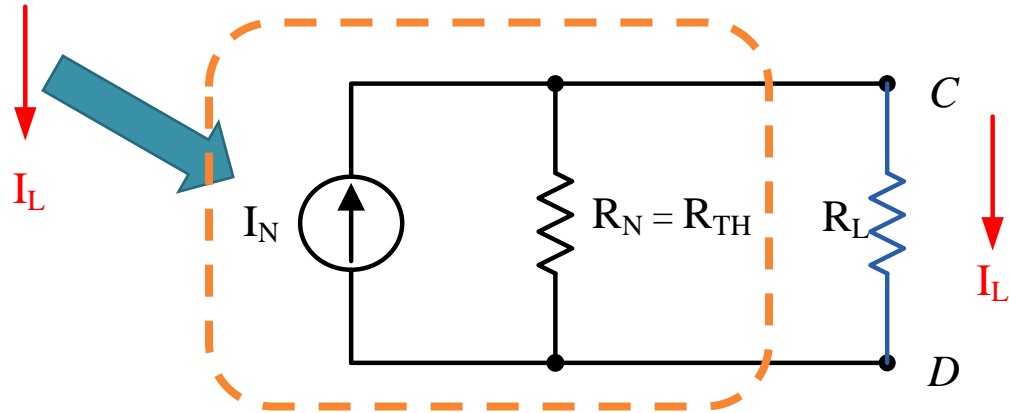
$$I_L = \frac{R_N}{R_L + R_N} I_N \quad (\text{B.7})$$



Part B




# Part B: Norton Equivalent

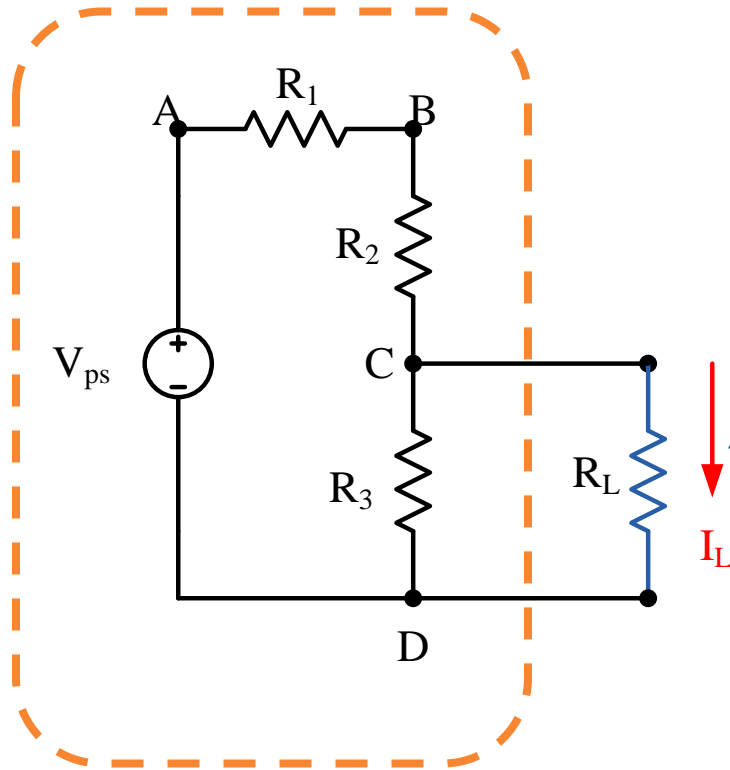


Directly measure  $I_N$  (B.2)

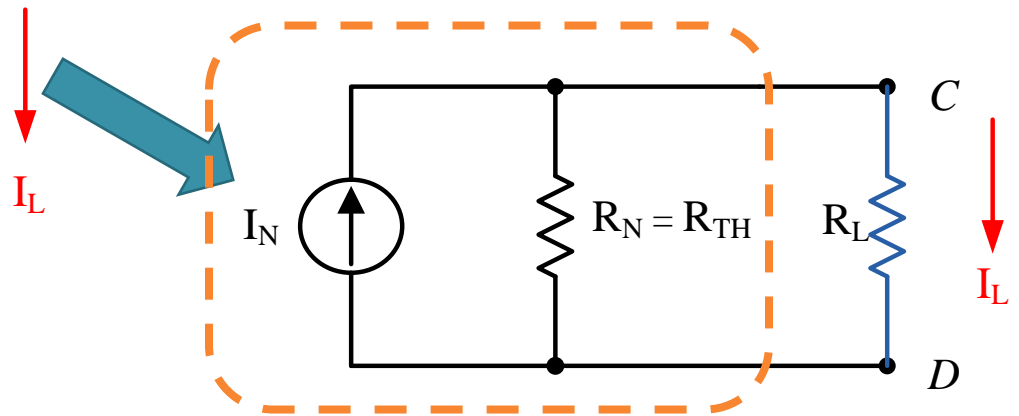Build simplified circuit to measure  $I_L$  (B.5)






Part B

# Lab 2: Summary

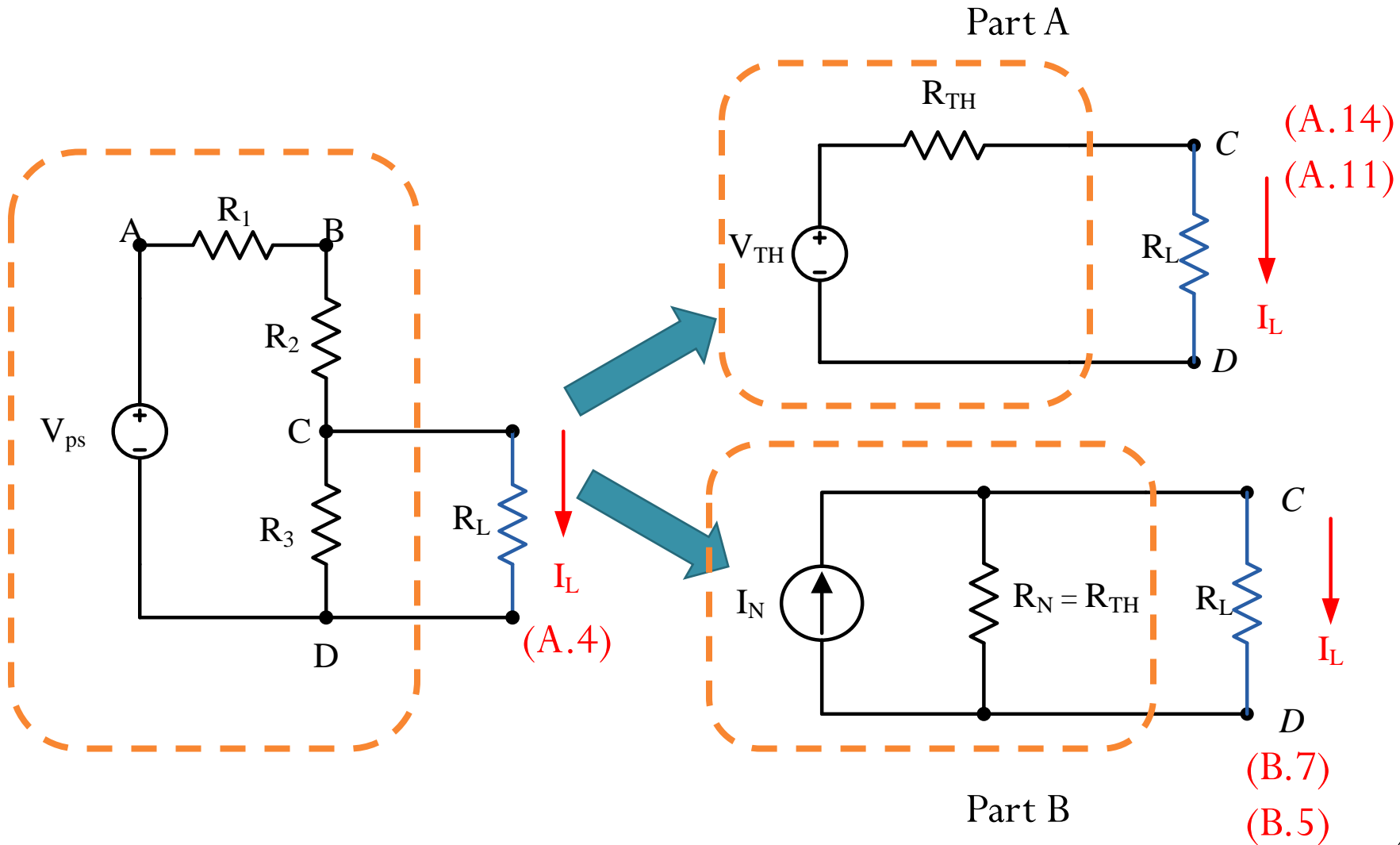

# Lab 2: Summary

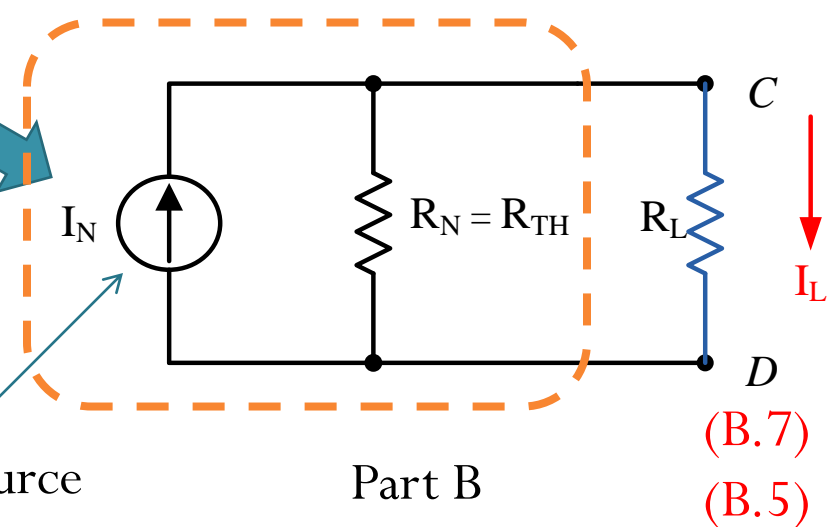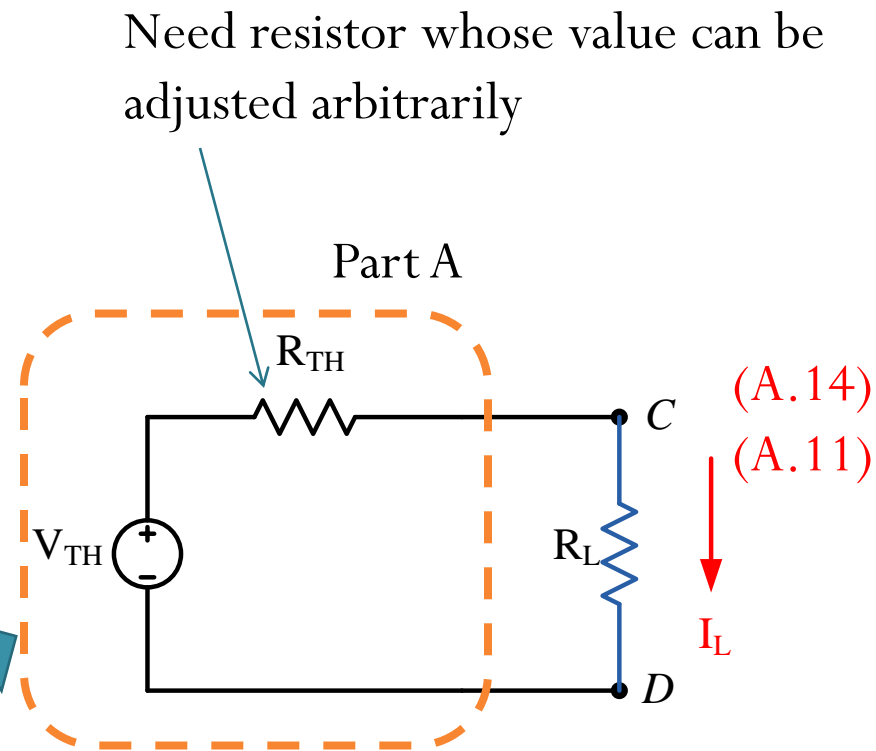
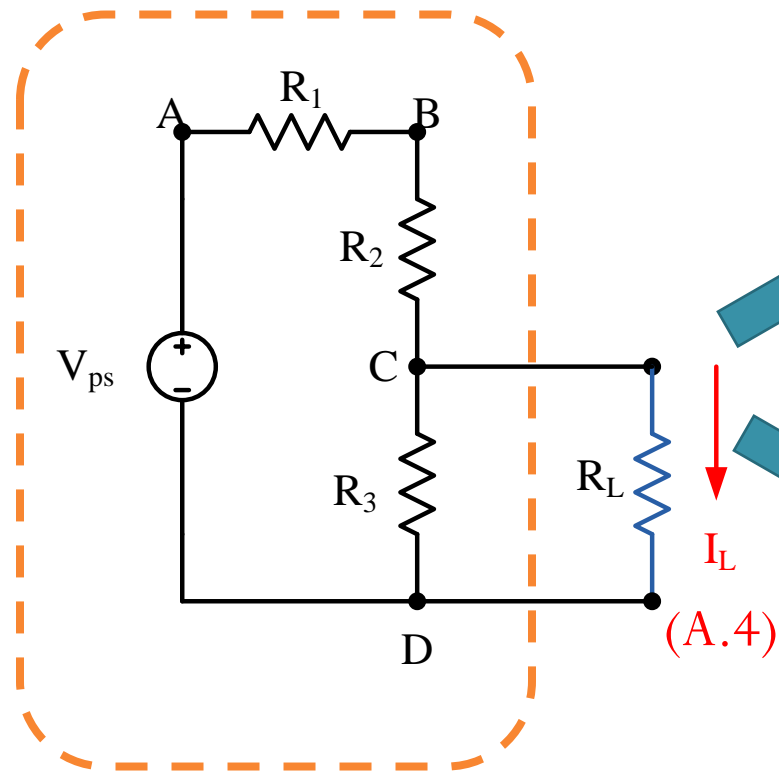


# Potentiometer (Pot)


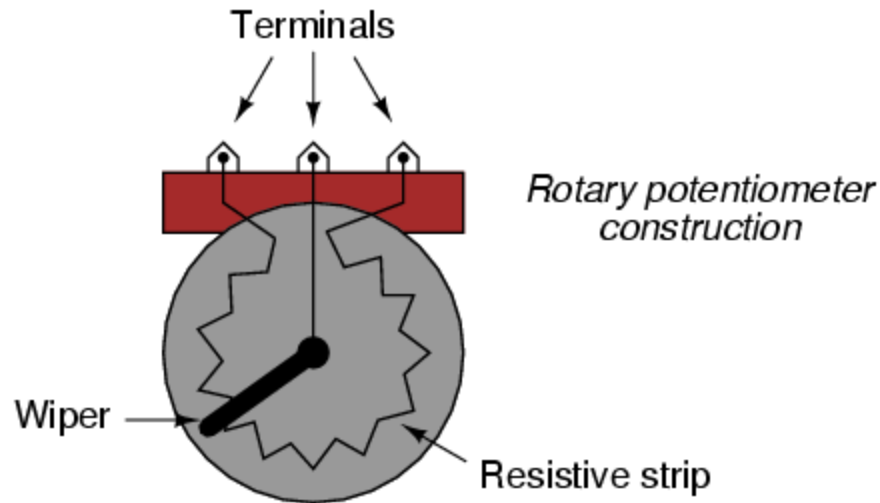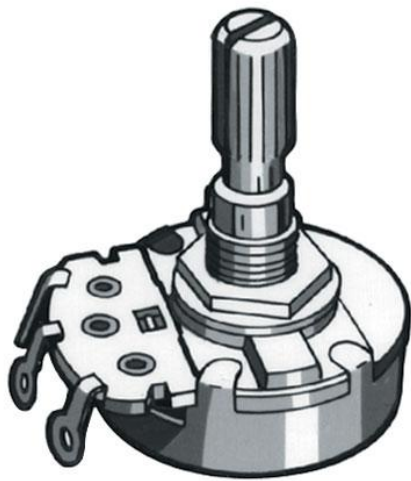
# Pot as a variable resistor

- Manually adjustable resistor
- Three terminals
- The resistance between the middle terminal and either of the two sides depends on the position of the wiper.



# Current source

- We do not have current source.
- We will modify voltage source (power supply) to give the specified amount of current.