

Basic Elec. Engr. Lab

ECS 204/210

Dr. Prapun Sukksompong

prapun@siit.tu.ac.th

Office Hours:

BKD 3601-7


Tuesday 9:30-10:30

Friday 14:00-16:00

Lab 8

- Filter
 - Passive LPF
 - Active LPF
 - Passive HPF
- Circuit Design

Lab 7.B: Inverting Integrator:

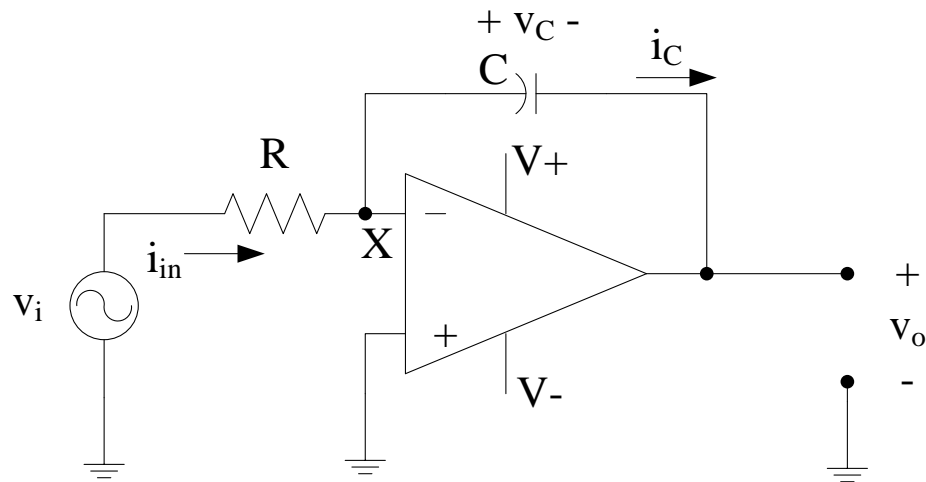


$$\begin{aligned} V_o &= -\left(\frac{Z_C}{R}\right)V_i \\ &= -\left(\frac{V_i}{R}\right) \times \frac{1}{j\omega C} \end{aligned}$$

- The gain at $f = 0$ is unbounded.

Lab 7.B: Inverting Integrator

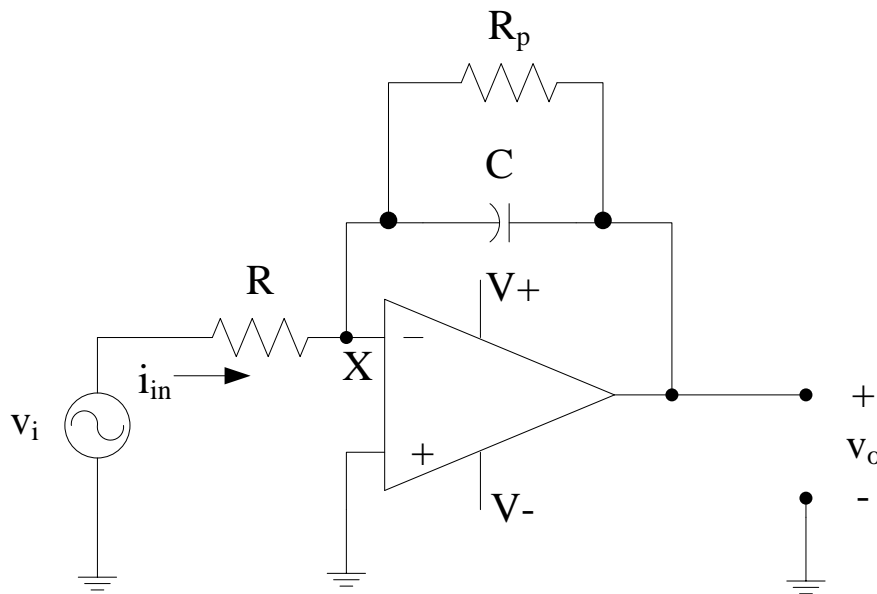- In practical circuit, a large resistor R_p is usually shunted across the capacitor




$$V_o = -\left(\frac{Z_C // R_p}{R}\right)V_i$$
$$= -\left(\frac{V_i}{R}\right) \times \frac{R_p}{j\omega R_p C + 1}$$

- Observe that at $f = 0$, the gain is finite.

Filter

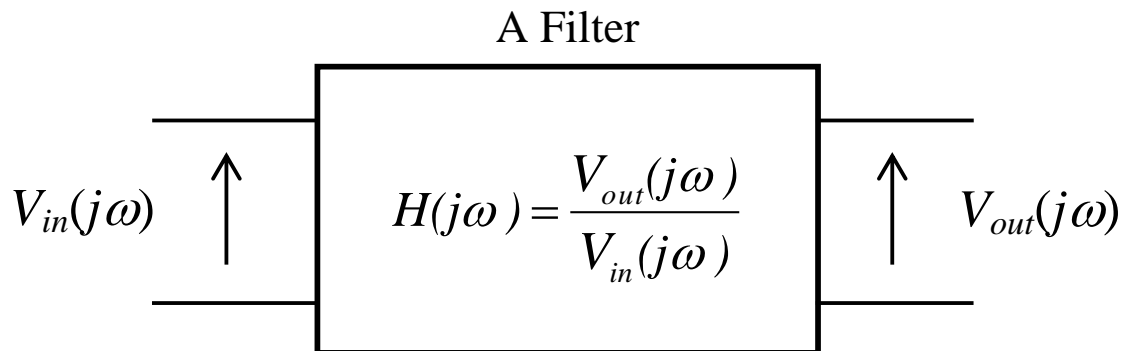- Used in circuits to
 - remove unwanted frequency components, or
 - enhance wanted ones, or
 - both
- Transfer function
 - Magnitude response (“voltage gain” or “frequency response”)
 - phase response (“phase shift”)




Filter

- By Function:


- Low-pass filter (LPF)
- High-pass filter (HPF)
- Bandpass filter (BPF)

- By Electronic Realization:

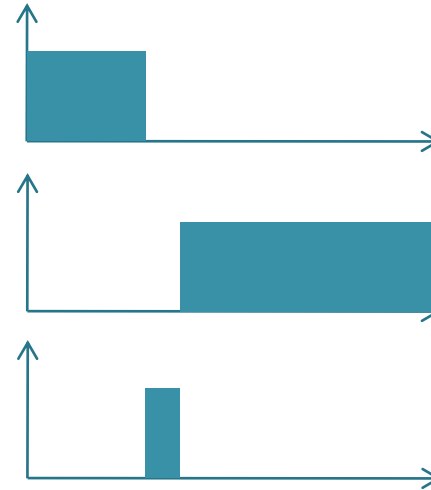- Active
 - contain amplifying devices such as transistors and amplifiers
- Passive



Low-pass filter (LPF)

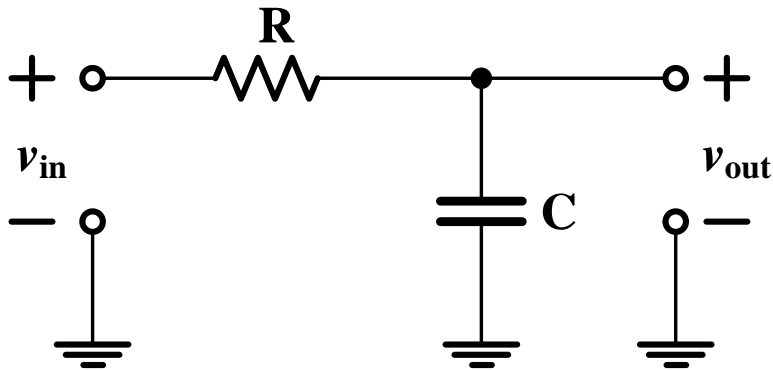


(a) A passive low-pass filter.

Transfer Function

$$H_{LP,passive}(j\omega) = \frac{1}{1 + j\omega RC}$$

Cut-off frequency
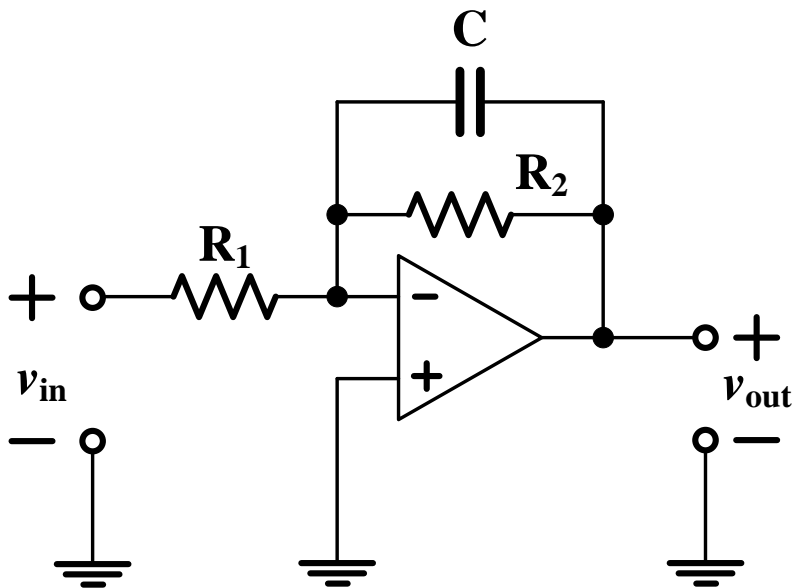
$$\omega_c = \frac{1}{\tau} = \frac{1}{RC} = 2\pi f_c$$



(b) An active low-pass filter


Transfer Function

$$H_{LP,active}(j\omega) = -\frac{R_2}{R_1} \left(\frac{1}{1 + j\omega R_2 C} \right)$$

Cut-off frequency

$$\omega_c = \frac{1}{\tau} = \frac{1}{R_2 C} = 2\pi f_c$$

Part A: Passive LPF

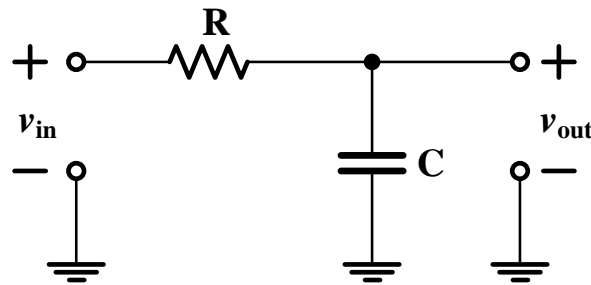


Transfer Function

$$H_{LP,passive}(j\omega) = \frac{1}{1 + j\omega RC}$$


Cut-off frequency

$$\omega_c = \frac{1}{\tau} = \frac{1}{RC} = 2\pi f_c$$

(a) A passive low-pass filter.

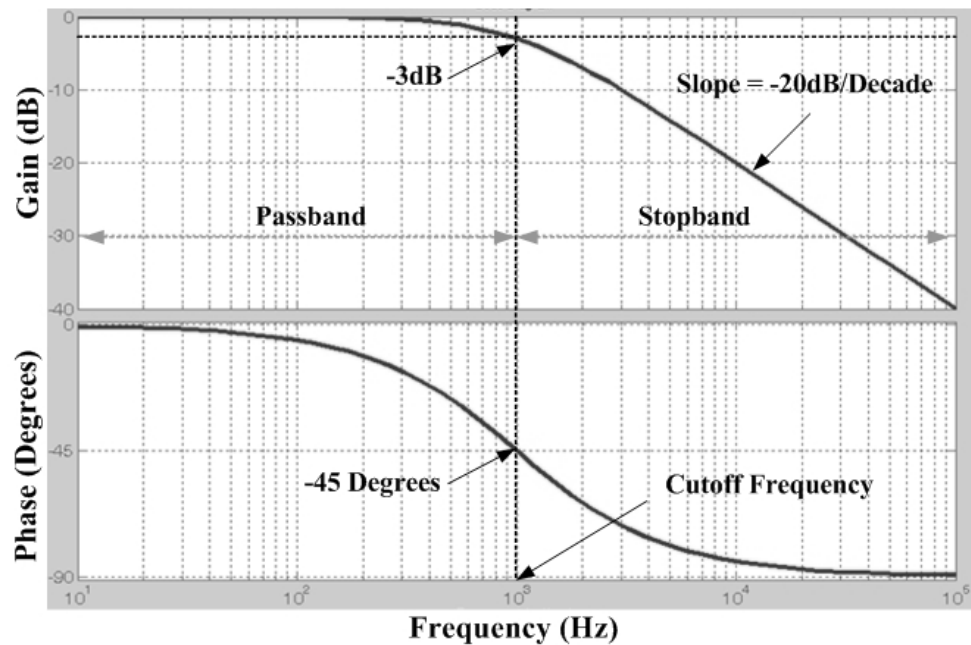

High-pass filter (HPF)

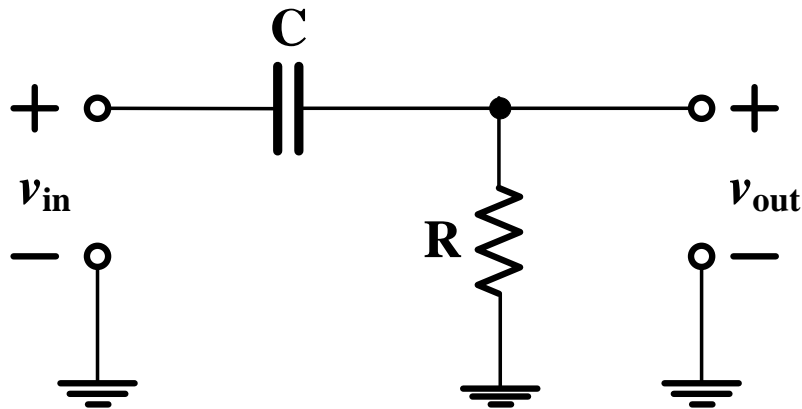


(a) A passive high-pass filter.

Transfer Function

$$H_{HP,passive}(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

Cut-off frequency
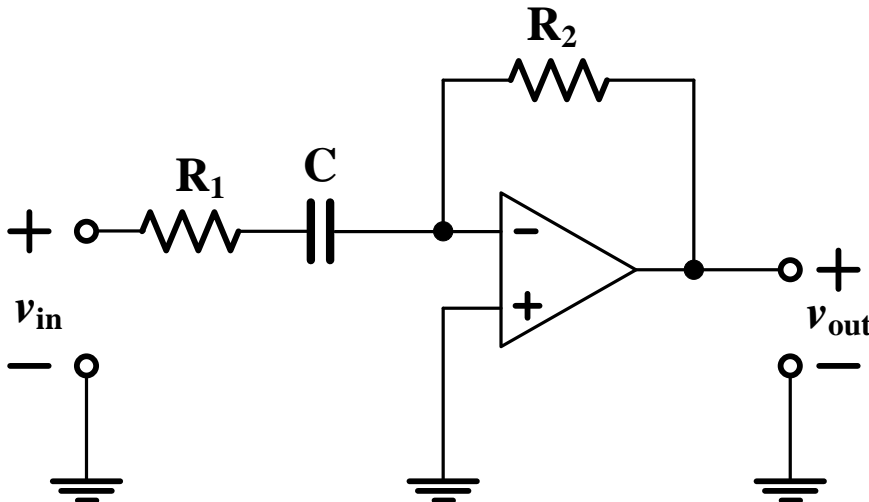
$$\omega_c = \frac{1}{\tau} = \frac{1}{RC} = 2\pi f_c$$



(b) An active high-pass filter


Transfer Function

$$H_{HP,active}(j\omega) = -\frac{j\omega R_2 C}{1 + j\omega R_1 C}$$

Cut-off frequency

$$\omega = \frac{1}{\tau} = \frac{1}{R_1 C} = 2\pi f$$

Part B: Passive HPF

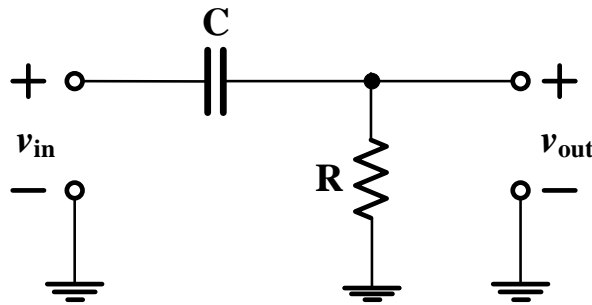


Transfer Function

$$H_{HP,passive}(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$$


Cut-off frequency

$$\omega_c = \frac{1}{\tau} = \frac{1}{RC} = 2\pi f_c$$


(a) A passive high-pass filter.

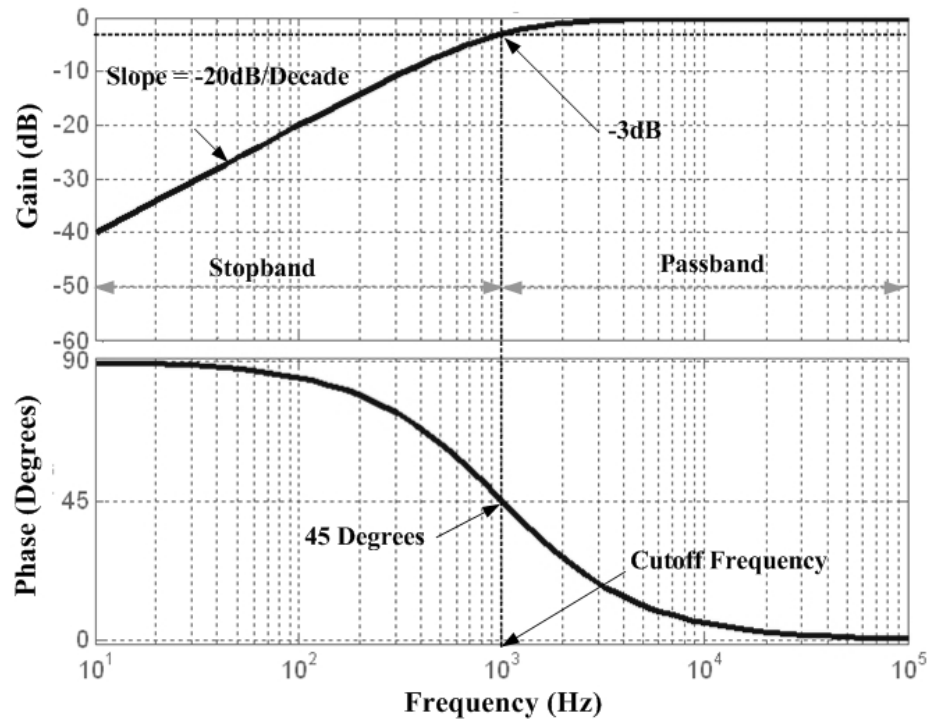

Part C: Active LPF Design

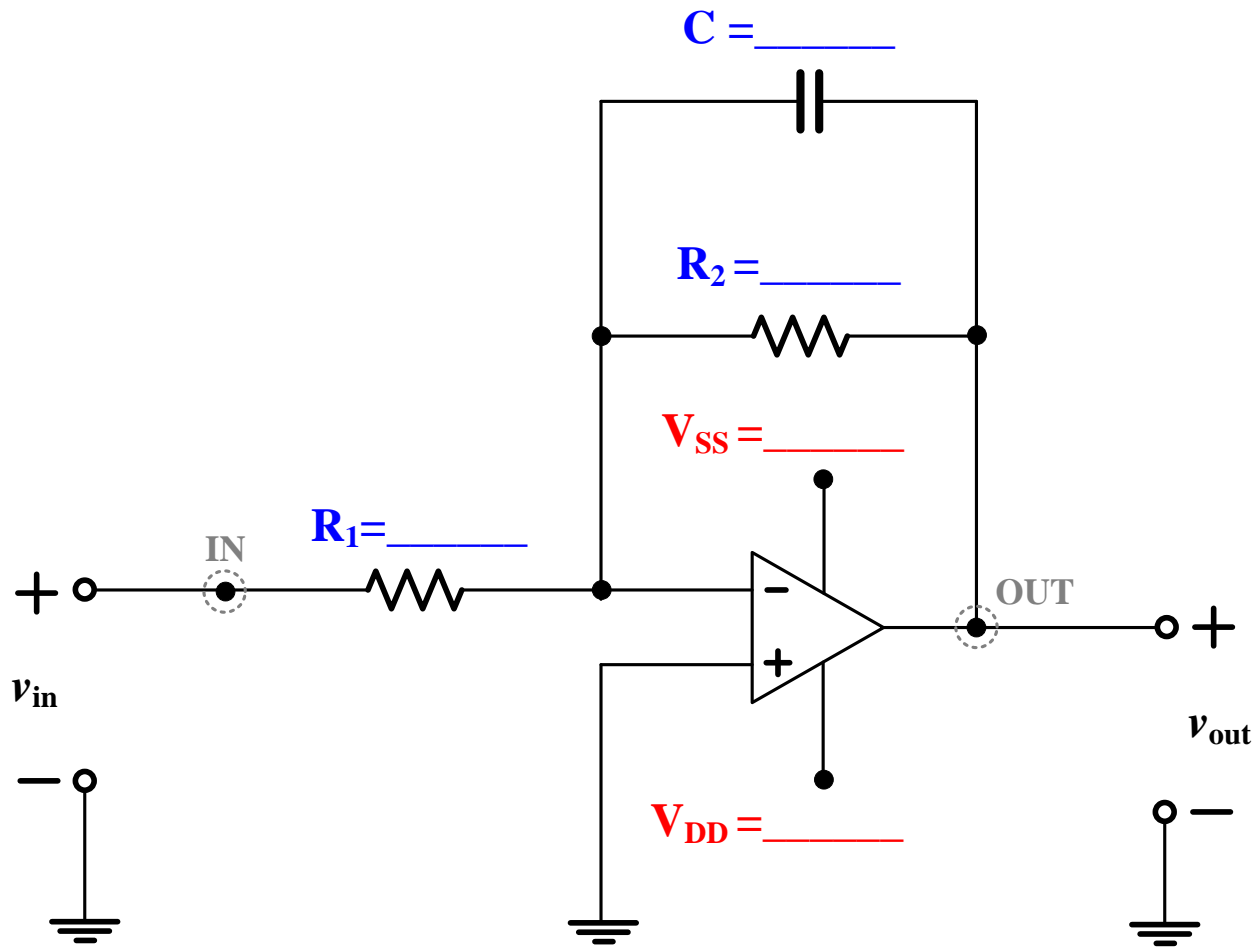

Part D: Bandpass filter (BPF) - Optional

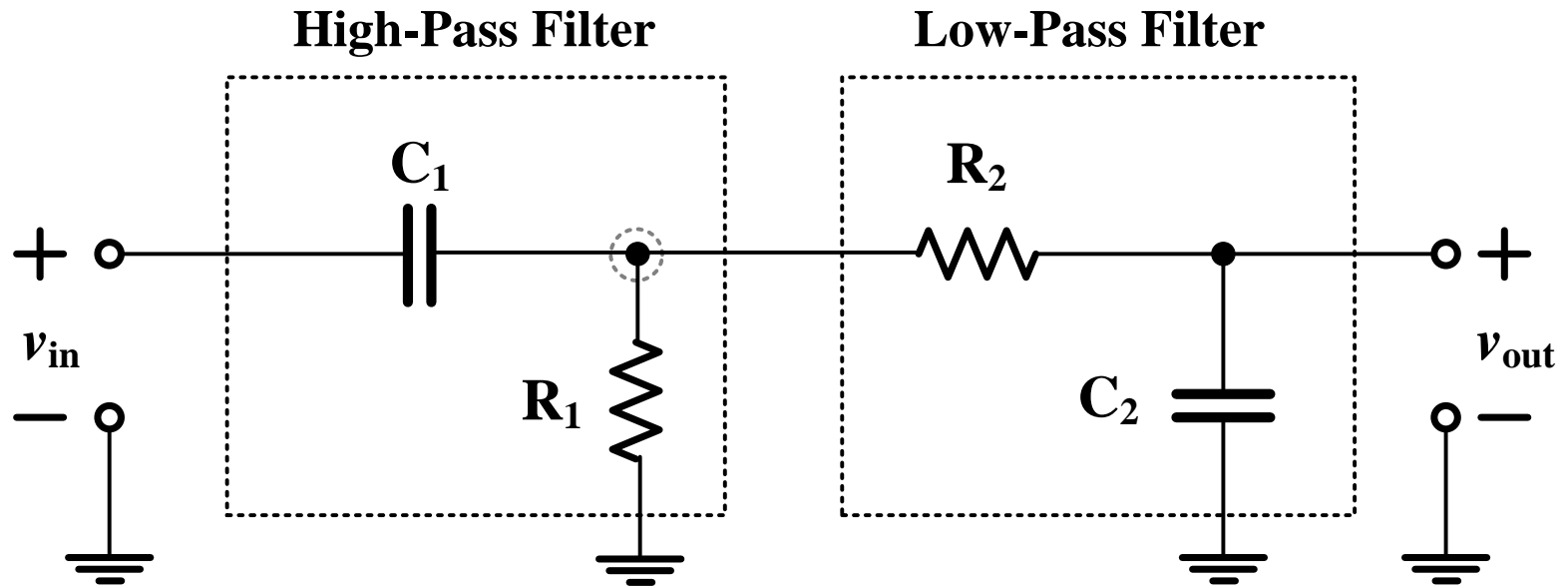

Lower cutoff frequency
(Determined by HP filter)

$$\omega_1 = \frac{1}{\tau_1} = \frac{1}{R_1 C_1} = 2\pi f_1$$

Upper cutoff frequency
(Determined by LP filter)

$$\omega_2 = \frac{1}{\tau_2} = \frac{1}{R_2 C_2} = 2\pi f_2$$