

Practice Midterm Exam

COURSE : ECS210 Basic Electrical Engineering Laboratory
INSTRUCTOR : Dr. Prapun Suksompong
TIME : _____ (45 minutes per subsection)
PLACE : BKD 3502

| | | | |
|---------|-------------------------------------------------------------|--------|--|
| Name | | ID | |
| Section | <input type="checkbox"/> 9 AM <input type="checkbox"/> 1 PM | Bench# | |

Instructions:

1. This is a practice exam for the midterm examination.
2. **Read these instructions and the questions carefully.**
3. **Closed book. Closed notes.**
4. **No calculator.**
5. For the problems that ask for **TA's signatures**, lack of the signature(s) means no credit for the whole problem. Having the signatures mean that the values recorded are the same as the values measured. These signatures **do not guarantee** that you have the **correct answers**.
6. **No TA's signature = 0 for the whole part.**
7. Allocate your time wisely. Some easy questions give many points.
8. **Do not cheat.** The use of communication devices including mobile phones is prohibited in the examination room.
9. The TAs will **not help you debug your circuit.**
10. **Record at least two decimal places** from the DMM. Do not write 12 mA when you see **12.00 mA** on the DMM's display.
11. Write your **first name** and the **last three digits of your ID** on each page of your examination paper, starting from page 2.
12. For the actual exam,
 - a. group a: **1:15 – 2:00 PM** ←
 - group b: **2:15 – 3:00 PM** ←
 - b. arrive at least **5 minutes early**
 - c. do not leave the exam room until the end of the allotted time.
13. **Clean your desk/bench before you leave** the exam room.
14. Do not panic.

| ID | Group |
|------------|-------|
| 5222770950 | a |
| 5222771164 | b |
| 5222780082 | a |
| 5222780256 | b |
| 5222780272 | b |
| 5222780363 | a |
| 5222780892 | b |
| 5222781387 | b |
| 5222781486 | a |
| 5222781510 | b |
| 5222781577 | b |
| 5222781619 | b |
| 5222781718 | b |
| 5222781825 | a |
| 5222781999 | a |
| 5222782161 | a |
| 5222782401 | b |
| 5222782427 | a |
| 5222790362 | a |
| 5222790479 | a |
| 5222790867 | b |
| 5222791030 | b |
| 5222791097 | a |
| 5222791253 | a |
| 5222791493 | b |
| 5222792129 | b |
| 5222792764 | a |
| 5222800138 | a |
| 5222800302 | a |
| 5222800658 | b |

Name _____

ID _____

Consider the circuit in Figure 1.

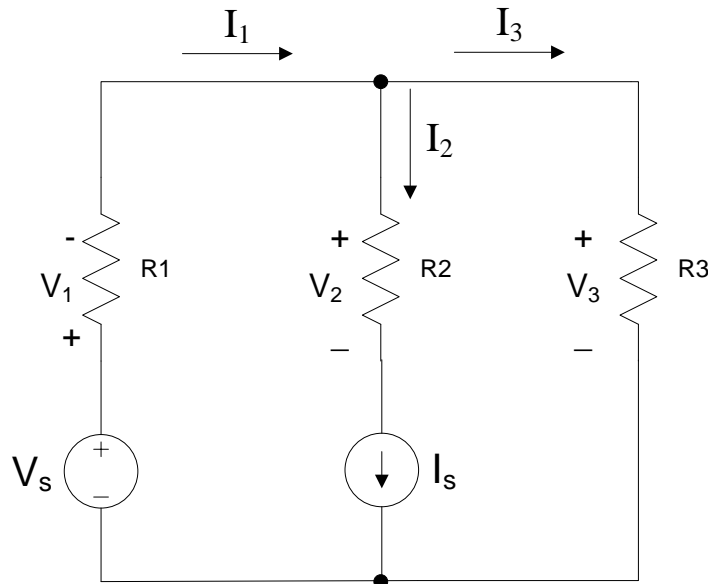


Figure 1

Let $R_1 = 820 \Omega$, $R_2 = 1.2 \text{ k}\Omega$, and $R_3 = 2.2 \text{ k}\Omega$, $V_S = 15 \text{ V}$, $I_S = 12 \text{ mA}$

1. Measure the exact values of R_1 to R_3 .

$R_1 =$ _____ $R_2 =$ _____ $R_3 =$ _____

2. Connect the circuit in Figure 1. Record the exact values of V_S and I_S .

$V_S =$ _____ V $I_S =$ 5 mA

Ask any lab supervisor to witness your measurement of I_S . Obtain his/her signature.

Signature for I_S 2 (5 mA)

(Having the signatures mean that the value recorded are the same as the value measured. This does not guarantee that you have the correct answer.)

3. Measure voltage and current in the following table.

| Only V_S is active (24 pt.) | | | | Only I_S is active (6 pt.) | | | | Both V_S and I_S are active (6 pt.) | | | |
|----------------------------------|--|-------|--|---------------------------------|--|-------|--|--------------------------------------------|--|-------|--|
| I_1 | | V_1 | | I_1 | | V_1 | | I_1 | | V_1 | |
| I_2 | | V_2 | | I_2 | | V_2 | | I_2 | | V_2 | |
| I_3 | | V_3 | | I_3 | | V_3 | | I_3 | | V_3 | |

Watch out for the signs and the units. Ask any lab supervisor to witness your measurement of V_3 for the case that only I_S is active. Obtain his/her signature.

Signature for V_3 _____

4. Find the Thevenin equivalent circuit at R_3 by considering R_3 as a load. Show the lab supervisor your *measurement* and obtain his/her signatures.

Name _____ ID _____

$V_{TH} =$ _____ $R_{TH} =$ _____

Signature for V_{TH} _____ Signature for R_{TH} _____

5. Draw the Thevenin equivalent circuit. Show the numerical values in your drawing.

6. Draw the Norton equivalent circuit. Show the numerical values in your drawing.