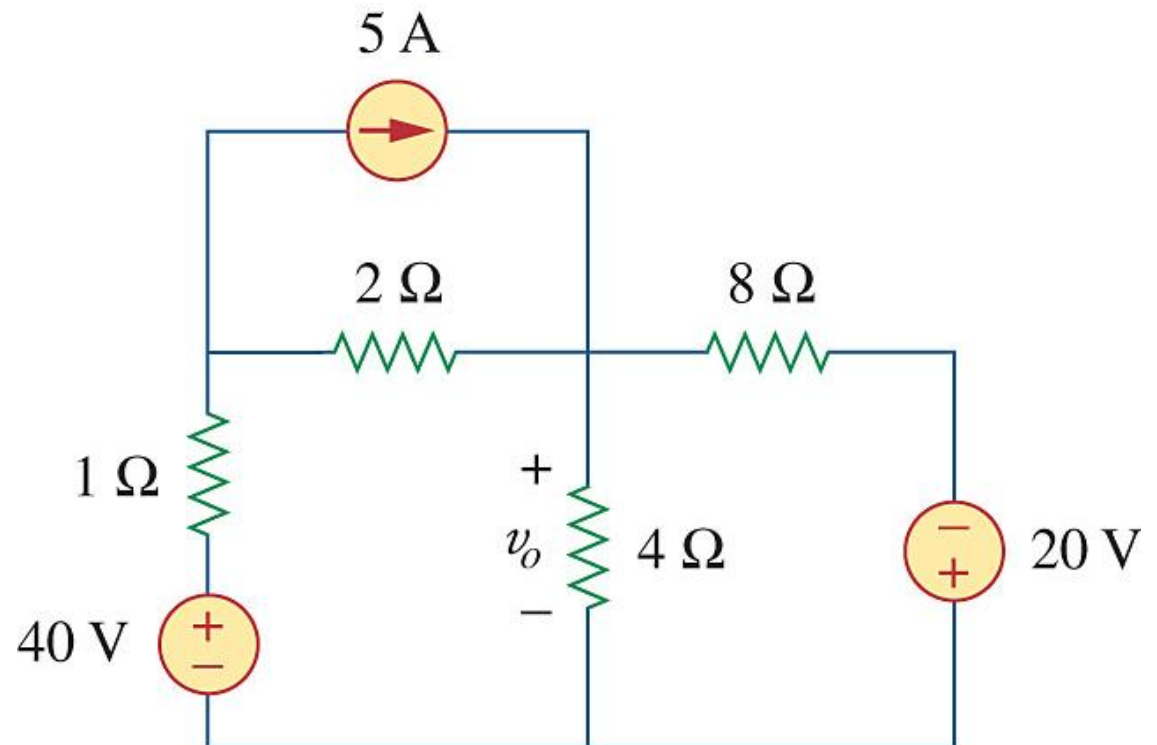


Big Question


Find v_o using

1. Nodal Analysis
2. Mesh Analysis
3. Superposition
4. Source Transformation
5. Thevenin equivalent
6. Norton equivalent



⑤ Thevenin Equivalent

R_{TH} :

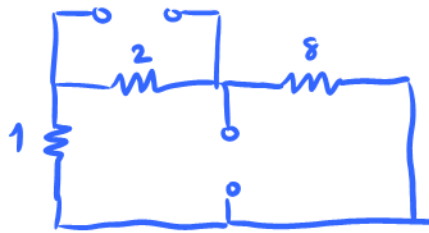

$$R_{TH} = 8 // (2+1) \Omega$$


$$= 8 // 3 = \frac{8 \times 3}{8+3}$$

$$= \frac{24}{11} \Omega$$

V_{TH} :

source transformation
40V

$5 \times 2 = 10V$


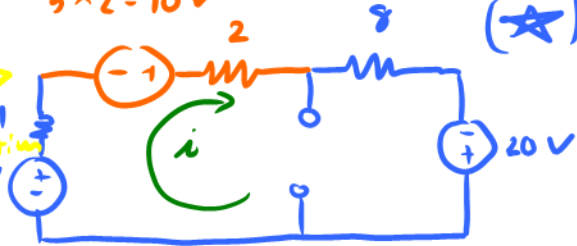


There is only one loop.

$$i = \frac{20 + 40 + 10}{11} = \frac{70}{11}$$

$$V_{TH} = -20 + \frac{70}{11} \times 8$$
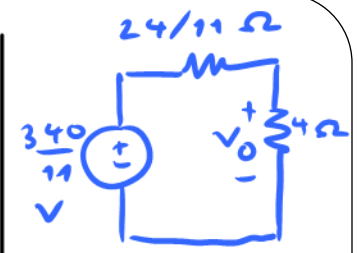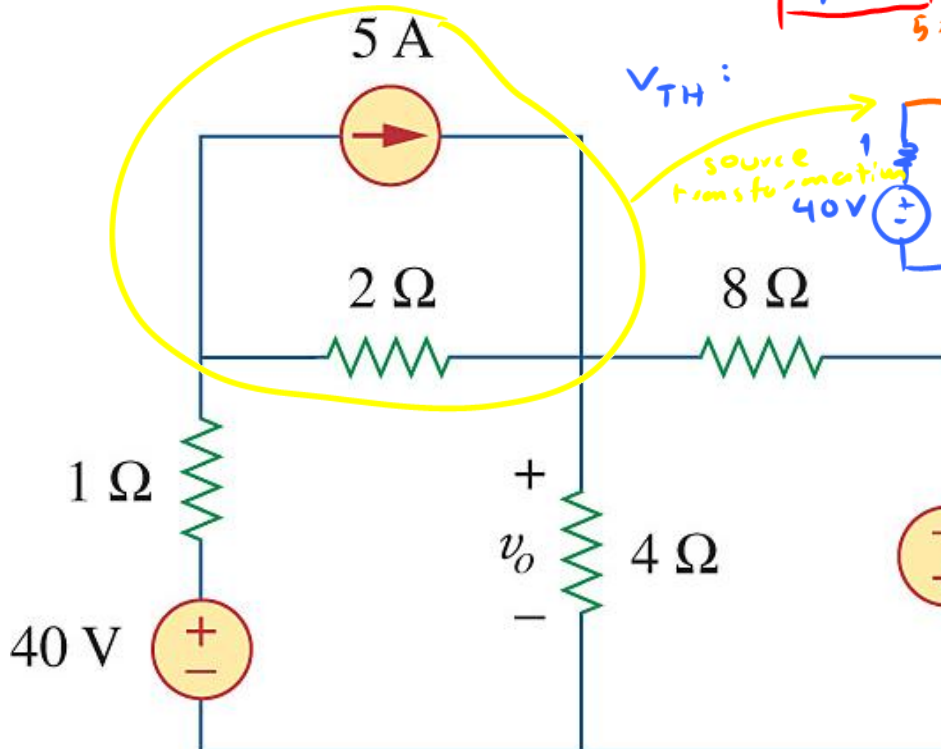
$$= \frac{560 - 220}{11} = \frac{340}{11} V$$



$$v_o = \frac{4}{4 + \frac{24}{11}} \times \frac{340}{11}$$


$$= \frac{4 \times 340}{\cancel{44} \times 2}$$

$$= \frac{20 \times 340}{44} = \frac{20 \times 34}{11} = \frac{680}{11} = 61.818 V$$


⑥ Norton Equivalent

R_N : Same as R_{TH} above = $\frac{24}{11} \Omega$

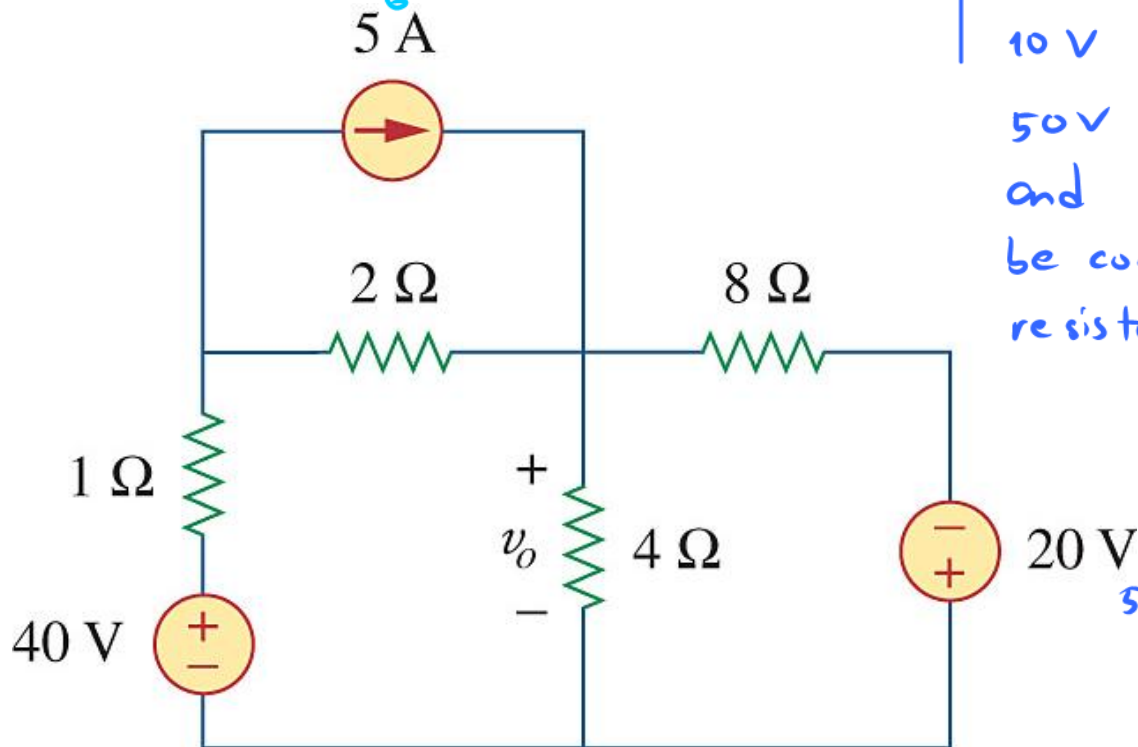$I_N = \frac{V_{TH}}{R_N} = \frac{\frac{85}{6}}{\frac{24}{11}} = \frac{85}{6} A$



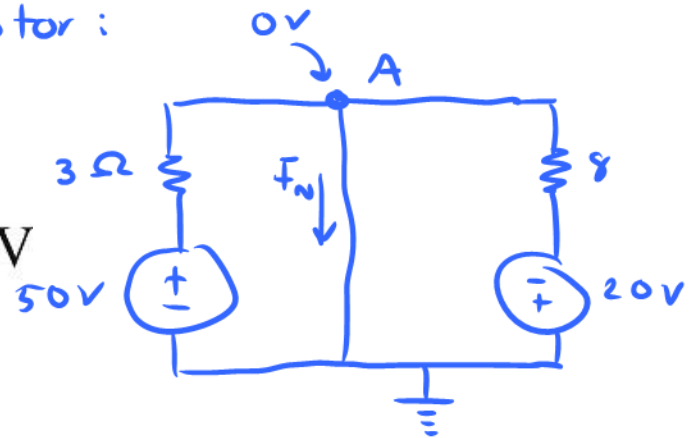Alternatively, to find I_N directly, we perform one source transformation as in the Thevenin case above. Then we combine 40V and 10V voltage sources into a 50V voltage source. The 1Ω and 2Ω resistors can also be combined into one 3Ω resistor:



KCL @ A: $I_N + \frac{0-50}{3} + \frac{0-(-20)}{8} = 0$

$v_o = \frac{85}{6} \times \left(\frac{24}{11} // 4 \right) = \frac{85}{6} \times \frac{24}{17} = 20V$

