

Basic Electrical Engineering

ECS 303

Dr. Prapun Sukksompong

prapun@siit.tu.ac.th

Lecture 8 (Review)

Office Hours:

BKD 3601-7

Tuesday 14:00-16:00


RS ETU (1st floor)

Friday 15:00-16:00

Announcement


- Reading assignment
 - Chapter 3: 3.1-3.5, 3.7
 - Chapter 4
 - Chapter 5

Op Amp

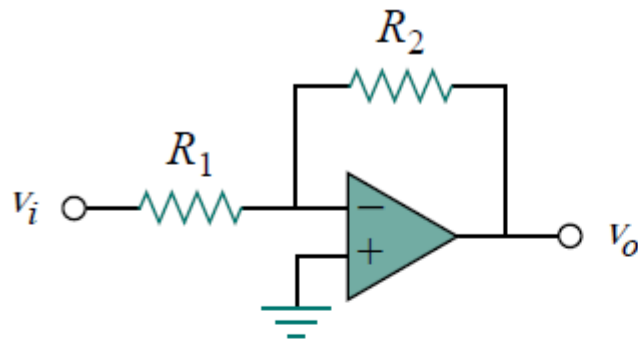


Inverting amplifier

$$v_o = -\frac{R_2}{R_1}v_i$$

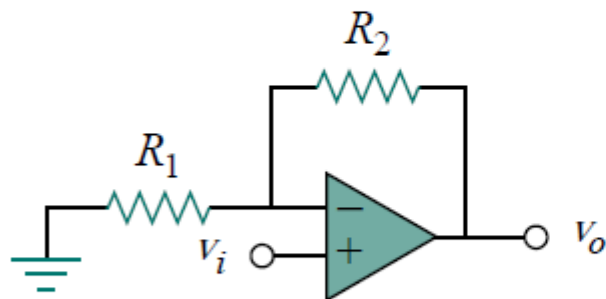

Noninverting amplifier

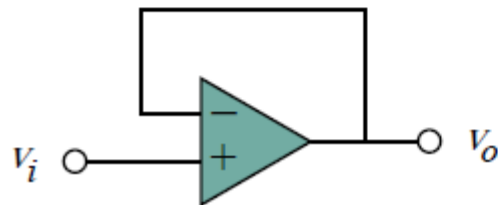
$$v_o = \left(1 + \frac{R_2}{R_1}\right)v_i$$



Voltage follower


$$v_o = v_i$$

Op Amp

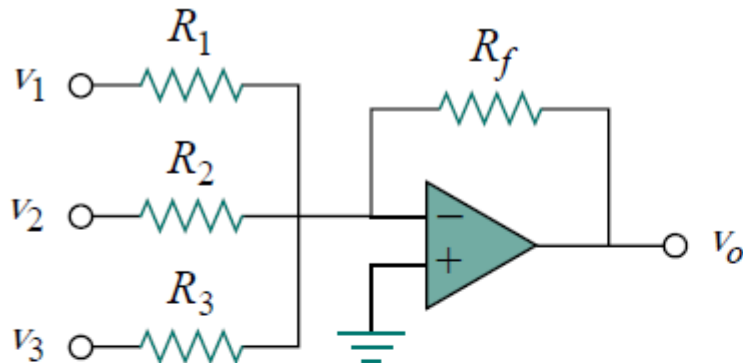

Summer
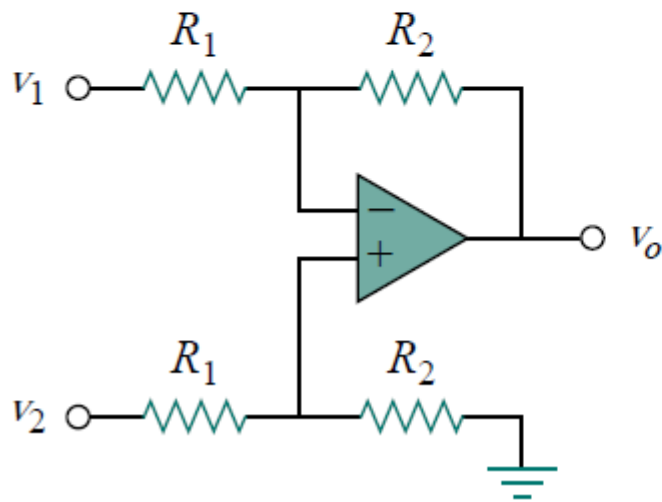
$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$





Difference amplifier

$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

Midterm Exam

- Not to torture you!
- Most questions are straightforward
- A few difficult ones
 - Worth 1 to 2 points each
- Study
 - HW questions
 - Only small parts of HWs are graded.
 - Please take a careful look at the solution.
 - Lecture notes
 - Textbook chapters
- Check the course web site!
 - There might be useful information for you.

Equivalent Resistance

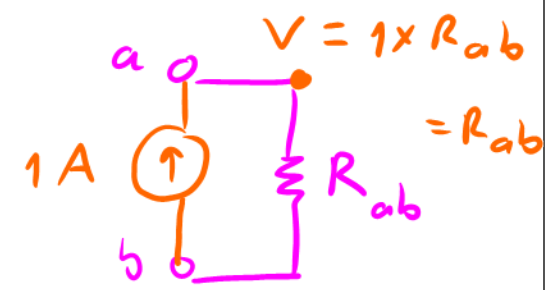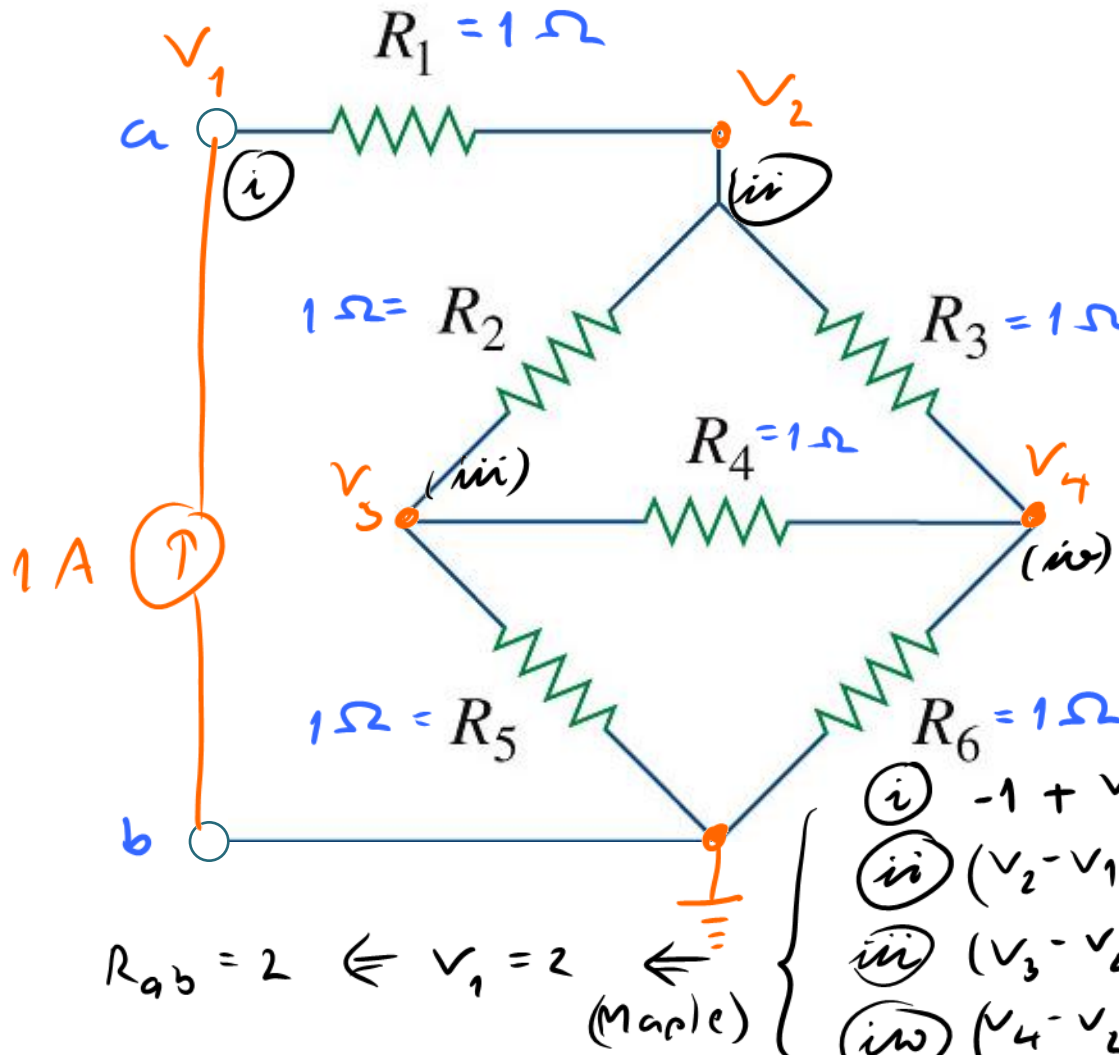

- ① these two circuits are equivalent; so $V_1 = R_{ab}$.
- ② Use nodal analysis to find V_1 .

$R_{ab} = 2 \leftarrow V_1 = 2$ (Marple)


 {

- ① $-1 + V_1 - V_2 = 0$
- ② $(V_2 - V_1) + (V_2 - V_3) + (V_2 - V_4) = 0$
- ③ $(V_3 - V_2) + (V_3 - V_4) + V_3 = 0$
- ④ $(V_4 - V_2) + (V_4 - V_3) + V_4 = 0$

Big Question

Find v_o using

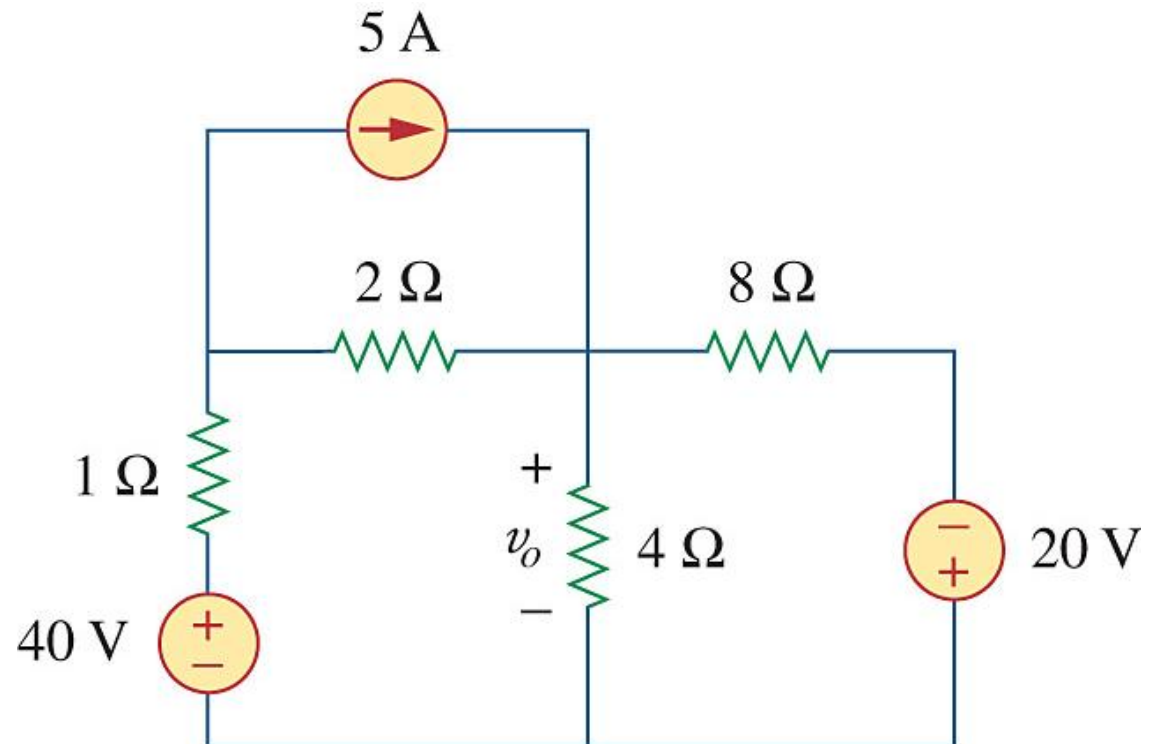1. Nodal Analysis
2. Mesh Analysis
3. Superposition
4. Source Transformation
5. Thevenin equivalent
6. Norton equivalent



Nodal Analysis

$$A + B : 5 + \frac{V_B - V_A}{2} + \frac{V_B - 40}{1} = 0$$


$$A + A :$$

$$5A$$

$$-5 + \frac{V_A - V_B}{2} + \frac{V_A + 20}{8} + \frac{V_A - 0}{4} = 0$$

$$\left. \begin{array}{l} \\ \\ \end{array} \right\} \text{maple} \Rightarrow \begin{array}{l} V_A = 20 \\ V_B = 30 \end{array}$$

$$V_o = 20V$$

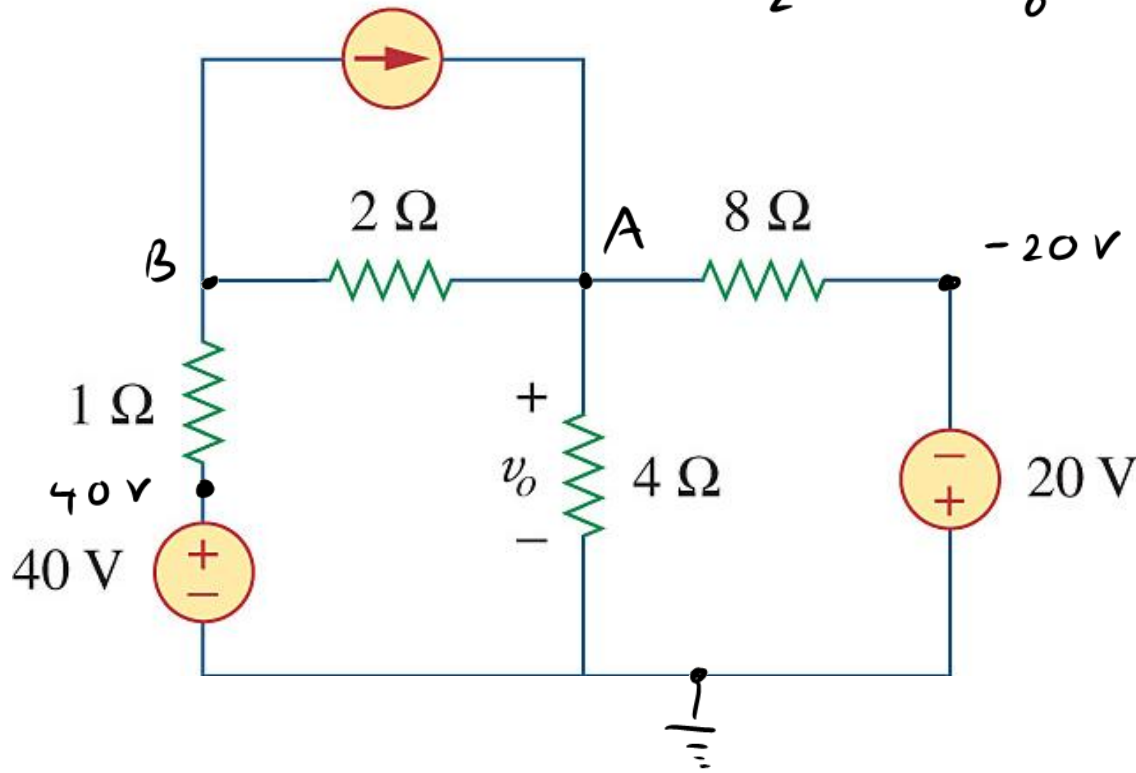


Mesh Analysis

$$\textcircled{1} \quad i_1 = 5A$$

$$\textcircled{2} : 40 - i_2 \times 1 - (i_2 - i_1) \times 2 - (i_2 - i_3) \times 4 = 0$$
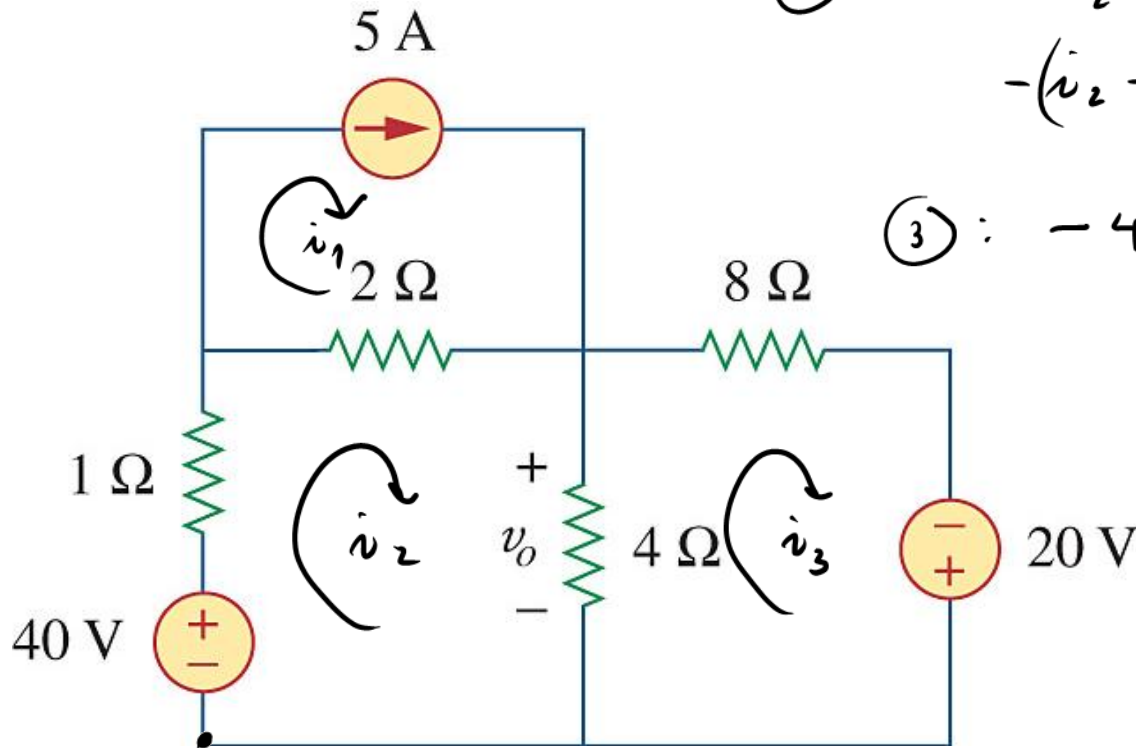
$$\textcircled{3} : -4 \times (i_3 - i_2) - 8 \times i_3 + 20 = 0$$




⇓ maple

$$i_2 = 10$$
$$i_3 = 5$$


$$v_o = (i_2 - i_3) \times 4 = 20V.$$

Superposition

①

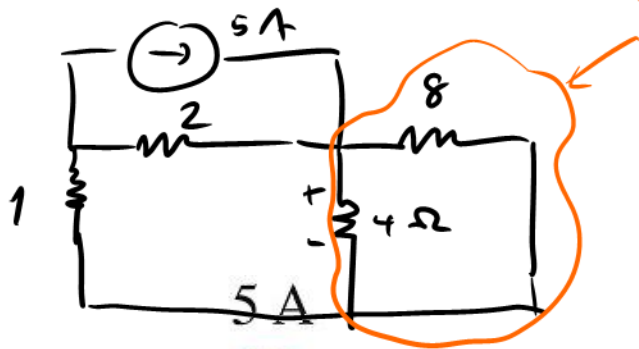


$$8 \parallel 4 = \frac{8}{3} \Omega$$

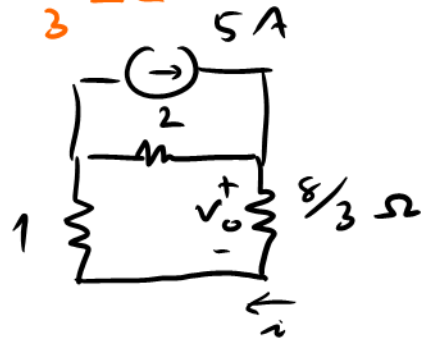


$$i = 5 \times \frac{2}{2 + (1 + \frac{8}{3})}$$

$$= \frac{30}{17}$$
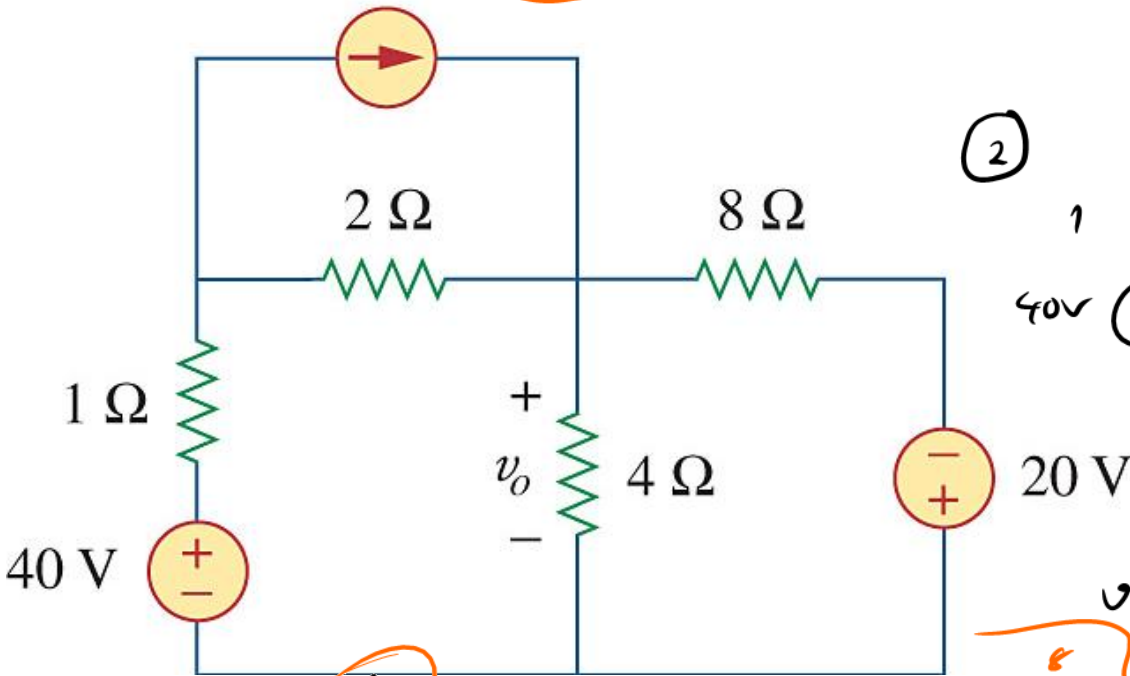
$$v_o = i \times \frac{8}{3} = \frac{80}{17}$$





②

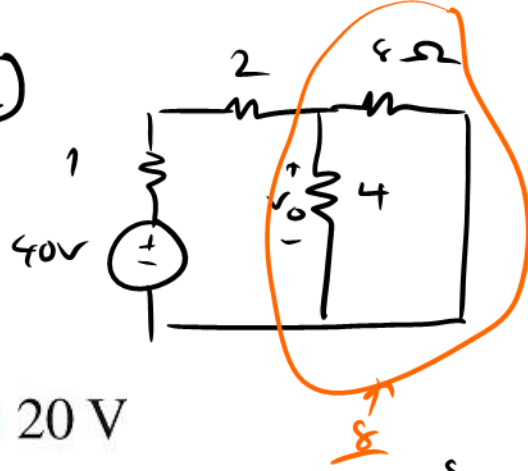

$$v_o = 40 \times \frac{\frac{8}{3}}{1 + 2 + \frac{8}{3}} = \frac{40 \times 8}{9 + 8} = \frac{320}{17}$$


③

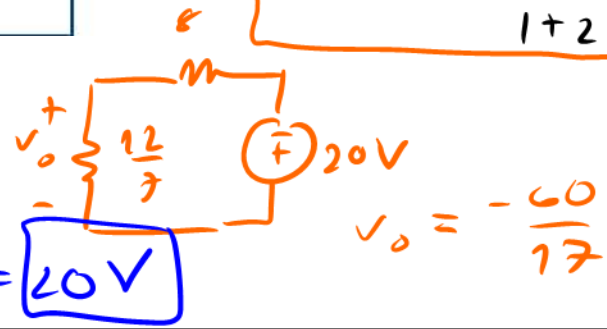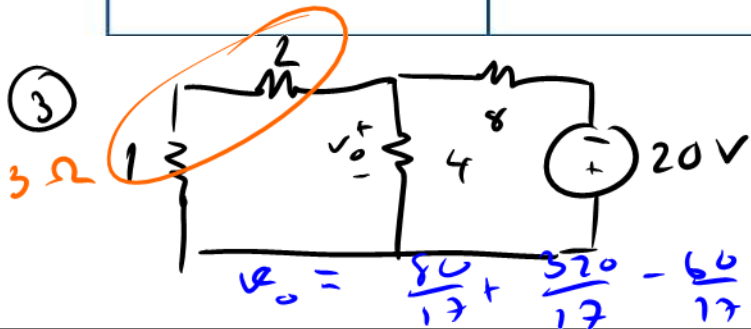

$$v_o = \frac{80}{17} + \frac{320}{17} - \frac{60}{17} = \boxed{20V}$$

$$v_o = -\frac{60}{17}$$

Source Transformation

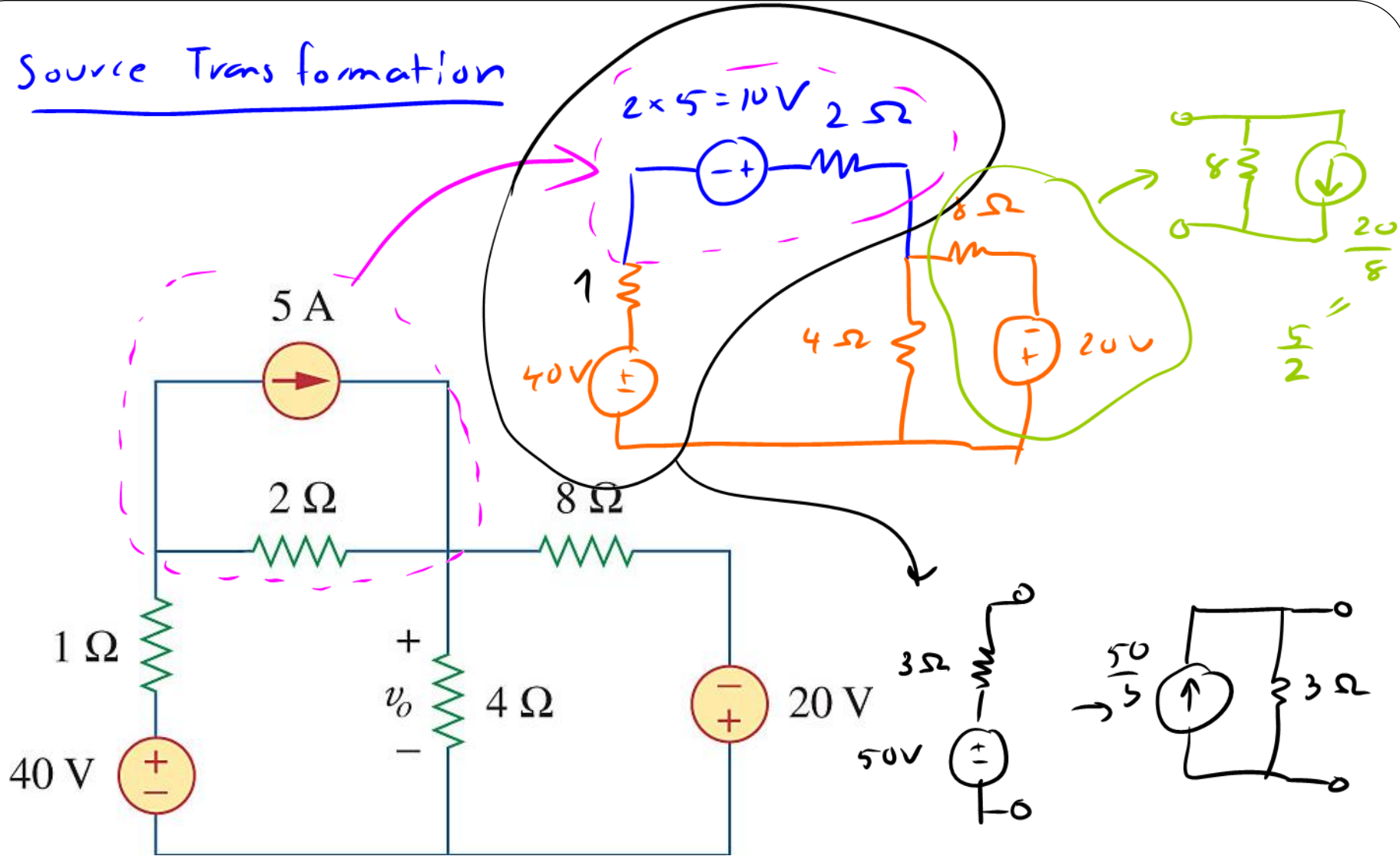

$$\frac{85}{6} = \frac{50}{5} - \frac{5}{2}$$

$$V_o = \frac{85}{6} \times \frac{24}{17} = 20V$$