

ECS 303 - Part 1B

Dr.Prapun Sukksompong

CHAPTER 3

Methods of Analysis

Here we apply the fundamental laws of circuit theory (Ohm's Law & Kirchhoff's Laws) to develop two powerful techniques for circuit analysis.

1. Nodal Analysis (based on KCL)
2. Mesh Analysis (based on KVL)

This is the *most important* chapter for our course.

3.1. Nodal Analysis


Analyzing circuit using **node voltages** as the circuit variables.

Steps to Determine Node Voltages:

Step 0: Determine the number of nodes n .

Step 1: Select a node as a reference node (ground node). Assign voltages v_1, v_2, \dots, v_{n-1} to the remaining $n - 1$ nodes. The voltage are referenced with respect to the reference node.

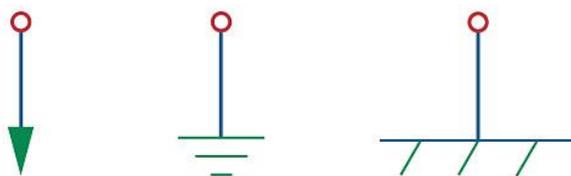- The ground node is assumed to have 0 potential.



Step 2: Apply KCL to each of the $n - 1$ nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.


Step 3: Solve the resulting *simultaneous equations* to obtain the unknown node voltages.

Remark:

- (a) Current flows from a higher potential to a lower potential in a resistor.
- (b) If a voltage source is connected between the reference node and a nonreference node, we simply set the voltage at the nonreference node equal to the voltage of the voltage source.
- (c) Multiple methods to solve the simultaneous equations in Step 3.

- Method 1: Elimination technique (good for a few variables)
- Method 2: Write in term of matrix and vectors (write $Ax = b$), then use Cramer's rule.
- Method 3: Use computer (e.g., Matlab) to find A^{-1} and $x = A^{-1}b$

Ex.

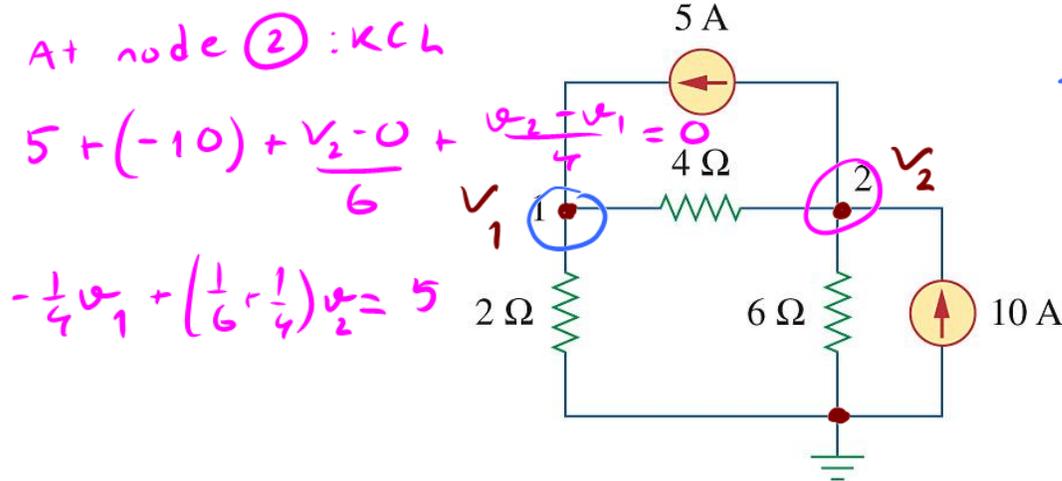


At node ①: KCL \rightarrow

$$-5 + \frac{V_1}{2} + \frac{V_1 - V_2}{4} = 0$$

$$\left(\frac{1}{2} + \frac{1}{4}\right)V_1 - \frac{1}{4}V_2 = 5$$

$$V_1 = \frac{40}{3}, V_2 = 20.$$

Ex.

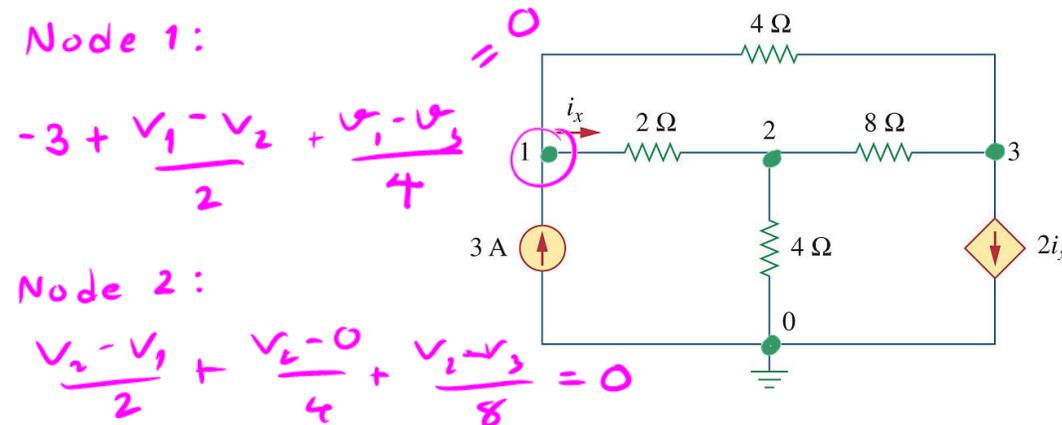

$$i_x = \frac{V_1 - V_2}{2}$$

Node 3:

$$\frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{8} + 2i_x = 0$$

$$V_1 - V_2$$

Special Case: If there is a voltage source connected between two non-reference nodes, the two nonreference nodes form a **supernode**. We apply both KCL and KVL to determine the node voltages.

$$V_1 = 4.8 \text{ V}$$

$$V_2 = 2.4 \text{ V}$$


$$V_3 = -2.4 \text{ V}$$

$$\text{KCL : } \frac{V_A - 21}{4} + \frac{V_A}{3} + \frac{V_B}{2} + \frac{V_B}{6} = 0$$

at supernode

$$V_B - V_A = 9$$

Ex.

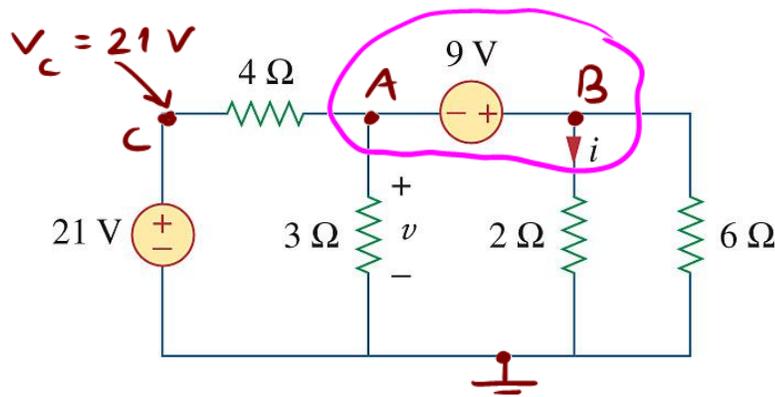

$$V_A = -0.6 \text{ V}$$

$$V_B = 8.4 \text{ V}$$

Remarks: Note the following properties of a supernode:

- (a) The voltage source inside the supernode provides a constraint equation needed to solve for the node voltages.
- (b) A supernode has no voltage of its own.
- (c) We can have more than two nodes forming a single supernode.
- (d) The supernodes are treated differently because nodal analysis requires knowing the current through each element. However, there is no way of knowing the current through a voltage source in advance.

3.2. Mesh Analysis

Mesh analysis provides another general procedure for analyzing circuits, using **mesh currents** as the circuit variables.

Mesh is a **loop which does not contain any other loop within it.**

Steps to Determine Mesh Currents:

Step 0: Determine the number of meshes n .

Step 1: Assign mesh current i_1, i_2, \dots, i_n , to the n meshes.

- The direction of the mesh current is arbitrary—(clockwise or counterclockwise)—and does not affect the validity of the solution.
- For convenience, we define currents flow in the clockwise (CW) direction.

Step 2: From the current direction in each mesh, define the voltage drop polarities.

Step 3: Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh current.

Step 4: Solve the resulting n simultaneous equations to get the mesh current.

Ex.

Use Nodal Analysis

Node D:

$$\frac{v_D - v_C}{6} + \frac{v_D - 0}{4} = 0$$

$$\left(\frac{1}{6} + \frac{1}{4}\right)v_D = \frac{v_C}{6}$$

$$\left(\frac{4+6}{4 \times 6}\right)v_D = \frac{v_C}{6}$$

$$v_D = v_C \times \frac{4}{10} = \frac{2}{5}v_C$$

Node C:

$$\frac{v_C - 15}{5} + \frac{v_C - 10}{10} + \frac{v_C - v_D}{6} = 0$$

$$\frac{7}{15} \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{6}\right)v_C - \frac{1}{6}v_D = 4$$

Use mesh analysis

Loop 1:

$$+15 - 5i_1 - 10 = 0$$

$$- (i_1 - i_2) 10$$

$$5 = 15i_1 - 10i_2$$

$$3i_1 - 2i_2 = 1$$

Loop 2:

$$+10 - (i_2 - i_1) \times 10 - i_2 \times 6 = 0$$

$$-i_2 \times 4$$

$$10 - 20i_2 + 10i_1 = 0$$

$$i_1 - 2i_2 = -1$$

Final solution:

$$\frac{7}{15}v_C - \frac{1}{6} \times \frac{2}{5}v_C = 4$$

$$\frac{6}{15}v_C = 4$$

$$v_C = \frac{4 \times 15}{6} = 10$$

$$v_D = \frac{2}{5} \times 10 = 4$$

Remarks:

- (a) Nodal analysis applies KCL to find unknown voltages in a given circuit, while mesh analysis applies KVL to find unknown currents.
- (b) Using mesh currents instead of element currents as circuit variables is convenient and reduces the number of equations that must be solved simultaneously.
- (c) Mesh analysis is not quite as general as nodal analysis because it is only applicable to a circuit that is *planar*.
 - A planar circuit is one that can be drawn in a plane with no branches crossing one another; otherwise it is nonplanar.

3.3. Nodal Versus Mesh Analysis

You should be familiar with both methods. However, given a network to be analyzed, how do we know which method is better or more efficient?

Suggestion: Choose the method that results in smaller number of variables or equations.

- A circuit with fewer nodes than meshes is better analyzed using nodal analysis, while a circuit with fewer meshes than nodes is better analyzed using mesh analysis.

You can also use one method to check your results of the other method.