

# ECS 303 - Part 1B

## Dr.Prapun Sukksompong

### CHAPTER 3

#### Methods of Analysis

Here we apply the fundamental laws of circuit theory (Ohm's Law & Kirchhoff's Laws) to develop two powerful techniques for circuit analysis.

1. Nodal Analysis (based on KCL)
2. Mesh Analysis (based on KVL)

This is the *most important* chapter for our course.

#### 3.1. Nodal Analysis


Analyzing circuit using **node voltages** as the circuit variables.

##### Steps to Determine Node Voltages:

**Step 0:** Determine the number of nodes  $n$ .

**Step 1:** Select a node as a reference node (ground node). Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n - 1$  nodes. The voltage are referenced with respect to the reference node.

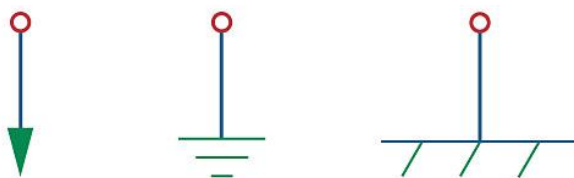- The ground node is assumed to have 0 potential.



**Step 2:** Apply KCL to each of the  $n - 1$  nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.


**Step 3:** Solve the resulting *simultaneous equations* to obtain the unknown node voltages.

Remark:

- (a) Current flows from a higher potential to a lower potential in a resistor.
- (b) If a voltage source is connected between the reference node and a nonreference node, we simply set the voltage at the nonreference node equal to the voltage of the voltage source.
- (c) Multiple methods to solve the simultaneous equations in Step 3.

- Method 1: Elimination technique (good for a few variables)
- Method 2: Write in term of matrix and vectors (write  $Ax = b$ ), then use Cramer's rule.
- Method 3: Use computer (e.g., Matlab) to find  $A^{-1}$  and  $x = A^{-1}b$

Ex.

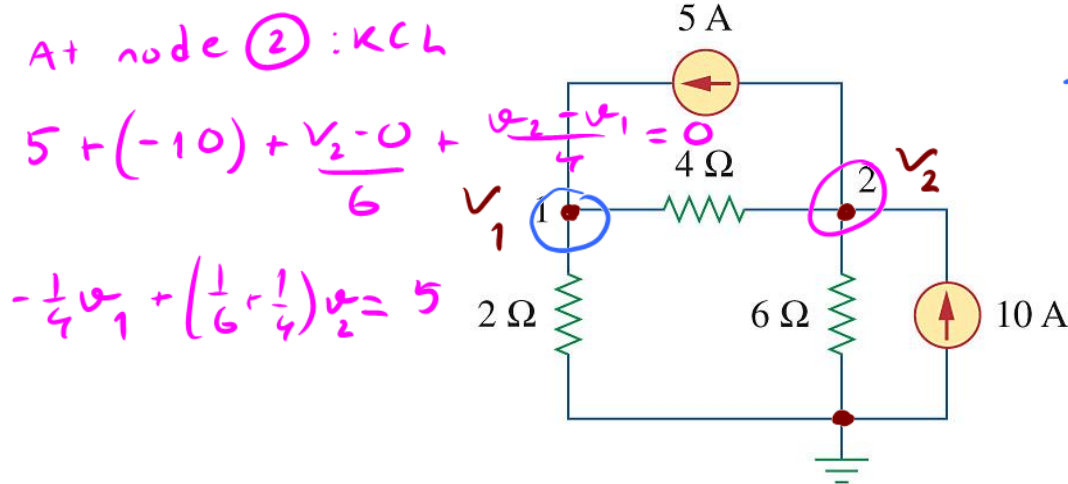


At node ①: KCL  $\rightarrow$

$$-5 + \frac{V_1}{2} + \frac{V_1 - V_2}{4} = 0$$

$$\left(\frac{1}{2} + \frac{1}{4}\right)V_1 - \frac{1}{4}V_2 = 5$$

$$V_1 = \frac{40}{3}, V_2 = 20.$$

Ex.

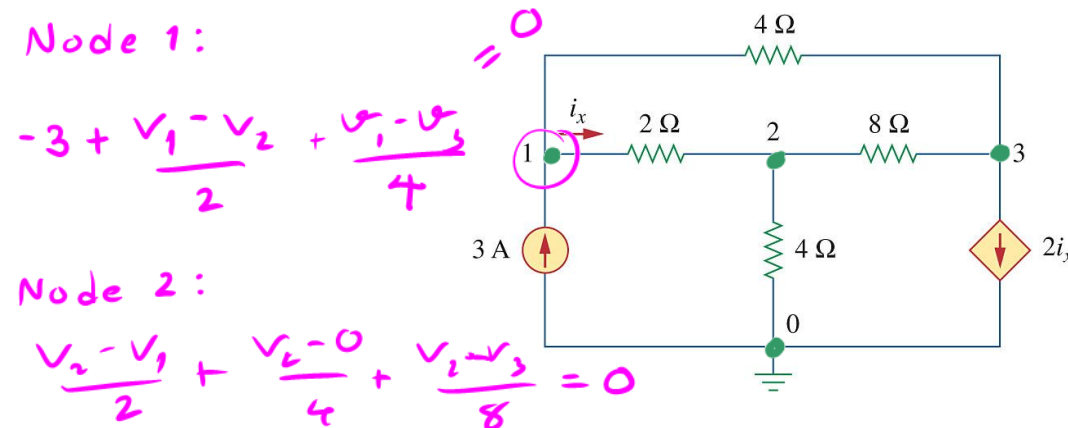

$$i_x = \frac{V_1 - V_2}{2}$$

Node 3:

$$\frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{8} + 2i_x = 0$$

$$V_1 - V_2$$

**Special Case:** If there is a voltage source connected between two non-reference nodes, the two nonreference nodes form a **supernode**. We apply both KCL and KVL to determine the node voltages.

$$V_1 = 4.8 \text{ V}$$

$$V_2 = 2.4 \text{ V}$$


$$V_3 = -2.4 \text{ V}$$

$$\text{KCL : } \frac{V_A - 21}{4} + \frac{V_A}{3} + \frac{V_B}{2} + \frac{V_B}{6} = 0$$

at supernode

$$V_B - V_A = 9$$

Ex.

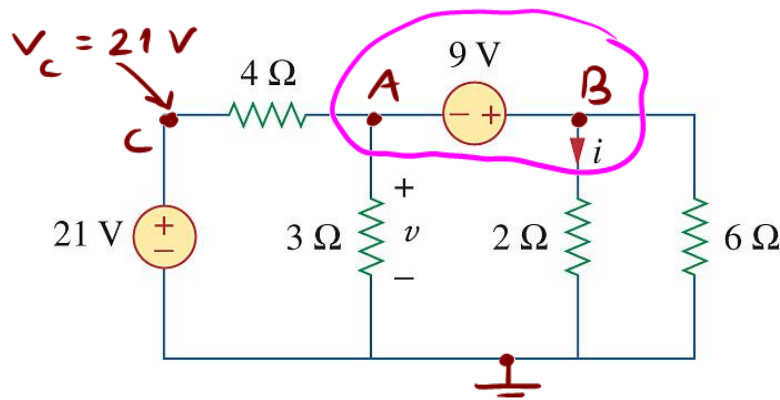

$$V_A = -0.6 \text{ V}$$

$$V_B = 8.4 \text{ V}$$

**Remarks:** Note the following properties of a supernode:

- (a) The voltage source inside the supernode provides a constraint equation needed to solve for the node voltages.
- (b) A supernode has no voltage of its own.
- (c) We can have more than two nodes forming a single supernode.
- (d) The supernodes are treated differently because nodal analysis requires knowing the current through each element. However, there is no way of knowing the current through a voltage source in advance.

### 3.2. Mesh Analysis

Mesh analysis provides another general procedure for analyzing circuits, using **mesh currents** as the circuit variables.

**Mesh** is a loop which does not contain any other loop within it.

#### Steps to Determine Mesh Currents:

**Step 0:** Determine the number of meshes  $n$ .

**Step 1:** Assign mesh current  $i_1, i_2, \dots, i_n$ , to the  $n$  meshes.


- The direction of the mesh current is arbitrary—(clockwise or counterclockwise)—and does not affect the validity of the solution.
- For convenience, we define currents flow in the clockwise (CW) direction.

**Step 2:** From the current direction in each mesh, define the voltage drop polarities.

**Step 3:** Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh current.

**Step 4:** Solve the resulting  $n$  simultaneous equations to get the mesh current.

**Ex.**

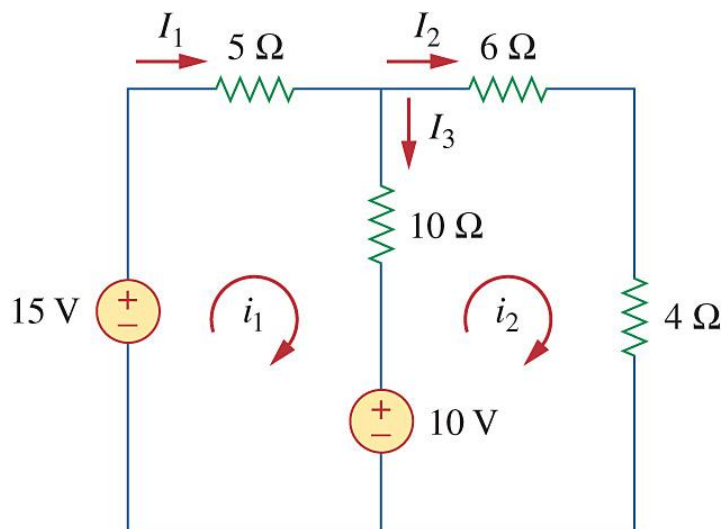

**Remarks:**

- (a) Nodal analysis applies KCL to find unknown voltages in a given circuit, while mesh analysis applies KVL to find unknown currents.
- (b) Using mesh currents instead of element currents as circuit variables is convenient and reduces the number of equations that must be solved simultaneously.
- (c) Mesh analysis is not quite as general as nodal analysis because it is only applicable to a circuit that is *planar*.
  - A planar circuit is one that can be drawn in a plane with no branches crossing one another; otherwise it is nonplanar.

**3.3. Nodal Versus Mesh Analysis**

You should be familiar with both methods. However, given a network to be analyzed, how do we know which method is better or more efficient?

Suggestion: Choose the method that results in smaller number of variables or equations.

- A circuit with fewer nodes than meshes is better analyzed using nodal analysis, while a circuit with fewer meshes than nodes is better analyzed using mesh analysis.

You can also use one method to check your results of the other method.