

1.1 The charge of an electron is -1.602×10^{-19} C.

(d) The charge of 1.628×10^{20} electrons is


$$1.628 \times 10^{20} [\text{electrons}] \times -1.602 \times 10^{-19} \left[\frac{\text{C}}{\text{electron}} \right]$$

$$= 1.628 \times (-1.602) \times 10$$


$$= \boxed{-26.08 \text{ C}}$$

1.18 We calculate the power using the passive sign convention.


$p = iv$

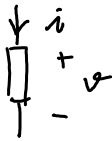

$p = -iv$

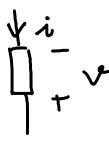

(a)

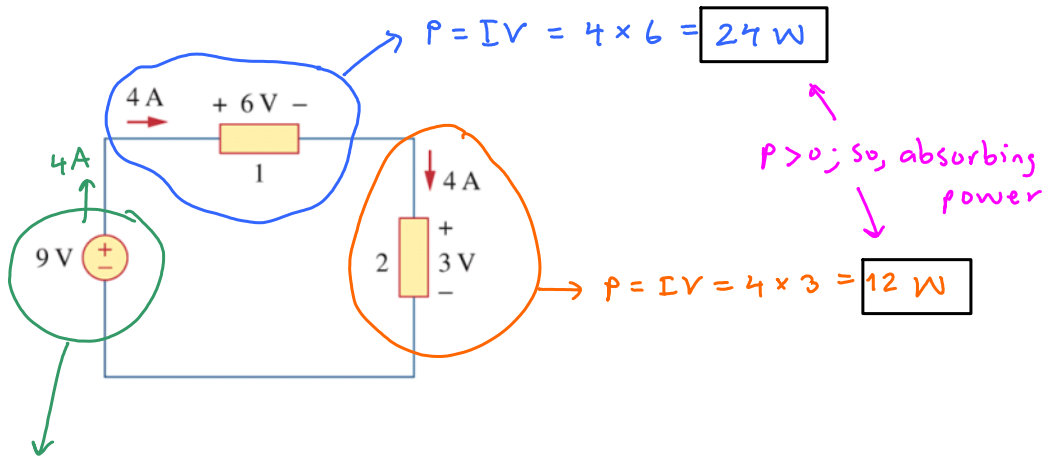

Again, the negative sign is here because the current flows from the negative to the positive polarity of the 9V.

1.22

$$i = \frac{dq}{dt} \quad \text{and} \quad q = \int i \, dt$$

In this case, $i(t) = 30 \text{ kA}$ during the time 0 to 2ms

If you start at time $T \neq 0$, then the endpoint will


the endpoint will
be $T + 2\text{ms}$,
I choose 0 because
it is easier.

$$So, q_f = \int_0^{2\text{ms}} (30\text{ kA}) dt = (30\text{ kA}) \times (2\text{ms} - 0)$$

$\underbrace{\hspace{2cm}}_{\text{constant}}$

$$= 30\text{ kA} \times 2\text{ms} = \boxed{60\text{ C}} \text{ are deposited on the plane.}$$

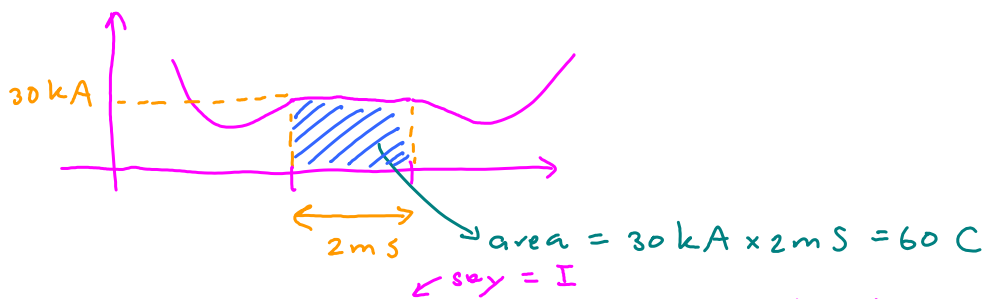Another way to see this answer is to find the area under the curve of $i(t)$




Tips: when $i(t)$ is constant (as in this question) we can calculate the amount of charge by

$$I \times \underbrace{\Delta t}_{\text{Time duration}}$$

HW1, Chapter 2

Friday, November 13, 2009
10:18 AM

2.7

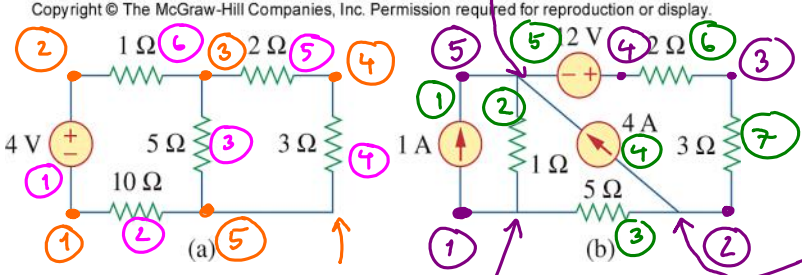

* branches = 6
* nodes = 5

* branches = 7
* nodes = 5


same as node 5

same as node 2

same as node 1

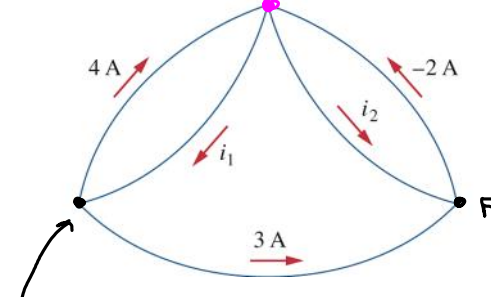2.10

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Applying KCL at this node, we have

$$4 + (-i_1) + 3 = 0$$

$$i_1 = 7 A$$

Applying KCL at this node, we have

$$-2 - i_2 - 3 = 0$$

$$i_2 = -5 A$$


We may check the answers by applying KCL at the top node:

$$-4 + i_1 + i_2 - (-2) = 0$$

$$-4 + 7 - 5 + 2 = 0 \quad \checkmark$$

use i_1, i_2 that we know.

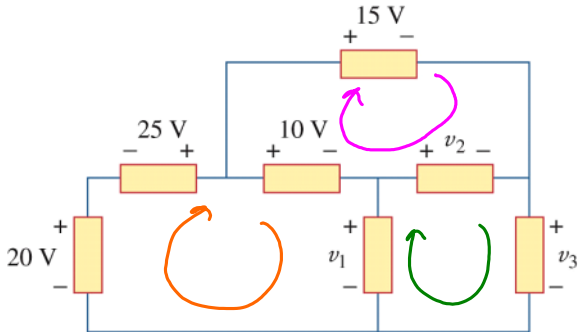2.12 We will try to pick small loop with few unknown variable



This loop gives
 $-20 - 25 + 10 + v_1 = 0$

$$v_1 = 45 - 10$$

$$v_1 = 35 \text{ V.}$$

This loop gives
 $-10 + 15 - v_2 = 0$

$$v_2 = 5 \text{ V}$$

This loop says
 $-v_1 + v_2 + v_3 = 0$


$$v_3 = v_1 - v_2$$

$$= 35 - 5$$

$$v_3 = 30 \text{ V}$$

Note: You may choose to work with different loops. The answers will be the same.

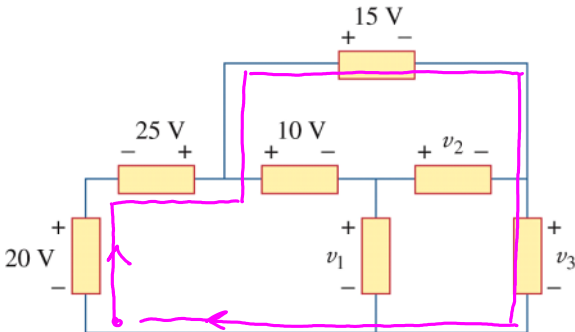For example, I may choose the largest loop below:



In which case, the KVL gives


$$-20 - 25 + 15 + v_3 = 0$$

$$v_3 = 45 - 15$$

$$= 30$$

which is the same as what we got from a different loop earlier.

2.17

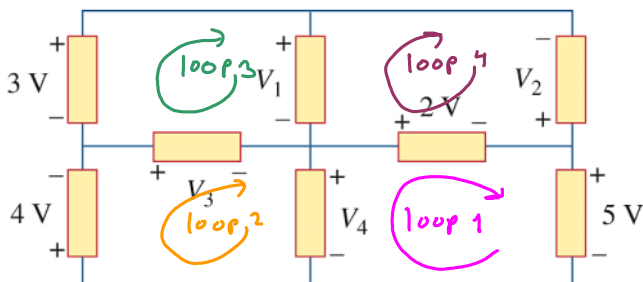

We will try to work with loop that has as few unknown variables as possible.

So, we start with "loop 1":

$$-V_4 + 2\text{V} + 5\text{V} = 0$$

$$V_4 = 7\text{V}$$

Because we already know V_4 , "loop 2" now has only one unknown variable (V_3):

$$2\text{V}$$

unknown variable (V_3):

$$4 + V_3 + V_4 = 0$$

$$V_3 = -4 - V_4 = -11 \text{ V}$$

Similarly, when we know V_3 , "loop 3" has only one unknown variable (V_1):

$$-3 + V_1 - V_3 = 0$$

$$-3 + V_1 + 11 = 0$$

$$V_1 = -8 \text{ V}$$

Finally, from "loop 4":

$$-V_1 - V_2 - 2 = 0$$

$$8 - V_2 - 2 = 0$$

$$V_2 = 6 \text{ V}$$

$$V_1 = -8 \text{ V}$$

$$V_2 = 6 \text{ V}$$

$$V_3 = -11 \text{ V}$$

$$V_4 = 7 \text{ V}$$