

Chapter 1, Solution 1

(a) $q = 6.482 \times 10^{17} \times [-1.602 \times 10^{-19} \text{ C}] = \underline{\underline{-0.10384 \text{ C}}}$

(b) $q = 1.24 \times 10^{18} \times [-1.602 \times 10^{-19} \text{ C}] = \underline{\underline{-0.19865 \text{ C}}}$

(c) $q = 2.46 \times 10^{19} \times [-1.602 \times 10^{-19} \text{ C}] = \underline{\underline{-3.941 \text{ C}}}$

(d) $q = 1.628 \times 10^{20} \times [-1.602 \times 10^{-19} \text{ C}] = \underline{\underline{-26.08 \text{ C}}}$

1.18 Calculate the power absorbed or supplied by each element in Fig. 1.29

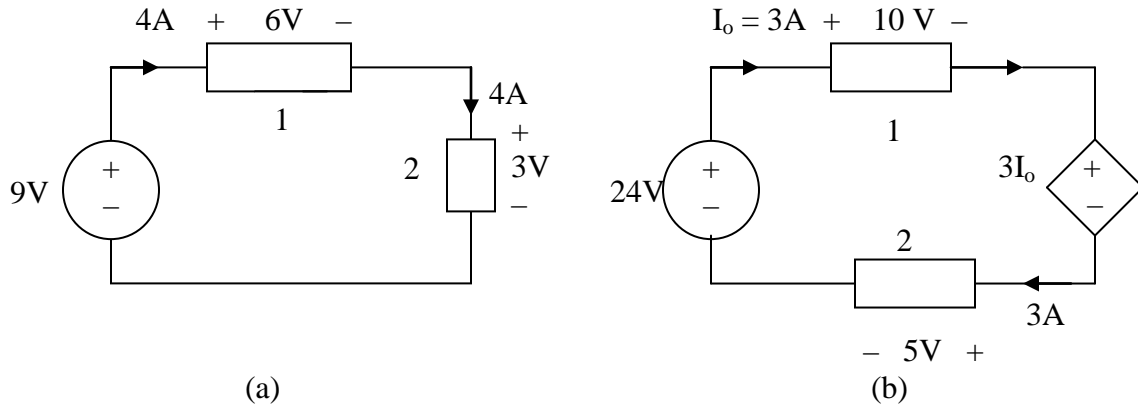


Figure 1.29
For Prob. 1.18

Solution: Note, we will express absorbed power as positive terms and delivered power as negative power absorbed.

- (a) For the 9-V voltage source, $p = -4(9) = -36 \text{ W}$
 For element 1, $p = 4(6) = 24 \text{ W}$
 For element 2, $p = 4(3) = 12 \text{ W}$

- (b) For the 24-V voltage source, $p = 24(-3) = -72 \text{ W}$
 For the current-controlled voltage source, $p = 3 I_o(3) = 27 \text{ W} = 27 \text{ W}$
 For element 1, $p = 10(3) = 30 \text{ W}$
 For element 2, $p = 3(5) = 15 \text{ W}$

Chapter 1, Solution 22

$$q = it = 30 \times 10^3 \times 2 \times 10^{-3} = \underline{60 \text{ C}}$$

2.7 Find the number of branches and nodes in each of the circuits of Fig. 2.71.


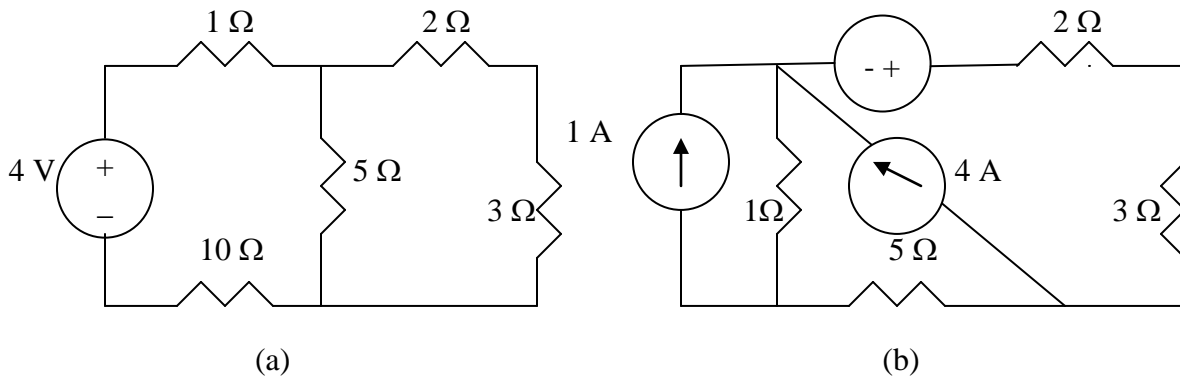


Figure 2.71
For Prob. 2.7


Solution

(a)

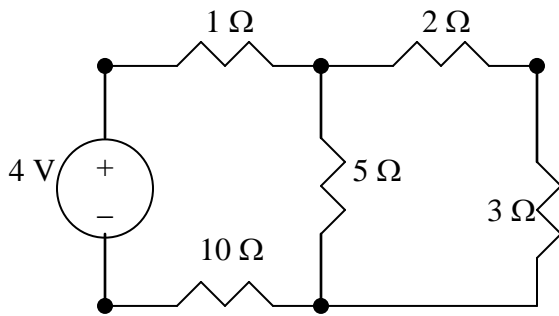


6 branches and 5 nodes.

(b)

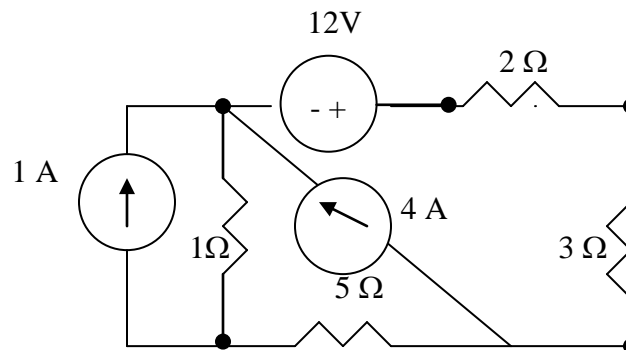


7 branches and 5 nodes.

Chapter 2, Solution 10

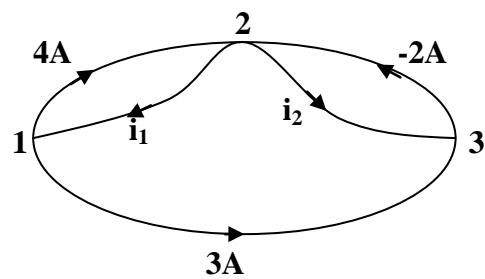

$$\begin{aligned} \text{At node 1,} \quad & 4 + 3 = i_1 \quad \longrightarrow \quad \underline{i_1 = 7A} \\ \text{At node 3,} \quad & 3 + i_2 = -2 \quad \longrightarrow \quad \underline{i_2 = -5A} \end{aligned}$$

Chapter 2, Solution 12

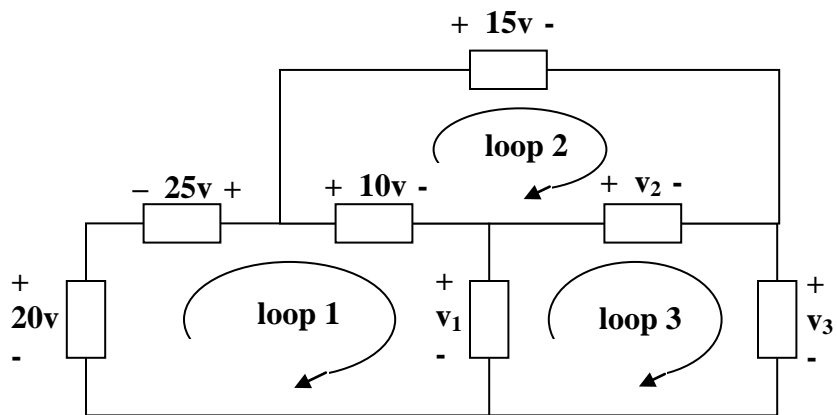


For loop 1, $-20 - 25 + 10 + v_1 = 0 \rightarrow \underline{v_1 = 35\text{V}}$

For loop 2, $-10 + 15 - v_2 = 0 \rightarrow \underline{v_2 = 5\text{V}}$

For loop 3, $-v_1 + v_2 + v_3 = 0 \rightarrow \underline{v_3 = 30\text{V}}$

Chapter 2, Solution 14

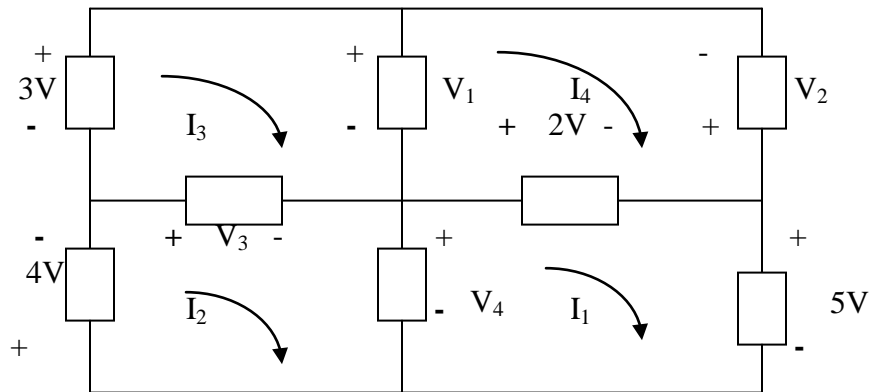

For mesh 1,

$$-V_4 + 2 + 5 = 0 \quad \longrightarrow \quad V_4 = 7V$$

For mesh 2,

$$+4 + V_3 + V_4 = 0 \quad \longrightarrow \quad V_3 = -4 - 7 = -11V$$

For mesh 3,

$$-3 + V_1 - V_3 = 0 \quad \longrightarrow \quad V_1 = V_3 + 3 = -8V$$

For mesh 4,

$$-V_1 - V_2 - 2 = 0 \quad \longrightarrow \quad V_2 = -V_1 - 2 = 6V$$

Thus,

$$\underline{V_1 = -8V, \quad V_2 = 6V, \quad V_3 = -11V, \quad V_4 = 7V}$$