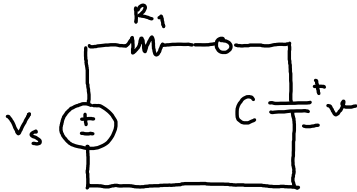


① Depending on the position of the switch (SW), we have two different circuits

(a) SW is at position 1



Note that the source V_s and the resistor R_1 are in the Thevenin equivalent circuit form already.

Therefore, we have

$$\begin{aligned}\tau_1 &= C \times R_{th} = C \times R_1 \\ &= 4 \times 10^{-6} \times 30 \times 10^3 \\ &= 12 \times 10^{-2} = 120 \text{ ms} \\ &= 0.12 \text{ sec}\end{aligned}$$


and

$$v(\infty) = V_s$$

When the circuit is in this setup, the voltage v across the capacitor is given by

$$\begin{aligned}v(t) &= v(\infty) + (v(t_0) - v(\infty)) e^{-(t-t_0)/\tau} \\ &= V_s + (v(t_0) - V_s) e^{-(t-t_0)/R_1 C}\end{aligned}$$

(b) SW is at position 2

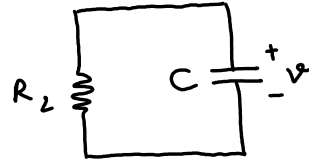

$$\begin{aligned}\text{Here, } \tau_2 &= R_2 \times C \\ &= 10 \times 10^3 \times 4 \times 10^{-6} \\ &= 4 \times 10^{-2} = 40 \text{ ms} \\ &= 0.04 \text{ sec}\end{aligned}$$

and

$$v(\infty) = 0$$

When the circuit is in this setup, the voltage v across the capacitor is given by

$$\begin{aligned}v(t) &= v(\infty) + (v(t_0) - v(\infty)) e^{-(t-t_0)/\tau} \\ &= v(t_0) e^{-(t-t_0)/R_2 C}\end{aligned}$$

Note that SW changes its position every 25 ms. 25 ms is much less than $5 \times \tau$ for both (a) and (b) above. Hence, the voltage will not reach (or even come close) to its long-term (∞) value.

Case 1: $t < t_1 = 0$, SW is at position 1

Because SW has been in position 1 for a long time, we may assume that it has already reached $v(\infty)$ which is V_s from (a) above, that is

$$v(0^-) = V_s = 10 \text{ V}$$

Because there cannot be any voltage jump across

Because there can not be any voltage jump across the capacitor,

$$v(0) = v(0^-) = v_s = 10 \text{ V.}$$

Case 2: $t_1 \leq t < t_2$, sw is at position 2
 \uparrow \downarrow
 0 25 ms

Start time for this case is $t_0 = t_1 = 0$

$$v(t) = v(t_0) e^{-(t-t_0)/R_2 C} = v(0) e^{-t/R_2 C} = 10 e^{-25t}$$

$$v(t_2^-) = 10 e^{-25 \times 10^{-3} / R_2 \times C} = 5.353 \text{ V}$$

Case 3: $t_2 \leq t < t_3$, sw is at position 1

\uparrow

Now this is the new t_0

$$v(t) = v_s + (v(t_2) - v_s) e^{-(t-t_2)/R_1 C}$$

$$= 10 - 4.647 e^{-8.333(t-t_2)}$$

$$v(t_3^-) = 10 - 4.647 e^{-(t_3-t_2)/R_1 C} = 10 - 4.647 e^{-25 \times 10^{-3} / R_1 C}$$

$$= 6.227 \text{ V}$$

Case 4: $t_3 \leq t < t_4$, sw is at position 2

$$v(t) = v(t_3) e^{-(t-t_3)/R_2 C}$$

$$= 6.227 e^{-25(t-t_3)}$$

$$v(t_4^-) = 6.227 e^{-25 \times 10^{-3} / R_2 C} = 3.333 \text{ V}$$

Case 5: $t_4 \leq t < t_5$, sw is at position 1

$$v(t) = v_s + (v(t_4) - v_s) e^{-(t-t_4)/R_1 C}$$

$$= 10 - 6.667 e^{-8.333(t-t_4)}$$

$$v(t_5^-) = 10 - 6.667 e^{-25 \times 10^{-3} / R_1 C}$$

$$= 4.587 \text{ V}$$

Case 6: $t > t_5$, sw is at position 2


$$v(t) = v(t_5) e^{-(t-t_5)/R_2 C} = 4.587 e^{-25(t-t_5)}$$

$$v(\infty) = 0$$

$$v(t) = 10 e^{-25t}$$

$$v(t) = \begin{cases} 10 e^{-8.333(t-25\text{ms})}, & 0 \leq t < 25\text{ms} \\ 10 - 4.647 e^{-8.333(t-25\text{ms})}, & 25\text{ms} \leq t < 50\text{ms} \\ 6.227 e^{-25(t-50\text{ms})}, & 50\text{ms} \leq t < 75\text{ms} \\ 10 - 6.667 e^{-8.333(t-75\text{ms})}, & 75\text{ms} \leq t < 100\text{ms} \\ 4.587 e^{-25(t-100\text{ms})}, & t \geq 100\text{ms} \end{cases}$$

Here is the plot of $v(t)$:

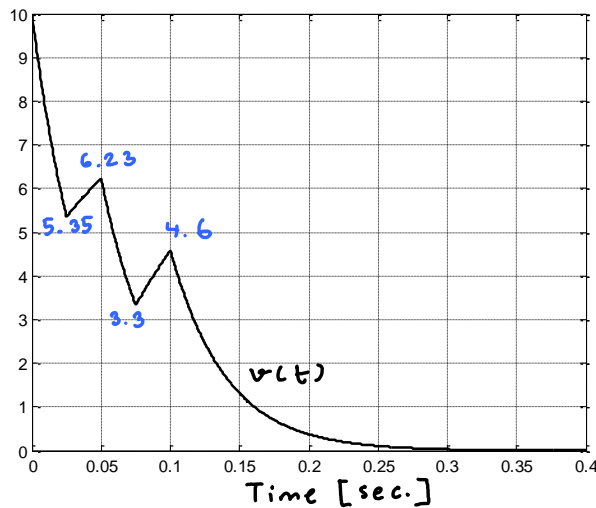

- ②
- 8
 - $500\pi \text{ rad/s} \approx 1571 \text{ rad/s}$
 - $\omega = 2\pi f \Rightarrow f = \omega/2\pi = 500\pi/2\pi = 250 \text{ Hz}$
 - $8 \cos(500\pi \times 2 \times 10^{-3} - 25^\circ) = -7.25$
- ③
- $V = 21 \angle -15^\circ$
 - $I = 8 \angle (70^\circ - 90^\circ + 180^\circ)$
 $= 8 \angle 160^\circ$ (negative sign in the front)
 - $V = 120 \angle (-50^\circ - 90^\circ)$
 $= 120 \angle -140^\circ$ (sin \rightarrow cos)
 - $I = 60 \angle (10^\circ - 180^\circ)$
 $= 60 \angle -170^\circ$ (negative sign)
 - $X = 10 \angle (75^\circ - 180^\circ)$
 $= 10 \angle -105^\circ$ (negative sign)

$$f) X = 5 \angle (-10^\circ - 90^\circ) \quad \leftarrow \sin \rightarrow \cos$$

$$= \boxed{5 \angle -100^\circ}$$

$$g) x(t) = 4 \cos 2t + 3 \sin 2t = 4 \cos 2t + 3 \cos (2t - 90^\circ)$$

$$= 4 \operatorname{Re} \{ e^{j2t} \} + 3 \operatorname{Re} \{ e^{j2t} (-j) \}$$

$$= \operatorname{Re} \{ \underbrace{(4 - 3j)} e^{j2t} \}$$

$$\hookrightarrow 5 \angle -36.87^\circ$$

$$X = \boxed{5 \angle -36.87^\circ}$$


Alternatively, you may perform the addition in phasor form

$$X = 4 \angle 0^\circ + 3 \angle -90^\circ$$

$$= 4 + (-3j) = 4 - 3j$$

$$= 5 \angle -36.87^\circ$$

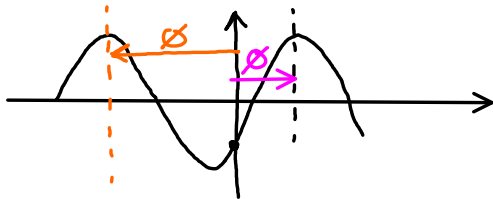- ④ First we observe that the waveform is the same as cosine function shifted to the right by ϕ where ϕ is between 90° and 180°



Shifting to the right means ϕ is negative.
So,

$$-180^\circ < \phi < -90^\circ$$

Equivalently, the graph is also the cosine function shifted to the left by ϕ where

$$180^\circ < \phi < 270^\circ$$

Now,

from the general form of sinusoidal waveform

$$x(t) = A \cos(\omega t + \phi)$$


From the plot, we have $A = 4$.

$$x(0) = 4 \cos(\phi)$$

$$\begin{aligned} & \text{ii} \\ & -3.356 \end{aligned}$$

$$\begin{aligned} \cos \phi &= -\frac{3.356}{4} \\ &\approx -0.839 \end{aligned}$$
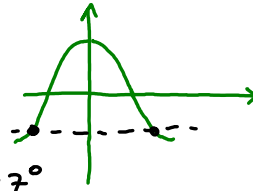
$$\phi = 147^\circ \text{ and } -147^\circ$$



Because ϕ must be between -180° and -90° , we know that $\phi = -147^\circ$.


Equivalently, $\phi = -147^\circ + 360^\circ = 213^\circ$

Therefore,

$$\vec{x} = 4 \angle -147^\circ$$

Note that $\phi = 147^\circ$ will give different graph.

Try it! You will get ↴

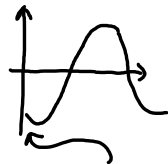

which start at the wrong position.