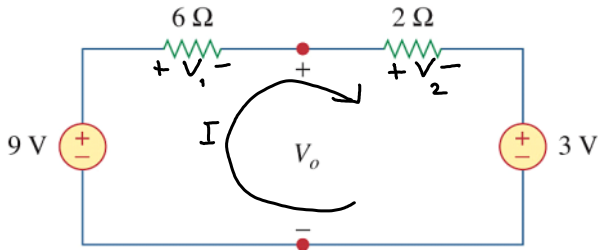


HW2, Chapter 2

Sunday, November 15, 2009
1:21 PM

2.16

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



KCL says that we can use one current I throughout the whole loop.

By KVL,

$$-9 + V_1 + V_2 + 3 = 0$$

By Ohm's law,

$$V_1 = I \times 6$$

$$V_2 = I \times 2$$


Therefore, $-9 + I \times 6 + I \times 2 + 3 = 0$

$$I = \frac{6}{8}$$

Now, we will use KVL on another "loop" shown below

In which case, we have

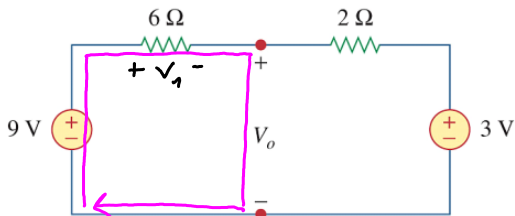Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$-9 + V_1 + V_0 = 0$$


$$V_0 = 9 - V_1$$

$$= 9 - \frac{6}{8} \times 6$$


$$= \frac{9}{2} = \boxed{4.5 \text{ V}}$$

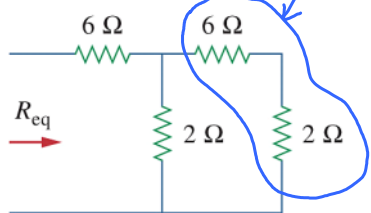2.30

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Series: $6 + 2 = 8 \Omega$

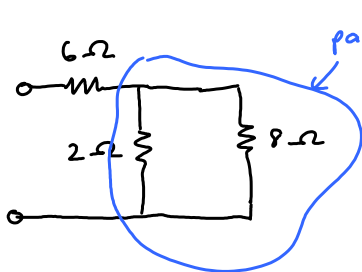

parallel: $\frac{8 \times 2}{8 + 2} = 1.6 \Omega$

$$\frac{1}{\frac{1}{8} + \frac{1}{2}}$$

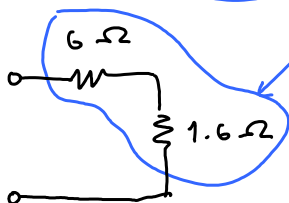


Series: $6 + 1.6 = 7.6 \Omega$

$$R_{eq} = 7.6 \Omega$$

(CDF)

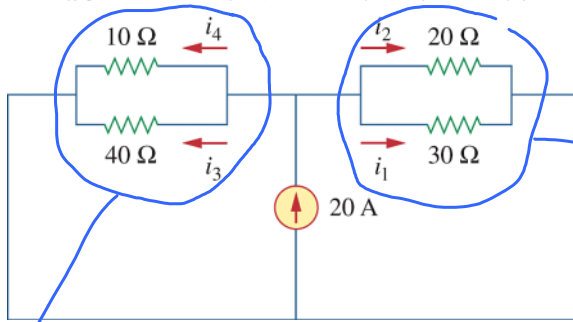
2.32 We will use the current divider formula.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



parallel: $\frac{20 \times 30}{20 + 30}$
 $= \frac{600}{50}$
 $= 12 \Omega$

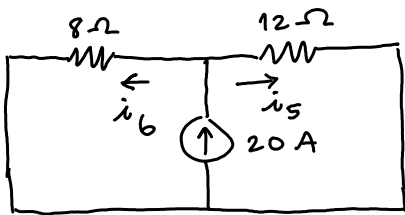parallel: $\frac{10 \times 40}{10 + 40} = \frac{400}{50} = 8 \Omega$



So, 20A is split into the 8Ω and 12Ω resistors.

By CDF,


$$i_5 = \frac{\frac{1}{12}}{\frac{1}{12} + \frac{1}{8}} \times 20 = \frac{1}{12} \times \frac{12 \times 8}{12 + 8} \times 20 = 8A.$$

$i_6 = 20A - 8A = 12A.$ ← We can apply CDF to get i_6 .

However, it is easier to use KCL:

$$i_6 + i_5 - 20 = 0.$$

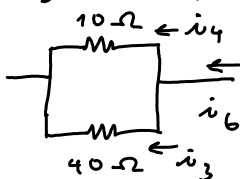The current i_6 is split again into i_3 and i_4 .




By CDF,

$$i_3 = \frac{\frac{1}{40}}{\frac{1}{10} + \frac{1}{40}} \times 12 = \frac{1}{40} \times \frac{1 \times 1}{4 + 1} \times 12 = \frac{12}{5} = \frac{24}{10} = 2.4A.$$

$$i_4 = i_6 - i_3 = 12 - 2.4 = 9.6A$$

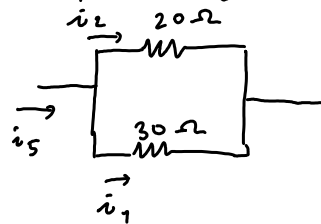The current i_5 is split again into i_1 and i_2 .




By CDF,

$$i_1 = \frac{\frac{1}{30}}{\frac{1}{20} + \frac{1}{30}} \times 8 = \frac{1}{30} \times \frac{20 \times 30}{20 + 30} \times 8 = \frac{16}{5} = \frac{32}{10} = 3.2A$$

$$i_2 = i_5 - i_1 = 8 - 3.2 = 4.8A$$

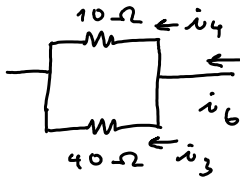The current i_6 is split again into i_3 and i_4 .



By CDF,

$$i_3 = \frac{1}{\frac{1}{10} + \frac{1}{40}} \times 12 = \frac{1}{\cancel{4} \times \frac{1}{4+1}} \times 12$$

$$= \frac{12}{5} = \frac{24}{10} = 2.4 \text{ A.}$$

$$i_4 = i_6 - i_3 = 12 - 2.4 = 9.6 \text{ A}$$


KCL

So,

$i_1 = 3.2 \text{ A}$
$i_2 = 4.8 \text{ A}$
$i_3 = 2.4 \text{ A}$
$i_4 = 9.6 \text{ A}$

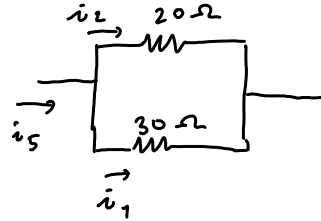(2.34)

The current i_5 is split again into i_1 and i_2 .




By CDF,

$$i_1 = \frac{1}{\frac{1}{30} + \frac{1}{20}} \times 8 = \frac{1}{\cancel{30} \times \frac{20+30}{20 \times 30}} \times 8$$

$$= \frac{16}{5} = \frac{32}{10} = 3.2 \text{ A}$$

$$i_2 = i_5 - i_1 = 8 - 3.2 = 4.8 \text{ A}$$


KCL

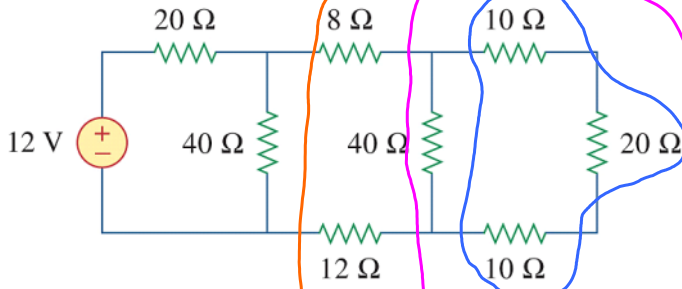

Series:
 $10 + 10 + 20 = 40 \Omega$


Parallel
 $40 // 40 = \frac{40 \times 40}{40 + 40} = \frac{40}{2} = 20 \Omega$

Series:
 $8 + 20 + 12 = 40 \Omega$

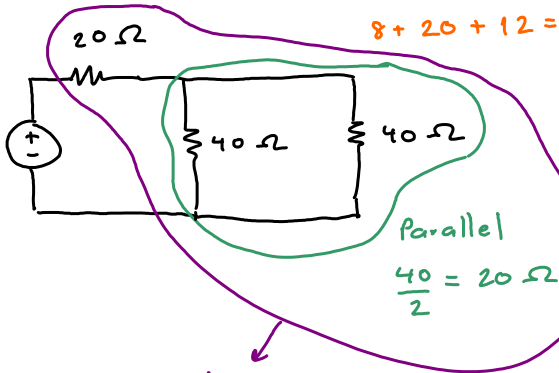

Parallel
 $\frac{40}{2} = 20 \Omega$


Series:
 $20 + 20 = 40 \Omega$

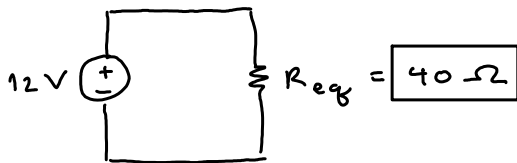


Over all dissipated power = $I V = \frac{V}{R_{eq}} \times V = \frac{V^2}{R_{eq}}$
 $= \frac{12^2}{40} = \frac{12 \times 12}{40} = \frac{144}{40} = 3.6 \text{ W}$

The power of each resistor has positive sign.
 We calculate the total power indirectly from the power of the source.

2.40


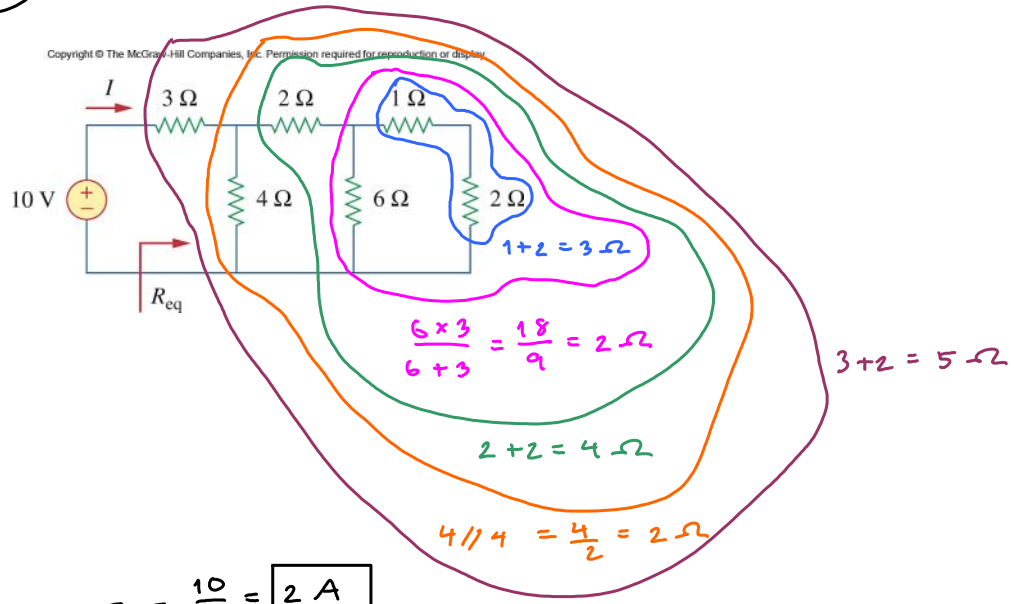


$$I = \frac{10}{5} = 2 \text{ A}$$

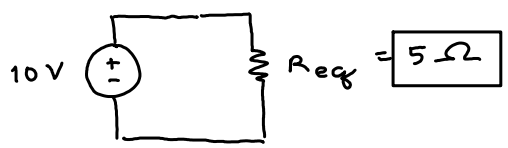

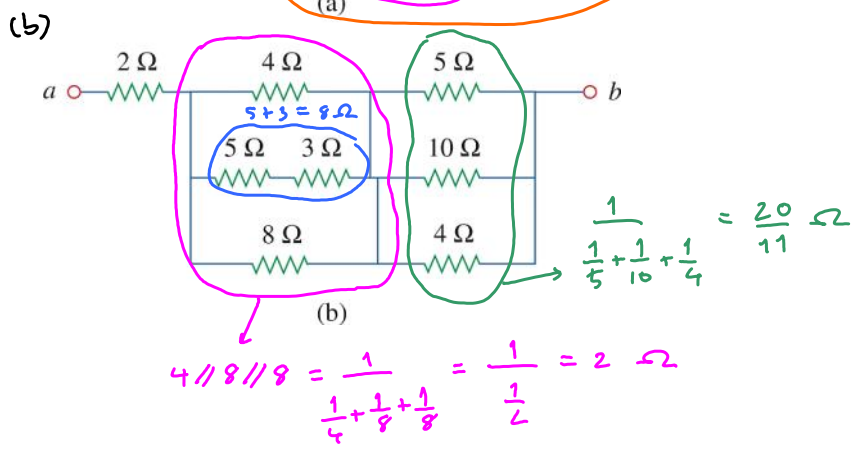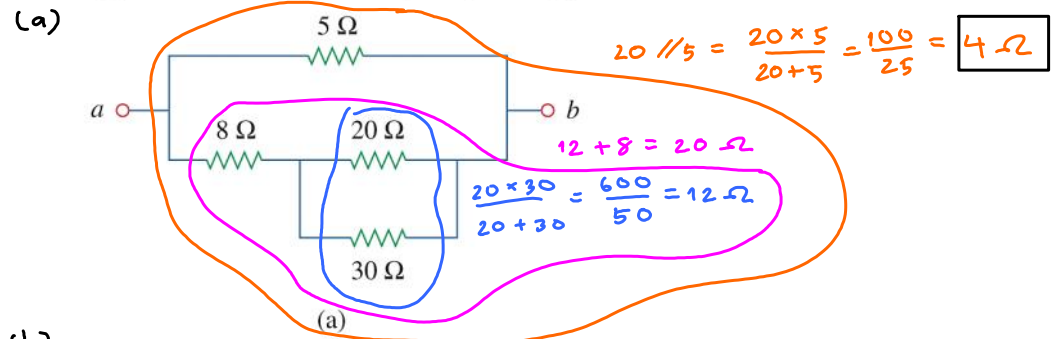2.42

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$R_{eq} = 2 \Omega + 2 \Omega + \frac{20}{11} \Omega = \frac{64}{11} \Omega \approx 5.818 \Omega$$

HW2, Chapter 3

Sunday, November 15, 2009
1:21 PM

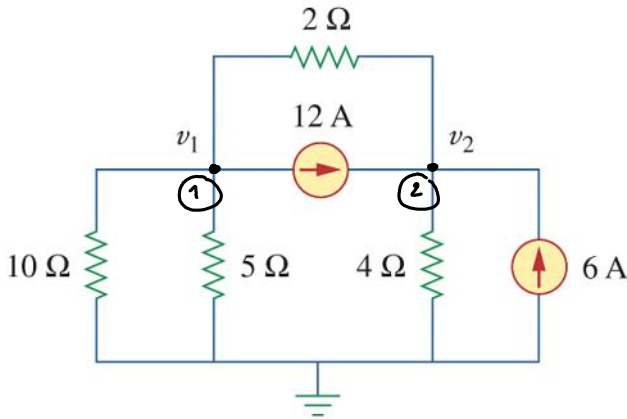3.2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



KCL at ①

$$\frac{v_1 - 0}{10} + \frac{v_1 - 0}{5} + \frac{v_1 - v_2}{2} + 12 = 0$$

KCL at ②

$$-12 + \frac{v_2 - v_1}{2} + \frac{v_2}{4} - 6 = 0$$


Mathcad

$$\begin{aligned} v_1 &= 0 \\ v_2 &= 24 \text{ V} \end{aligned}$$

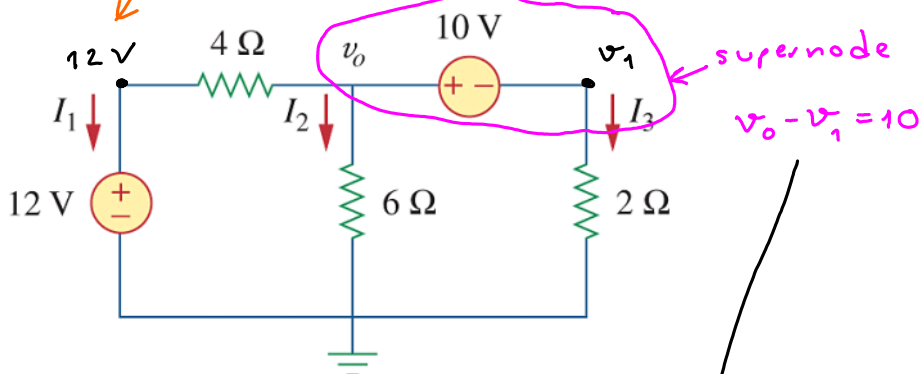3.6

we get the voltage at this non-reference node immediately because a voltage source is between this node and the ground.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




KCL at supernode:

$$\frac{v_0 - 12}{4} + \frac{v_0 - 0}{6} + \frac{v_1}{2} = 0$$

Mathcad

$$\begin{aligned} v_0 &\approx 8.727 \\ v_1 &\approx -1.273 \end{aligned}$$

3.14

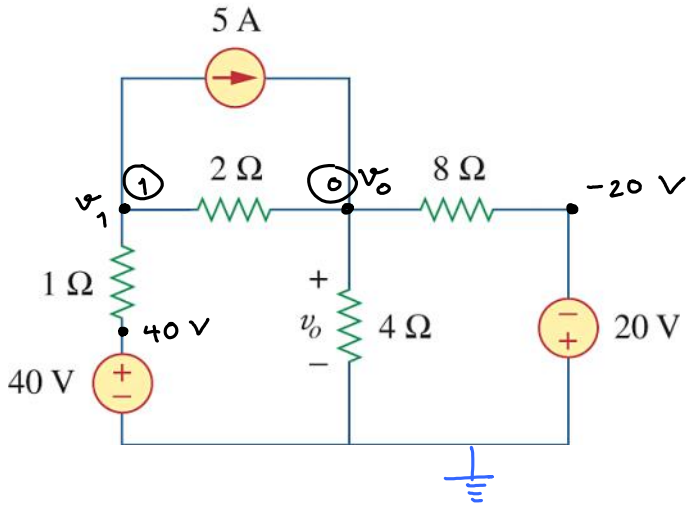

KCL at node ①

$$\frac{v_1 - 40}{1} + \frac{v_1 - v_0}{2} + 5 = 0$$

KCL at node ②


$$\frac{v_0 - v_1}{2} - 5 + \frac{v_0 - 0}{4} + \frac{v_0 - (-20)}{8} = 0$$

Mathcad

$$\Rightarrow \boxed{v_0 = 20 \text{ V}}$$

$$v_1 = 30 \text{ V}$$

3.18

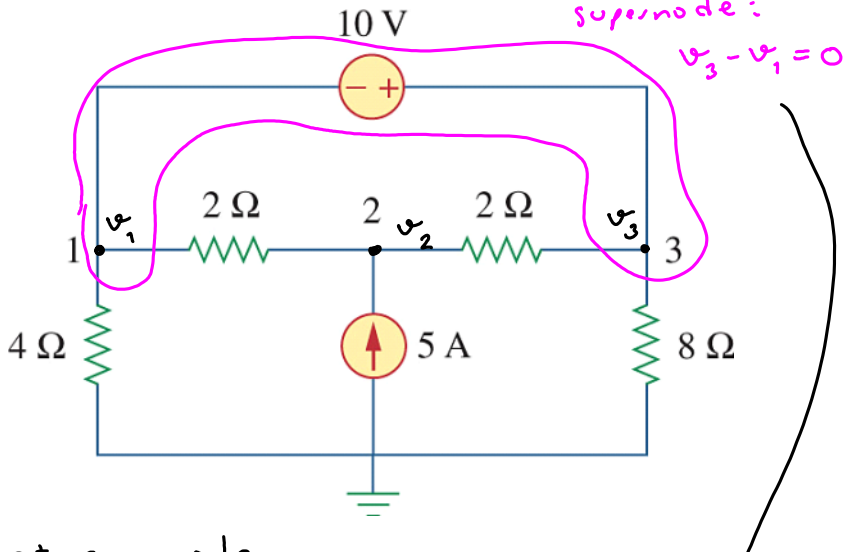

KCL at supernode

$$\frac{v_1 - 0}{4} + \frac{v_1 - v_2}{2} + \frac{v_3 - v_2}{2} + \frac{v_3 - 0}{8} = 0$$

KCL at node ②

$$\frac{v_2 - v_1}{2} - 5 + \frac{v_2 - v_3}{2} = 0$$

Mathcad
⇒

$v_1 = 10 \text{ V}$
$v_2 = v_3 = 20 \text{ V}$