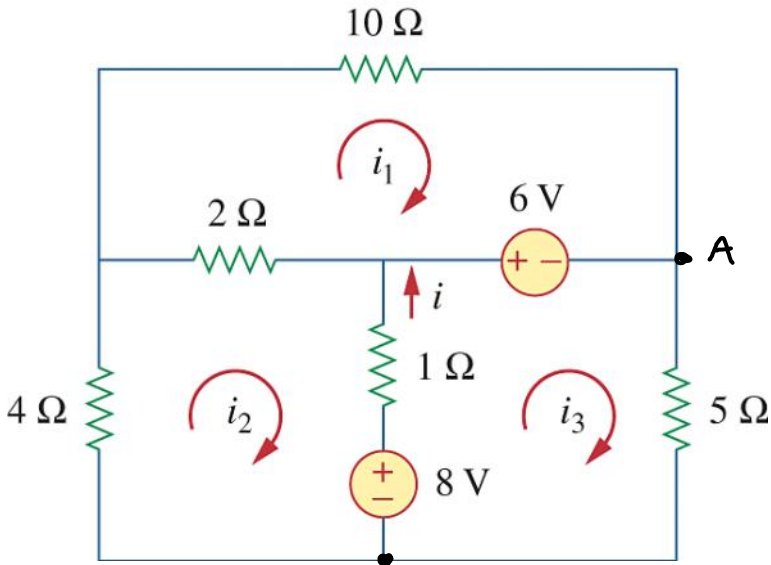


HW3, Chapter 3

Wednesday, December 02, 2009  
2:38 PM

3.41

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



For loop 1: We apply KVL starting from node A:

$$+6 - 2 \times (i_1 - i_2) - 10 i_1 = 0$$


Moving from - to + terminal of a 6V voltage source means I gain 6V.

Moving pass the resistor means I lose IR volts

The current here must be  $i_1 - i_2$  because both  $i_1$  and  $i_2$  passes this  $2\Omega$  resistor.

If you feel uncomfortable with the above method for getting the equation, we may get the same equation via another method:

In loop 1, we have

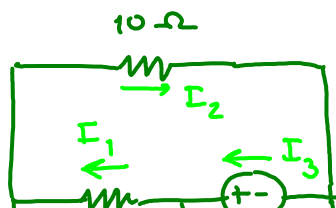



We first need to find the currents passing through the elements:  $I_1, I_2, I_3$

It turns out that I will apply KVL later and hence I don't really care about the  $I_3$ . So, we will focus only on  $I_1$  and  $I_2$ .

Notice how the mesh currents are defined.

We see that  $I_2$  is the same as  $i_1$ .

However, for  $I_1$  we have two mesh currents  $i_1$  and  $i_2$  going in opposite direction. For my  $I_1$  above, I have

$$I_1 = i_1 - i_2.$$

Next, by Ohm's law, we have

$$\begin{array}{c} + \overset{V_2}{10\Omega} - \\ \text{---} \text{---} \text{---} \\ \rightarrow \\ I_2 \end{array} \quad \begin{array}{l} V_2 = I_2 \times 10 \\ = i_1 \times 10 \text{ V} \end{array}$$


and

$$\begin{array}{c} - \overset{I_1}{\leftarrow} + \\ \text{---} \text{---} \text{---} \\ \underset{V_1}{2\Omega} \end{array} \quad \begin{array}{l} V_1 = I_1 \times 2 \\ = (i_1 - i_2) \times 2 \text{ V} \end{array}$$

Note that I don't have any minus sign in my Ohm's law because I defined the directions of my currents and polarities of my voltages so that the current flows from a higher potential (+) to a lower potential (-).

Return to loop 1, we now have

$$+ \overset{V_2}{-}$$

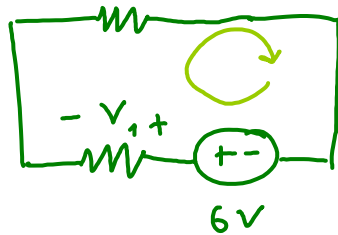

So, by KVL, we have

$$-6 + V_1 + V_2 = 0.$$

(here I use the trick that we discussed in class, the sign on each voltage is the polarity of the terminal encountered first as we travel around the loop)

Plugging the values for  $V_1$  and  $V_2$ , we then have

$$-6 + (i_1 - i_2) \times 2 + i_1 \times 10 = 0$$

which is the same equation that we got earlier.

Once you did this KVL equation reading for many times, you should be able to "read" the equation directly from a loop without thinking much.

with correct signs

For loop 2, starting from the bottom, we have

$$-4 \times i_2 - 2 \times (i_2 - i_1) - 1 \times (i_2 - i_3) - 8 = 0$$

For loop 3, starting from A, we have


$$-5 i_3 + 8 - (i_3 - i_2) \times 1 - 6 = 0$$

$$\Rightarrow i_1 = \frac{77}{239}, \quad i_2 = -\frac{40}{39}, \quad i_3 = \frac{19}{117}$$

Therefore,  $i = i_3 - i_2 = \boxed{\frac{139}{117} \approx 1.19 \text{ A}}$

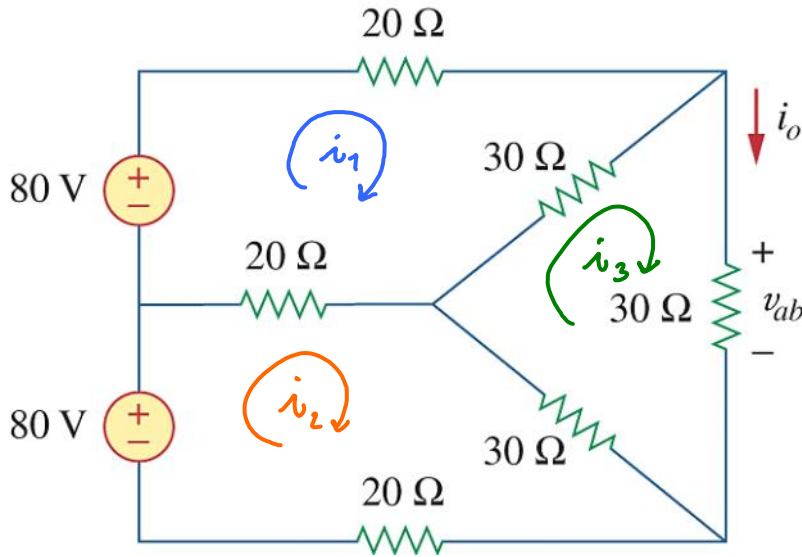3.43

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$\text{Loop 1: } 80 - i_1 \times 20 - 30 \times (i_1 - i_3) - 20(i_1 - i_2) = 0$$

$$\text{Loop 2: } 80 - (i_2 - i_1) \times 20 - (i_2 - i_3) \times 30 - 20i_2 = 0$$

$$\text{Loop 3: } -30(i_3 - i_2) - 30(i_3 - i_1) - 30i_3 = 0$$


$$\Rightarrow i_3 = \frac{16}{9} \quad (i_1 = i_2 = \frac{8}{3})$$

Note that  $i_o = i_3$ .

$$\text{So, } i_o = \frac{16}{9} \text{ A} \approx 1.78 \text{ A}$$

$$v_{ab} = i_o \times 30 = \frac{16}{9} \times 30 = \frac{160}{3} \text{ V} \approx 53.33 \text{ V}$$

3.46

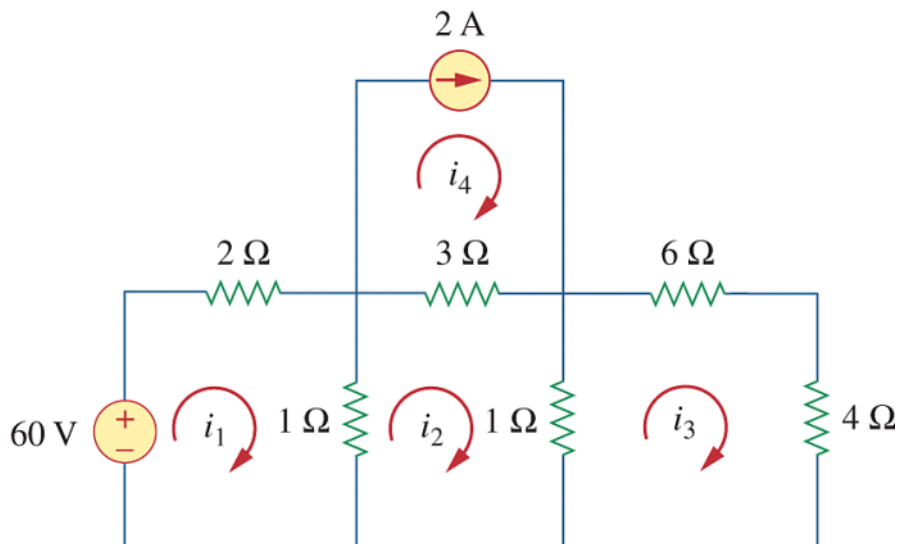

In this problem, because  $i_4$  is the only current that passes through 2A current source. We automatically get

$$i_4 = 2A.$$

$$\text{Loop 1: } +60 - 2i_1 - (i_1 - i_2) = 0$$


$$\text{Loop 2: } -(i_2 - i_1) - 3(i_2 - i_4) - (i_2 - i_3) = 0$$

$$\text{Loop 3: } -(i_3 - i_2) - 6i_3 - 4i_3 = 0$$

$$\Rightarrow i_1 = \frac{3306}{151}, \quad i_2 = \frac{858}{151}, \quad i_3 = \frac{78}{151}$$

$$i_1 \approx 21.89A, \quad i_2 \approx 5.68A, \quad i_3 \approx 0.52A$$

3.48

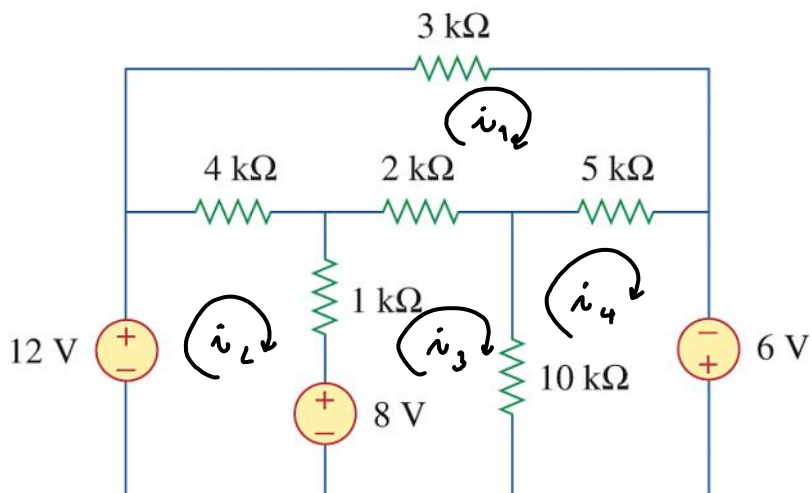

$$\text{Loop 1: } -3i_1 - 4(i_1 - i_2) - 2(i_1 - i_3) - 5(i_1 - i_4) = 0$$

$$\text{Loop 2: } 12 - 4(i_2 - i_1) - (i_2 - i_3) - 8 = 0$$

$$\text{Loop 3: } 8 - (i_3 - i_2) - 2(i_3 - i_1) - 10(i_3 - i_4) = 0$$

$$\text{Loop 4: } -10(i_4 - i_3) - 5(i_4 - i_1) + 6 = 0$$

$$\Rightarrow i_1 = 6 \text{ mA}, i_2 = \frac{166}{23} \text{ mA}, i_3 = \frac{186}{23} \text{ mA}, i_4 = \frac{896}{115} \text{ mA}$$


↑  
currents are in mA because resistances are in kΩ.

The current through the 10 kΩ is

$$\text{pointing up } \rightarrow i_4 - i_3 = \frac{896}{115} - \frac{186}{23} = -0.296 \text{ mA}$$

So, it is 0.296 mA pointing down.

3.58

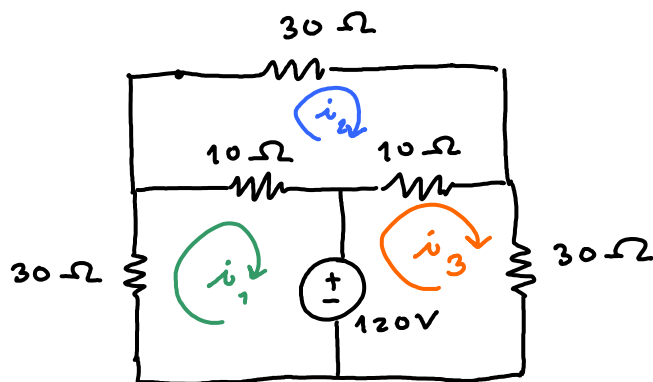

By KVL

$$\begin{aligned} \text{Loop 1: } -3\cancel{i_1} - (i_1 - i_2) \times 10\cancel{\phantom{i_1}} - 12\cancel{\phantom{i_1}} &= 0 \\ -4i_1 + i_2 &= 12 \quad (1) \end{aligned}$$

$$\begin{aligned} \text{Loop 2: } -10\cancel{(i_2 - i_1)} - i_2(3\cancel{\phantom{i_2}}) - 10\cancel{\phantom{i_2}} \times (i_2 - i_3) &= 0 \\ i_1 - 5i_2 + i_3 &= 0 \quad (2) \end{aligned}$$

$$\begin{aligned} \text{Loop 3: } 12\cancel{\phantom{i_2}} - 10\cancel{\phantom{i_2}} \times (i_3 - i_2) - 30\cancel{\phantom{i_2}} \times i_3 &= 0 \\ i_2 - 4i_3 &= -12 \quad (3) \end{aligned}$$

solving (1), (2), (3), we get

$$\begin{array}{l} i_1 = -3A \\ i_2 = 0A \\ i_3 = 3A \end{array}$$