

4.6

Method 1:

From experiment 1,  $V_s^{(1)} = 12 \rightarrow V_o^{(1)} = 4$


For experiment 2,  $V_o^{(2)}$  becomes  $3 \times V_o^{(1)}$  same factor  
 so,  $V_s^{(2)}$  should be  $3 \times V_s^{(1)} = 48 \text{ V}$

For experiment 3,  $V_o^{(3)}$  becomes  $\frac{1}{12} V_o^{(1)}$  same factor  
 so,  $V_o^{(3)}$  should be  $\frac{1}{12} \times V_o^{(1)} = \frac{1}{12} \times 4$   
 $= \frac{1}{3} \text{ V}$

For experiment 4,  $V_o^{(4)}$  becomes  $-\frac{1}{2} V_o^{(1)}$  same factor  
 so,  $V_s^{(4)}$  should be  $-\frac{1}{2} V_s^{(1)} = -\frac{1}{2} \times 12$   
 $= -6 \text{ V}$

Method 2:

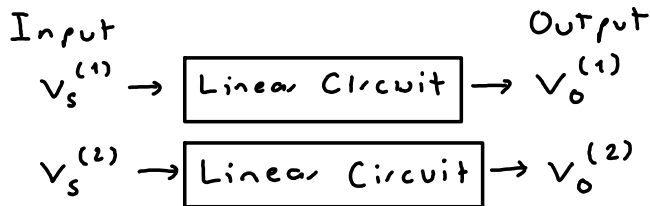Consider two experiments on the same linear circuit:



If we write  $V_s^{(2)} = \frac{V_s^{(2)}}{V_s^{(1)}} \times V_s^{(1)}$ ,

then

$V_o^{(2)}$  should be  $\frac{V_s^{(2)}}{V_s^{(1)}} \times V_o^{(1)}$  use same factor

Hence,  $\frac{V_o^{(2)}}{V_s^{(2)}} = \frac{V_o^{(1)}}{V_s^{(1)}} = \frac{V_o^{(3)}}{V_s^{(3)}} = \frac{V_o^{(4)}}{V_s^{(4)}}$  By similar reasoning.

In other words,  $\frac{V_o}{V_s}$  should be constant for all experiments.

From experiment 1, we have  $\frac{V_o}{V_s} = \frac{4}{12} = \frac{1}{3}$ .

From experiment 1, we have  $\frac{V_o}{V_s} = \frac{4}{12} = \frac{1}{3}$ .

For experiment 2, we should have  $\frac{V_o}{V_s} = \frac{16}{V_s} = \frac{1}{3}$

$$\Rightarrow V_s = 3 \times 16 = \boxed{48 \text{ V}}$$

For experiment 3, we should have  $\frac{V_o}{V_s} = \frac{V_o}{1} = \frac{1}{3}$


$$\Rightarrow V_o = \boxed{\frac{1}{3} \text{ V}}$$

For experiment 4, we should have  $\frac{V_o}{V_s} = \frac{-2}{V_s} = \frac{1}{3}$


$$\Rightarrow V_s = -2 \times 3 = \boxed{-6 \text{ V}}$$

4.8 We will turn on one source at a time

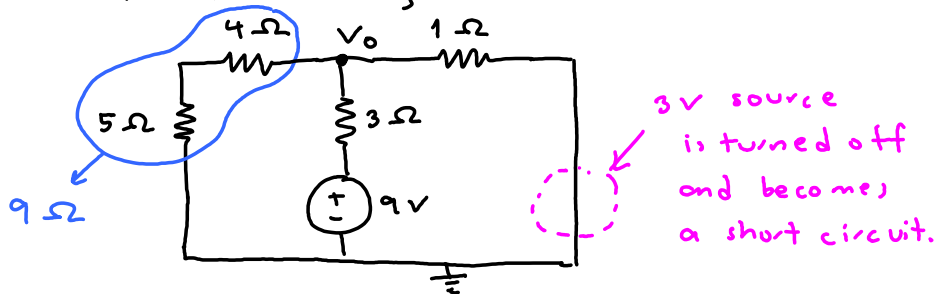a) When the 9V is on, the circuit becomes



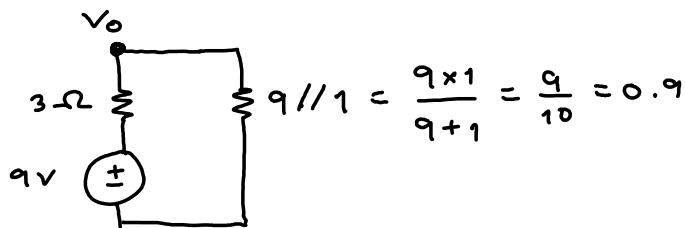Note that the 9Ω and 1Ω are in parallel. Hence, we have




By the voltage divider formula,

$$V_o = \frac{0.9}{3 + 0.9} \times 9 = \frac{0.9}{3.9} \times 9 = \frac{27}{13} \text{ V}$$

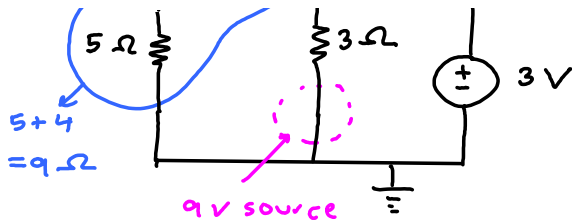
b) When the 3V is on, the circuit becomes





is turned off and becomes a short circuit.

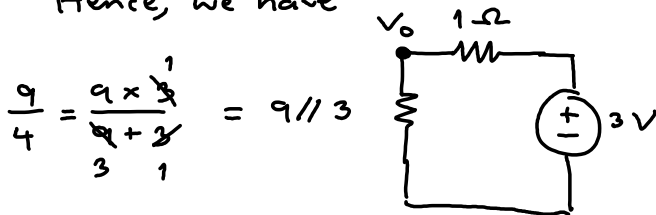Note that the  $9\Omega$  and  $3\Omega$  are in parallel.  
Hence, we have



By the voltage divider formula,



$$V_o = \frac{\frac{9}{4}}{\frac{9}{4} + 1} \times 3 = \frac{9}{9+4} \times 3 = \frac{27}{13}$$


c) By superposition theorem,

$$V_o = V_o^{(a)} + V_o^{(b)} = \frac{27}{13} + \frac{27}{13} = \boxed{\frac{54}{13} \text{ V}} \approx 4.154 \text{ V}$$

4.12

a) When only  $4\text{A}$  is on:

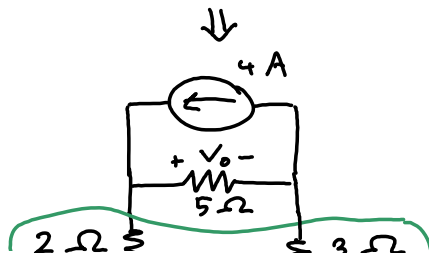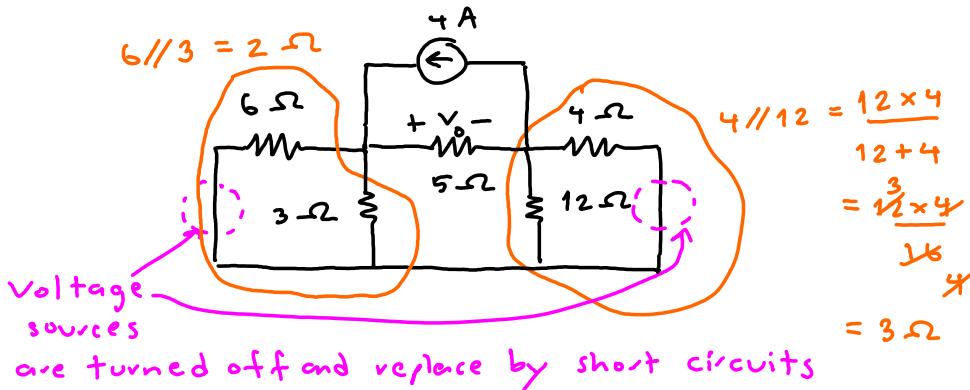



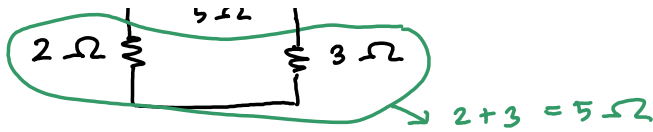


So, 4A is split between the two  $5\Omega$  resistors  
 Hence 2A passes through each  $5\Omega$  and

$$V_o = 5 \times 2 = 10V$$

(By ohm's law,  $\frac{2A}{+V_o^-}$   $V_o = I \times R$ )

b) When only  $\oplus$  is on,

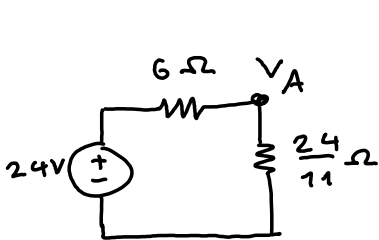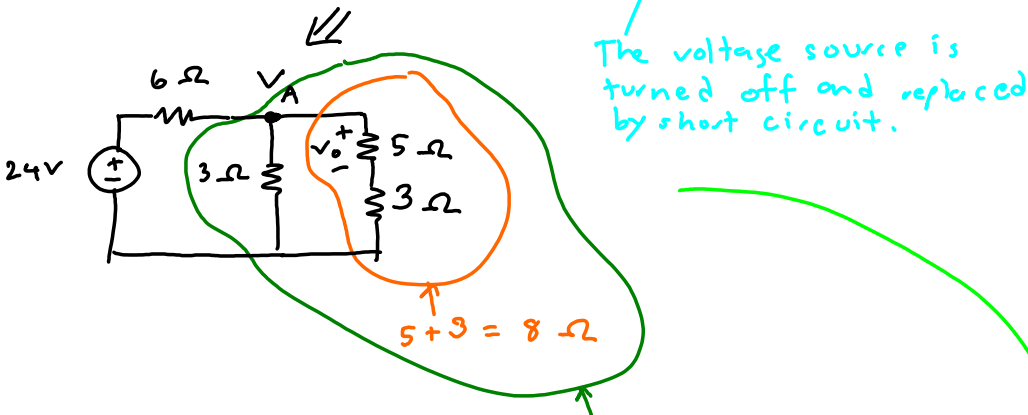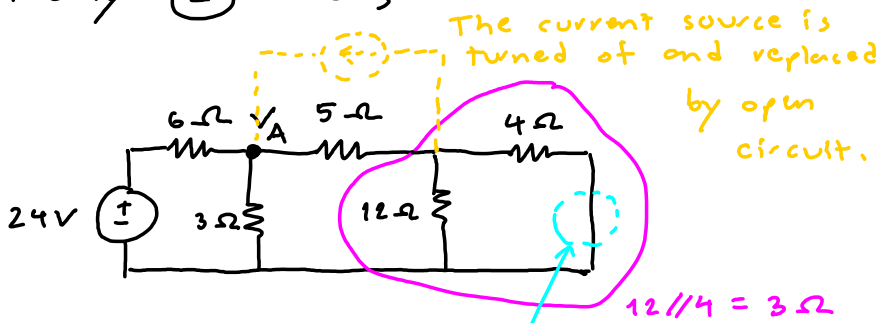

By voltage divider formula,


$$V_A = \frac{\frac{24}{11}}{\frac{24}{11} + 6} \times 24 = \frac{24}{24 + 66} \times 24$$

$$= \frac{24^2}{90} = \frac{8}{10}$$

Again, by voltage divider formula

$$V_o = \frac{5}{5+3} \times V_A = \frac{5}{8} \times \frac{8}{10} = 4V$$

c) When only  $\oplus$  is on,

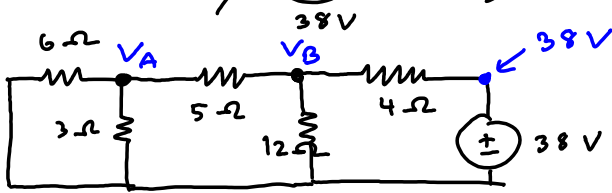

Here, let's try nodal analysis:


$$\left. \begin{aligned} \frac{V_A}{6} + \frac{V_A}{3} + \frac{V_A - V_B}{5} &= 0 \\ \frac{V_B - V_A}{5} + \frac{V_B}{12} + \frac{V_B - 38}{4} &= 0 \end{aligned} \right\} \Rightarrow \begin{aligned} V_A &= \frac{57}{10} \\ V_B &= \frac{399}{20} \end{aligned}$$

$$\Rightarrow V_o = V_A - V_B = \frac{57}{10} - \frac{399}{20} = -\frac{57}{4} V \approx -14.25 V$$


d) By superposition theorem,

$$V_o = 10 + 4 + (-14.25) = -0.25 V = \boxed{-250 mV}$$

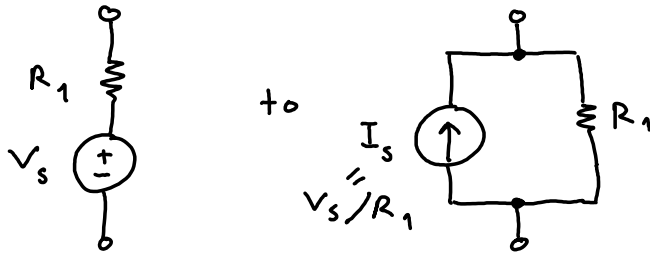(4.20) By source transformation, we will convert



So, the circuit becomes

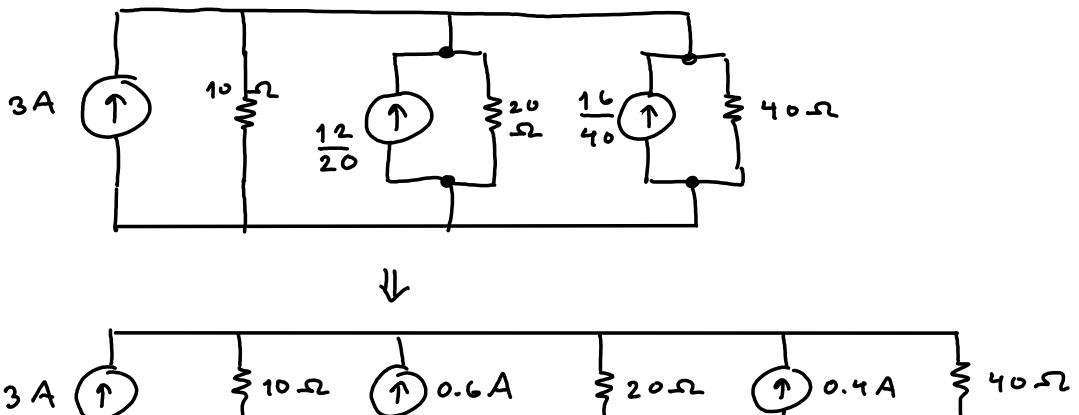




The three parallel current sources can be combined into  
 $3 + 0.6 + 0.4 = 4 \text{ A}$  current source

The three parallel resistors can be combined into

$$\frac{1}{\frac{1}{10} + \frac{1}{20} + \frac{1}{40}} = \frac{40}{4+2+1} = \frac{40}{7} \Omega \text{ resistor.}$$

Hence, we have

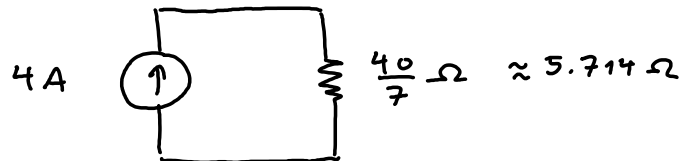


Remark: This is merely an exercise in applying source transformation.


The final answer we have has no real purpose.

In a practical situation, we will need some kind of reference (terminals).

This is shown in the next question.

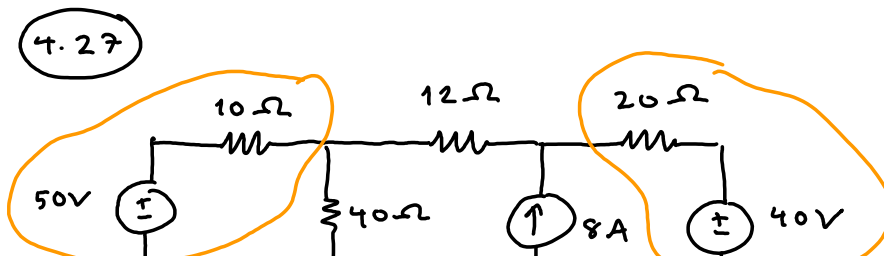\* You may get different answers, depending on the choice of your transformation.



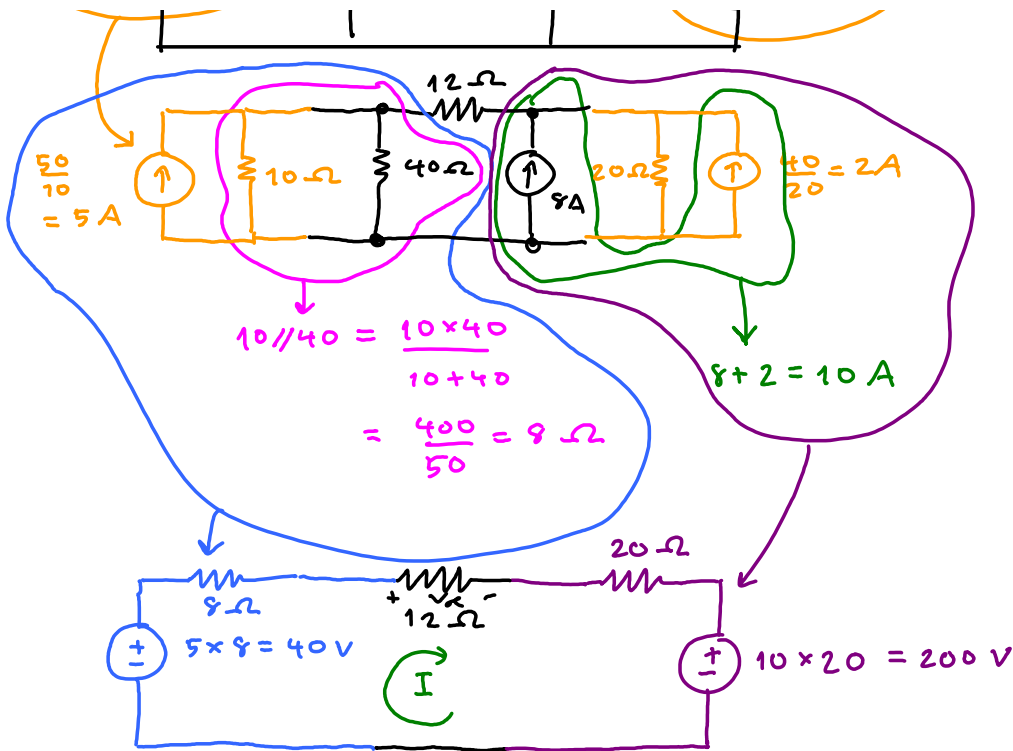

By KVL

$$+40 - 8I - 12I - 20I - 200 = 0$$

$$-40I = 160$$

$$I = -4 \text{ A}$$

$$V_o = I \times 12 \Omega$$


$$= -4 \times 12$$

$$= \boxed{-48 \text{ V}}$$

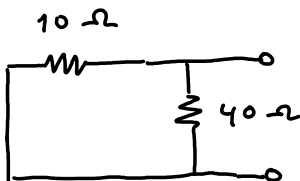
4.33

$$(a) \quad V_{TH} = \frac{4 \text{ A}}{1 \text{ A} + 4 \text{ A}} \times 20 = \frac{4}{5} \times 20 = \boxed{16 \text{ V}}$$

$$R_{TH} = 10 \parallel 40 = \frac{10 \times 40}{10 + 40} = \boxed{8 \Omega}$$



(b)

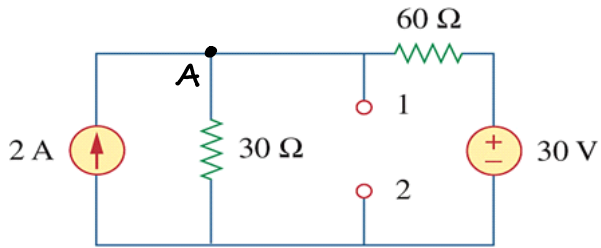

(b)

At node A

$$-2 + \frac{V_A}{30} + \frac{V_A - 30}{60} = 0$$


$$-120 + 2V_A + V_A - 30 = 0$$

$$3V_A = 150V$$

$$V_A = 50V$$

$$V_{TH} = V_A = \boxed{50V}$$

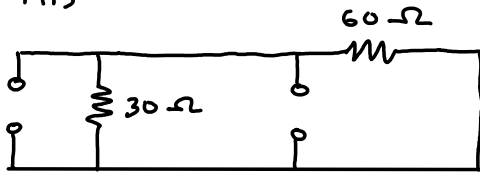
For  $R_{TH}$ , we deactivate all the sources:



$$R_{TH} = 30 // 60 = \frac{30 \times 60}{30 + 60} = \frac{10^2}{\cancel{30} \times \cancel{60}} = \boxed{20\Omega}$$

4.36

Find  $V_{TH}$ :

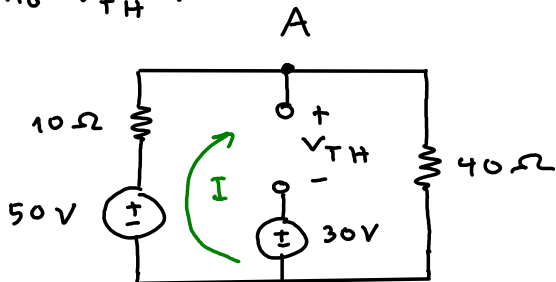


$$I = \frac{50}{10 + 40} = 1A \quad (\text{There is no current through the } 30V \text{ source.})$$

$$V_A = 50 - 10 \times I = 40V$$




$$V_{TH} = V_A - 30 = 10 \text{ V}$$

Find  $R_{TH}$ :

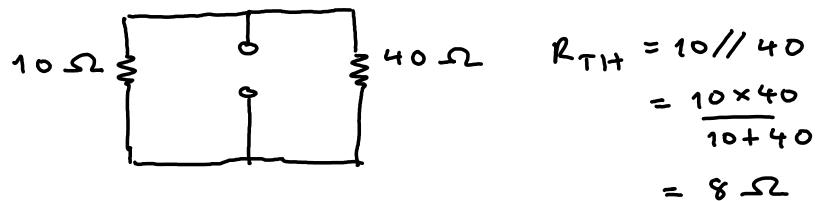


So, an equivalent circuit is

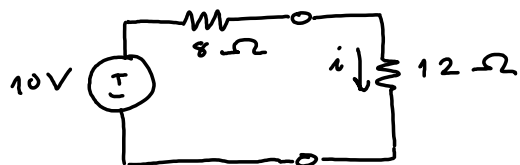

$$\text{So, } i = \frac{10}{8+12} = \frac{10}{20} = \frac{1}{2} = \boxed{0.5 \text{ A}}$$

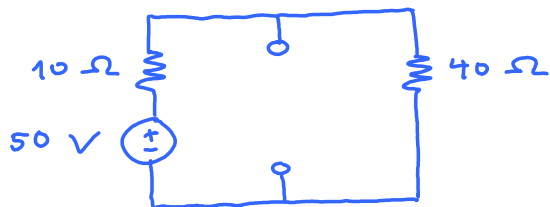Note: it is possible to find the Thevenin equivalent of



However, I modify the question so that you can not do this!!

I ask specifically for the Thevenin equivalent as seen by the 12 ohm resistor!