
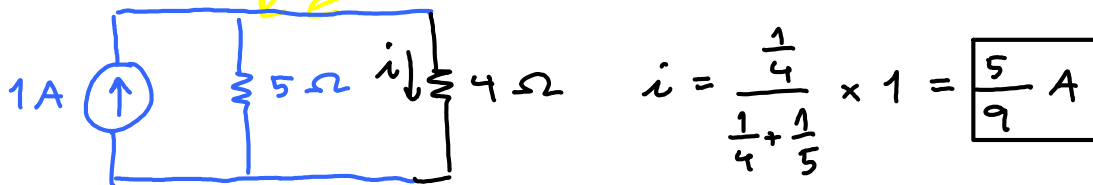
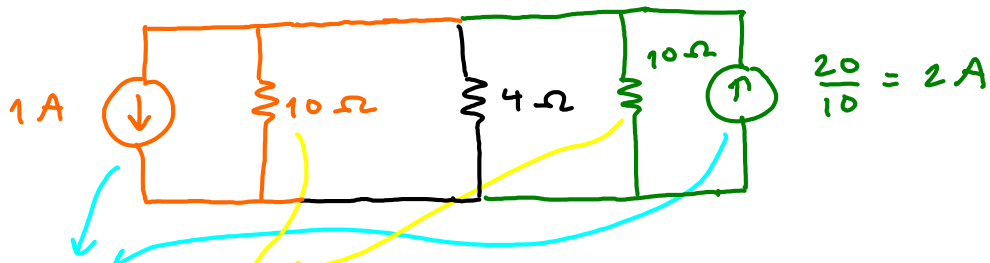
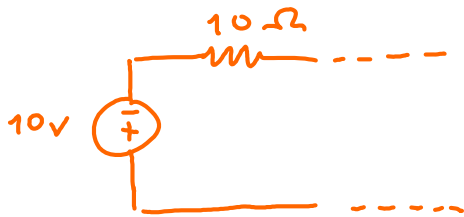
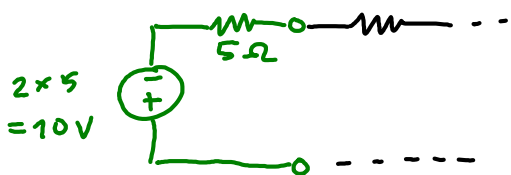


HW 6 Chapter 4


Thursday, December 10, 2009

8:34 PM

4.22

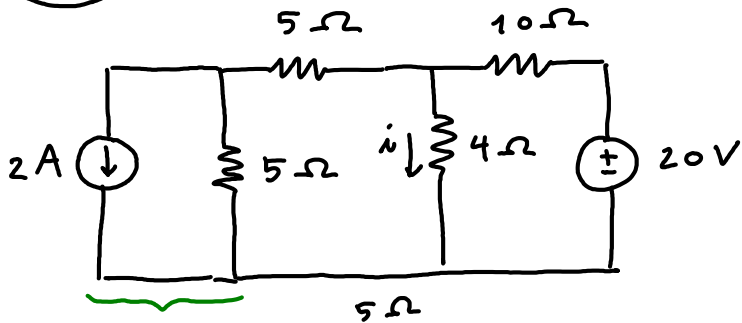


4.26

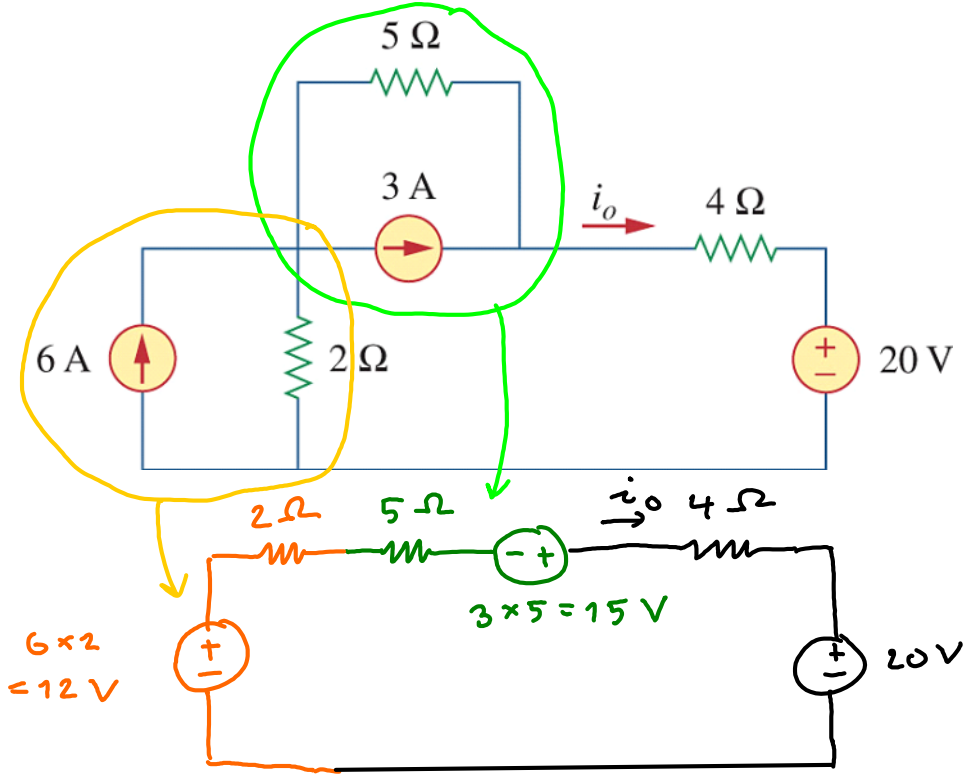

$$i_o = \frac{12 + 15 - 20}{2 + 5 + 4} = \boxed{\frac{7}{11} \text{ A}}$$

4.59 For V_{TH} :

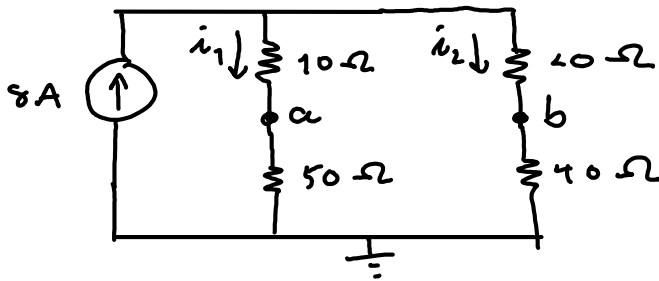

Because $10 + 50 = 20 + 40 = 60 \Omega$,


$$i_1 = i_2 = \frac{8}{2} = 4 \text{ A.}$$

$$\text{So, } V_a = 50 \times i_1 = 200 \text{ V}$$

$$V_b = 40 \times i_2 = 160 \text{ V}$$

$$V_{ab} = 200 - 160 = 40 \text{ V} = V_{TH}$$


For R_{TH} :

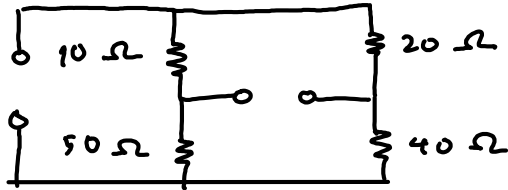

$$R_{TH} = (10 + 20) \parallel (50 + 40) = 30 \parallel 90$$

$$= \frac{30 \times 90}{30 + 90} = \frac{2700}{120} = \frac{45}{2} \Omega = 22.5 \Omega$$


So, the Thevenin equivalent is given by

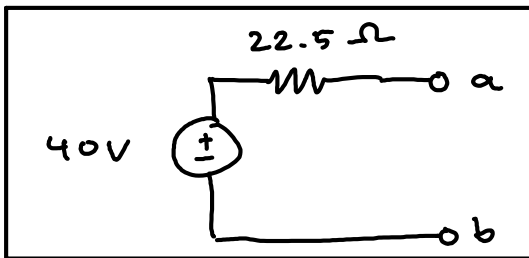

We use $I_N = \frac{V_{TH}}{R_{TH}} = \frac{40}{45/2} = \frac{80}{45} = \frac{16}{9} A \approx 1.778 A$


$$R_N = R_{TH} = 22.5 \Omega$$


So, the Norton equivalent is given by

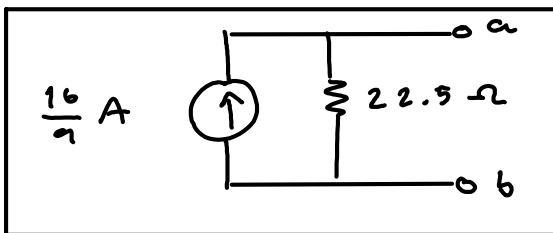


4.66

R_{TH} :

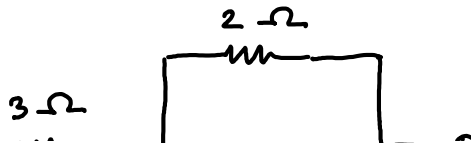

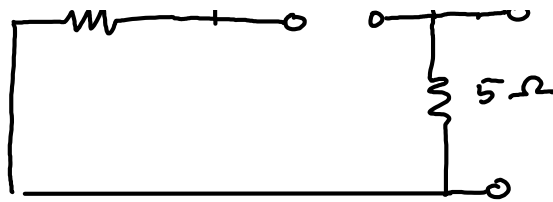
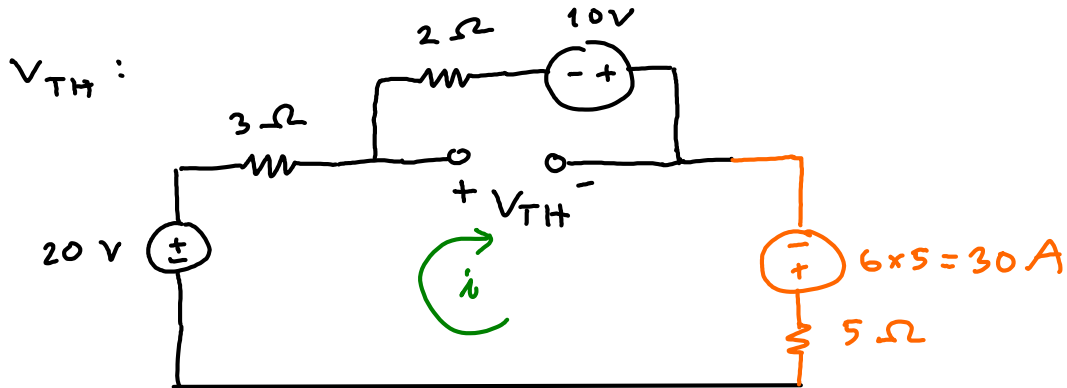
$$R_{TH} = 2 // (3 + 5) = 2 // 8 = \frac{2 \times 8}{10} = 1.6 \Omega$$



$$i = \frac{20 + 10 + 30}{3 + 2 + 5} = 6 \text{ A}$$


$$V_{TH} = -10 + 2 \times 6 = 2 \text{ V}$$

$$S_o, \text{ max power} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{2^2}{4 \times 1.6} = \frac{10}{16} = \boxed{\frac{5}{8} \text{ W}} \approx 0.625 \text{ W}$$

HW 6 Chapter 5

Thursday, December 10, 2009
7:25 PM

5.20

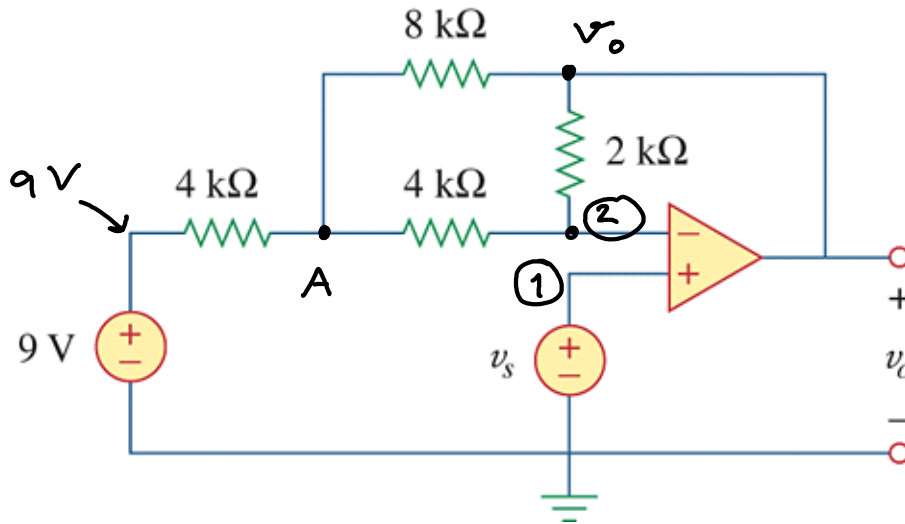

① $v_+ = v_o$

② $v_- = v_+ = v_o$ by Rule #2.

③ At A $\frac{v_A - 9}{4} + \frac{v_A - v_o}{8} + \frac{v_A - v_s}{4} = 0$


At (-) $\frac{v_o - v_A}{4} + \frac{v_o - v_o}{2} = 0$

$$\Rightarrow v_A = \frac{7}{11} v_o$$

$$v_o = \frac{13}{11} v_o - \frac{18}{11}$$

If $v_o = 0$, we have $v_o = -\frac{18}{11} \text{ V}$

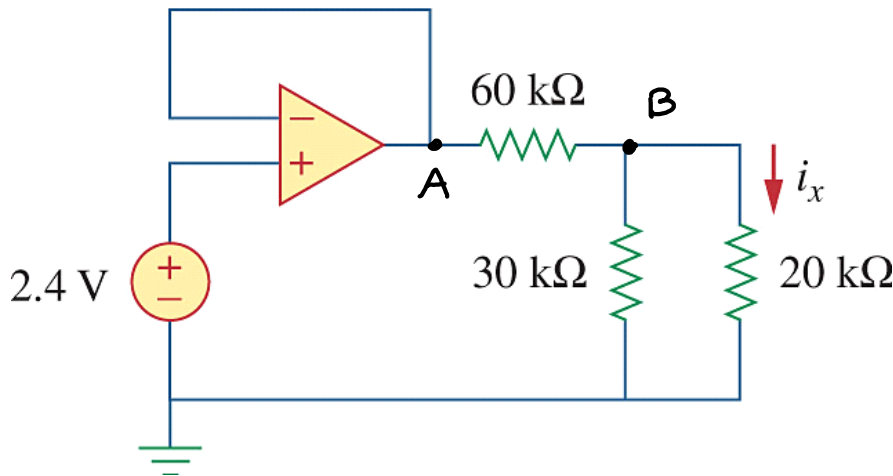5.30 This is a voltage follower. So, $v_A = 2.4 \text{ V}$



$$V_B = \frac{20 // 30}{60 + 20 // 30} \times V_A = \frac{12}{72} V_A = \frac{1}{6} V_A = 0.4 V$$

$$i_x = \frac{V_B}{20k} = \frac{0.4}{20k}$$


$$20 // 30 = \frac{20 \times 30}{20 + 30}$$

$$= \frac{600}{50} = 12$$

$$= 0.02 \text{ mA} = \boxed{20 \mu\text{A}}$$

$$P = i_x \times V_B = 0.4 \text{ V} \times 20 \mu\text{A} = \boxed{8 \mu\text{W}}$$

5.34

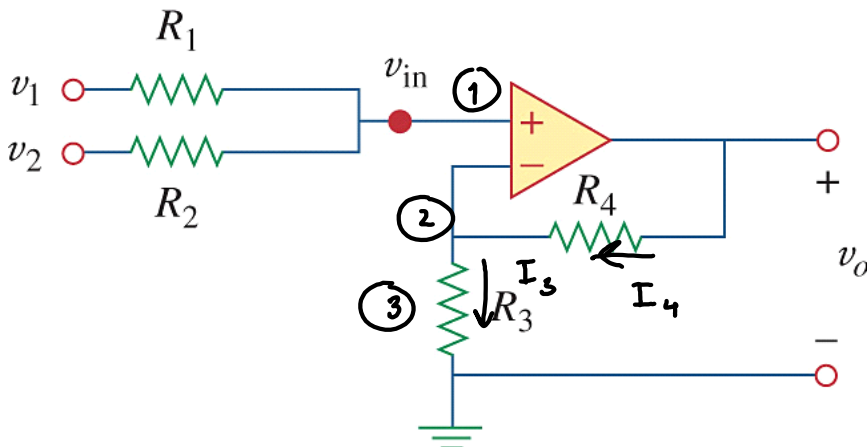

$$\textcircled{1} \quad i_+ = 0 \quad \text{so,} \quad v_{in} \frac{-v_1}{R_1} + v_{in} \frac{-v_2}{R_2} = 0$$

$$v_{in} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_1}{R_1} + \frac{v_2}{R_2}$$

$$v_{in} = \frac{R_2 v_1 + R_1 v_2}{R_1 + R_2}$$

$$\textcircled{2} v_- = v_+ = v_{in}$$

$$\textcircled{3} I_3 = \frac{v_-}{R_3} = \frac{v_{in}}{R_3}$$

$$\textcircled{4} I_4 = I_3 \text{ because } i_- = 0$$

$$\textcircled{5} v_o = v_- + I_4 R_4 = v_{in} + \frac{v_{in}}{R_3} R_4$$

$$= v_{in} \left(1 + \frac{R_4}{R_3} \right)$$

$$= \left(1 + \frac{R_4}{R_3} \right) \left(\frac{R_2 v_1 + R_1 v_2}{R_1 + R_2} \right)$$

$$\textcircled{5.37} v_o = - \left(\frac{30}{10} \times 1 + \frac{30}{20} \times 2 + \frac{30}{30} \times (-3) \right) = \boxed{-3V}$$

(This is a summer.)

$$\textcircled{5.47} R_1 = 2k, R_2 = 30k, R_3 = 2k, R_4 = 20k$$

$$\frac{R_2}{R_1} = 15, \quad \frac{R_3}{R_4} = \frac{1}{10}$$

$$v_o = -15 v_1 + \frac{1+15}{1+\frac{1}{10}} v_2 = -15 + \frac{160}{11} \times 2$$

$$\approx \boxed{14.09 V}$$