


HW7

Friday, January 29, 2010
10:54 AM

The first four exercises in this HW deal with capacitor combination. To simplify our notation, we will use

series(C_1, C_2, \dots, C_n)

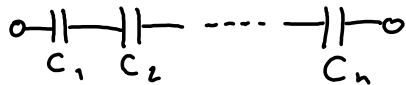
to mean the combined value of C_1, C_2, \dots, C_n when they are all connected in series:



We will use

parallel(C_1, C_2, \dots, C_n)

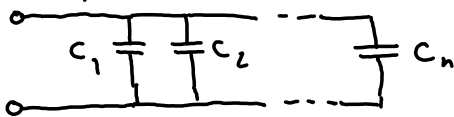to mean the combined value of C_1, C_2, \dots, C_n when they are all connected in parallel:







We know that $\text{series}(C_1, \dots, C_n) = \left(\frac{1}{C_1} + \dots + \frac{1}{C_n}\right)^{-1}$

$\text{parallel}(C_1, \dots, C_n) = C_1 + \dots + C_n$

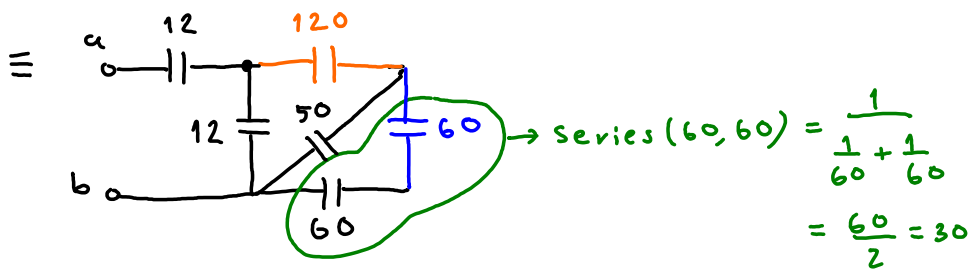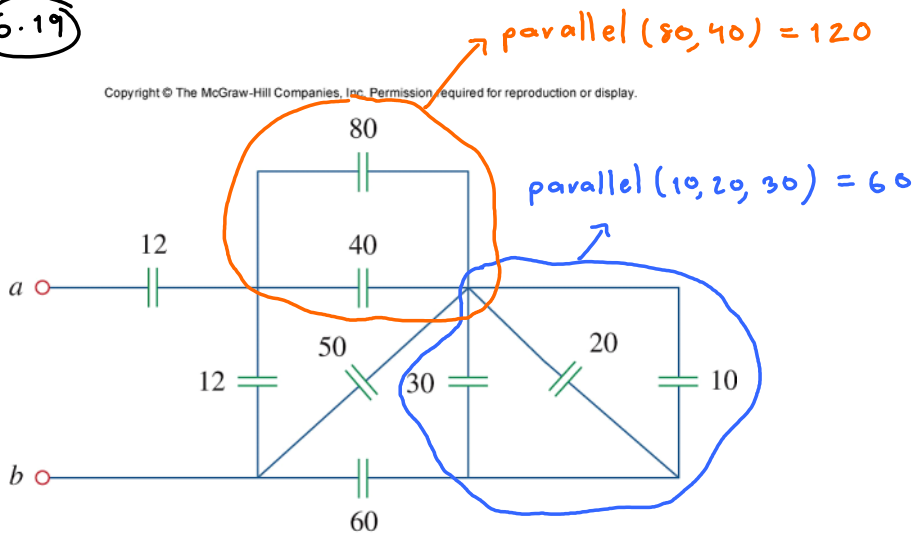6.19

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



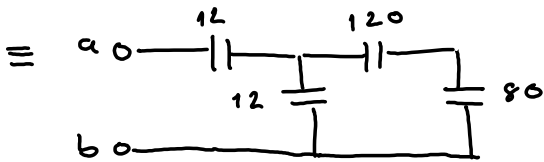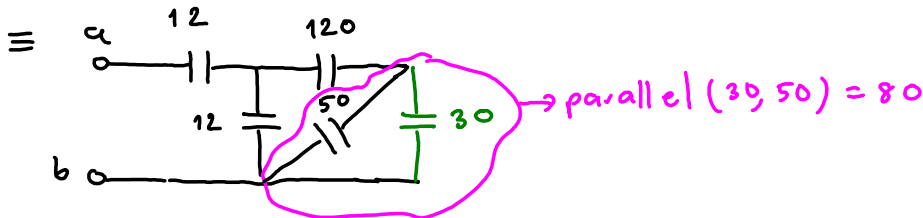

At this point, I'm too lazy to draw more pictures. Our simplified combination above is easy enough to be represented in a one-line expression:

$$C_{ab} = \text{series} \left(12, \text{parallel} \left(12, \text{series} \left(120, 80 \right) \right) \right)$$

$$\frac{120 \times 80}{120 + 80} = \frac{120 \times 80}{200} = 48$$

$$48 + 12 = 60$$



$$\frac{60 \times 12}{60 + 12} = \frac{60 \times 12}{72} = 10$$

$$= 10 \mu\text{F}$$

→ don't forget the unit!!

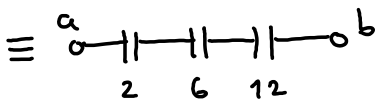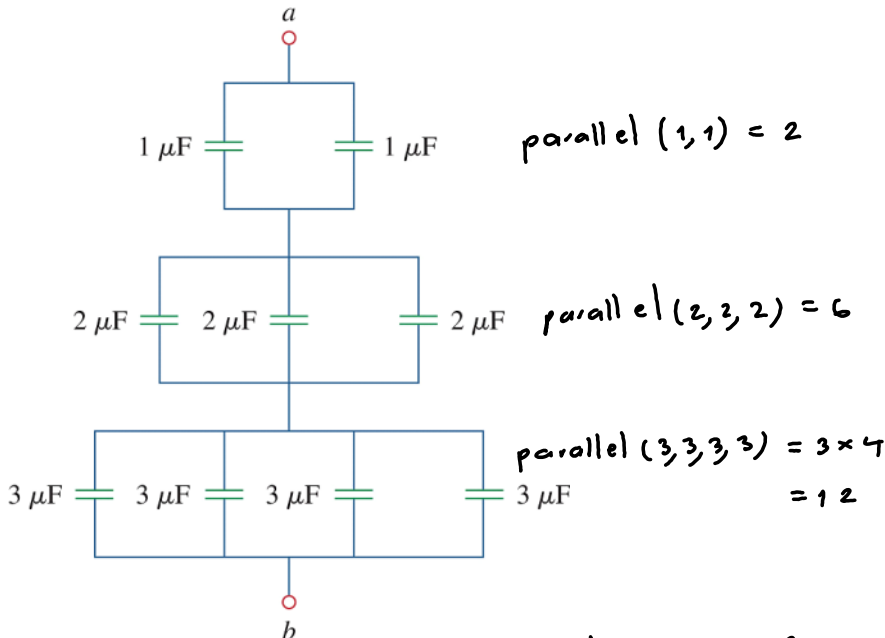6.20

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$C_{ab} = \frac{1}{\frac{1}{2} + \frac{1}{6} + \frac{1}{12}} = \frac{2}{1 + \frac{1}{3} + \frac{1}{6}} = \frac{4}{3} \mu\text{F}$$

6.21

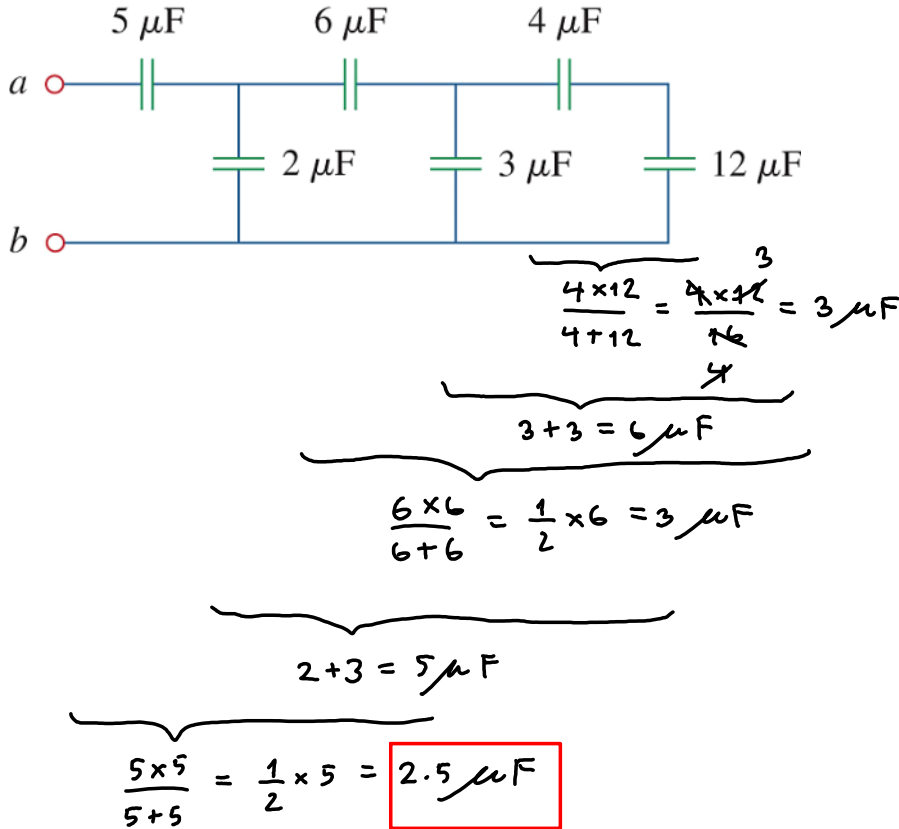6.21


2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



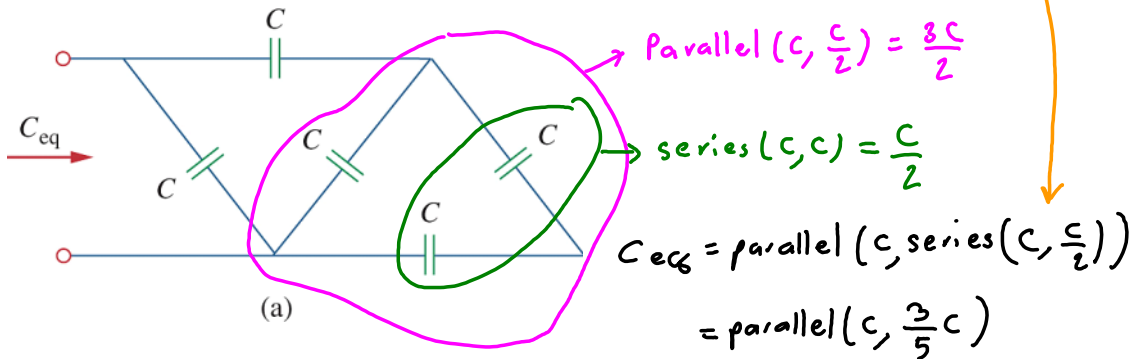
6.29

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$\frac{1 \times \frac{3}{2}}{1 + \frac{3}{2}} = \frac{3}{2+3} = \frac{3}{5}$$

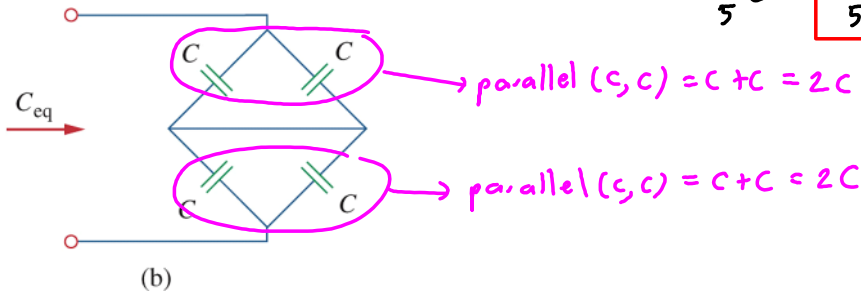Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.





$$C_{eq} = \text{series}(2C, 2C) = \frac{2C}{2} = C$$

$$C_{\text{eff}} = \text{series}(2C, 2C) = \frac{2C}{2} = C$$

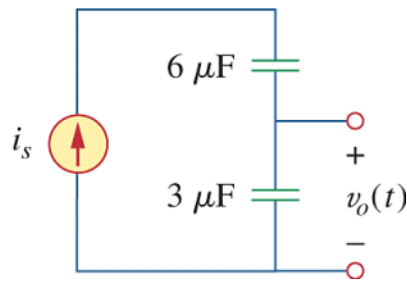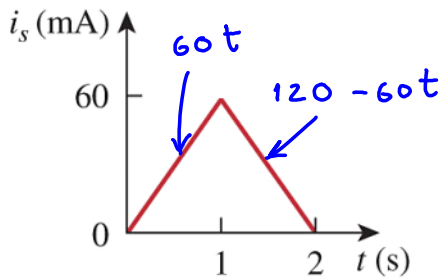6.30

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



For capacitor, $i_c(t) = C \frac{dv_c(t)}{dt}$
 \parallel
 $i_s(t)$ $= v_o(t)$

$$v_o(t) = v_c(t) = \frac{1}{C} \int_0^t i_c(x) dx + v_o(0)$$

$$= \frac{1}{C} \int_0^t i_s(x) dx + 0$$

← when there is no charge ($q(0) = 0$) in the capacitor,
 $v_c(0) = \frac{q(0)}{C} = \frac{0}{C} = 0$
 \parallel
 $v_o(0)$

Note that $i_s(x) = \begin{cases} 60x \text{ mA}, & 0 \leq x \leq 1 \\ 120 - 60x \text{ mA}, & 1 \leq x \leq 2 \end{cases}$

So, for $0 \leq t \leq 1$

$$v_o(t) = \frac{1}{C} \int_0^t 60x dx \times 10^{-3} = \frac{1}{C} 30 \frac{t^2}{2} \times 10^{-3}$$

At $t = 1$,

$$v_o(1) = \frac{1}{C} 30 \times 10^{-3}$$

For $1 \leq t \leq 2$

$$v_o(t) = v_o(1) + \frac{1}{C} \int_1^t (120 - 60x) dx \times 10^{-3}$$

$$\begin{aligned}
 & 120(t-1) - 30(t^2-1) \\
 & = 120t - 120 + 30 - 30t^2 \\
 & = 30(4t - 3 - t^2)
 \end{aligned}$$

Now, we combine all the cases:

$$v_o(t) = \frac{1}{C} \times 10^{-3} \times \begin{cases} 30t^2, & 0 \leq t \leq 1 \\ 30 + 30(4t - 3 - t^2), & 1 \leq t \leq 2 \end{cases}$$

$$\begin{aligned}
 & = \underbrace{\frac{1}{C} \times 30 \times 10^{-3}}_{\substack{\frac{1}{30 \times 10^{-6}} \\ 3 \times 10^{-6} \\ " \\ 10 \times 10^3}} \times \begin{cases} t^2, & 0 \leq t \leq 1 \\ 4t - 2 - t^2, & 1 \leq t \leq 2 \end{cases}
 \end{aligned}$$

$$= \begin{cases} 10t^2, & 0 \leq t \leq 1 \\ 40t - 20 - 10t^2, & 1 \leq t \leq 2 \end{cases} \text{ kV}$$