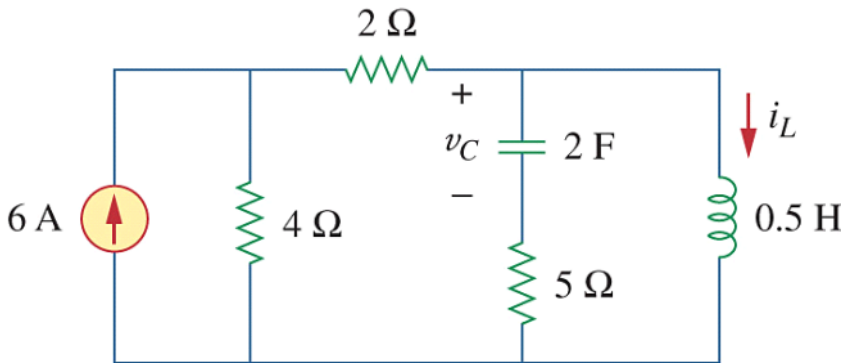


HW8 Chapter 6


Saturday, January 16, 2010
9:50 PM

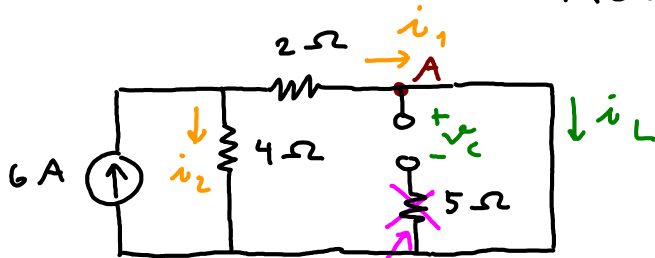6.46

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Under DC conditions, capacitor \rightarrow open circuit
inductor \rightarrow short circuit



No current through this resistor because of the open connection at the capacitor.

By current divider formula, $i_1 = 4A$
 $i_2 = 2A$

$$i_L = i_1 = 4A$$

$$v_C = v_A = 0V$$

no current through the 5Ω resistor

(There is a short connection from the top to the bottom of the circuit)

The energy stored in the capacitor is $w_C = \frac{1}{2} C v_C^2 = 0J$



The energy stored in the inductor is $w_L = \frac{1}{2} L i_L^2$

$$= \frac{1}{L} \times \frac{1}{L} \times 4^2 = 4 \text{ J}$$

$v_c = 0 \text{ V}$	$w_c = 0 \text{ J}$
$i_L = 4 \text{ A}$	$w_L = 4 \text{ J}$

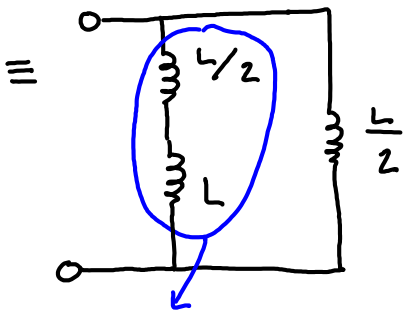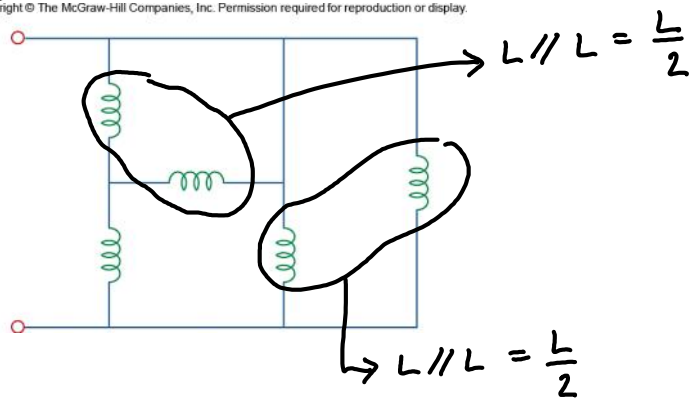6.49

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$\frac{L}{2} + L = \frac{3L}{2}$$

$$L_{eq} = \frac{3L}{2} // \frac{L}{2}$$


$$= \frac{L}{2} (3 // 1)$$

$$= \frac{L}{2} \frac{3}{4} = \frac{3L}{8}$$


When $L = 10$,

$$L_{eq} = \frac{3 \times 10}{8} = 3.75 \text{ H}$$


6.56

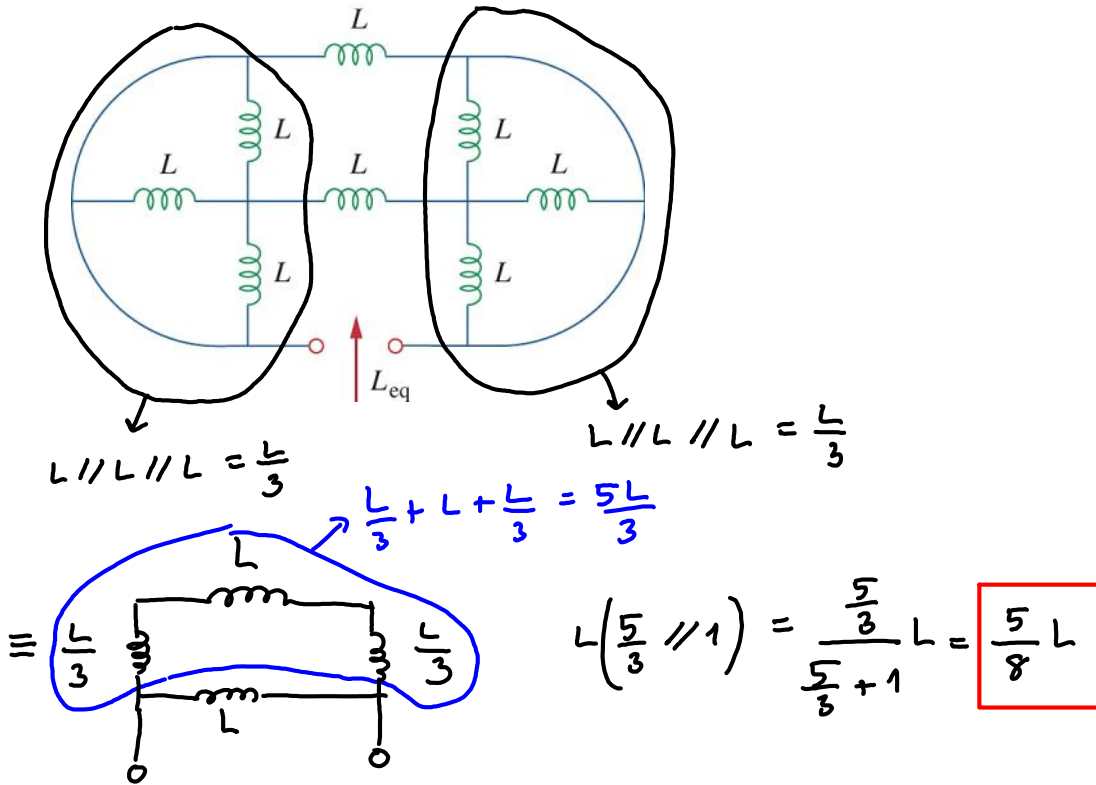

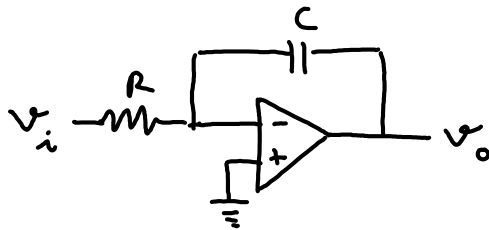6.71 In class, an integrator circuit is given in the following form:



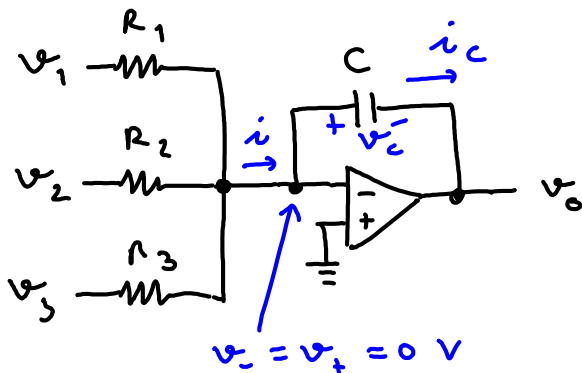We have seen how to extend an inverting amplifier into a summer. Here, we will use a similar extension:



In which case, we have

In which case, we have

$$i_c = i$$

$$C \frac{dv_c}{dt} \rightarrow i = \frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \frac{v_3 - 0}{R_3}$$

$$v_c = 0 - v_o = -v_o$$

Therefore,

$$-C \frac{dv_o}{dt} = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3}$$

$$v_o(t) = - \int_0^t \left(\frac{1}{R_1 C} v_1(x) + \frac{1}{R_2 C} v_2(x) + \frac{1}{R_3 C} v_3(x) \right) dx$$

We want


$$v_o(t) = - \int_0^t \left(1 v_1(x) + 4 v_2(x) + 10 v_3(x) \right) dx.$$

Hence,

$$\frac{1}{R_1 C} = 1 \Rightarrow R_1 = \frac{1}{C} = \frac{1}{2 \mu} = 500 \text{ k}\Omega$$


$$\frac{1}{R_2 C} = 4 \Rightarrow R_2 = \frac{1}{4C} = 125 \text{ k}\Omega$$
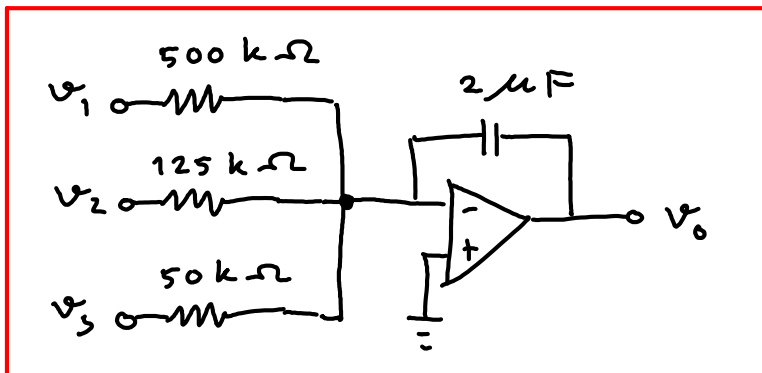
$$\frac{1}{R_3 C} = 10 \Rightarrow R_3 = \frac{1}{10C} = 50 \text{ k}\Omega$$



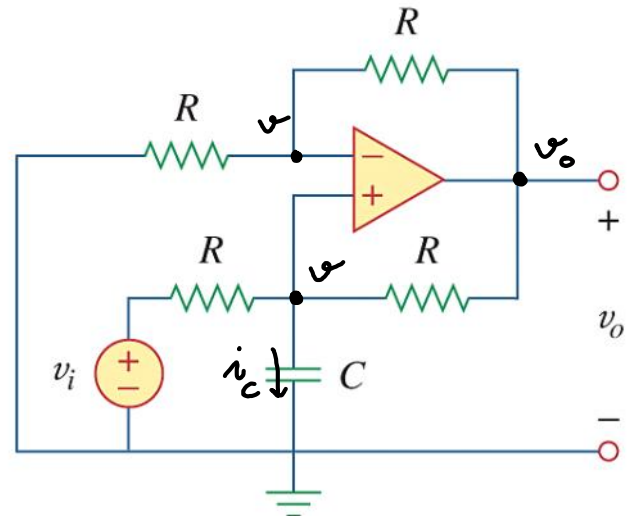6.73

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



For ideal op amp : $v_- = v_+ \equiv v$
 $i_- = i_+ = 0$

At the negative input terminal:

$$\frac{v-0}{R} + \frac{v-v_o}{R} = 0$$

$$2v = v_o \Rightarrow v = \frac{v_o}{2}$$

At the positive input terminal:

$$\frac{v-v_i}{R} + i_c + \frac{v-v_o}{R} = 0$$

$$i_c = C \frac{dv_c}{dt} = C \frac{d}{dt}(v-0) = C \frac{d}{dt} \left(\frac{v_o}{2} \right)$$

$$= \frac{C}{2} \frac{dv_o}{dt}$$

~~$$\frac{v_o}{2} - v_i + \frac{RC}{2} \frac{dv_o}{dt} + \frac{v_o}{2} - v_o = 0$$~~

$$\frac{dv_o}{dt} = \frac{2}{RC} v_i$$

$$v_o(t) = v_o(t_0) + \frac{2}{RC} \int_{t_0}^t v_i(\alpha) d\alpha$$

HW8 Ch7

Saturday, January 16, 2010
10:38 PM

7.1

Remark: can find C
by $i = C \frac{dv_c}{dt}$

(b) $\tau = \frac{1}{200} = 5 \text{ ms}$

(a) $R = \frac{v}{i} = \frac{56}{8 \text{ mA}} = 7 \text{ k}\Omega$

Note that
 $v_c = -v$.

$C = \frac{\tau}{R} = \frac{5}{7} \text{ mF} = 0.714 \mu\text{F}$

$\tau = RC$

(c) $v(0) = v(0^+) = 56 \text{ V}$

no voltage jump
for capacitor


We want to find t such that

$v(t) = 56 e^{-200t} = \frac{56}{2} = 28 \text{ V}$

$e^{-200t} = \frac{1}{2}$

$t = \frac{\ln 2}{200} = 3.466 \text{ ms}$

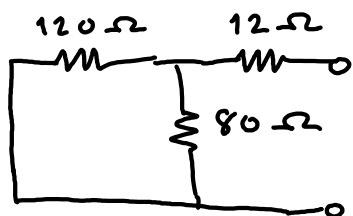7.2 First, find the Thevenin equivalent R
at the capacitor's terminals



$R_{TH} = 12 + 120 // 80$
 $= 12 + 48 = 60 \Omega$

$\tau = R_{TH} \times C = 60 \times 0.5 \text{ m} = 30 \text{ ms}$

7.3 R_{TH} at the terminals of capacitor

$= 10 + 40 // (20 + 30) \text{ k}\Omega$

$$= 10 + 40 // 50 = 290/9 \text{ k}\Omega$$

$$\tau = R_{TH} \times C = \frac{290}{9} \text{ k} \times 100 \times 10^{-12} = 3.22 \mu\text{s}$$

7.8

$$(b) \tau = \frac{1}{4} \text{ s}$$

$$(a) R = \frac{v}{i} = \frac{10}{0.2} = 50 \Omega$$

$$C = \frac{\tau}{R} = \frac{1}{4 \times 50} = 5 \text{ mF}$$

$$(c) v(0^+) = 10 \text{ V} = v(0)$$

↑
no voltage jump across capacitor

$$w_c = \frac{1}{2} \times C \times v_c^2 = \frac{1}{2} \times 5 \times 10^{-3} \times 10^2 = 0.25 \text{ J}$$

$$(d) w_c(t) = \frac{1}{2} C \times v_c^2(t)$$

$$w_c(0) = \frac{1}{2} C v_c^2(0)$$

want to find t such that

$$w_c(t) = \frac{1}{2} w_c(0)$$

$$\frac{1}{2} C v_c^2(t) = \frac{1}{2} \times \frac{1}{2} C v_c^2(0)$$

$$v_c(t) = \frac{1}{\sqrt{2}} v_c(0)$$

$$\cancel{10} e^{-4t} = \frac{1}{\sqrt{2}} \cancel{10}$$

$$t = \frac{\ln \sqrt{2}}{4} = 87 \text{ ms}$$