

Chapter 4, Problem 22.

For the circuit in Fig. 4.90, use source transformation to find i .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

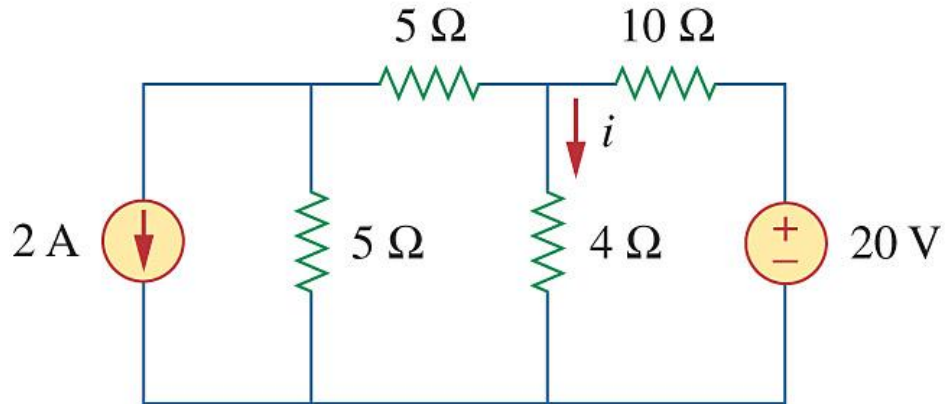


Figure 4.90