

Digital Circuits

ECS 371

Dr. Prapun Suksompong

prapun@siit.tu.ac.th

Lecture 10

Office Hours:

BKD 3601-7

Monday 9:00-10:30, 1:30-3:30

Tuesday 10:30-11:30

ECS371.PRAPUN.COM

Announcement


- HW4 posted on the course web site
 - Chapter 5: 4(b,c,e), 20a, 22a, 56
 - **Write down all the steps** that you have done to obtain your answers.
 - Due date: July 16, 2009 (Thursday)

Combinational Logic

- We studied the **theoretical** principles used in combinational logic design.
- We will build on that foundation and describe many of the devices, structures, and methods used by engineers to solve **practical** digital design problems.
- A complex circuit or system is conceived as a collection of smaller subsystems, each of which has a much simpler description.

Digital System Concept

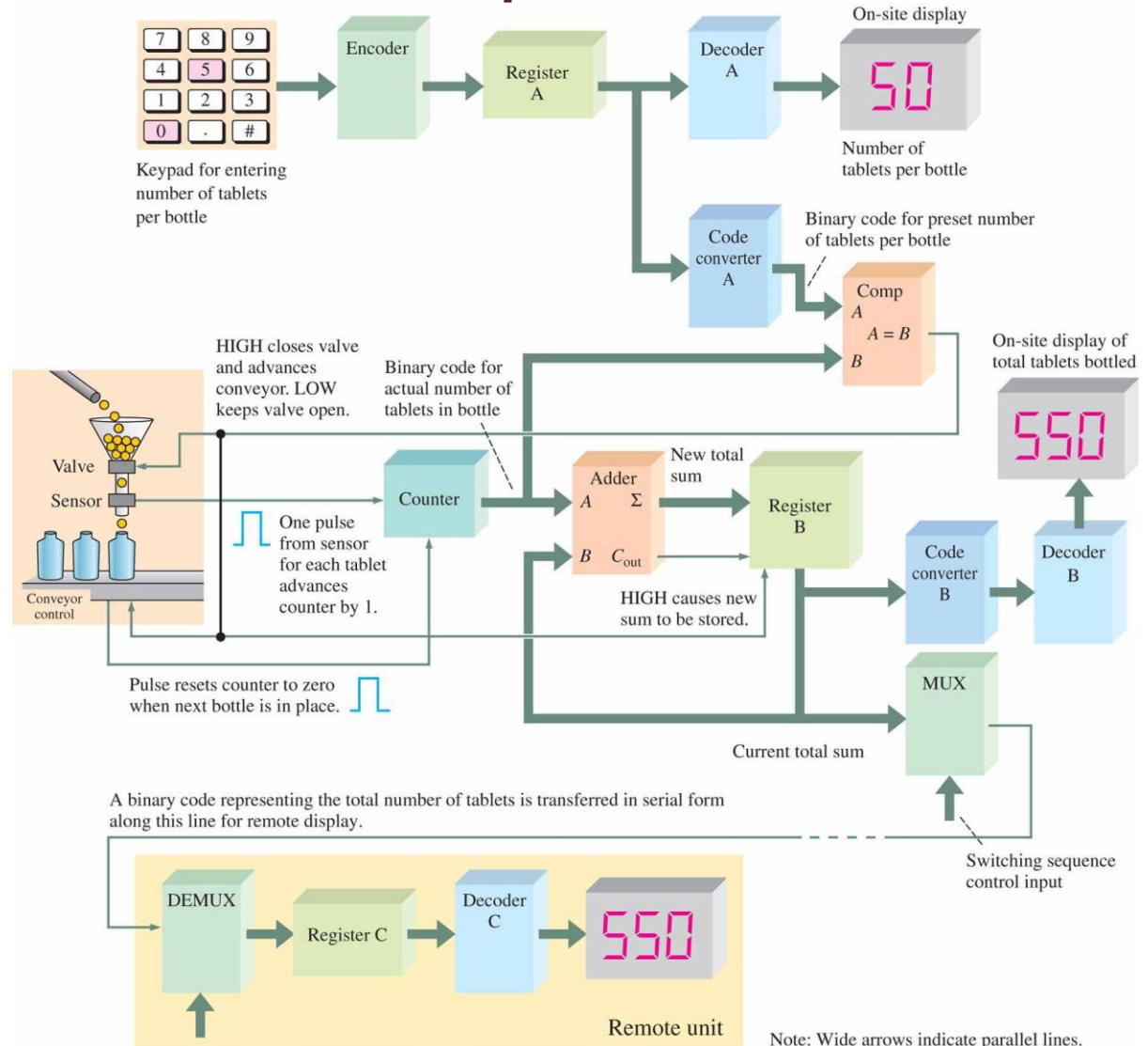
A **digital system** is an arrangement of the individual logic functions connected to perform a specified operation or produce a defined output.



Combinational Building Blocks

- There are several straightforward structures that turn up quite regularly as building blocks in larger systems.

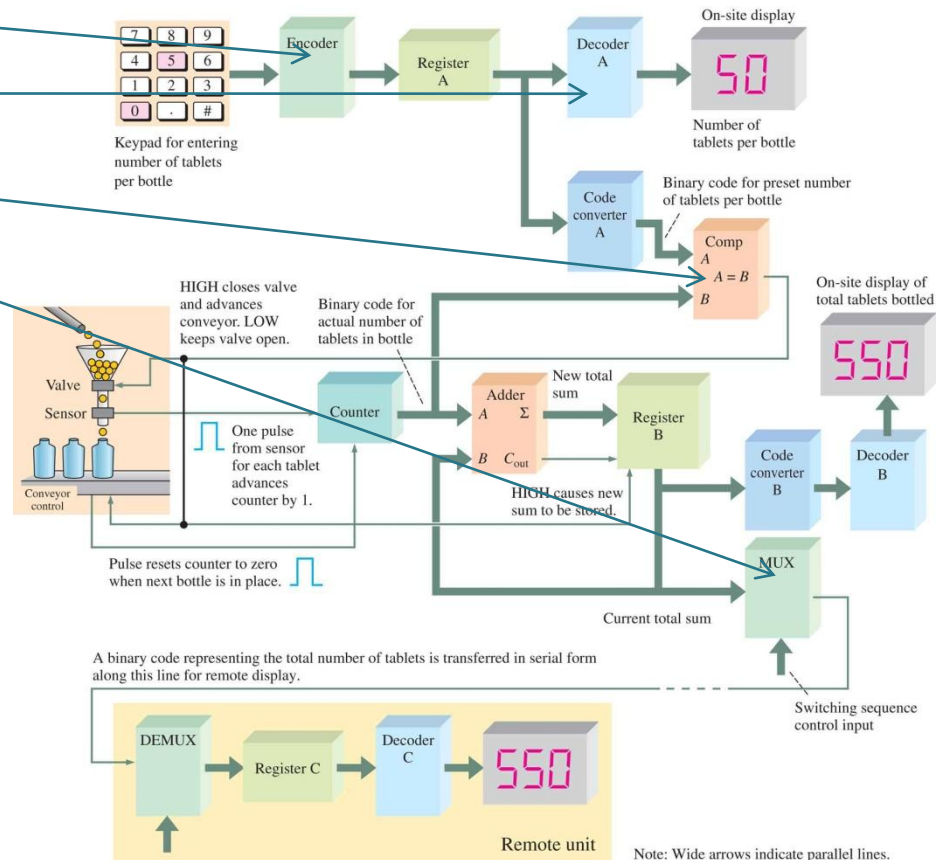- Encoder
- Decoders
- Comparators
- Multiplexers




Where can we find these building blocks?

Fixed-function IC

- An integrated circuit (IC) is an electronic circuit that is constructed entirely on a single small chip of silicon.
- Two broad categories of digital ICs.
 1. Fixed-function logic
 2. Programmable logic
- In **fixed-function logic**, the logic functions are set by the manufacturer and cannot be changed.

Fixed-function IC package

 


Cutaway view of DIP (Dual-In-line Pins) chip

Complexity Classifications


Fixed-function digital ICs are classified according to their complexity.

- **Small-scale integration (SSI)**
 - up to ten equivalent gate circuits on a single chip
 - basic gates and flip-flops.
- **Medium-scale integration (MSI)**
 - from 10 to 100 equivalent gates on a chip.
 - encoders, decoders, counters, registers, multiplexers, arithmetic circuits, small memories
- Large-scale integration (LSI)
- Very large-scale integration (VLSI)
- Ultra large-scale integration (ULSI)


SSI

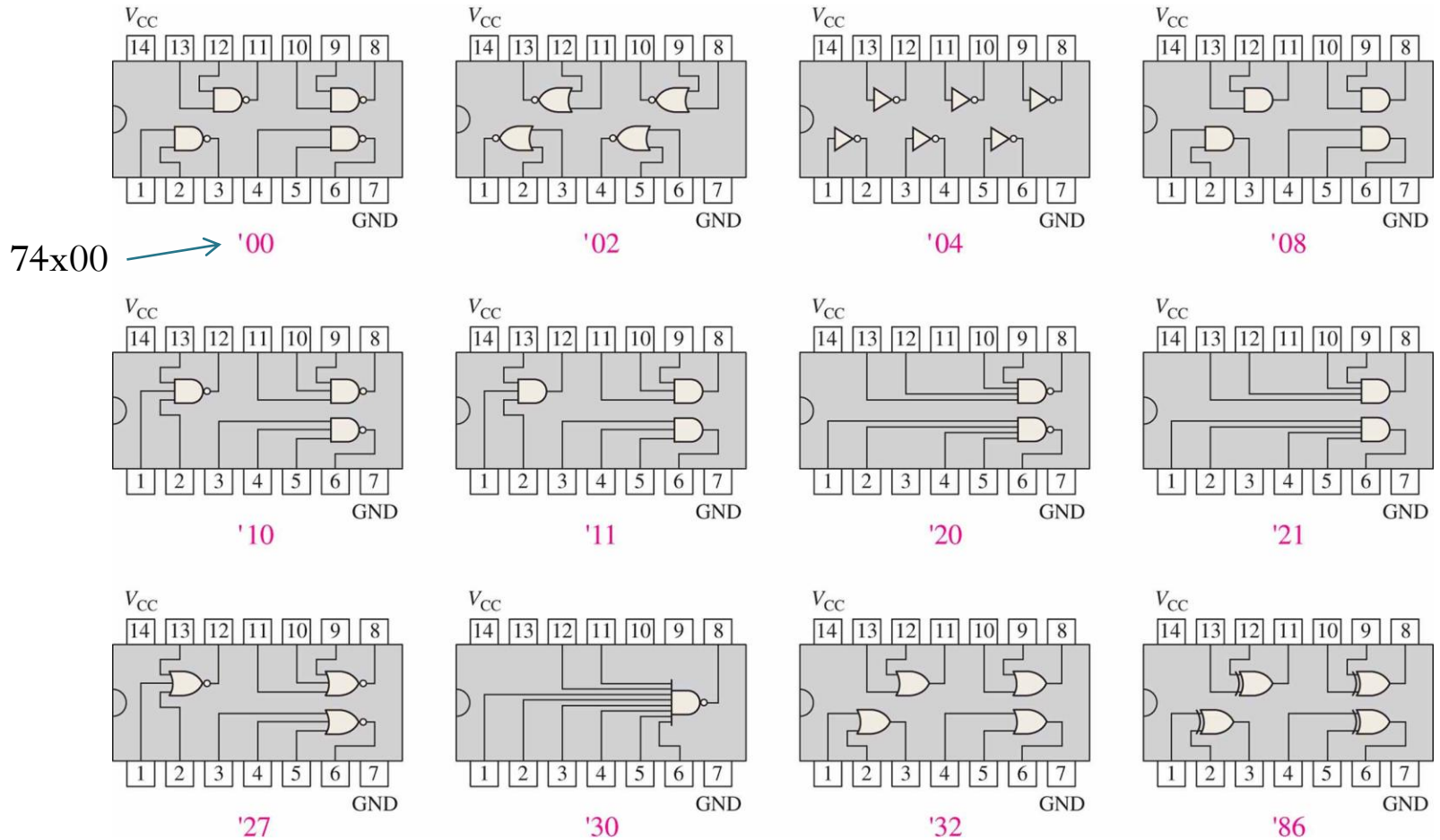


MSI

 


74HC42
BCD-to-decimal decoder

 


74LS47
BCD-to-7-segment decoder/driver

 


74LS85
4-bit magnitude comparator

 


74LS138
3-line-to-8-line decoder

 

74LS139
Dual 2-line-to-4-line decoder

 


74HC147
Decimal-to-BCD priority encoder

 


74LS148
Octal-to-binary encoder

 
For the next couple lectures, we will study most of these 74-series MSI.



 
74LS151
8-input data selector/multiplexer




74HC154
1-of-16-line decoder

 

 74HC157
Quad 2-input data selector/multiplexer















74LS280
9-bit parity generator/checker

 

74LS283
4-bit adder


MSI

            


Simple Decoder

A **decoder** is a logic circuit that detects the presence of a specific combination of bits at its input.

 Two simple decoders that **detect the presence** of the binary code 0011 are shown below. The first has an active HIGH output; the second has an active LOW output.



Active HIGH decoder for 0011

 


Active LOW decoder for 0011

(A_0 is the LSB and A_3 is the MSB)

 
Exercise

Assume the output of the decoder shown below is a logic 1.
What are the inputs to the decoder?




Binary-to-Decimal Decoder

 The binary-to-decimal decoder shown here has 16 outputs – one for each combination of binary inputs.




Application: Port Address Decoder

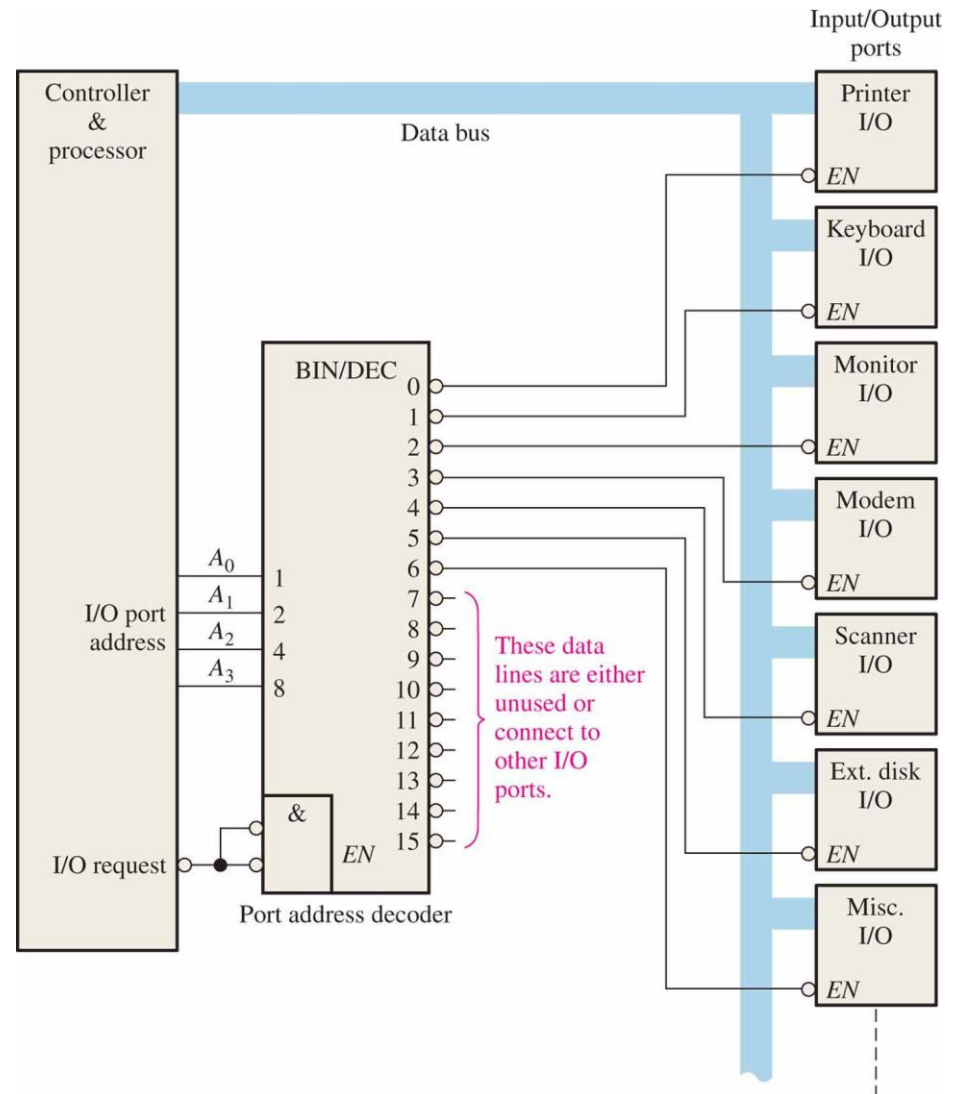- Decoder can be used in computers for input/output selection.
- Computers communicate with peripherals by sending and/or receiving data through what is known as input/output (I/O) ports.
- A decoder can be used to select the I/O port so that data can be sent or received from a specific external device.



2:4 decoder

2-to-4 line decoder with enable input

 

Inputs			Outputs			
E	I1	I0	Y3	Y2	Y1	Y0
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Exercise

Find the truth table of the 1-to-2 line decoder below.


Then, implement the 1-to-2 line decoder.



74x139: Dual 2:4 Decoder

Most MSI decoders were originally designed with active-LOW output.

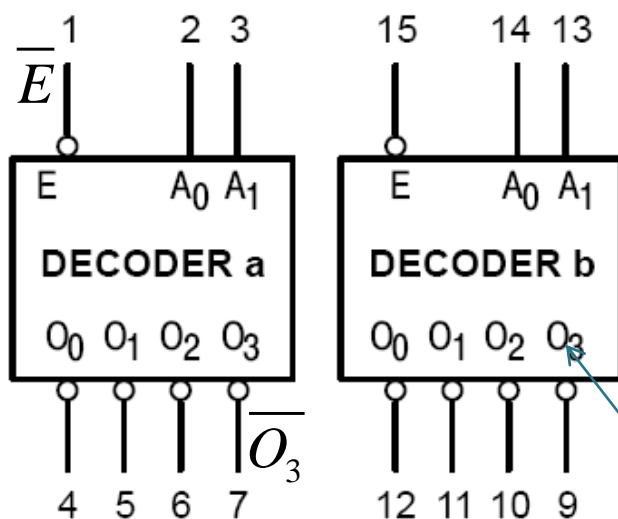- Two independent 2:4 decoders
- The outputs and the enable (E) input are active-LOW.
- When *E* is HIGH all outputs are forced HIGH.





V_{CC} = PIN 16
GND = PIN 8

INPUTS			OUTPUTS			
E	A ₀	A ₁	O ₀	O ₁	O ₂	O ₃
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	H	L	H	L	H	H
L	L	H	H	H	L	H
L	H	H	H	H	H	L


Notice that all of the signal names inside the symbol outline are active-HIGH, and that bubbles indicate active-LOW inputs and outputs.

74x139

 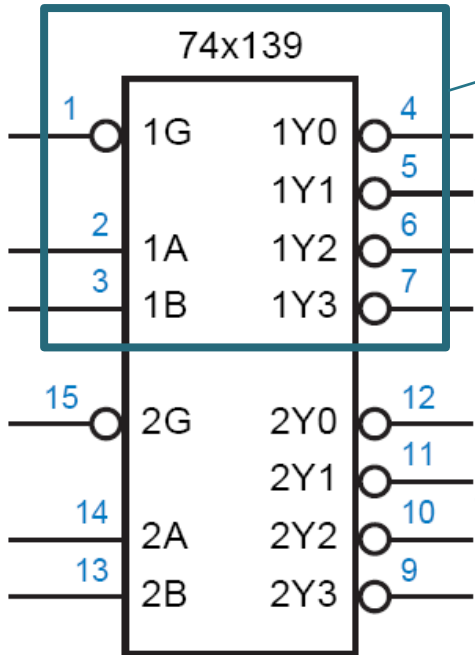


<i>Inputs</i>			<i>Outputs</i>			
G_L	B	A	Y3_L	Y2_L	Y1_L	Y0_L
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

74x139: Logic diagram

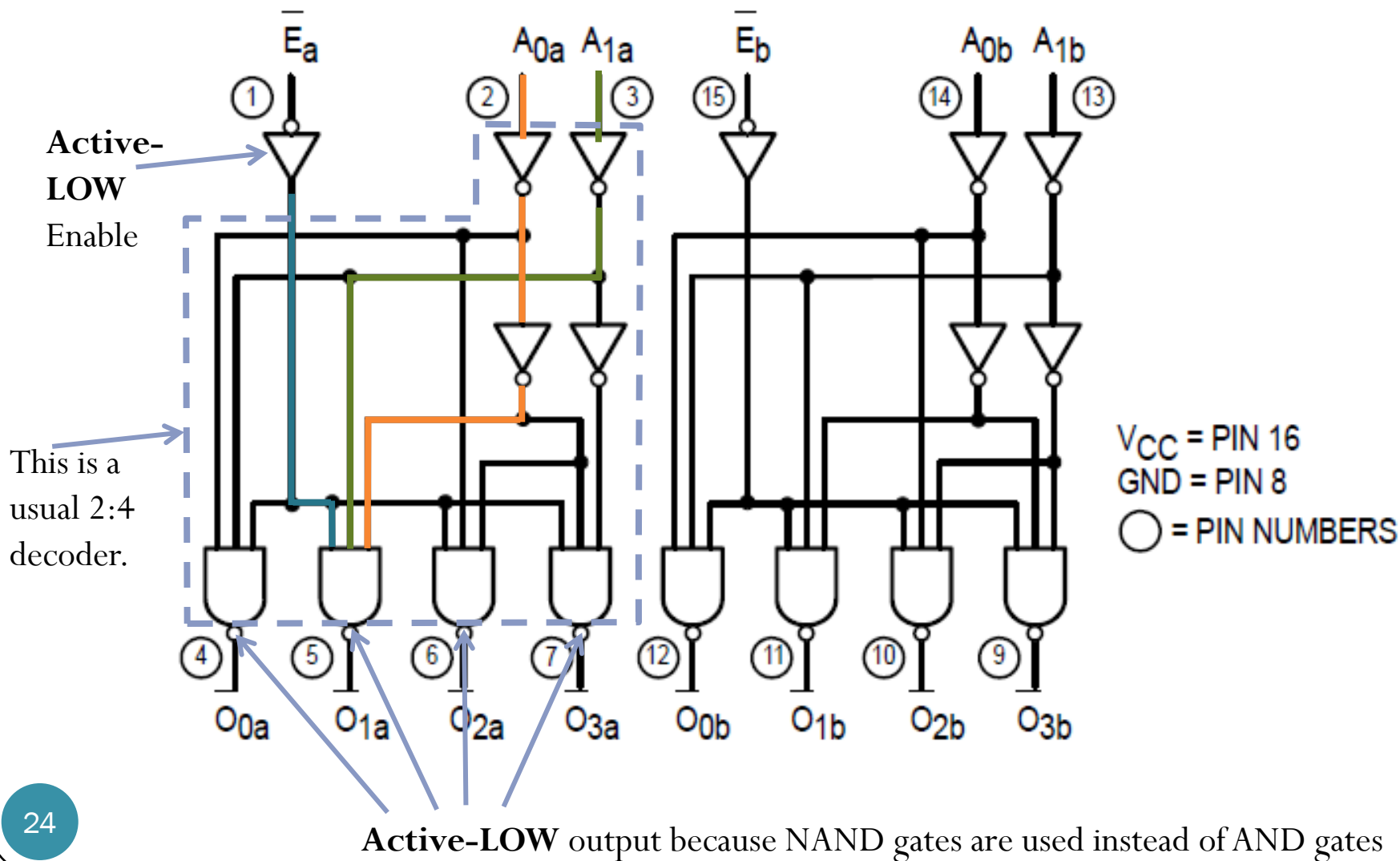

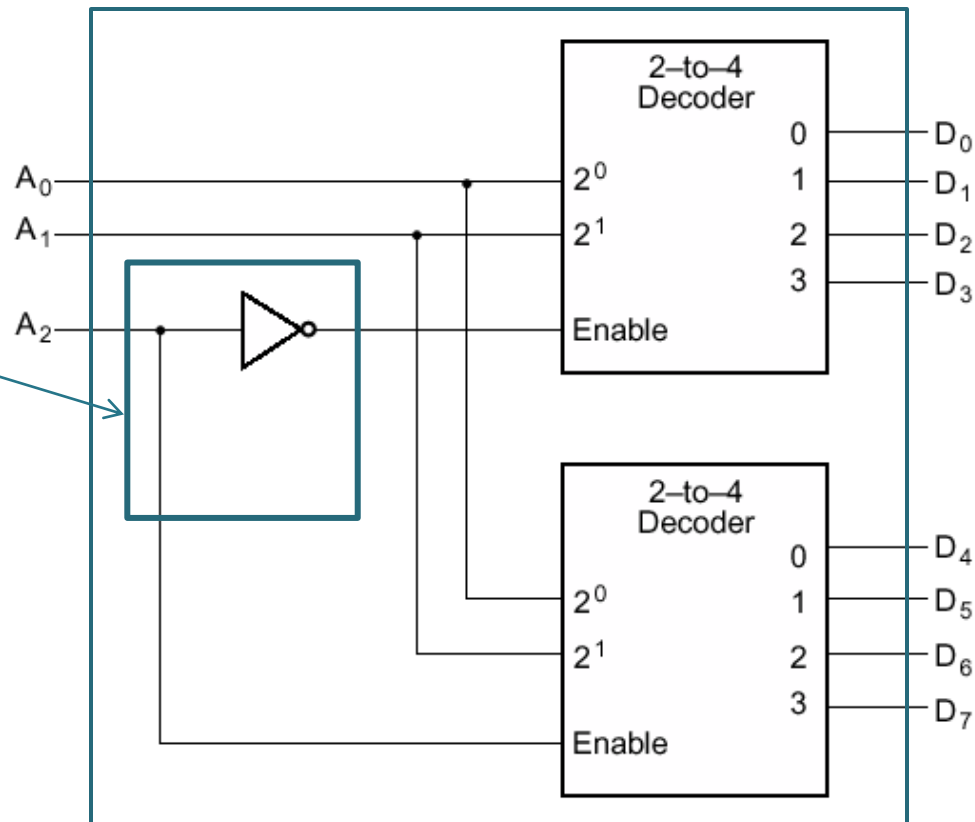Example: Building a larger decoder

Construct a 3-to-8 decoder from two 2-to-4 decoders



Notice that this part is equivalent to a 1:2 decoder.

How can we add an active-HIGH enable input?


Low order bits (A_1, A_0) select within decoders. High order bit (A_2) controls which decoder is active.

Building larger decoder from smaller ones

- To construct $(k+n)$ -to- 2^{n+k} decoders, can use
 1. 2^n of k -to- 2^k decoders with enable input and
 2. one n -to- 2^n decoders.
- The connections are:
 - For each of the k -to- 2^k decoder with enable input,
 - all have k input
 - we put in $A_0 \dots A_{k-1}$.
 - The enable line of the r^{th} decoder is connected to D_r of the n -to- 2^n decoders.
 - The inputs of the n -to- 2^n decoder get A_k to A_{n+k-1} .
- Basically, each k -to- 2^k decoder works on the last k bits.
- We use the first n bit, via the n -to- 2^n decoder, to select which one (and only one) of the k -to- 2^k decoders will be enabled.

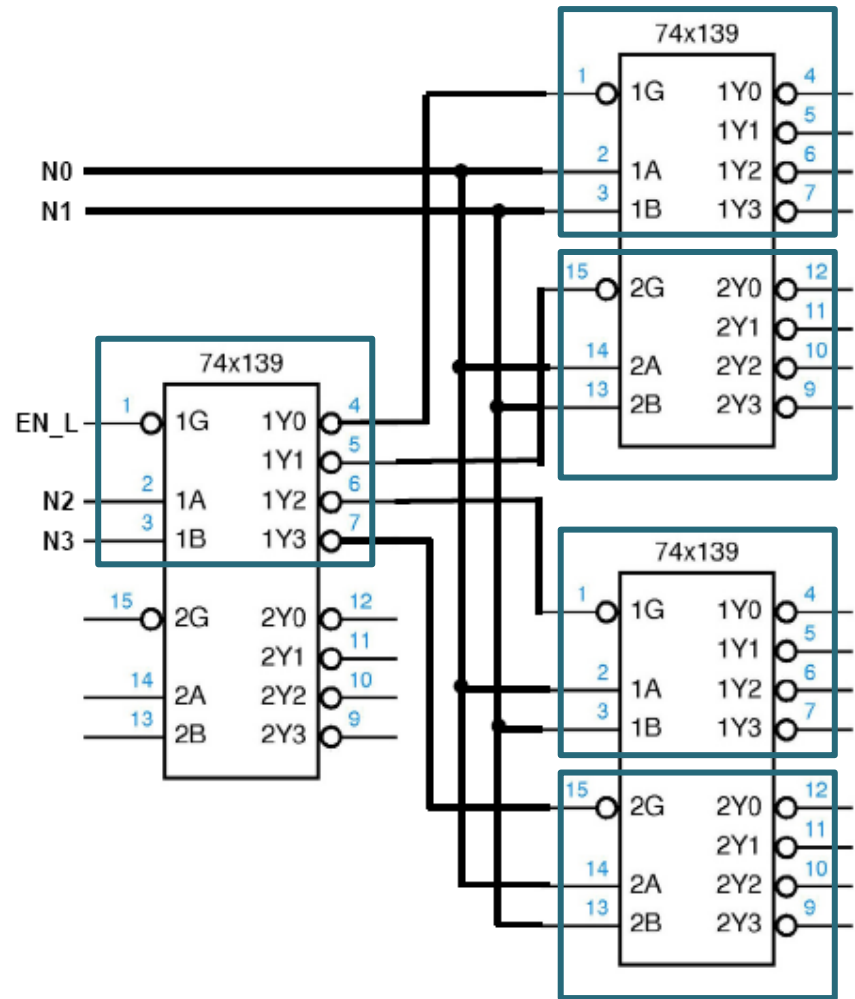
Example

Construct a 4:16 decoder with an active-LOW enable from three 2:4 decoders.



74x138: 3:8 Decoder

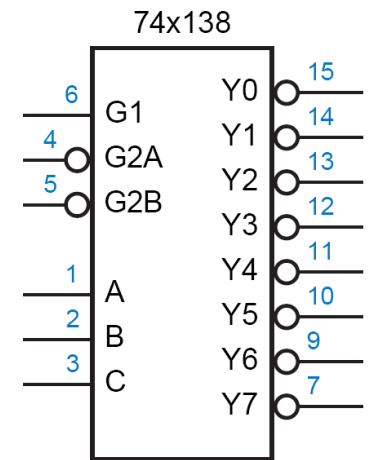
- Active-LOW outputs
- Three enable inputs.



<i>Inputs</i>						<i>Outputs</i>							
G1	G2A_L	G2B_L	C	B	A	Y7_L	Y6_L	Y5_L	Y4_L	Y3_L	Y2_L	Y1_L	Y0_L
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1

 
Example

Construct a 4:16 decoder with an active-LOW enable (EN) from two 74x138 decoders.




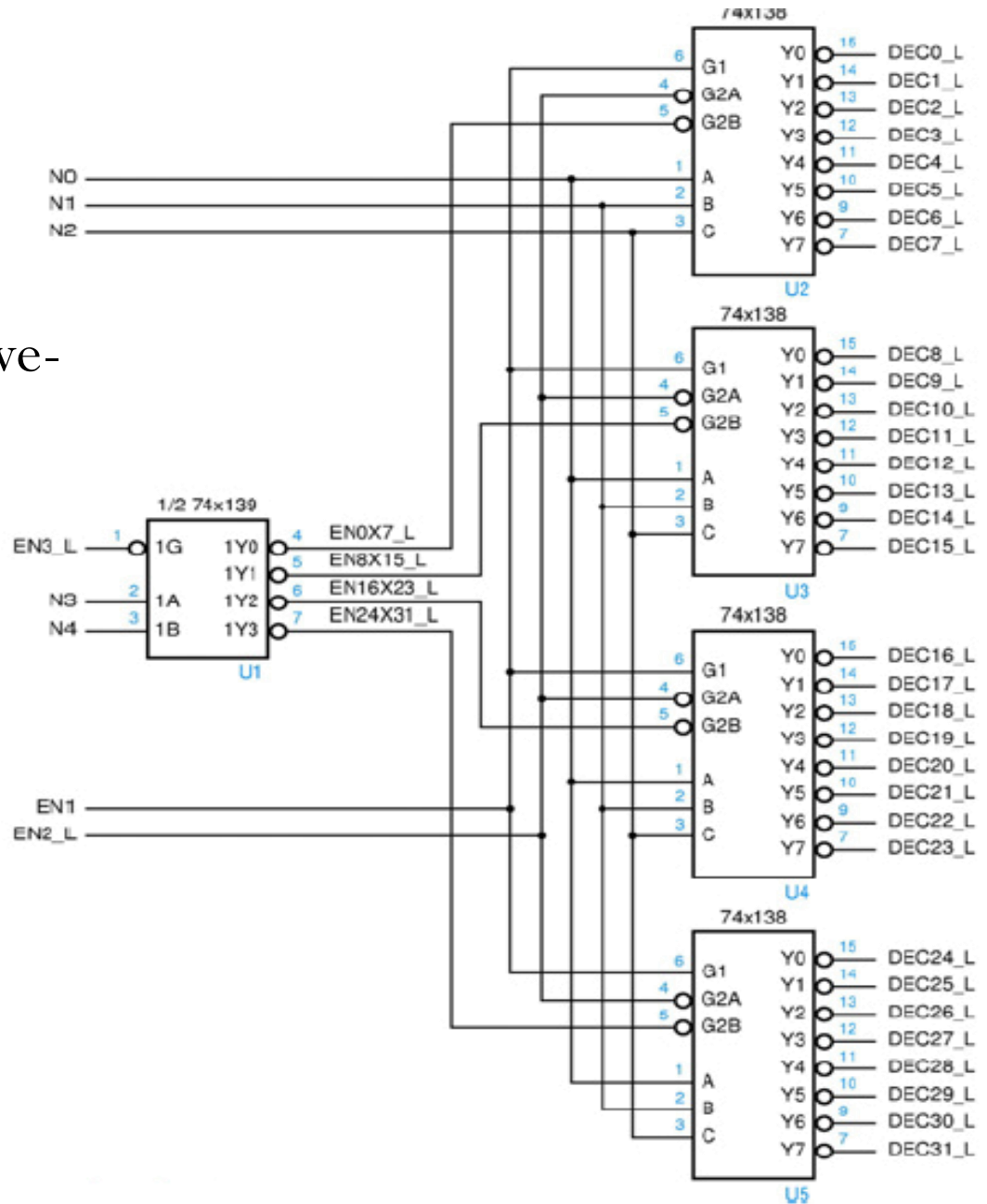Example


Construct a 5:32 decoder with two active-low enable and one active-high enable from four 74x138 and one 74x139.



74x154: 4:16 Decoder

 


(a) Pin diagram

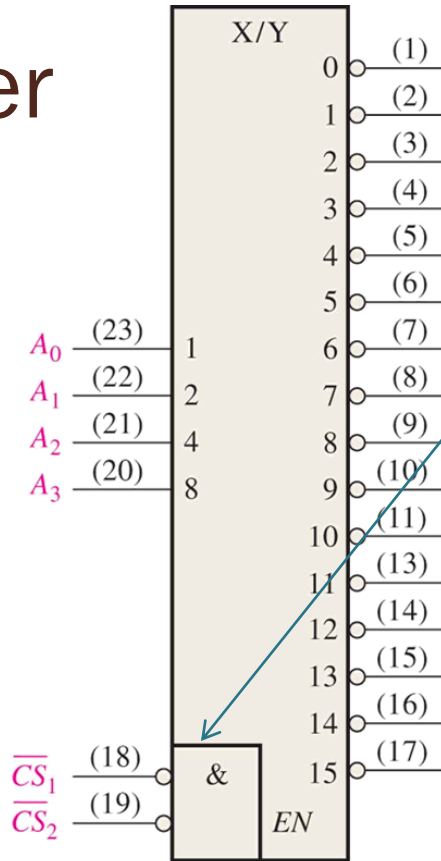

(b) Logic symbol


A LOW level on each chip select input is required to make the **enable** gate output (EN) HIGH.

Alternative logic symbol

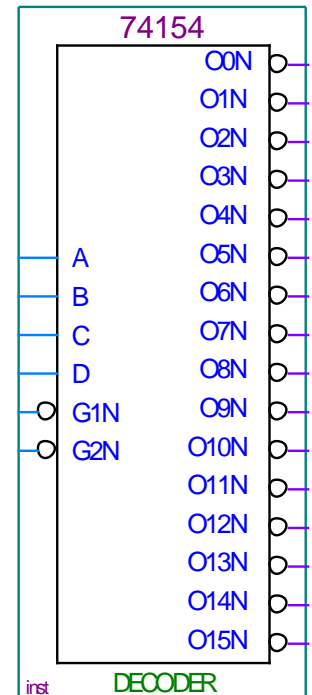

Include two **active-LOW** chip select (CS) lines which must be at the active level to enable the outputs. These lines can be used to expand the decoder to larger inputs.


5:32 Decoder

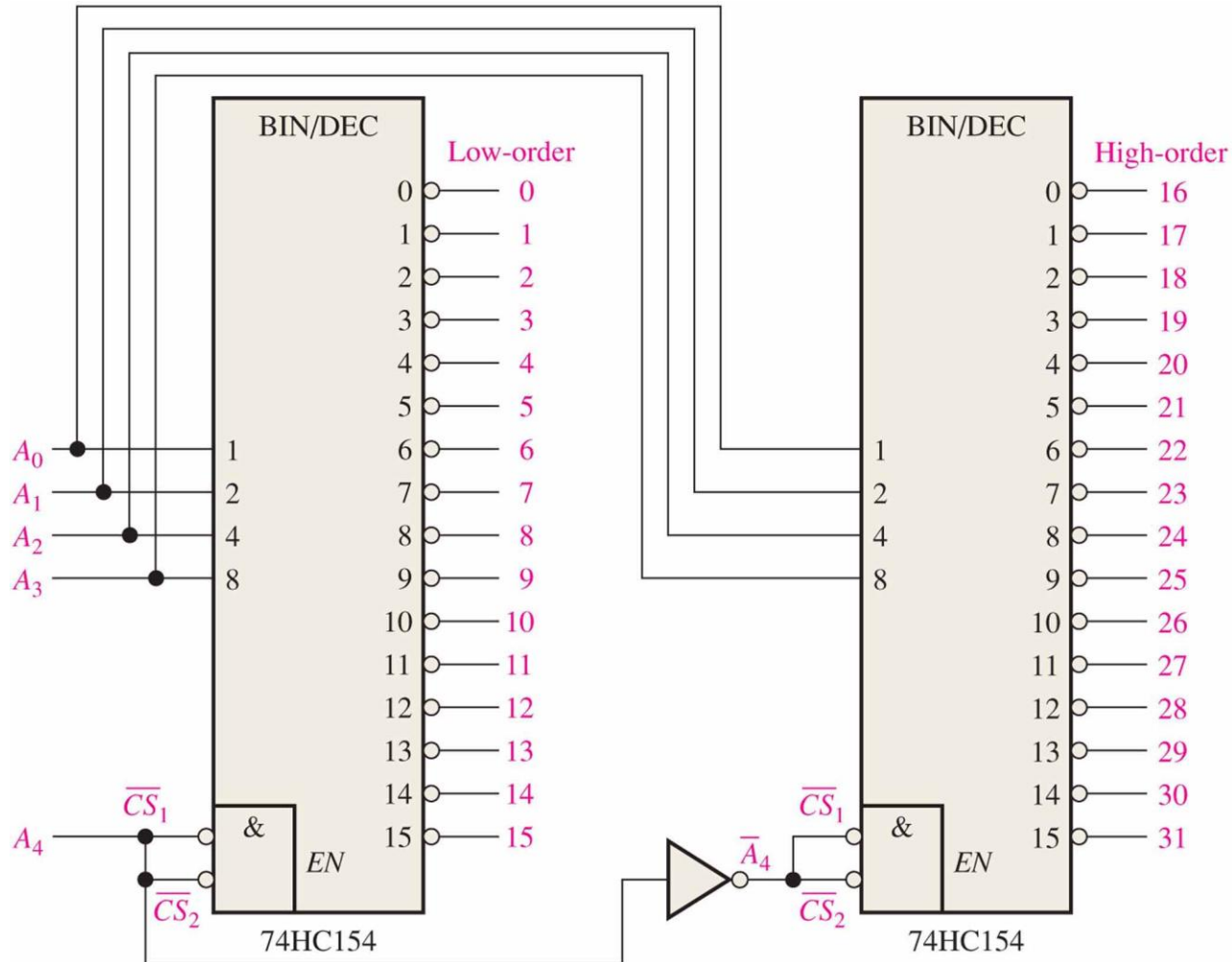

Decoder as general purpose logic

Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n -line decoder and m OR gate

 Observe that the 3:8 decoder generates all possible minterms.




Example

Implement a full adder circuit with a decoder and OR gates

- $S = \sum_{X,Y,Z}(1,2,4,7)$
- $C = \sum_{X,Y,Z}(3,5,6,7)$

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

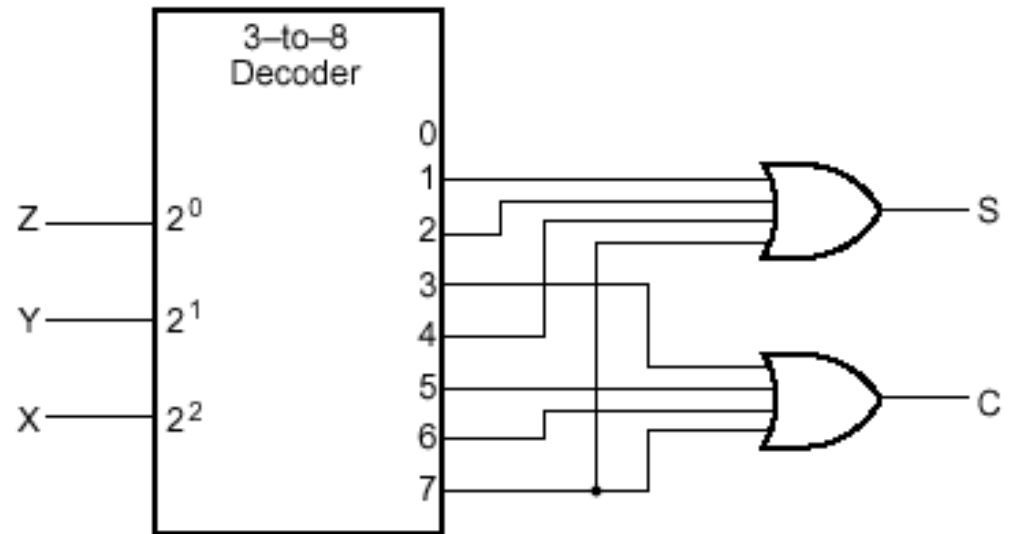

Other Decoders

In general, a decoder converts coded information, such as binary number, into non-coded form.

Later, (if time permitted) we will talk about other types of decoder.

