

Digital Circuits

ECS 371

Dr. Prapun Suksompong

prapun@siit.tu.ac.th

Lecture 12

Office Hours:

BKD 3601-7

Monday 9:00-10:30, 1:30-3:30

Tuesday 10:30-11:30


ECS371.PRAPUN.COM

Announcement

- No new HW.
- Reading Assignment
 - Chapter 6: 6-5, 6-8, 6-9

Review: BIN/DEC Decoder

 
- Many output lines.
- Only one of the output line is asserted at any time.
- To find out which output line is asserted, consider the inputs as one binary number. Convert this binary number to a decimal number. This decimal number tells which output line is asserted by the inputs.



Truth Tables of Basic Decoder


2:4 DEC

Input		Output			
I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

3:8 DEC


Input			Output							
A_2	A_1	A_0	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

 

Decoder Expansion

How can we build a larger decoder from smaller ones?

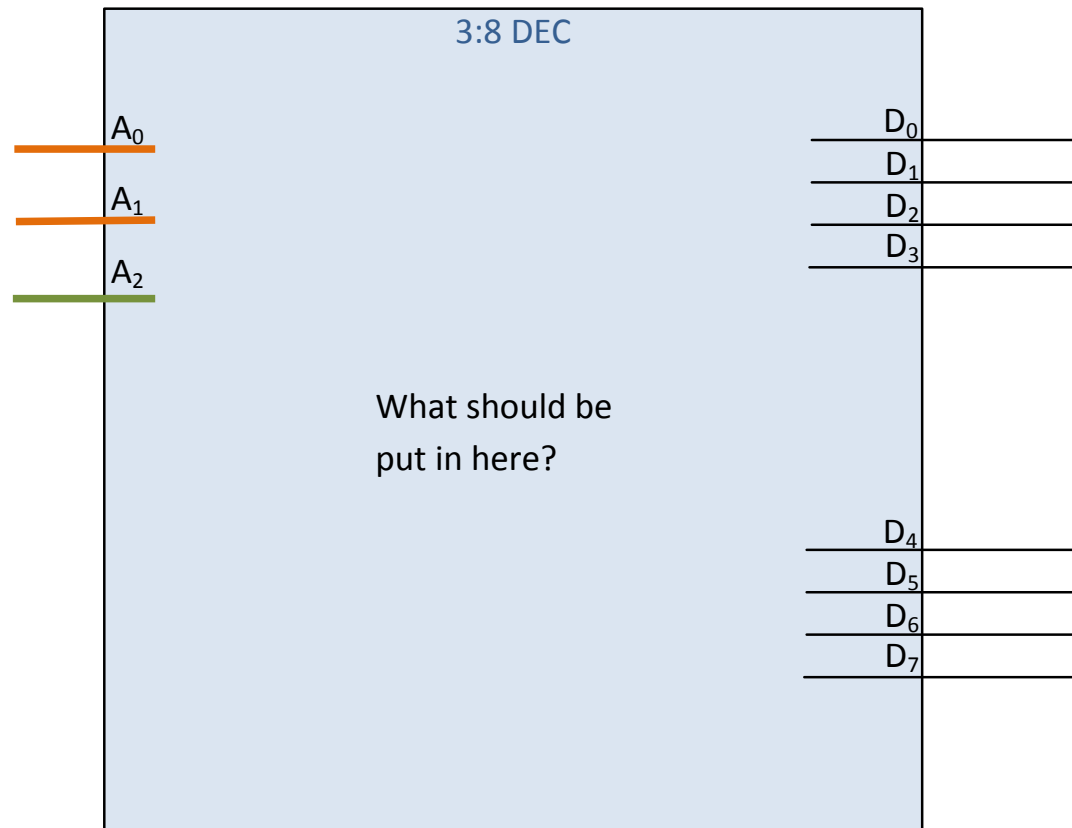
Construct a 3-to-8 decoder from two 2-to-4 decoders



Decoder Expansion

How can we build a larger decoder from smaller ones?

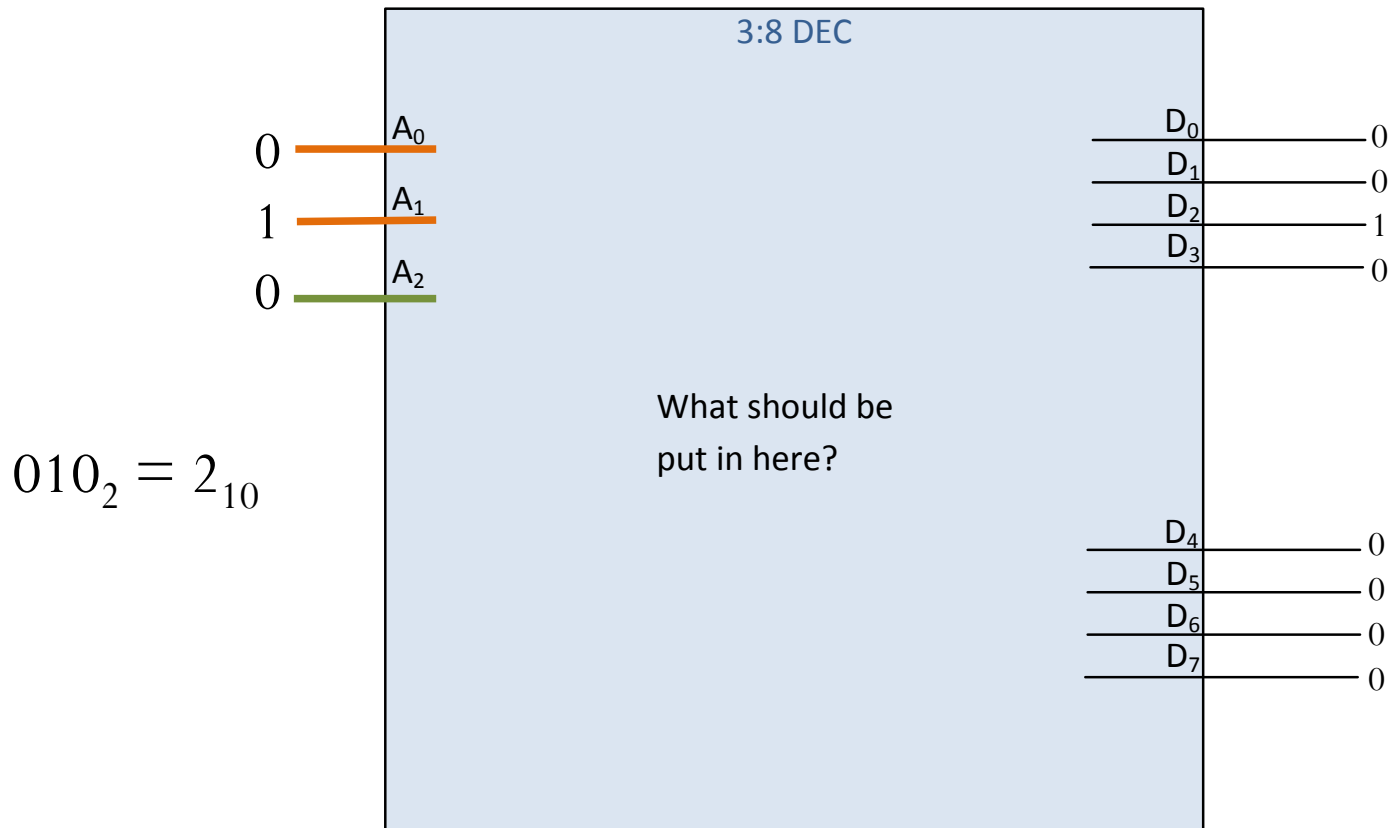
Construct a 3-to-8 decoder from two 2-to-4 decoders



Decoder Expansion

How can we build a larger decoder from smaller ones?

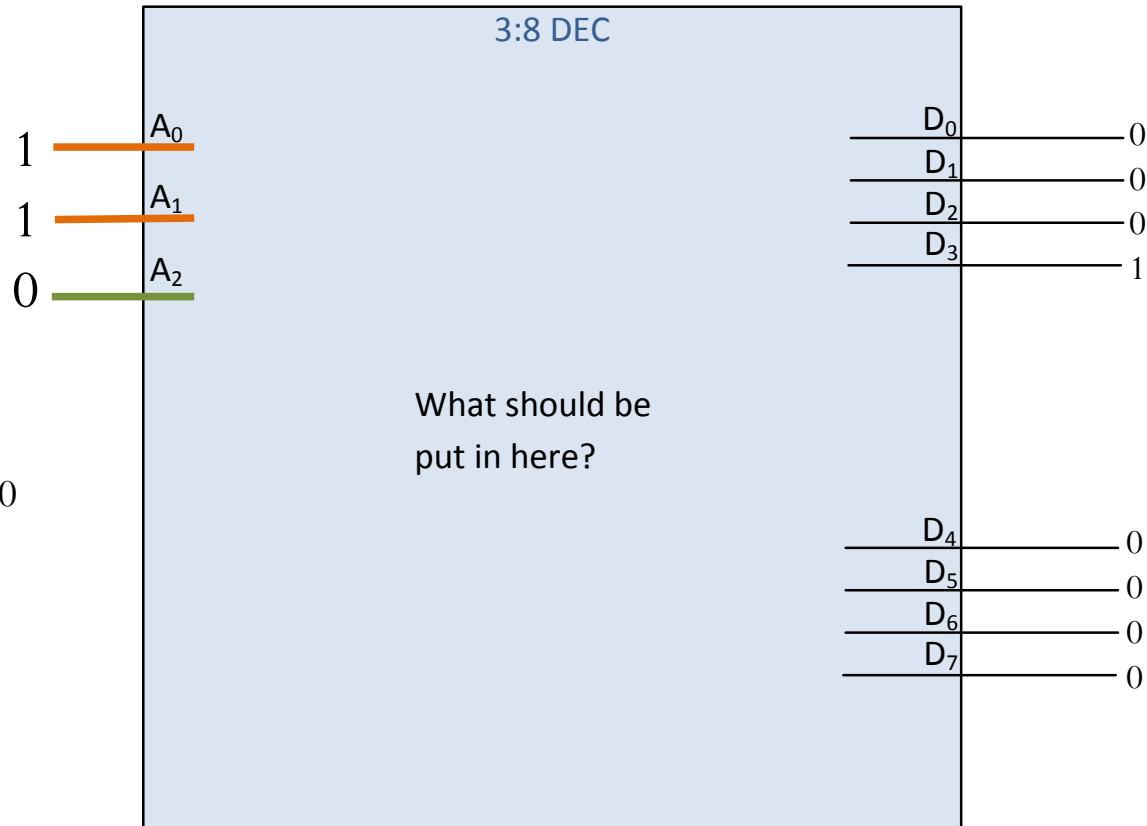Construct a 3-to-8 decoder from two 2-to-4 decoders




$$011_2 = 3_{10}$$

Decoder Expansion

How can we build a larger decoder from smaller ones?

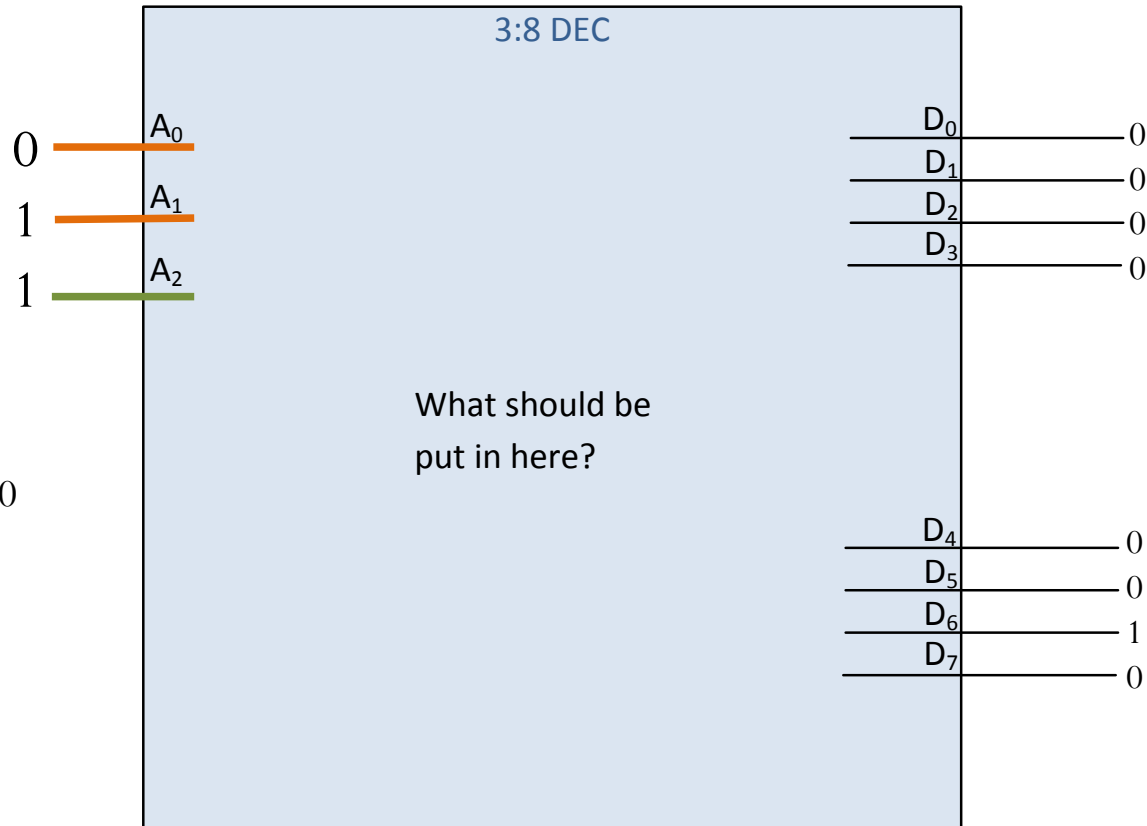Construct a 3-to-8 decoder from two 2-to-4 decoders




$$110_2 = 6_{10}$$

Decoder Expansion

How can we build a larger decoder from smaller ones?

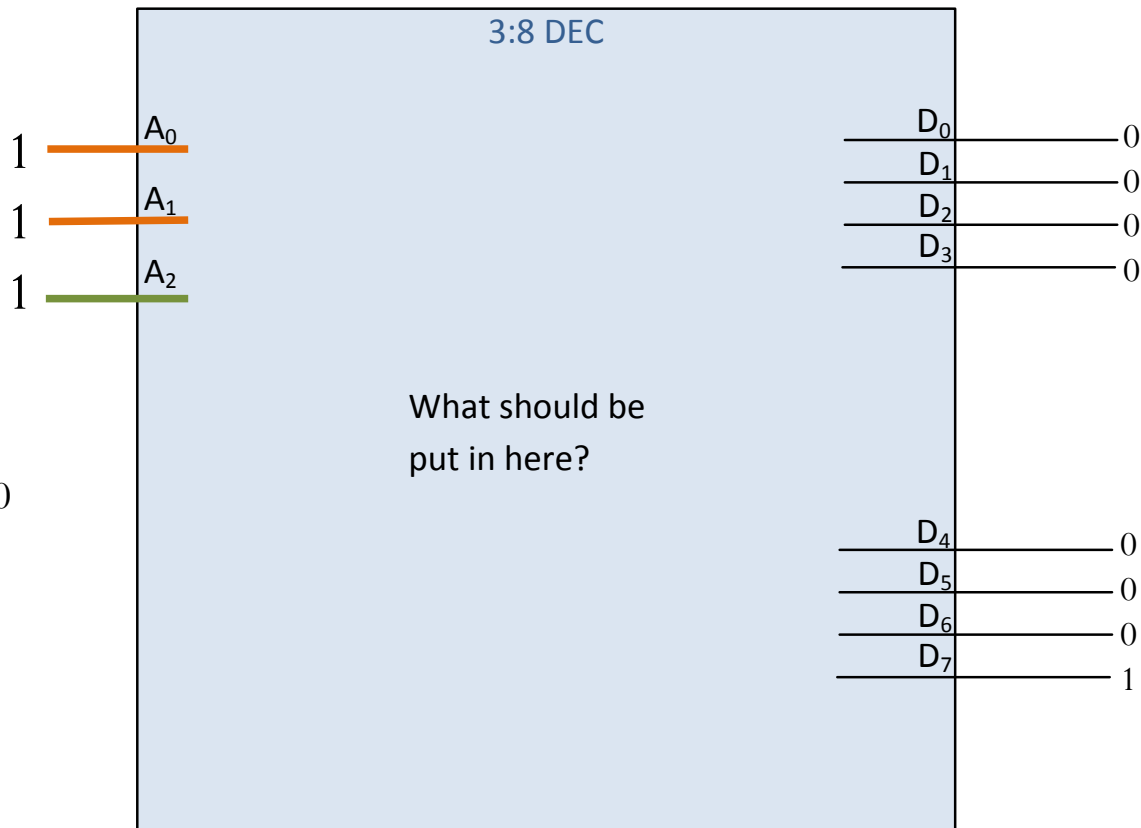Construct a 3-to-8 decoder from two 2-to-4 decoders



$$111_2 = 7_{10}$$

Decoder Expansion

Construct a 3-to-8 decoder from two 2-to-4 decoders:

Observe that the truth table of the 3:8 DEC contains two truth tables of the 2:4 DEC.

3:8 DEC

Input			Output							
A ₂	A ₁	A ₀	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

2:4 DEC


Input		Output			
I ₁	I ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Two large areas of 0s (negated)

These areas correspond to A₂.


Decoder Expansion

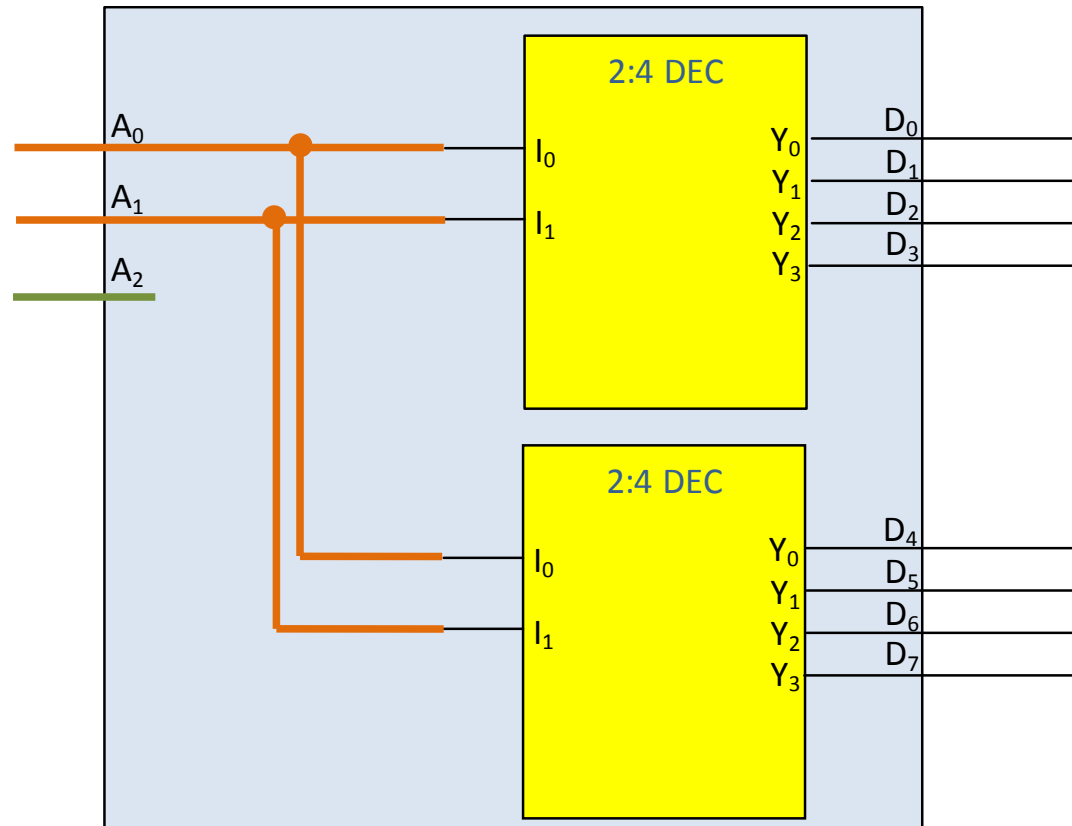Construct a 3-to-8 decoder from two 2-to-4 decoders:




Decoder Expansion

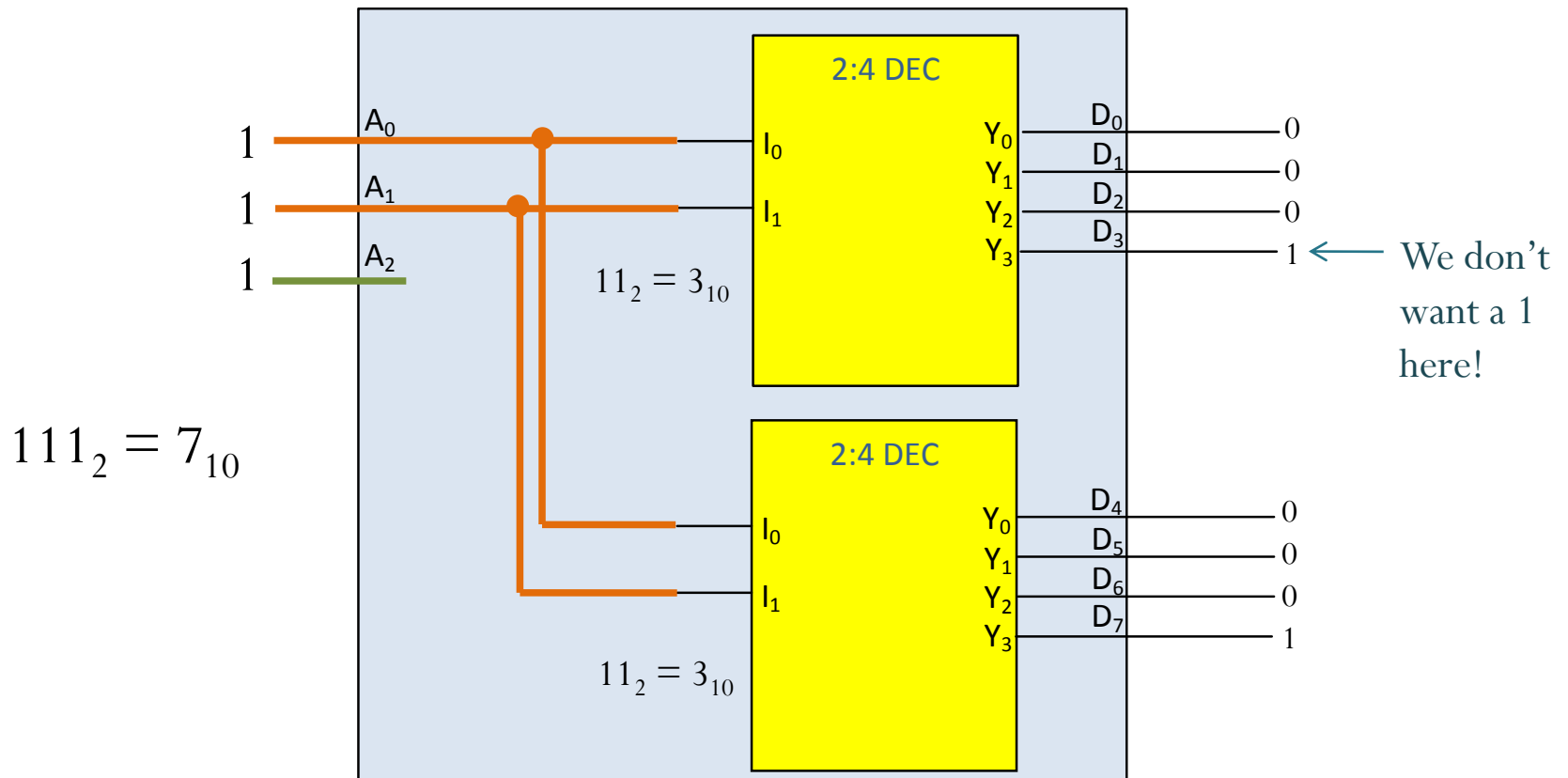Construct a 3-to-8 decoder from two 2-to-4 decoders:




Decoder Expansion

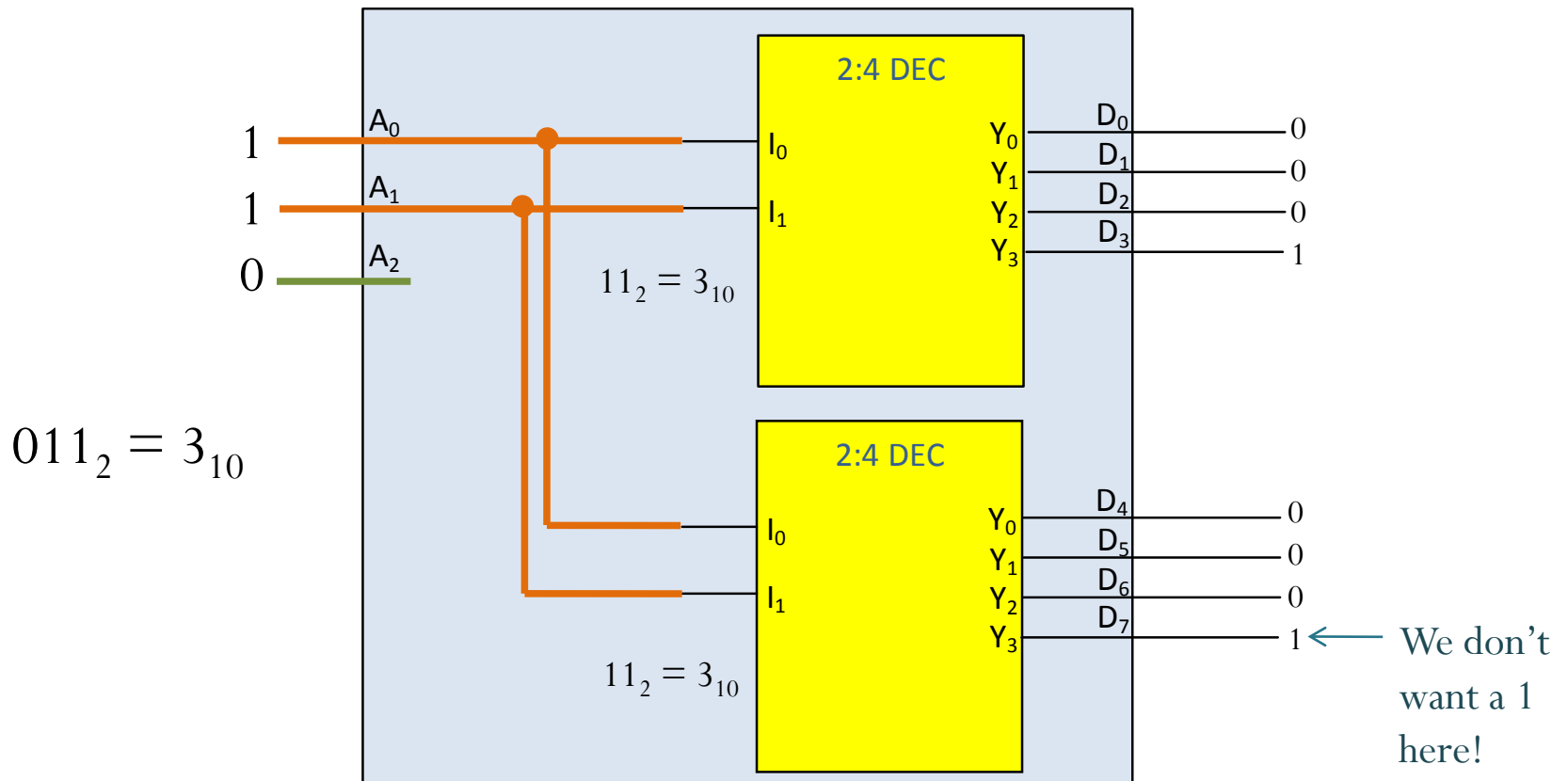Construct a 3-to-8 decoder from two 2-to-4 decoders:




Decoder Expansion

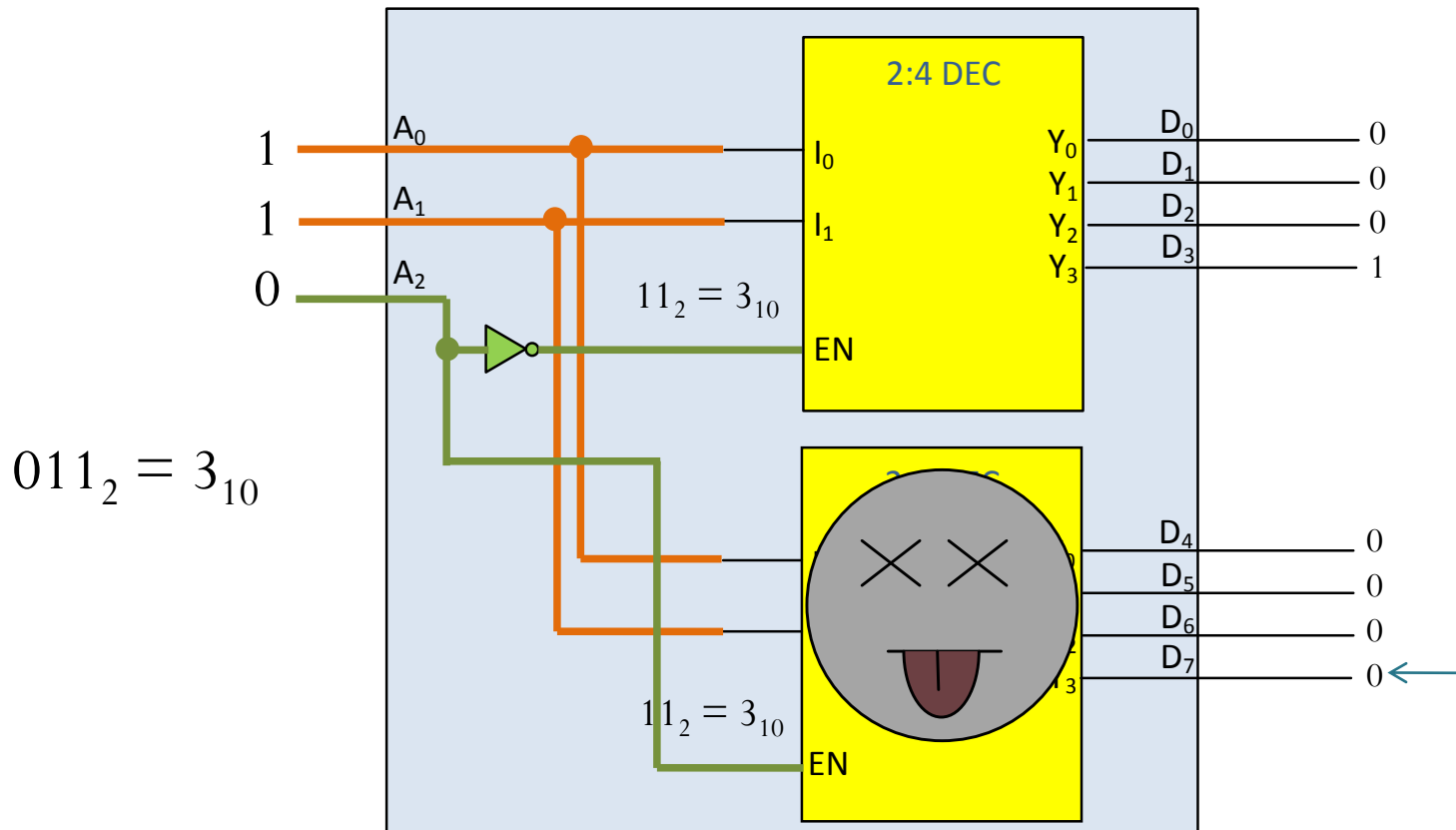A_2 is connected to the EN of each 2:4 decoder to choose the 1 that we want.



Decoder Expansion

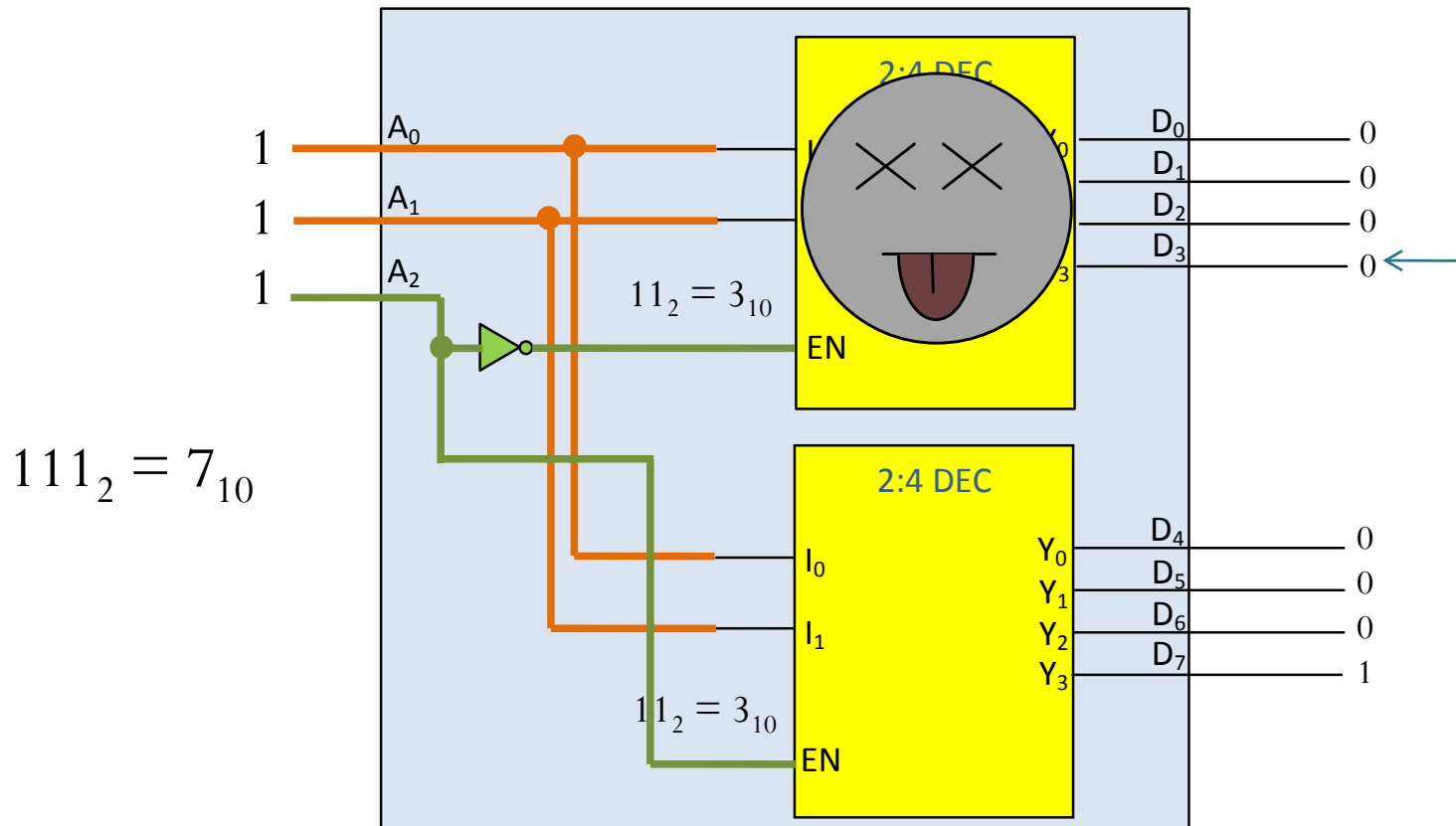A_2 is connected to the EN of each 2:4 decoder to choose the 1 that we want.




Decoder Expansion: Summary

- To increase the input by one bit (2:4 to 3:8)
 - Use two smaller decoders.
 - Connect the lower significant bits to both decoders.
 - Use the MSB to control which decoder is enabled.
- To increase the input by two bits (2:4 to 4:16)
 - Start with four smaller decoders.
 - Connect the lower significant bits to all four decoders.
 - Use the two higher significant bits to control which decoder is enabled.

Example

Construct a 4:16 decoder with an active-LOW enable from three 74x139.


Four 2:4 DEC in this column.

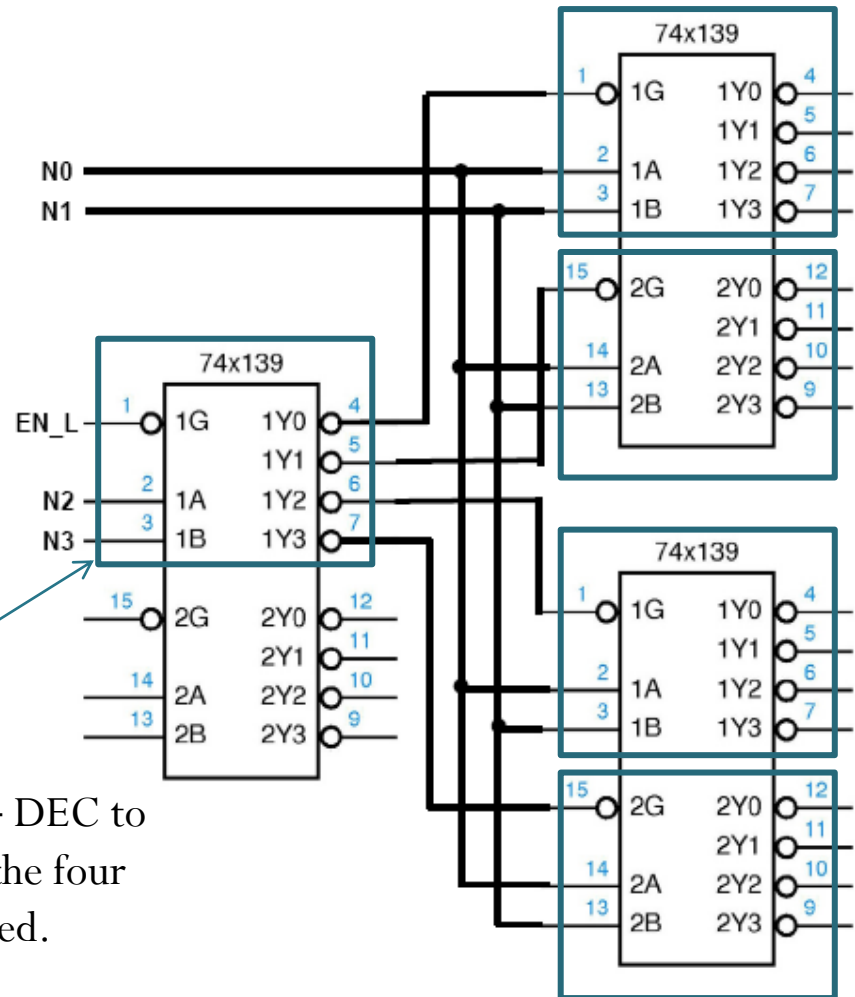

Use one more 2:4 DEC to control which of the four decoders is enabled.

74x138: 3:8 Decoder

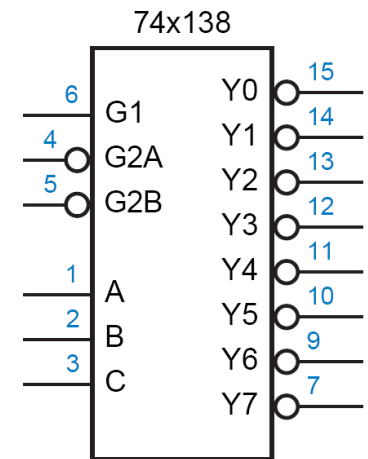- Active-LOW outputs
- Three enable inputs.




Inputs						Outputs							
G1	G2A_L	G2B_L	C	B	A	Y7_L	Y6_L	Y5_L	Y4_L	Y3_L	Y2_L	Y1_L	Y0_L
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1

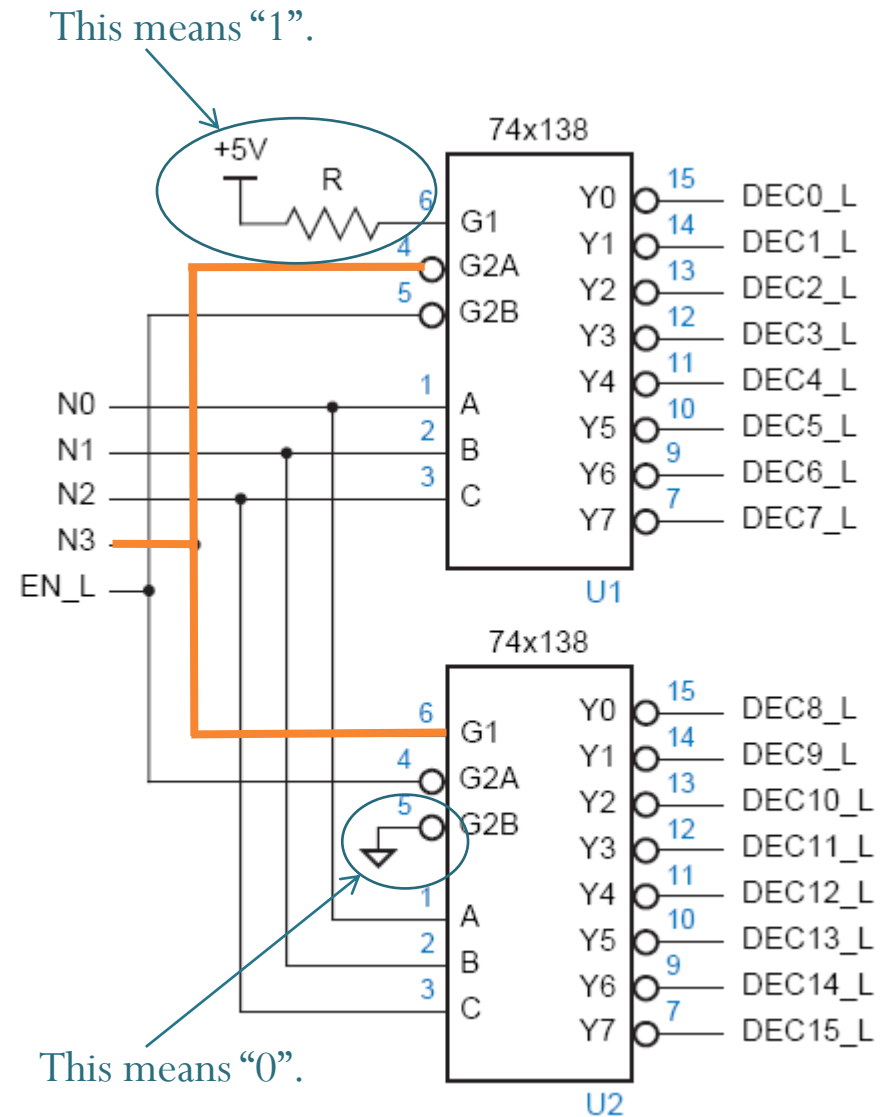Example


Construct a 4:16 decoder with an active-LOW enable (EN) from two 74x138 decoders.

Because the 74x138 have both active-LOW EN and active-HIGH EN, we can use the extra bubble to replace the extra NOT gate.



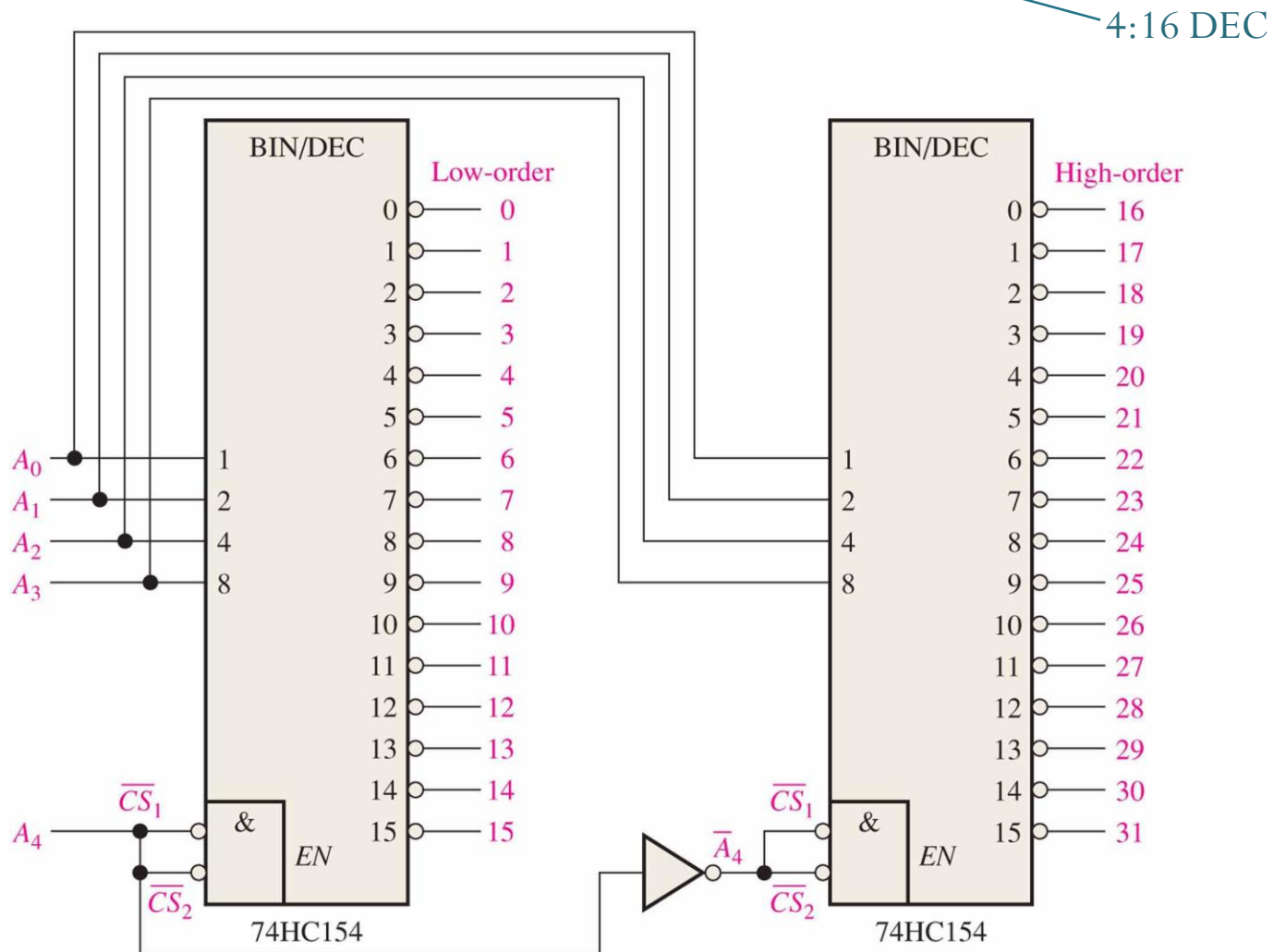Example


Construct a 5:32 decoder with active-LOW outputs from two 74x154 and one inverter.




(Midterm: July 30!)

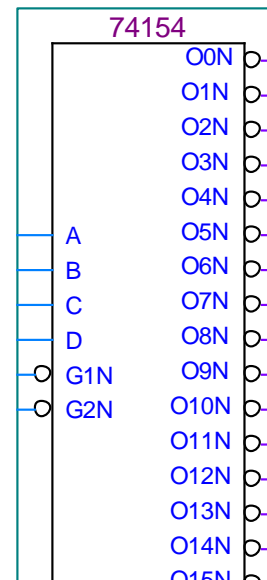Exercise (Sample Exam Problem)

- Construct a 5:32 decoder with active-LOW outputs and one active-LOW EN.
- Use two 74x154 and one inverter.




Solution

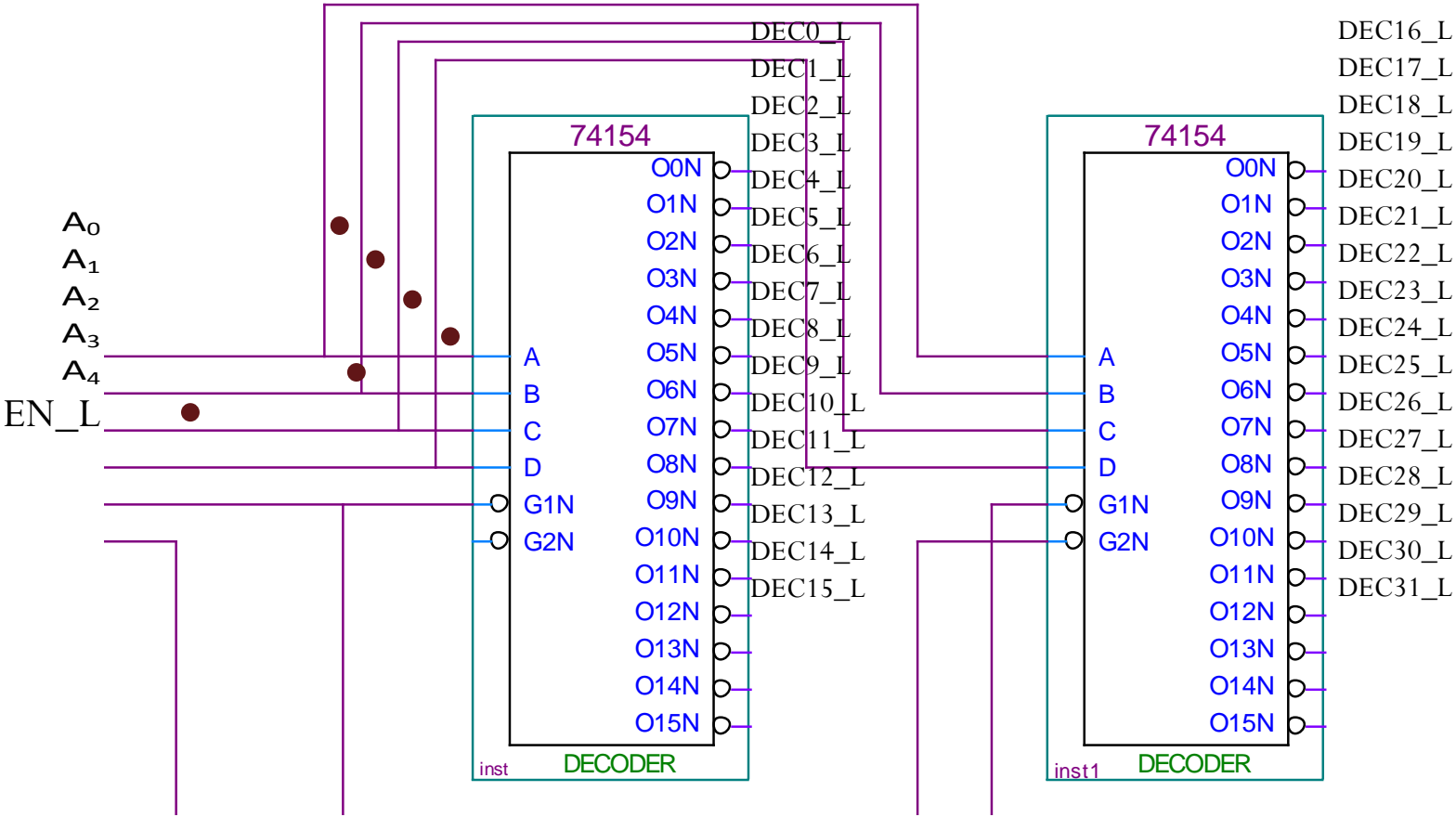

Decoder as General Purpose Logic

Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n -line decoder and m OR gate

 Observe that the 3:8 decoder generates all possible minterms.




Example

Implement a full adder circuit with a decoder and OR gates

- $S = \sum_{X,Y,Z}(1,2,4,7)$
- $C = \sum_{X,Y,Z}(3,5,6,7)$

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

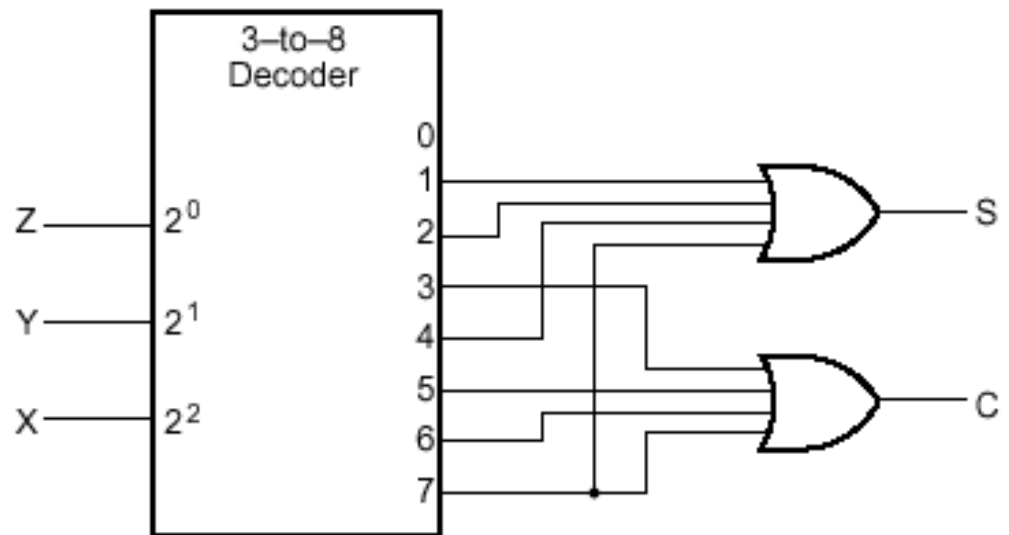


Note: If the decoder's output is active-LOW, then we use NAND gates instead of the OR gates.

Other Decoders


In general, a decoder converts coded information, such as binary number, into non-coded form.

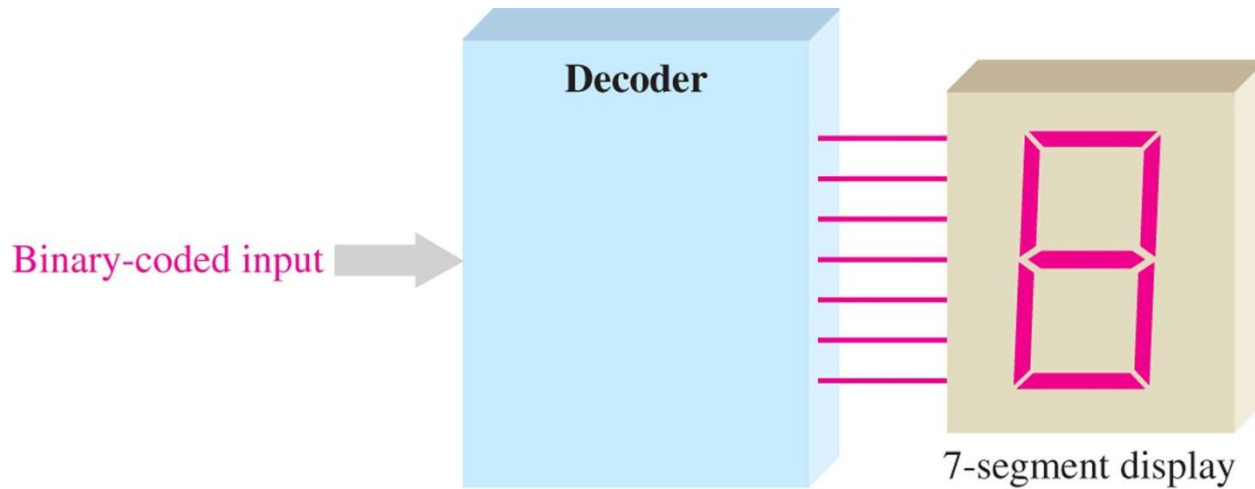Later, (if time permitted) we will talk about other types of decoder.




Multiplexing/Demultiplexing

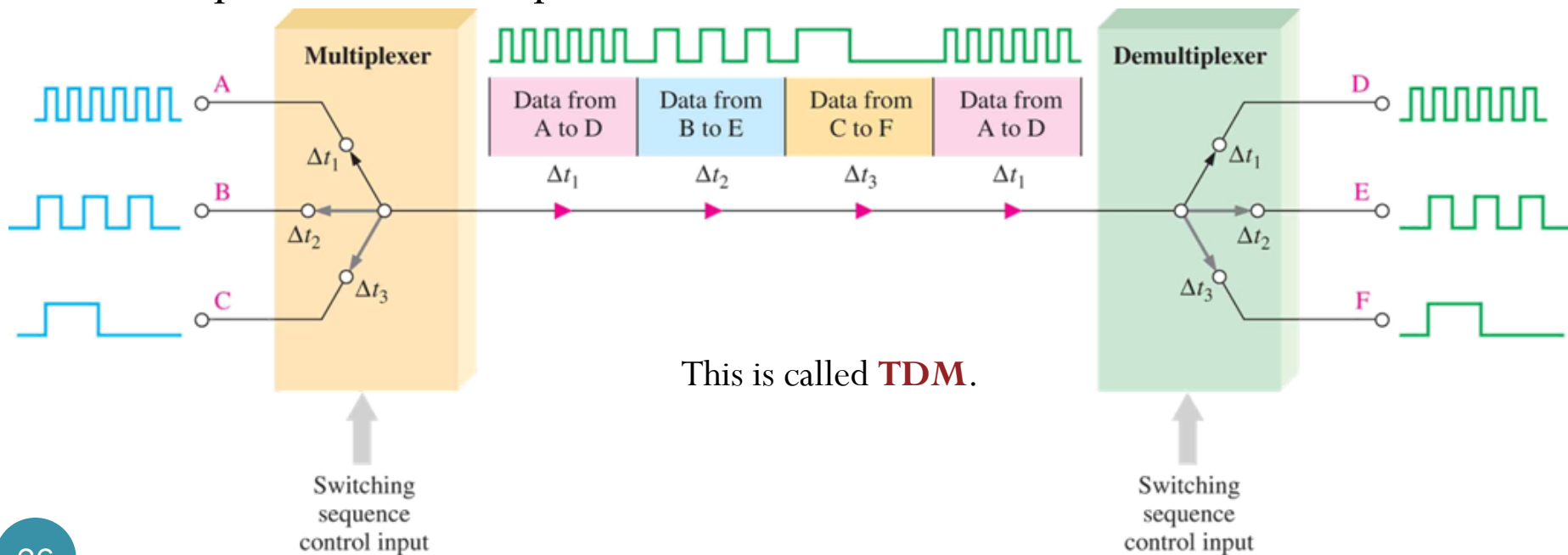- The **multiplexer**, or **mux** for short, is a logic circuit that switches digital data from several input lines onto a single output line in a specified time sequence.
- The **demultiplexer (demux)** is a logic circuit that switches digital data from one input line to several output lines in a specified time sequence




Multiplexer (Data Selector)

 
- Select binary information from one of many input lines and directs the information to a single output line.
- Allow digital information from several sources to be routed onto a single line for transmission over that line to a common destination.
- Basic multiplexer has
 1. Data-input lines
 2. Single output line.
 3. Data-select (control) inputs





Example: 4-to-1-line multiplexer

 

4:1 MUX: Logic Diagram & Truth Table

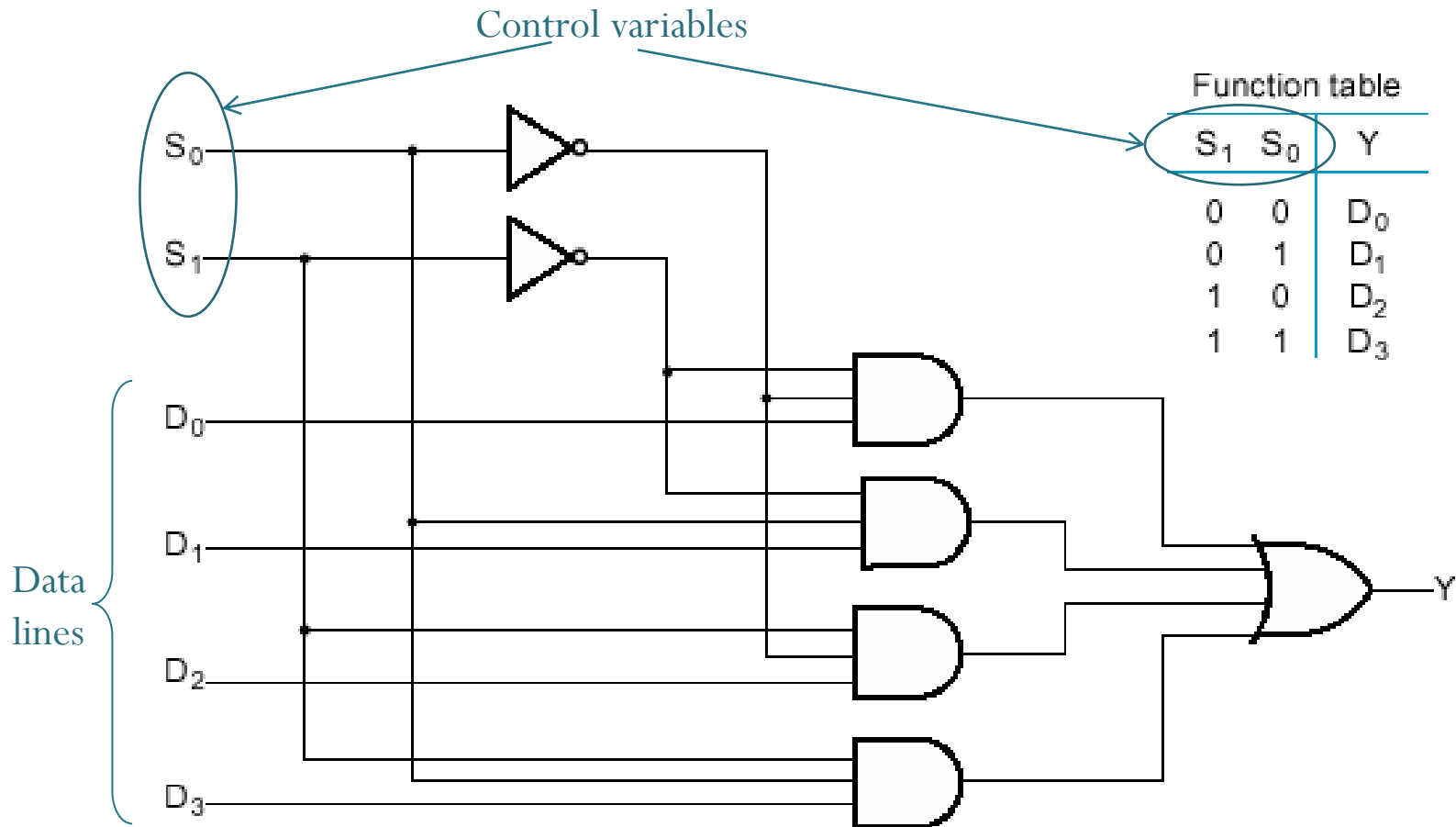


Example

  


Multiplexer Expansion

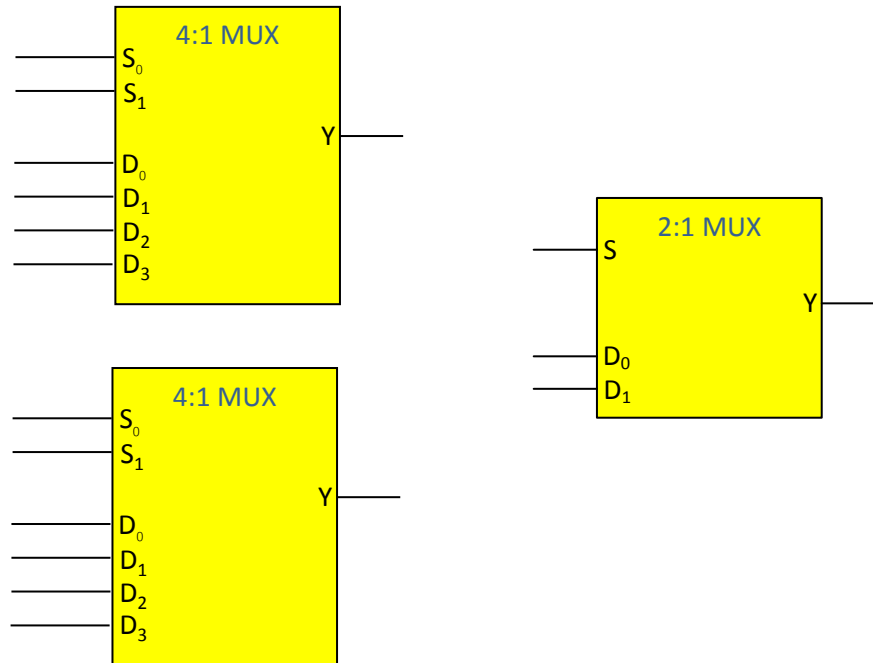Use two 4:1 MUXs and one 2:1 to create 8:1 MUX.




Multiplexer Expansion

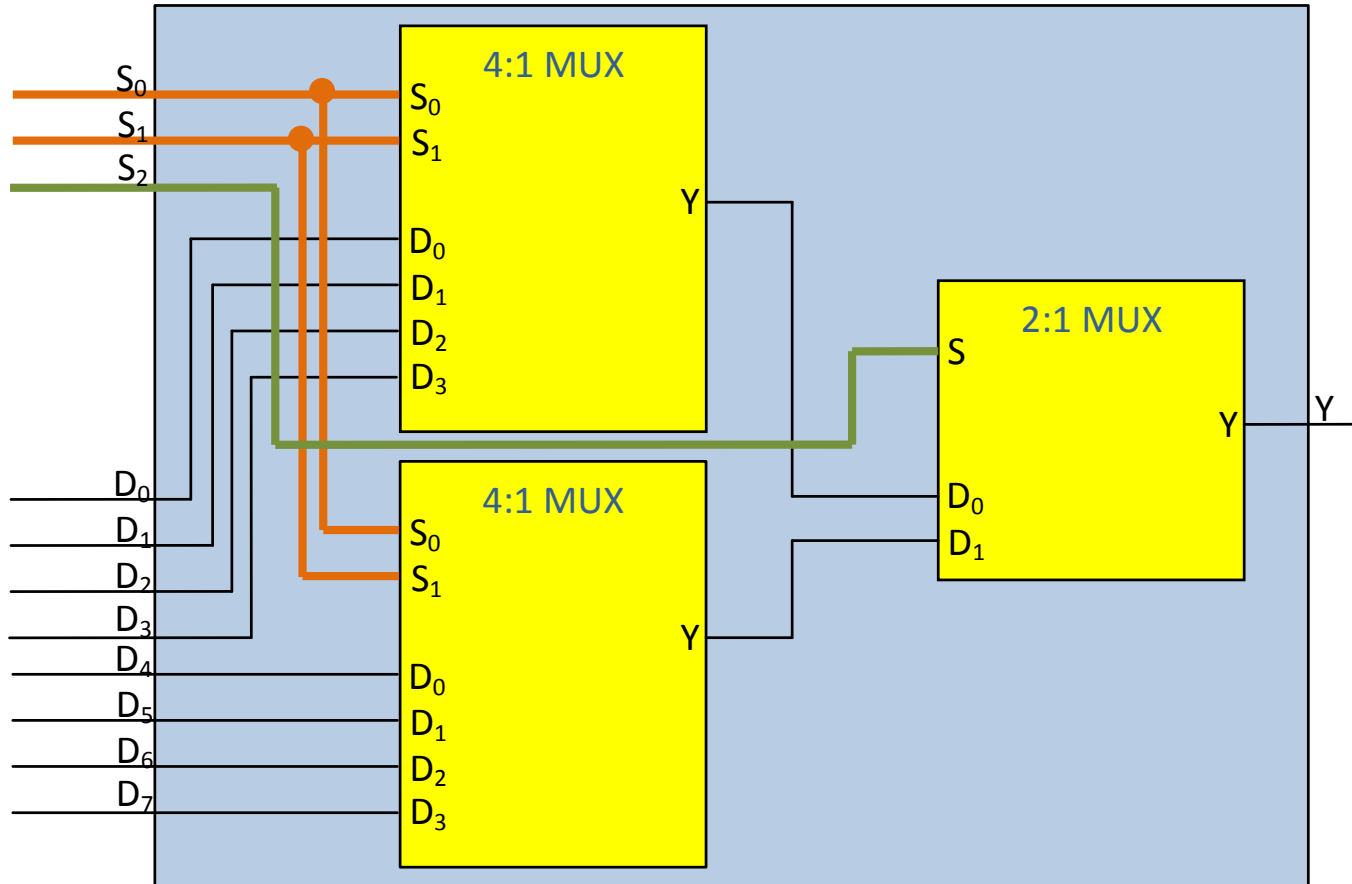


Multiplexer Expansion

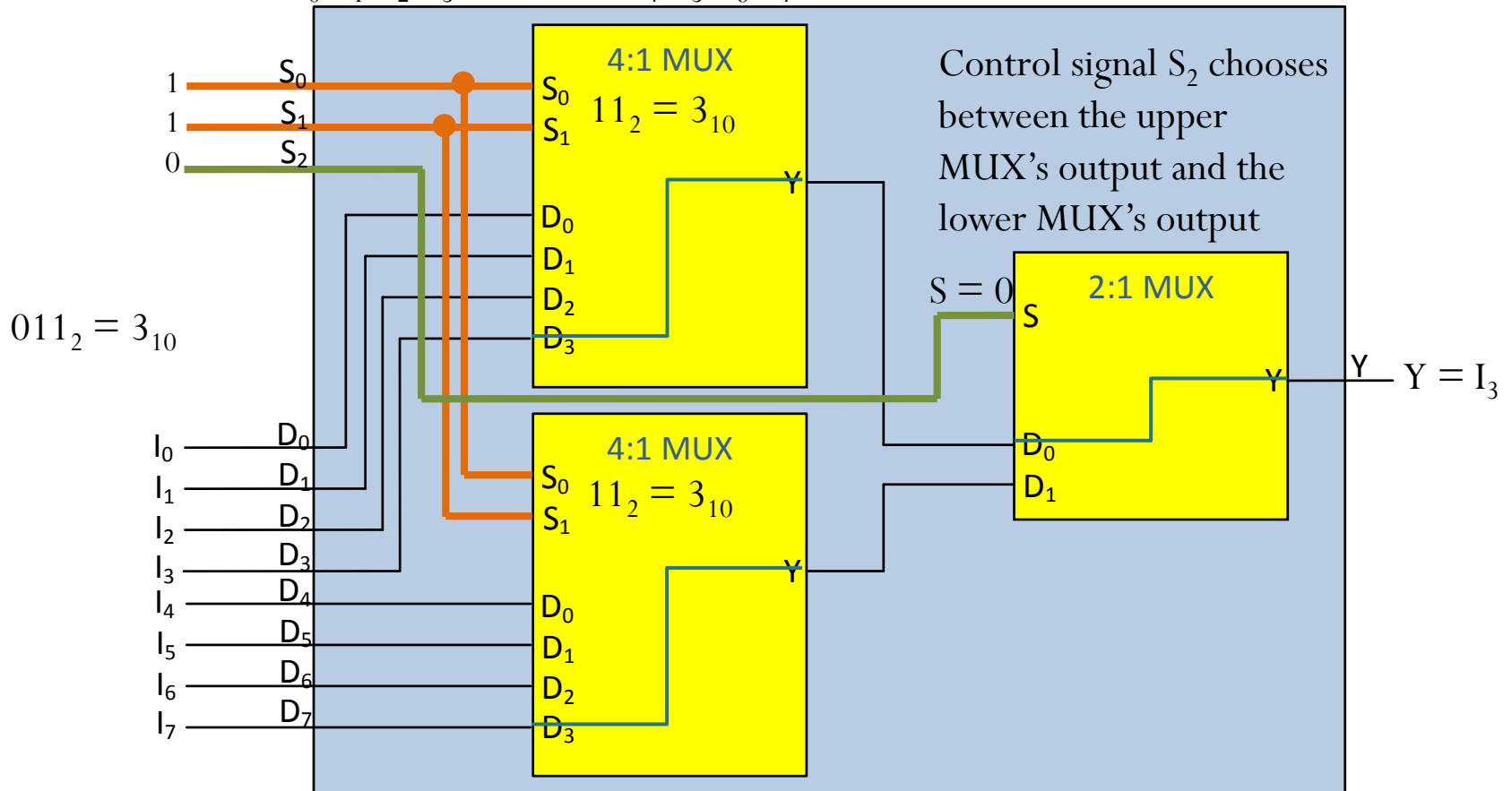Control signals S_0, S_1 simultaneously choose one of I_0, I_1, I_2, I_3 and one of I_4, I_5, I_6, I_7




Multiplexer Expansion

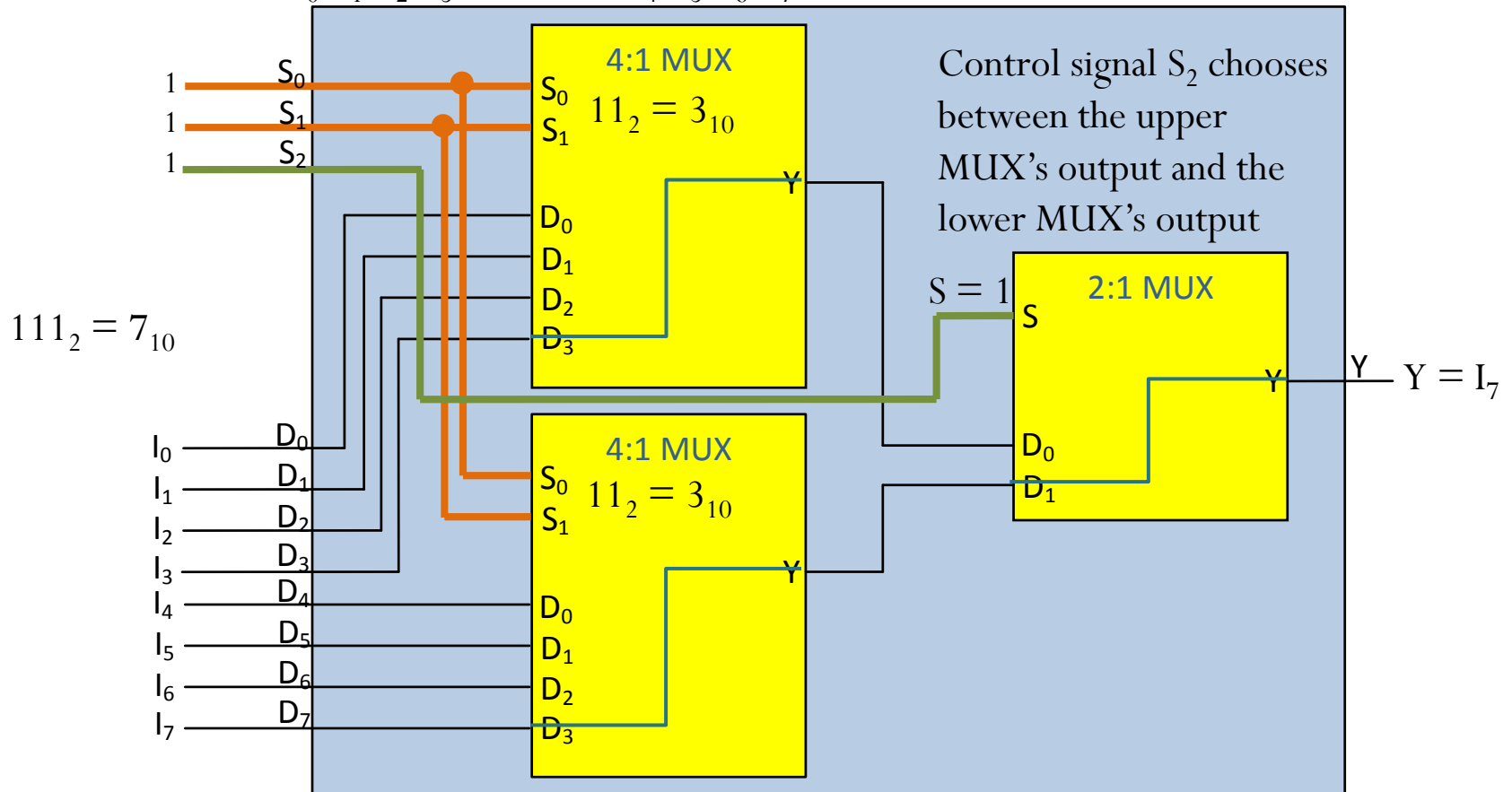Control signals S_0, S_1 simultaneously choose one of I_0, I_1, I_2, I_3 and one of I_4, I_5, I_6, I_7



MUX and Minterms

 - 2:1 mux: $Z = A'I_0 + AI_1$
- 4:1 mux: $Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$
- 8:1 mux: $Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3$
 $+ AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$




Mathematically, we may say that the output of the MUX is the weighted sum of all minterms (generated from the control variables) where the weights are the data inputs.

MUX as a Logic Function Generator

$2^n:1$ MUX can be used to implement any function of n variables.


Example:

$$F = \sum_{A,B,C} (0,2,6,7)$$


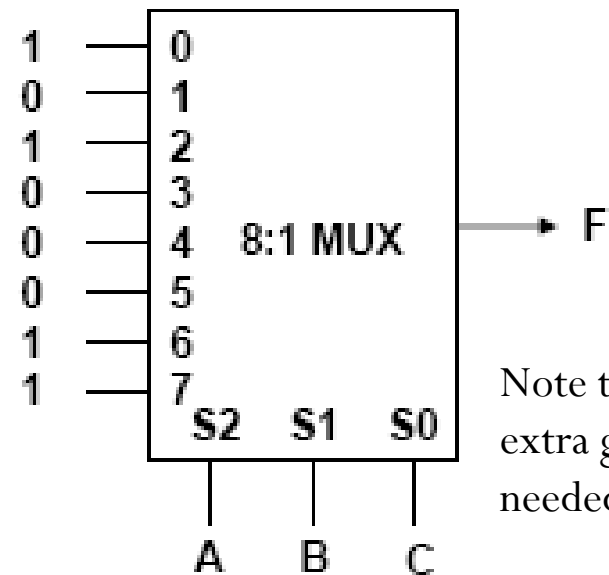


Explanation:
 
$$Z = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot I_0 + \bar{A} \cdot \bar{B} \cdot C \cdot I_1 + \bar{A} \cdot B \cdot \bar{C} \cdot I_2 + \bar{A} \cdot B \cdot C \cdot I_3 \\ + A \cdot \bar{B} \cdot \bar{C} \cdot I_4 + A \cdot \bar{B} \cdot C \cdot I_5 + A \cdot B \cdot \bar{C} \cdot I_6 + A \cdot B \cdot C \cdot I_7$$




74x151: 8:1 MUX

  

\bar{E}	S_2	S_1	S_0	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	\bar{Z}	Z
H	X	X	X	X	X	X	X	X	X	X	X	H	L
L	L	L	L	L	X	X	X	X	X	X	X	H	L
L	L	L	L	H	X	X	X	X	X	X	X	L	H
L	L	L	H	X	L	X	X	X	X	X	X	H	L
L	L	L	H	X	H	X	X	X	X	X	X	L	H
L	L	H	L	X	X	L	X	X	X	X	X	H	L
L	L	H	L	X	X	H	X	X	X	X	X	L	H
L	L	H	H	X	X	X	L	X	X	X	X	H	L
L	L	H	H	X	X	X	H	X	X	X	X	L	H
L	H	L	L	X	X	X	X	L	X	X	X	H	L
L	H	L	L	X	X	X	X	H	X	X	X	L	H
L	H	L	H	X	X	X	X	X	L	X	X	H	L
L	H	L	H	X	X	X	X	X	H	X	X	L	H
L	H	H	L	X	X	X	X	X	X	L	X	H	L
L	H	H	L	X	X	X	X	X	X	H	X	L	H
L	H	H	H	X	X	X	X	X	X	X	L	H	L
L	H	H	H	X	X	X	X	X	X	X	H	L	H

74x151: 8:1 MUX

Connection Diagram

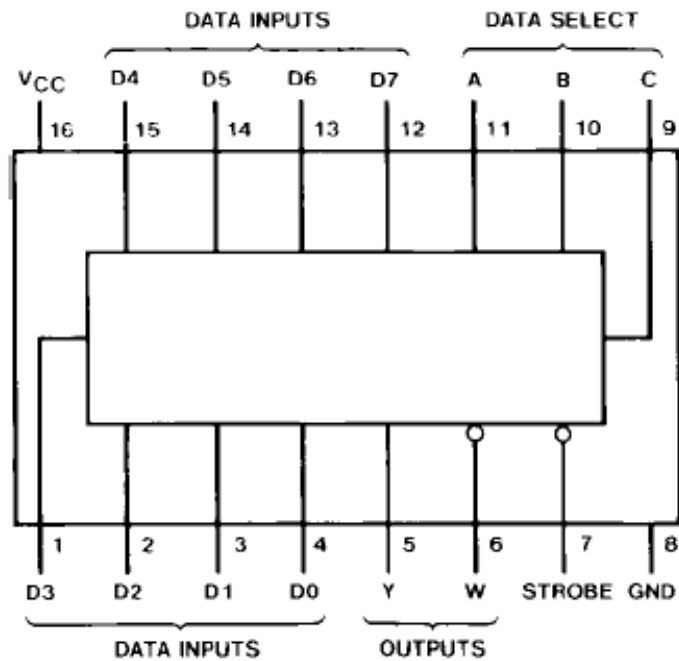

Truth Table

Inputs			Strobe	Outputs	
Select				Y	W
C	B	A	S		
X	X	X	H	L	H
L	L	L	L	D0	$\overline{D0}$
L	L	H	L	D1	$\overline{D1}$
L	H	L	L	D2	$\overline{D2}$
L	H	H	L	D3	$\overline{D3}$
H	L	L	L	D4	$\overline{D4}$
H	L	H	L	D5	$\overline{D5}$
H	H	L	L	D6	$\overline{D6}$
H	H	H	L	D7	$\overline{D7}$


H = HIGH Level

L = LOW Level

X = Don't Care

D0, D1...D7 = the level of the respective D input

74x151: Logic Diagram

 

74x157 Quad 2-Input MUX

- Four separate 2-input multiplexer.
- Each of the four multiplexers shares a common data-select line and a common Enable.

