

Digital Circuits

ECS 371

Dr. Prapun Suksompong

prapun@siit.tu.ac.th

Lecture 15

Office Hours:

BKD 3601-7

Monday 9:00-10:30, 1:30-3:30

Tuesday 10:30-11:30

ECS371.PRAPUN.COM



Some questions...

- Is the exam too difficult?
- Is the exam too long?



Announcement

- Reading Assignment:
 - Chapter 7: 7-1, 7-2, 7-4

Digital Logic Circuit Types

- Combinational Circuit
 - Output depends only on current inputs
 - No feedback loops
 - “memoryless”
- Sequential Circuit
 - Output depends on past history plus current inputs
 - Contains feedback loops
 - Has memory
- Up to this point, we have focused on “**combinatorial logic circuits**” (i.e. the output of the circuit is dependent on the current input ONLY).
- Now we will shift our focus to “**sequential logic circuits**” (i.e. the output depends not only on the present input but also on the **history** of the input).
- The basic building blocks for sequential logic circuits are “**latches**” and “**flip-flops**”

Sequential Logic Circuits

- Memory is represented in the form of states.
- “State” embodies all the information about the past needed to predict current output based on current input.
- State variables are one or more bits of information representing logic signals in a circuit
 - Tell you “where the circuit is”
 - Used in conjunction with inputs to derive current outputs of a sequential circuit
- In combinational circuits, only need to look at the current inputs to get the current output.





Exercise

- Separate into a group of two persons.
- Can you come up with a simple device that is a good example for sequential circuit?


S-R Latch

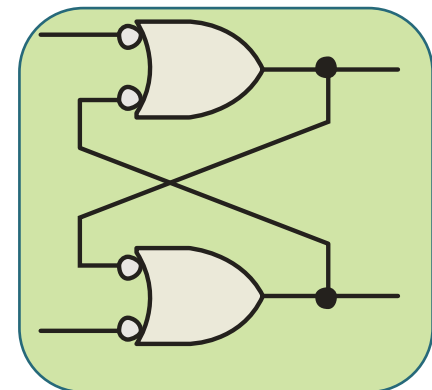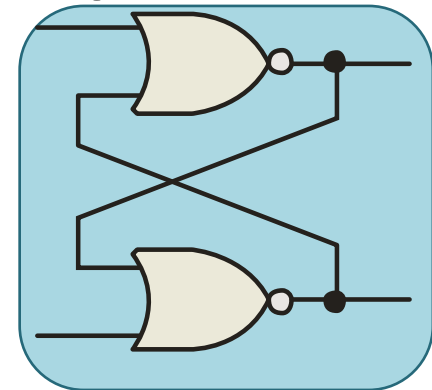- A **latch** is a temporary storage device that has two stable states (bistable). It is a basic form of memory.
- The **S-R (Set-Reset) latch** is the most basic type.
 - It can be constructed from NOR gates or NAND gates.
 - With two cross-coupled **NOR gates**, the latch responds to **active-HIGH inputs**.
 - With two cross-coupled **NAND gates**, the latch responds to **active-LOW inputs**.




S-R Latch


 
- There are two versions of SET-RESET (S-R) latches.




(a) Active-HIGH input S-R latch

 

  (b) Active-LOW input \bar{S} - \bar{R} latch



The “Old Q”-“New Q” Analysis

 


$$\begin{aligned} Q_{new} &= \overline{R + X} \\ &= \overline{R + \overline{R \cdot (Q_{old} + S)}} \\ &= \overline{R} \cdot (Q_{old} + S) \end{aligned}$$

Input		Output
S	R	Q_{new}
0	0	Q_{old}
0	1	0
1	0	1
1	1	0

Active-HIGH S-R latch


Input		Output
S	R	Q_{new}
0	0	Q_{old}
0	1	0
1	0	1
1	1	0

 Assume the latch is initially RESET ($Q = 0$) and the inputs are at their inactive level (0). To SET the latch ($Q = 1$), a momentary HIGH signal is applied to the S input while the R remains LOW.



To RESET the latch ($Q = 0$), a momentary HIGH signal is applied to the R input while the S remains LOW.

The “Old Q”-“New Q” Analysis (2)

 

$$Q_{new} = ?$$

Input		Output
\overline{S}	\overline{R}	Q_{new}
0	0	
0	1	
1	0	
1	1	