

# Digital Circuits

ECS 371

**Dr. Prapun Suksompong**

[prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th)

**Lecture 16**

**Office Hours:**

**BKD 3601-7**


**Monday 9:00-10:30, 1:30-3:30**

**Tuesday 10:30-11:30**


**ECS371.PRAPUN.COM**
 
# S-R Latch



- There are two versions of SET-RESET (S-R) latches.



(a) Active-HIGH input S-R latch

 


  (b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch



 
# S-R Latch (Remember This!)

- Two inputs
  - **S** for **set**
  - **R** for **reset**
- Two useful states (for normal operation)
  - When output  $Q = 1$  and  $\bar{Q} = 0$ , the latch is said to be in the **set state**.
  - When output  $Q = 0$  and  $\bar{Q} = 1$ , the latch is said to be in the **reset state**.




(a) Active-HIGH input S-R latch

 

(b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch


# The “Old Q”-“New Q” Analysis

 

$$\begin{aligned} Q_{new} &= \overline{R + X} \\ &= \overline{R + \overline{R + Q_{old} + S}} \\ &= \overline{R} \cdot (Q_{old} + S) \end{aligned}$$

Input		Output
S	R	$Q_{new}$
0	0	$Q_{old}$
0	1	0
1	0	1
1	1	0


# The “Old Q”-“New Q” Analysis (2)

 


$$\begin{aligned} Q_{new} &= \overline{\overline{S}} + \overline{X} \\ &= \overline{\overline{S}} + \overline{\overline{Q_{old} + \overline{R}}} \\ &= \overline{\overline{S}} + Q_{old} \cdot \overline{\overline{R}} \end{aligned}$$

Input		Output
$\overline{S}$	$\overline{R}$	$Q_{new}$
0	0	1
0	1	1
1	0	0
1	1	$Q_{old}$

# “Old Q”/“New Q” Analysis

 

(a) Active-HIGH input S-R latch

 


(b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch


Input		Output
S	R	$Q_{\text{new}}$
0	0	$Q_{\text{old}}$
0	1	0
1	0	1
1	1	0

Input		Output
$\bar{S}$	$\bar{R}$	$Q_{\text{new}}$
0	0	1
0	1	1
1	0	0
1	1	$Q_{\text{old}}$

# Expanded Version

 


Inputs		Outputs		Mode of Operation	Comment
$S$	$R$	$Q$	$\bar{Q}$		
0	0	NC	NC	Hold	No change.
0	1	0	1	Reset	For RESETting Q to 0
1	0	1	0	Set	For SETTING Q to 1
1	1	0	0	Prohibited	Invalid Condition

 


Inputs		Outputs		Mode of Operation	Comment
$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$		
0	0	1	1	Prohibited	Invalid Condition
0	1	1	0	Set	For SETTING Q to 1
1	0	0	0	Reset	For RESETting Q to 0
1	1	NC	NC	Hold	No change.

# Short Version (Remember This!)

 

Input		Mode
S	R	
0	0	HOLD
0	1	RESET
1	0	SET

 

Inputs		Mode
$\bar{S}$	$\bar{R}$	
0	1	SET
1	0	RESET
1	1	HOLD



# Operating S-R latch

Input		Mode
S	R	
0	0	HOLD
0	1	RESET
1	0	SET

- Under normal conditions, both inputs of the latch remain at 0 unless the state is to be change.
- The application of a 1 to the **S input** causes the latch to go to the **set state**.
  - The S input must go back to 0 before R is changed to 1 to avoid occurrence of the undefined state.
  - Applying a 0 to S with  $R = 0$  leaves the circuit in the same state.
- The application of a 1 to the **R input** causes the latch to go to the **reset state**.
  - We can then remove the one from R, and the circuit remains in the reset state.

# (1,1) Problem for S-R Latch



- If a 1 is applied to both the inputs of the latch, both outputs go to 0.
- This produces an undefined state.
- It results in an indeterminate or unpredictable next state when both inputs return to 0 simultaneously.
- In normal operation, these problems are avoided by making sure that 1's are not applied to both inputs simultaneously.

# Operating $\overline{S}$ - $\overline{R}$ latch

Inputs		Mode
$\overline{S}$	$\overline{R}$	
0	1	SET
1	0	RESET
1	1	HOLD


- Under normal conditions, both inputs of the latch remain at **1** unless the state is to be change.
- The application of a **0** to the  $\overline{S}$  **input** causes the latch to go to the **set state**.
  - The S input must go back to **1** before R is changed to 1 to avoid occurrence of the undefined state.
  - Applying a **1** to S with  $R = 1$  leaves the circuit in the same state.
- The application of a **0** to the  $\overline{R}$  **input** causes the latch to go to the **reset state**.
  - We can then remove the **0** from R, and the circuit remains in the reset state.

# Example

  

 
# Gated Latch

- A **gated latch** is a variation on the basic latch.
- The gated latch has an additional input, called enable ( $EN$ ) that must be HIGH in order for the latch to respond to the  $S$  and  $R$  inputs.



(a) Logic diagram

 

(b) Logic symbol


# Gated Latch

Observe that:


$$A = \overline{S \cdot EN} = \overline{S} + \overline{EN}$$

$$B = \overline{R \cdot EN} = \overline{R} + \overline{EN}$$


EN	A	B
0 $\Rightarrow$	1	1
1 $\Rightarrow$	$\overline{S}$	$\overline{R}$

 


# Example: Gated S-R Latch

 

(a) Logic diagram


 


(b) Logic symbol

 

  
# Gated D latch

- The D latch is a variation of the S-R latch.
- Has only one input in addition to EN.
  - This input is called the D (data) input.
- Combine the S and R inputs into a single D input.





# Gated D Latch: Operation

 


- A simple rule for the D latch is:
  - Q follows D when the Enable is active/asserted.
    - In this situation, the latch is said to be “open” and the path from D input to Q output is “transparent”.
    - The circuit is often called a transparent latch for this reason.
- When EN is LOW, the state of the latch is not affected by the D input.
  - In this situation, the latch is said to be “close”
  - The Q output retains its last value and no longer changes in response to D, as long as EN remains negated.
- Output is “latched” at the last value when the enable signal becomes not asserted.

• Truth Table:  $\longrightarrow$


$Q_0$  is the prior output level before the indicated input conditions were established.

Inputs		Outputs		Comments
$D$	$EN$	$Q$	$\bar{Q}$	
0	1	0	1	RESET
1	1	1	0	SET
X	0	$Q_0$	$\bar{Q}_0$	No change

# Example: Gated D Latch

 

Q follows D when the Enable is active.

 



# Flip-Flop

- Latches sample their inputs (and change states) any time the EN bit is asserted
- Many times we want more control over when to sample the input
- A **flip-flop** differs from a latch in the manner it changes states.
- A flip-flop is a *clocked* device.
- Flip-flops are **synchronous**: the output changes state only at a specified point on the triggering input called the **clock (CLK)**
  - In other words, changes in the output occur in synchronization with the clock.
- An **edge-triggered flip-flop** changes state either at the **positive edge (rising edge)** or at the **negative edge (falling edge)** of the clock pulse.
  
# Edge-Triggered Flip-Flops


“Edge-triggered flip-flop” is redundant (all flip-flops are edge-triggered)

Positive edge-triggered (no bubble at C input)



Negative edge-triggered (bubble at C input)

# D Flip-Flop

 

- The truth table for a positive-edge triggered D flip-flop shows an up arrow to remind you that it is sensitive to its D input only on the **rising edge of the clock**.
- The truth table for a negative-edge triggered D flip-flop is identical except for the direction of the arrow.

Inputs		Outputs		Comments
D	CLK	Q	$\bar{Q}$	
1	↑	1	0	SET
0	↑	0	1	RESET

(a) Positive-edge triggered



Inputs		Outputs		Comments
D	CLK	Q	$\bar{Q}$	
1	↓	1	0	SET
0	↓	0	1	RESET

(b) Negative-edge triggered


↑ = clock transition LOW to HIGH
  
# Ex: Positive-edge triggered D Flip-Flop

- Determine the  $Q$  output waveform if the flip-flop starts out RESET




# Exercise: What is this?

 
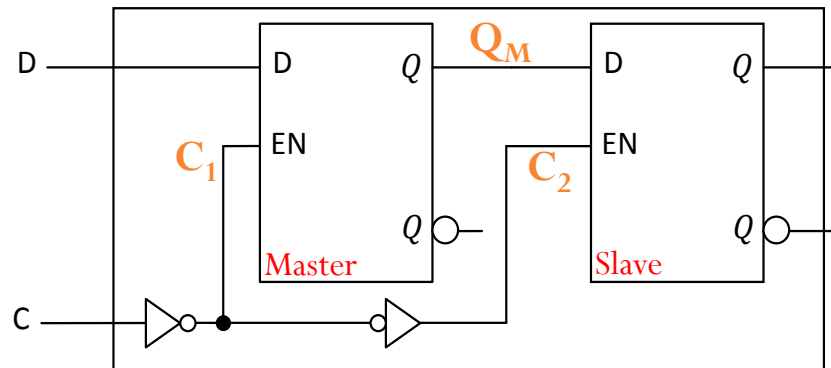
# D Flip Flop: Implementation

- Tie two D-latches together to make a D flip-flop




- When  $C$  is 0 ( $C_1 = 1$ ), the master latch is open and follows the  $D$  input.
- When  $C$  is 1 ( $C_1 = 0$ ,  $C_2 = 1$ ), the master latch is closed and its output is transferred to the slave latch.
  - The slave latch is open all the while that  $C$  is 1, but changes only at the beginning of this interval, because the master is closed and unchanging during the rest of the interval.


 
# J-K Flip-Flop



- Has two inputs, labeled J and K (along with the CLK).
- When both J and K = 1, the output changes states (toggles) on the rising clock edge.



Inputs			Outputs		Comments
J	K	CLK	Q	$\bar{Q}$	
0	0	↑	$Q_0$	$\bar{Q}_0$	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\bar{Q}_0$	$Q_0$	Toggle


A J-K flip-flop connected for toggle operation is sometimes called a **T flip-flop**.

# Example: J-K Flip-Flop

 
 

 
# Asynchronous Inputs


- Most flip-flops have other inputs that are *asynchronous*, meaning they affect the output independent of the clock.
- Two such inputs are normally labeled **preset (PRE)** and **clear (CLR)**.
- These inputs are usually active-LOW.
- A J-K flip flop with active-LOW preset and CLR is shown.




# Example

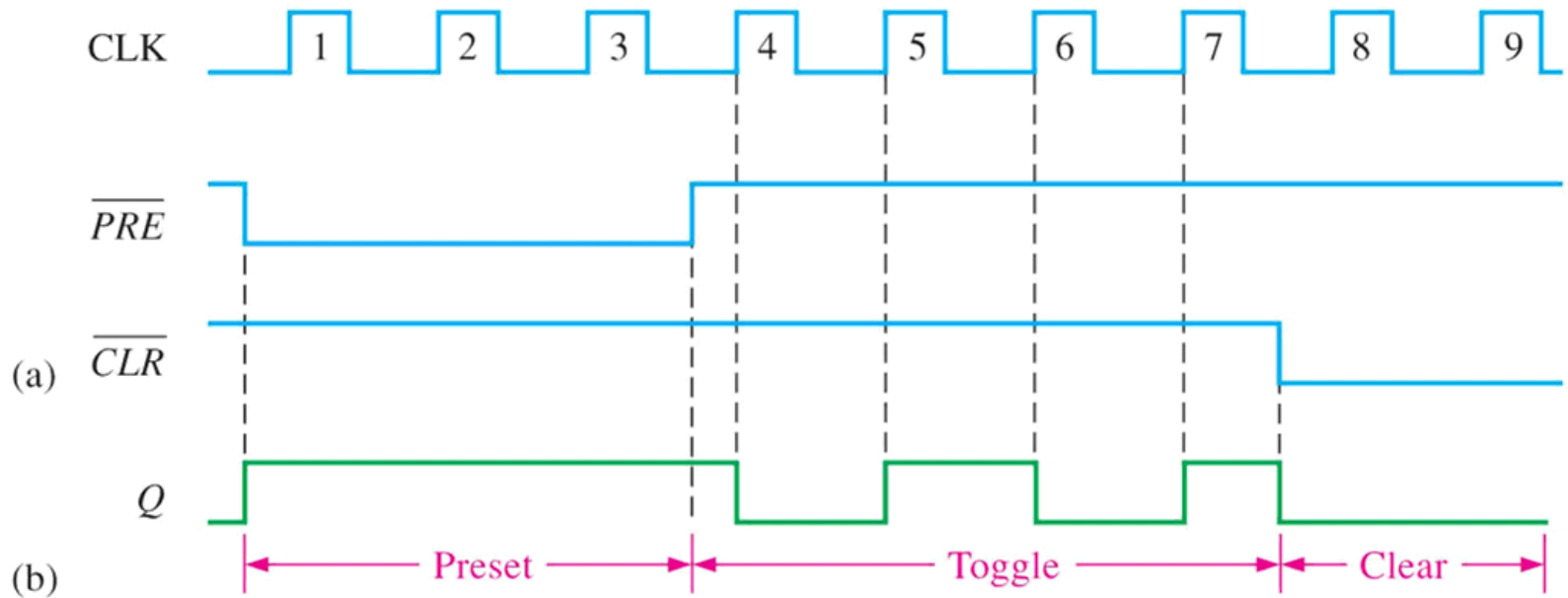 


# Logic Symbols: Latches and Flip-Flops

 


(a) Active-HIGH  
input S-R latch

 

 
(b) Active-LOW input  
 $\bar{S}$ - $\bar{R}$  latch




(c) Gated S-R latch

 


(d) Gated D latch

 

(e) S-R edge-triggered  
flip-flops

 

(f) D edge-triggered  
flip-flops

 



(g) J-K edge-triggered  
flip-flops

# Latches and Flip-Flops

- Can maintain a binary state indefinitely (as long as power is delivered to the circuit), until directed by an input signal to switch states.
- The major differences among the various types of latches and flip-flops are the number of inputs the process and the manner in which the inputs affect the binary state.
- The most basic storage elements are latches, from which flip-flops are usually constructed.
- Although latches are most often used within flip-flops, they can also be used with more complex clocking methods to implement sequential circuits directly.
  - The design of such circuits is, however, beyond the scope of this class.

# Some Applications

- Divide the clock frequency by 2

  

# Some Applications

- Divide the clock frequency by 4

