



Current Q_1, Q_0	Next Q_1, Q_0	J_1, K_1	J_0, K_0
0 0	1 0	1 X	0 X
0 1	0 0	0 X	X 1
1 0	0 1	X 1	1 X
1 1	X X	X X	X X

Q
 $0 \rightarrow 1$

J, K
1 1 (toggle)
1 0 (set)


Q	J, K
0 \rightarrow 0	0 0 (Hold)
0 \rightarrow 1	0 1 (reset)
1 \rightarrow 0	1 X
1 \rightarrow 1	X 1
	X 0

Circuit Construction

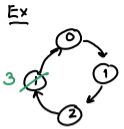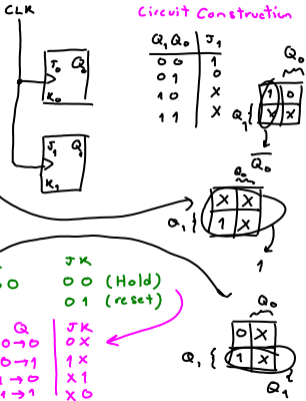


Current Q_1, Q_0	Next Q_1, Q_0
0 0	0 1
0 1	1 0
1 0	0 0
1 1	1 1

Can't have this.

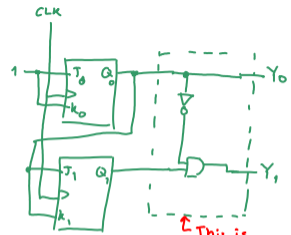

Input Q_1, Q_0	Output Y_1, Y_0
0 0	0 0
0 1	0 1
1 0	1 0
1 1	0 1

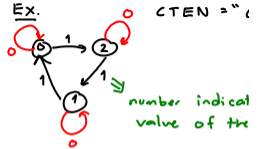This is added to change 3 \rightarrow 1 on the output.



Use D-FF:

When $CTEN = 1$,
 $D_1 = \bar{Q}_0 \cdot \bar{Q}_1$
 $D_0 = Q_1$
 When $CTEN = 0$,
 $D_1 = Q_1$
 $D_0 = Q_0$

Count Enable²

tes

CTEN

$$D_1 = \square \times \text{CTEN} + \bigcirc \times \overline{\text{CTEN}}$$

$$= \overline{Q_0} \cdot \overline{Q_1} \times \text{CTEN} + Q_1 \times \overline{\text{CTEN}}$$