

Digital Circuits

ECS 371

Dr. Prapun Suksompong

prapun@siit.tu.ac.th

Lecture 5-6

Office Hours:

BKD 3601-7

Monday 1:30-3:30

Tuesday 10:30-11:30

ECS371.PRAPUN.COM

Announcement

- I scanned the questions for HW1 and posted them on the course website.
 - Use it if you haven't obtained the textbook.
- Need to do something about the office hours.
- The old office hours
 - ✓ Monday 1:30-3:30PM: Conflict with ITS325, MAS210
 - ✓ Tuesday 10:30-11:30AM: Conflict with ITS221
- Let's add
 - ✓ **Monday 9:00-10:30** ←
- I'm not limited to these time slots.
 - Usually in my office (BKD3601-7) from 8AM-5PM

Problem Set 1

- Chapter 2

6, 9, 13, 19, 20, 22, 25, 28

- Chapter 3

6, 8, 16, 20, 23

- Due date: June 25, 2009 (Thursday)

- Please submit **your HW** to the instructor **3 minutes BEFORE your class starts**.


- Late submission will not be accepted.
- **Earlier submission is possible**. There are two HW boxes in the EC department (6th floor) for ECS 371. (One for CS. Another one for IT.)

Question




- How many people will participate in the SIIT day activities during our class time on Thursday?

Review


Draw the logic circuit represented by

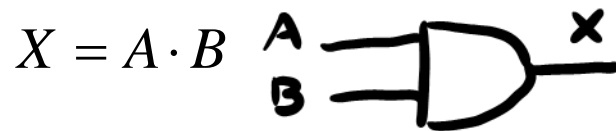

$X = (A + B)C + B$

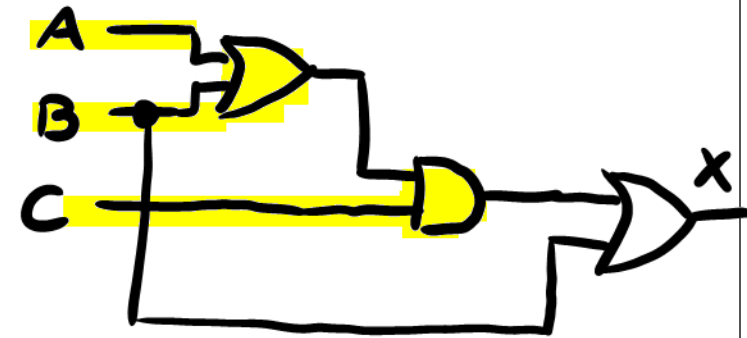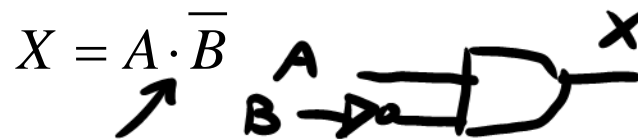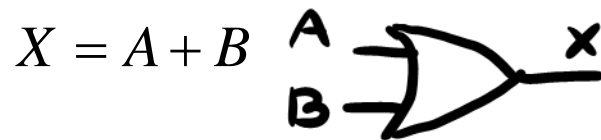

$X = \overline{A \cdot B}$

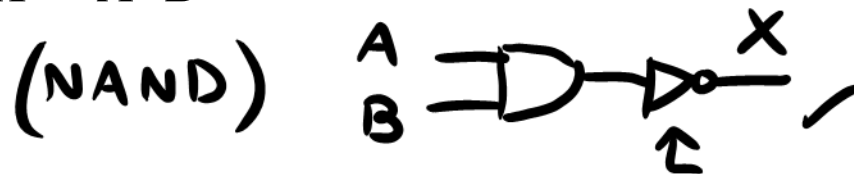


Remark

- Precedence:

✓ $A + B \cdot \bar{C}$ is the same as $A + (B \cdot \bar{C})$


$A + B \cdot \bar{C}$ is NOT the same as $(A + B) \cdot \bar{C}$

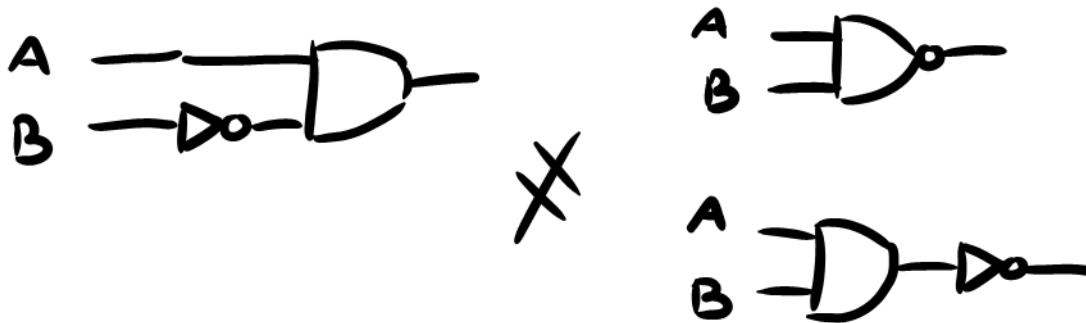$A \cdot \bar{B}$ is NOT the same as $\overline{A \cdot B}$




Truth Table

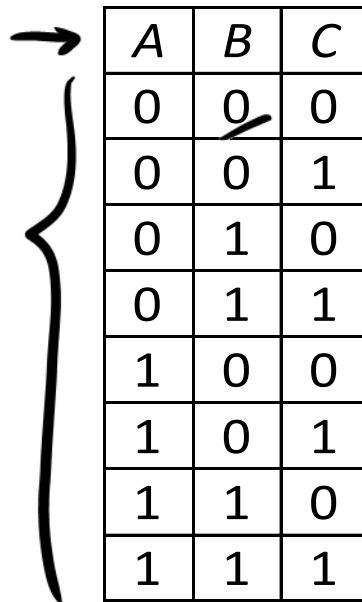Example: Find the value of X for all possible values of the variables when



A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
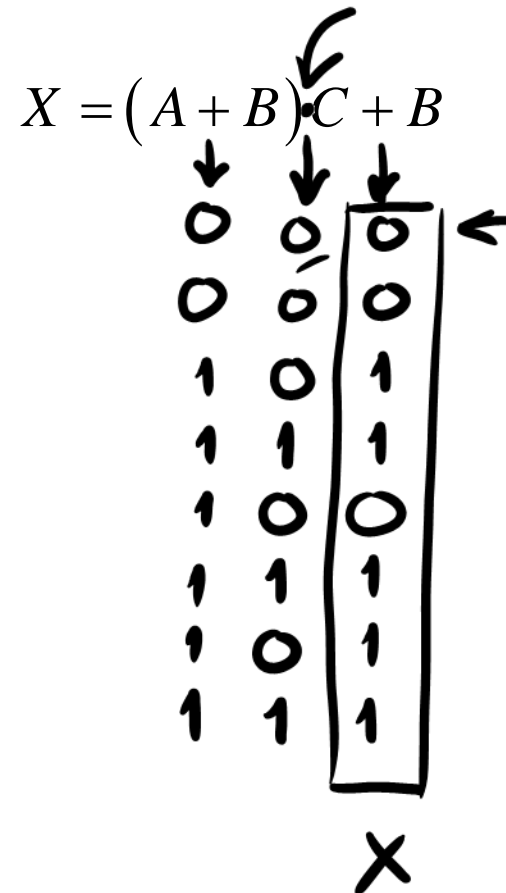
$$X = (A + B) \cdot C + B$$


0	0	0	0
0	0	1	0
1	0	0	0
1	1	0	1
1	0	1	0
1	0	1	1
1	1	0	1
1	1	1	1

X

Proving Identities/Rules/Laws

Example: Check that

$$AB + A(B + C) = A(B + C)$$

Method 1: Use Algebraic Manipulation

$$\begin{aligned} & AB + A(B + C) \\ &= AB + AB + AC \\ &= A \cdot B + AC \\ &= A(B + C) \quad \# \end{aligned}$$

Method 2: Use Truth Table

A	B	C	$AB + A(B + C)$				$A(B + C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	0	1	0
0	1	1	0	0	0	1	0
1	0	0	0	0	0	0	0
1	0	1	0	1	1	1	1
1	1	0	1	1	1	1	1
1	1	1	1	1	1	1	1

The truth table shows that the two expressions are equivalent for all combinations of A, B, and C. A red arrow points from the 5th column to the 7th column, indicating their equality.

Comparison

	① Algebraic Manipulation	② Truth Table
Advantage	<ul style="list-style-type: none">• Quick (usually) ✓• Simple ✓	<ul style="list-style-type: none">• Straightforward ✓
Disadvantage	<ul style="list-style-type: none">• Need to remember many rules/laws. ✓• Need to know when to apply them. ✓	<ul style="list-style-type: none">• Tedious/Boring/Time-wasting ✓

For ECS371, make sure that you know **both** method.

Later, we will use another method (K-map).

Principle of Duality

Any theorem or identity remains true if $0 \leftrightarrow 1$

Example:

$\cdot \leftrightarrow +$

$$X + 1 = 1$$

$$X + \bar{X} = 1$$

$$X \cdot 0 = 0$$

$$X \cdot \bar{X} = 0$$

Caution: $X + (X \cdot Y) = X$

\Rightarrow

~~$X \cdot X + Y = X$~~
 ~~$X + Y = X$~~

$$X \cdot (X + Y) = X$$

- Parenthesize an expression fully before taking its dual!

$$(X \cdot Y) + (X \cdot Z) = X \cdot (Y + Z)$$

$$(X + Y) \cdot (X + Z) = X + (Y \cdot Z)$$

Duality Principle in Action


(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
(T4)	$(X')' = X$			(Involution)
(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complements)

(T6)	$X + Y = Y + X$	(T6')	$X \cdot Y = Y \cdot X$	(Commutativity)
(T7)	$(X + Y) + Z = X + (Y + Z)$	(T7')	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	(Associativity)
(T8)	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$	(T8')	$(X + Y) \cdot (X + Z) = X + Y \cdot Z$	(Distributivity)
(T9)	$X + X \cdot Y = X$	(T9')	$X \cdot (X + Y) = X$	(Covering)
(T10)	$X \cdot Y + X \cdot Y' = X$	(T10')	$(X + Y) \cdot (X + Y') = X$	(Combining)

$$X \cdot Y + X \cdot Y' = X \quad \longrightarrow \quad (X + Y) \cdot (X + \bar{Y}) = X$$

DeMorgan's Theorem

$$\overline{X \cdot Y \cdot Z}$$

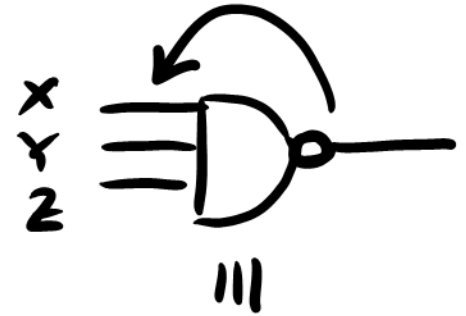


Part 1:


$$\overline{A_1 \cdot A_2 \cdots A_n} = \overline{A_1} + \overline{A_2} + \cdots + \overline{A_n}$$

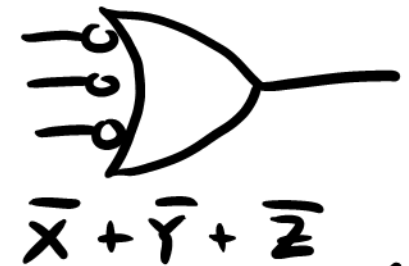Part 2:

$$\overline{A_1 + A_2 + \cdots + A_n} = \overline{A_1} \cdot \overline{A_2} \cdots \overline{A_n}$$



Example:

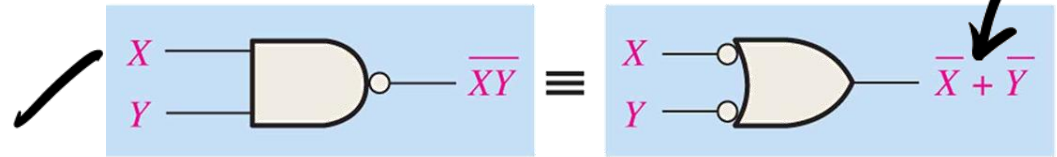


NAND

Negative-OR


$$X \text{ NAND } Y = \overline{X \cdot Y} = \overline{\overline{\overline{X} + \overline{Y}}} \quad (\text{Negative-OR})$$
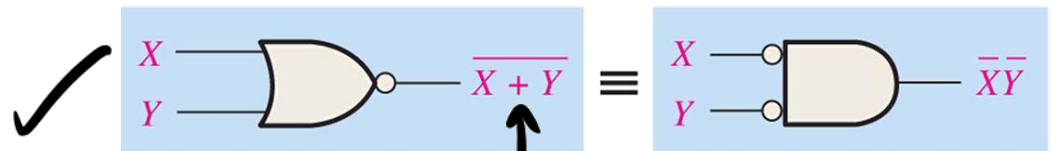
$$X \text{ NOR } Y = \overline{X + Y} = \overline{\overline{\overline{X} \cdot \overline{Y}}} \quad (\text{Negative-AND})$$



NOR

Negative-AND

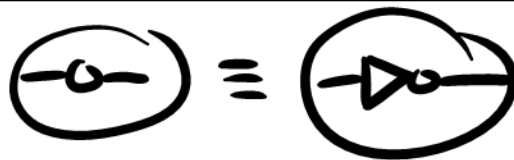


Play with the bubbles

Recall that each bubble means a “NOT” operation.


1. You can create a pair of bubbles out of nothing and move them freely on the wire.
2. DeMorgan's Theorem: When you move bubble through the AND gate or the OR gate, the gate changes.
3. If you want to leave an isolated bubble in your final design/answer, write an actual inverter instead of a bubble.

~~—○—~~ is not a gate

→ ~~—▷○—~~ is a NOT gate

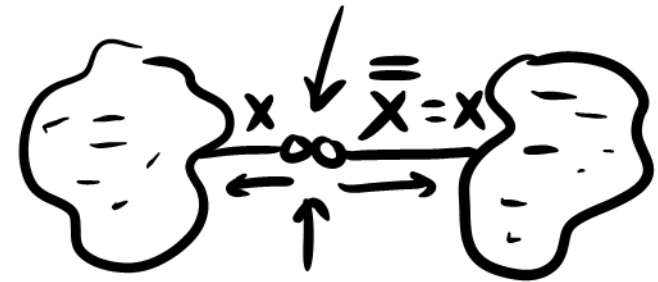

This does not change anything.

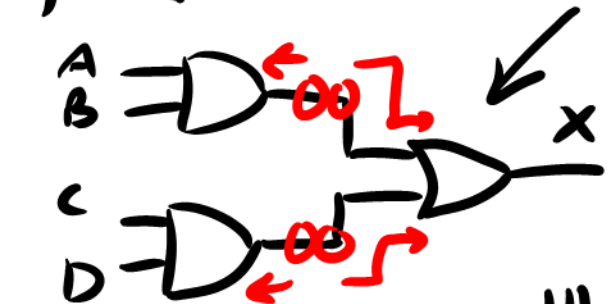

Product Term

A single literal or a product of two or more literals.

Example:

$$A \cdot \bar{B} \cdot C$$

$$A \cdot C$$

$$A$$

$$A \cdot \bar{B} \cdot C \cdot D$$

$$\bar{A} \cdot \bar{B} \cdot \bar{C}$$

variable or its complement

$$\bar{A}$$

Caution:

$\overline{A \cdot B \cdot C}$ is not a product term.

Q: When does $A \cdot \bar{B} \cdot C = 1$?

$$\begin{array}{l} A = 1 \\ \bar{B} = 1 \\ C = 1 \end{array}$$

$$(A, B, C) = (1, 0, 1)$$