

# Digital Circuits

ECS 371

**Dr. Prapun Suksompong**

[prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th)

**Lecture 9**

**Office Hours:**

**BKD 3601-7**

**Monday 9:00-10:30, 1:30-3:30**

**Tuesday 10:30-11:30**

**ECS371.PRAPUN.COM**

# Announcement

- HW3 posted on the course web site
  - Chapter 4: 5(b,d), 26b, 30b, 32a, 34a, 44
  - **Write down all the steps** that you have done to obtain your answers.
  - Due date: July 9, 2009 (Thursday)
- Today
  - Use handout from lecture 8 first.
  - The new handout is for Chapter 5 (except the first few slides).

# Caution

When you see  $\overline{ABC}$  or  $\overline{ABC}$  on quiz/HW/exam, please always **double-check** whether the bars on the top are disconnected.

This is the K-map for  
 $X = \overline{ABC}$  which is the  
same as  $X = \overline{A} \cdot \overline{B} \cdot \overline{C}$

			C	
	AB			C
A		1	0	B
		0	0	
		0	0	
		0	0	


This is the K-map for  $X = \overline{ABC}$   
which is equivalent to  
 $X = \overline{A} + \overline{B} + \overline{C}$

			C	
	AB			C
A		1	1	B
		1	1	
		1	0	
		1	1	
 
# Example

Use a K-map to minimize the following expression

$$X = \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C}$$




$$X = \overline{B} + AC$$

# Non-uniqueness

Use a K-map to minimize the following expression

$$AB + \overline{A}\overline{B} + \overline{A}BC$$

 

Solution 1:  $AB + \overline{A}\overline{B} + \overline{A}C$

Solution 2:  $AB + \overline{A}\overline{B} + BC$


# “Don’t Care” Input Combinations

- Sometimes the output doesn’t matter for certain input combinations.
  - For example, the combinations are not allowed in the first place.
- These combinations are called “don’t care”.
- The “don’t care” term can be used to advantage on K-map.
- For each “don’t care” term, place an X in the corresponding cell.
- When grouping the 1s,
  - the Xs can be treated as 1s to make a larger grouping
  - or as 0s if they cannot be used to advantage.

# Example

INPUTS				OUTPUT
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

(a) Truth table

 

(b) Without "don't cares"  $Y = \bar{A}\bar{B}\bar{C} + \bar{A}BCD$   
 With "don't cares"  $Y = A + BCD$

# Alternative Methods

- Disadvantages of using K-maps
  - Not applicable for more than five variables
  - Practical only for up to four variables
  - Difficult to automated in a computer program
- There are other ways to minimize Boolean functions.
  - More practical for more than four variables
  - Easily implemented with a computer
    1. Quine-McClusky method
      - Inefficient in terms of processing time and memory usage
    2. Espresso Algorithm
      - de facto standard



# New Perspective: 0

- So far, all of our techniques focus on the 1s in the truth tables/K-maps.
- We can look at the 0s as well.

Caution: From this perspective, you are in a different world. In fact, it is a dual world. Techniques used here will be the dual of what we used before.

# Canonical Product

- Product-of-Sums (POS) Form

Example:  $(A + \bar{B}) \cdot (A + B + C)$

- Standard POS Form (Canonical Product)

Example:  $(A + \bar{B} + C) \cdot (A + \bar{B} + \bar{C}) \cdot (A + B + C)$

- Convert expression in POS form into canonical product:

Hint:

$$\begin{aligned} X &= X + 0 \\ &= X + Y \cdot \bar{Y} \\ &= (X + Y) \cdot (X + \bar{Y}) \end{aligned}$$

# Truth Table for Canonical Product

Find the value of  $X$  for all possible values of the variables when

$$X = (A + \bar{B} + C) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + C)$$

Old way: Convert to SOP form

$$\begin{aligned} X &= (A + \bar{B} + C) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + C) \\ &= \left( (A + \bar{B}) \cdot (\bar{A} + B) \cdot (\bar{A} + \bar{B}) \right) + C \\ &= \left( (A + \bar{B}) \cdot (\bar{A} + (B \cdot \bar{B})) \right) + C \\ &= \left( (A + \bar{B}) \cdot \bar{A} \right) + C \\ &= (\bar{A} \cdot \bar{B}) + C \end{aligned}$$



$A$	$B$	$C$	$X$	$\bar{A} \cdot \bar{B}$	$C$
0	0	0	1	1	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	1	0	1

Then, construct the truth table.

We can use the property of sum terms to construct the truth table directly.

# Maxterm

- A sumterm in a canonical product is called a **maxterm**.
- A maxterm is equal to 0 for only one combination of variable values.

$$A + \bar{B} + C = 0 \text{ iff } (A, B, C) = (0, 1, 0)$$

$$A + \bar{B} + \bar{C} = 0 \text{ iff } (A, B, C) = (0, 1, 1)$$

$$A + B + C = 0 \text{ iff } (A, B, C) = (0, 0, 0)$$

- We say that the maxterm  $A + \bar{B} + C$  has a binary value of 010 (decimal 2)
- Maxterm list:  $(A + \bar{B}) \cdot (A + B + C) = \prod_{A,B,C} (0, 2, 3)$

because

$$(A + \bar{B}) \cdot (A + B + C) = (A + \bar{B} + C) \cdot (A + \bar{B} + \bar{C}) \cdot (A + B + C)$$

# Truth Table for Canonical Product

Find the value of  $X$  for all possible values of the variables when

$$X = (A + \bar{B} + C) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + C)$$

New way:

$A$	$B$	$C$	$X$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$\leftarrow A + \bar{B} + C$

$\leftarrow \bar{A} + B + C$

$\leftarrow \bar{A} + \bar{B} + C$

# Minterm/Maxterm & Truth Table

Row #	A	B	C	Minterm	Maxterm
0	0	0	0	$\bar{A} \cdot \bar{B} \cdot \bar{C}$	$A + B + C$
1	0	0	1	$\bar{A} \cdot \bar{B} \cdot C$	$A + B + \bar{C}$
2	0	1	0	$\bar{A} \cdot B \cdot \bar{C}$	$A + \bar{B} + C$
3	0	1	1	$\bar{A} \cdot B \cdot C$	$A + \bar{B} + \bar{C}$
4	1	0	0	$A \cdot \bar{B} \cdot \bar{C}$	$\bar{A} + B + C$
5	1	0	1	$A \cdot \bar{B} \cdot C$	$\bar{A} + B + \bar{C}$
6	1	1	0	$A \cdot B \cdot \bar{C}$	$\bar{A} + \bar{B} + C$
7	1	1	1	$A \cdot B \cdot C$	$\bar{A} + \bar{B} + \bar{C}$

In the same way that each minterm corresponds to a unique row of the truth table,

each maxterm corresponds to a unique row of the truth table (in a dual way).

“1”

“0”

# Conversion

Row #	A	B	C	Minterm	Maxterm
0	0	0	0	$\bar{A} \cdot \bar{B} \cdot \bar{C}$	$A + B + C$
1	0	0	1	$\bar{A} \cdot \bar{B} \cdot C$	$A + B + \bar{C}$
2	0	1	0	$\bar{A} \cdot B \cdot \bar{C}$	$A + \bar{B} + C$
3	0	1	1	$\bar{A} \cdot B \cdot C$	$A + \bar{B} + \bar{C}$
4	1	0	0	$A \cdot \bar{B} \cdot \bar{C}$	$\bar{A} + B + C$
5	1	0	1	$A \cdot \bar{B} \cdot C$	$\bar{A} + B + \bar{C}$
6	1	1	0	$A \cdot B \cdot \bar{C}$	$\bar{A} + \bar{B} + C$
7	1	1	1	$A \cdot B \cdot C$	$\bar{A} + \bar{B} + \bar{C}$

This tells that the output column of the truth table is 1 on row # 0, 1, 2, 3.

This tells that the output column of the truth table is 0 on row # 4, 5, 6, 7.

$$\Sigma_{A,B,C}(0,1,2,3) = \Pi_{A,B,C}(4,5,6,7)$$

$$\Sigma_{X,Y}(1) = \Pi_{X,Y}(0,2,3)$$

$$\Sigma_{W,X,Y,Z}(0,1,2,3,5,7,11,13) = \Pi_{W,X,Y,Z}(4,6,8,9,10,12,14,15)$$

# K-Map POS Minimization

- Goal: Find the “Minimal Product”
- Appendix B in the textbook.
- For a POS expression in standard form, a 0 is placed on the K-map for each sumterm in the expression.
- The cells that do not have a 0 are the cells for which the expression is 1.
- Group 0s to produce instead of grouping 1s.




# Combinational Logic

- Chapter 5 and 6
- Reading Assignment:
  - Read Section 5-1 to 5-5.
- Definition: A **combinational logic** is a combination of logic gates interconnected to produce a specified Boolean function with no storage or memory capability.
- Sometimes called **combinatorial logic**.
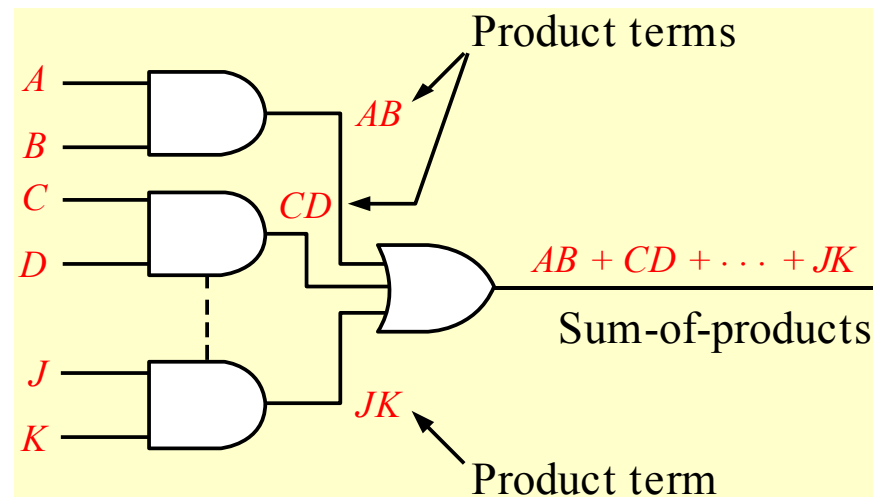
# SOP Implementation: AND-OR Circuit


In Sum-of-Products (SOP) form, basic combinational circuits can be directly implemented with AND-OR combinations: first forming the AND terms; then the terms are ORed together.



This is called the **AND-OR configuration**.
 
# Example

Write the output expression of the following circuit as it appears in the figure and then change it to an equivalent AND-OR configuration.




Solution:

$$X = (A + B) \cdot (C + D)$$

$$= (A + B) \cdot C + (A + B) \cdot D$$


$$= AC + BC + AD + BD$$

 

(a)
 
# Example

Write the output expression of the following circuit as it appears in the figure and then change it to an equivalent AND-OR configuration.





# Solution

$$X = \overline{\overline{\overline{A+B}} \cdot \overline{B \cdot C}} + D$$

$$= \overline{\overline{A+B}} \cdot \overline{B \cdot C} + D$$

$$= \overline{A} + B + B \cdot C + D$$

$$= \overline{A} + B + D$$

  


# Remark

1. From any logic expression, you can construct a truth table.
2. From the truth table you can get a canonical sum or a minterm list. (This can be simplified to a minimal sum. In any case, you get a SOP expression)
3. Any SOP expression can be implemented using AND gates, OR gates, and inverters.
 
# AND-OR-Invert (AOI) circuit

When the output of a SOP form is inverted, the circuit is called an **AND-OR-Invert circuit**.

The AOI configuration lends itself to product-of-sums (POS) implementation.




# Universal gate

- The term **universal** refers to a property of a gate that permits any logic function to be implemented by that gate or by a combination of gates of that kind.
- Example: NAND gates, NOR gates



 
# NAND Gate as a Universal Gate


NAND gates are sometimes called **universal** gates because they can be used to produce the other basic Boolean functions.




Inverter

 

AND gate

 


OR gate

 

NOR gate

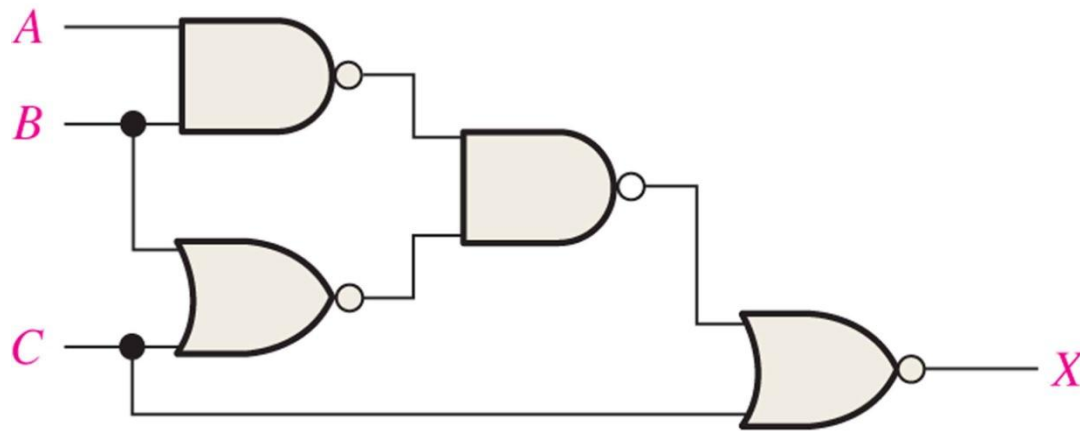
# Example

Implement the following logic circuit using only NAND gates:




Solution:

Negative-OR  $\equiv$  NAND

 

 
# Example

Implement the following logic circuit using only NAND gates:




Solution:

 

 
# NOR Gate as a Universal Gate


NOR gates are also **universal** gates and can form all of the basic gates.




Inverter

 

OR gate

 


AND gate

 

NAND gate
 
# Example

Implement the following logic circuit using only NOR gates:



Solution:

